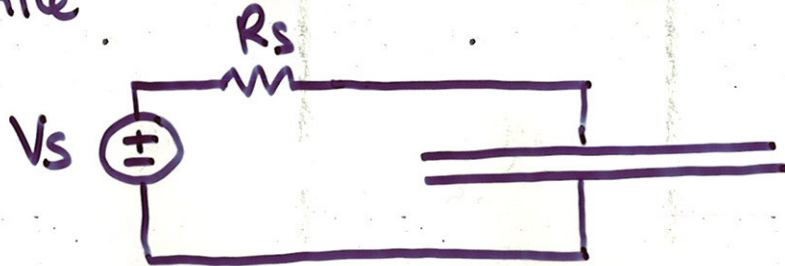


ENERGY STORAGE

- Apply a ^(constant) voltage to two parallel conducting plates and wait awhile



- What do we have?
 - no current flowing
 - positive charge on top plate
 - negative charge on bottom plate

⇒ electric field across the gap.
- Now remove/disconnect the source
 - nowhere for charge to flow
 - electric field remains
 - energy stored in ~~cap~~ potential of charges.
- How to use this?

Interesting idea! Let's try to model it so that we can use it.

Idealized setup

- infinite plates
- perfect conductors
- perfect insulator
- perfectly uniform dielectric

In that case,

charge stored \propto voltage applied

Actually,

$$q = CV$$


$$C = \frac{\epsilon A}{d}$$

ϵ = permittivity

A = area.

d = separation

CIRCUIT MODEL

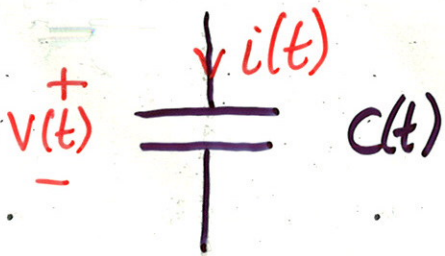

$$q(t) = C(t)v(t)$$

what about current?

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} [C(t)v(t)]$$

If capacitance is constant,

$$i(t) = C \frac{dv(t)}{dt}$$

So what is $v(t)$?

Assume $v(t)|_{t=t_0}$ is known.

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

Sometimes ~~assume~~ choose $t_0 = -\infty$
and assume $v(-\infty) = 0$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$$

The idea was to store energy

How much did we store?

$$E(t) = \int_{-\infty}^t p(x) dx.$$

where $p(t)$ is power.

$$p(t) = v(t) i(t) = C v(t) \frac{dv(t)}{dt}$$

$$\begin{aligned} \Rightarrow E(t) &= \int_{-\infty}^t C v(x) \frac{dv(x)}{dx} dx \\ &= C \int_{v(-\infty)}^{v(t)} v(x) dv(x) \\ &= \frac{1}{2} C v(x)^2 \Big|_{v(-\infty)}^{v(t)} \end{aligned}$$

If we assume $v(-\infty) = 0$,


$$E(t) = \frac{1}{2} C v(t)^2$$

* Sometimes desirable + engineered

* Sometimes undesirable + to be engineered away

PROPERTIES

APPLICATIONS

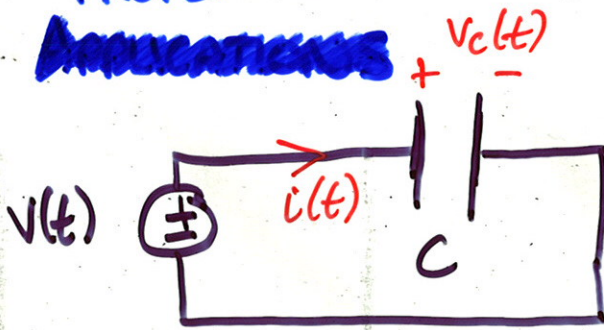

$$i(t) = C \frac{dV_c(t)}{dt}$$

* what if $v(t)$ is constant?

- current = 0, no matter how big $v(t)$ is

⇒ open circuit

- have you seen this idea in use?

* what if $v(t)$ changes rapidly?

- $|i(t)|$ is large, even if $v(t)$ is small

→ short circuit

$$* \quad v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$$

what does this tell us about $v(t)$?

Continuous