
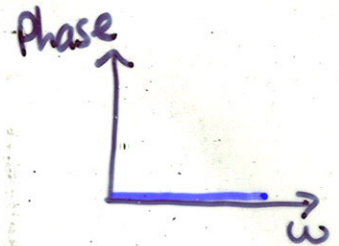




FREQUENCY RESPONSE

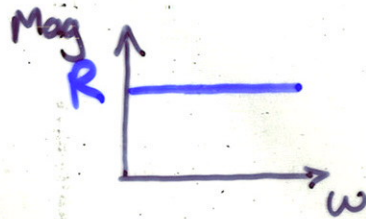



$$Z = R$$



$$Z = j\omega L$$

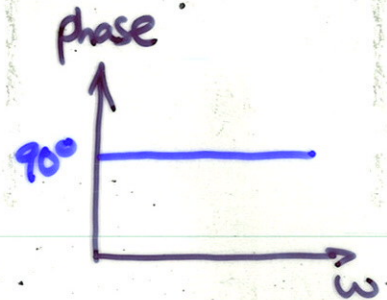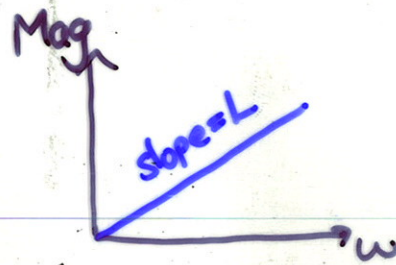

$$Z = \frac{1}{j\omega C}$$

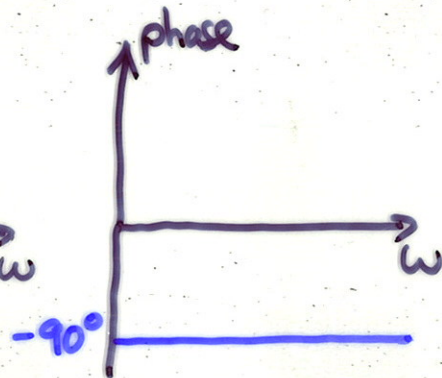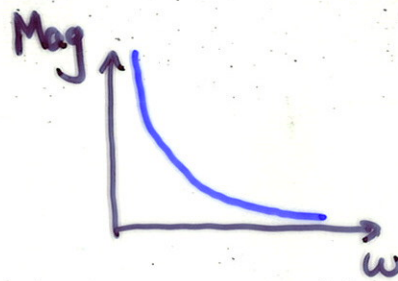


Consider the following circuit



Find $V_{out}(t)$ if circuit is in the steady state and
 $V_{in}(t) = A \cos(\omega t + \theta)$

Phasor equivalent

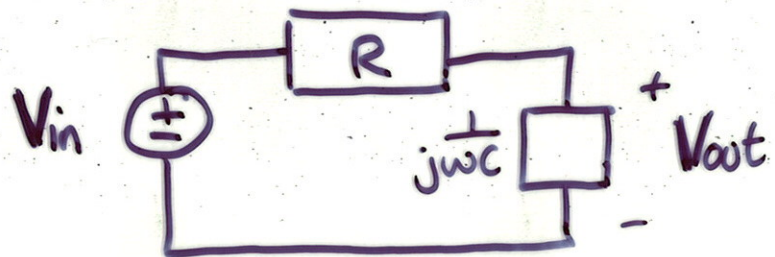

By voltage division:

$$\begin{aligned}
 V_{out} &= \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in} \\
 &= \frac{1}{1 + j\omega CR} V_{in} \\
 &= \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}} e^{-j \tan^{-1}(\omega CR)} V_{in} \\
 &= \frac{A}{\sqrt{1 + \omega^2 C^2 R^2}} e^{j(\theta - \tan^{-1}(\omega CR))}
 \end{aligned}$$

$$\Rightarrow V_{out}(t) = \frac{A}{\sqrt{1 + \omega^2 C^2 R^2}} \cos(\omega t + \theta - \tan^{-1}(\omega CR))$$

Look at magnitude : $\frac{A}{\sqrt{1+\omega^2 R^2 C^2}}$

At low frequencies $\approx A$

At high frequencies $\approx \frac{A}{\omega RC}$



At $(\omega = \frac{1}{RC})$ $= \frac{A}{\sqrt{2}}$

Look at phase $\theta - \text{atan}(\omega RC)$


At low frequencies $\approx \theta$

At high frequencies $\approx \theta - 90^\circ$

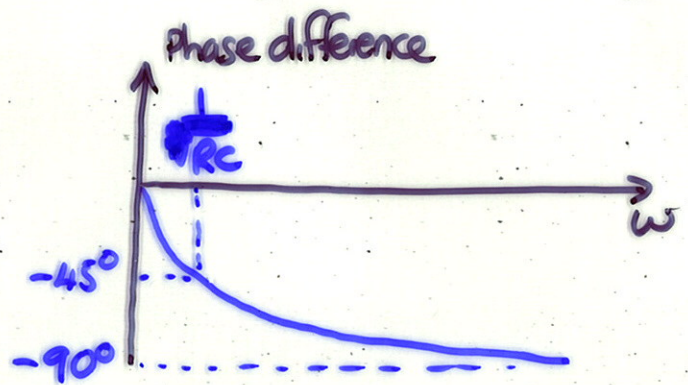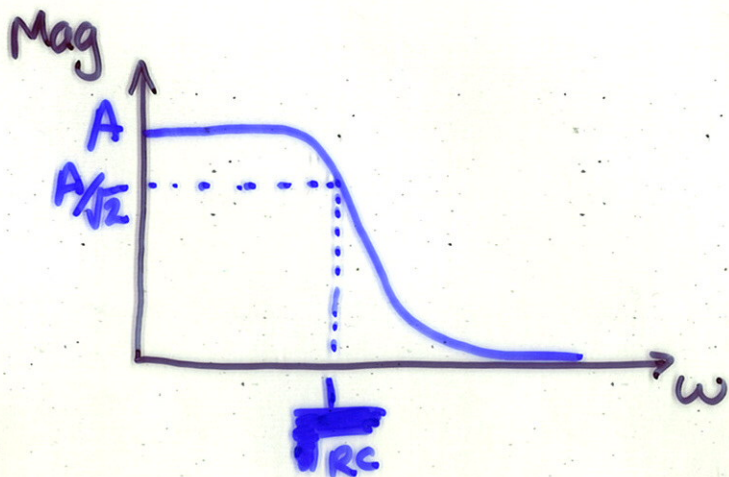
At $(\omega = \frac{1}{RC})$ $= \theta - 45^\circ$



Now what about:

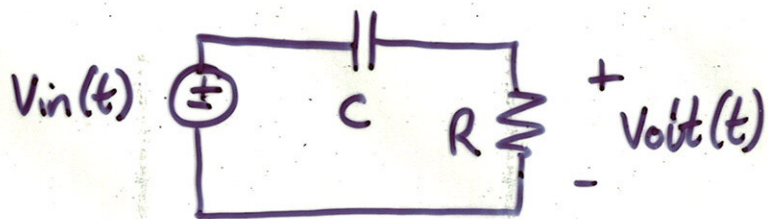

Phasor domain

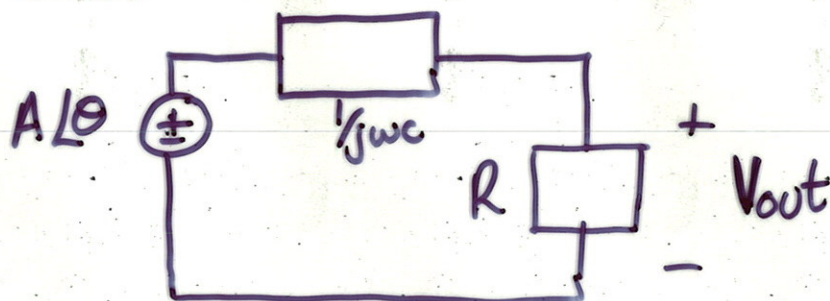

$$V_{out} = \frac{R}{R + \frac{1}{j\omega C}} \cdot A\angle\theta$$

$$= \frac{j\omega CR}{1 + j\omega CR} A\angle\theta$$

$$= \frac{\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}} e^{j(90^\circ - \arctan(\omega CR))} A e^{j\theta}$$

$$\Rightarrow V_{out}(t) = \frac{A\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}} \cos(\omega t + \theta + 90^\circ - \arctan(\omega CR))$$

MAGNITUDE

$$\frac{AwCR}{\sqrt{1+\omega^2 C^2 R^2}}$$

At low frequencies $\approx AwCR$

At high frequencies $\approx \frac{AwCR}{\omega CR} = A$



$$At(\omega = \frac{1}{RC}) = \frac{A}{\sqrt{2}}$$

Phase difference: $90^\circ - \text{atan}(\omega CR)$



At low frequencies $\approx 90^\circ$

At high frequencies $\approx 0^\circ$

$$At(\omega = \frac{1}{RC}) = 45^\circ$$

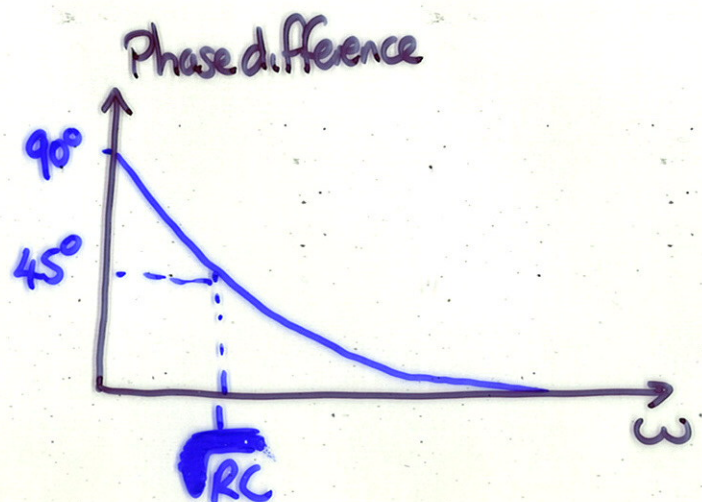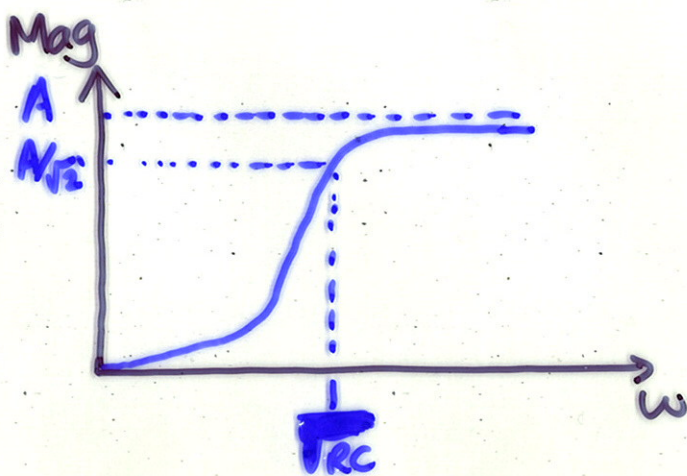

RELATED CIRCUITS

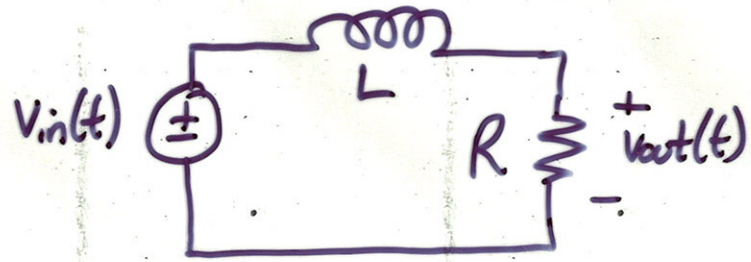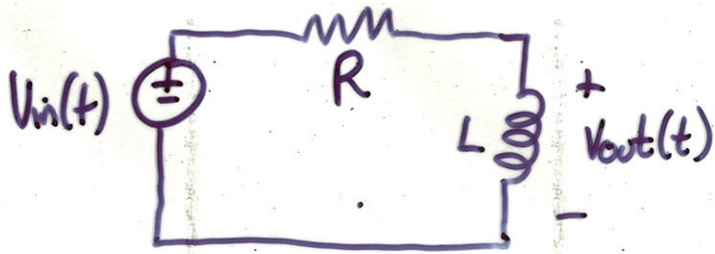


SHOW THAT:


$$\frac{V_{out}}{V_{in}} = \frac{j\omega L/R}{1 + j\omega L/R}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega L/R}$$

ANOTHER EXAMPLE

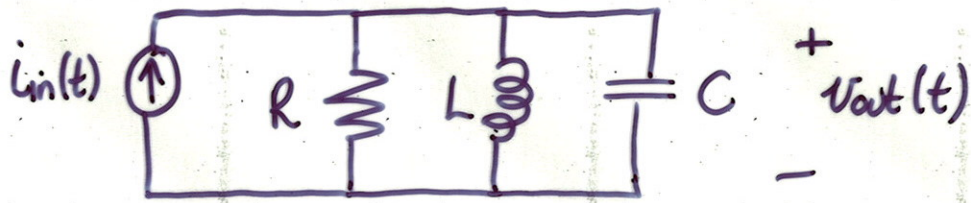

Find: $\frac{V_{out}}{I_{in}}$

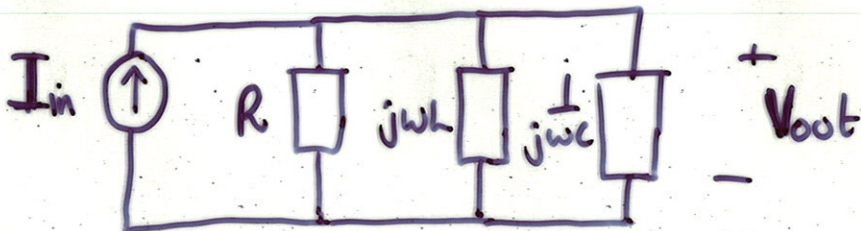

$$V_{out} = Z_{eq} \cdot I_{in}$$

$$\frac{1}{Z_{eq}} = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$= \frac{RL/C}{R + j(\omega L - 1/\omega C)}$$

$$= \frac{RL/C}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} e^{-j \tan^{-1}(\omega L - 1/\omega C)/R}$$

MAGNITUDE

$$\frac{RLC}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

At low frequencies $\approx \omega L R$

At high frequencies $\approx \frac{R}{\omega C}$

Where is the max magnitude?



where $\omega L - 1/\omega C = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$


Phase difference $-\text{atan}((\omega L - 1/\omega C)/R)$

At low frequencies $\approx 90^\circ$

At high frequencies $\approx -90^\circ$

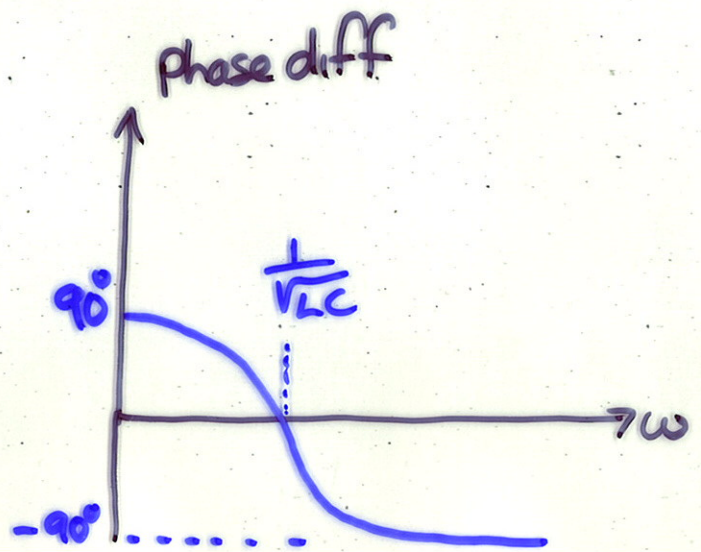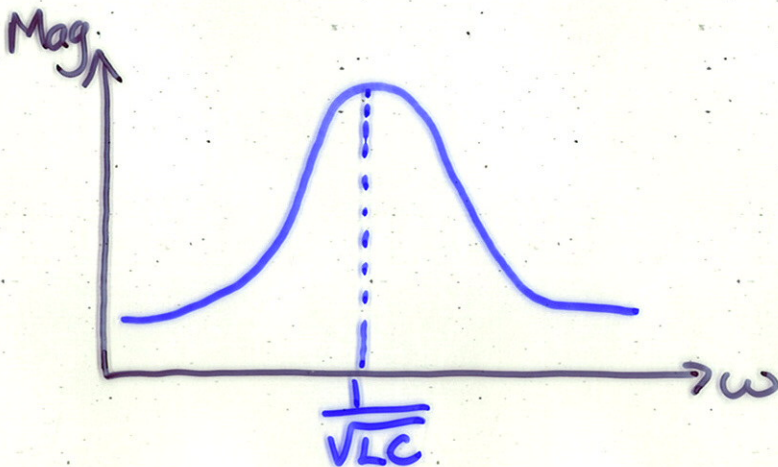At $(\omega = \frac{1}{\sqrt{LC}})$ $= 0^\circ$



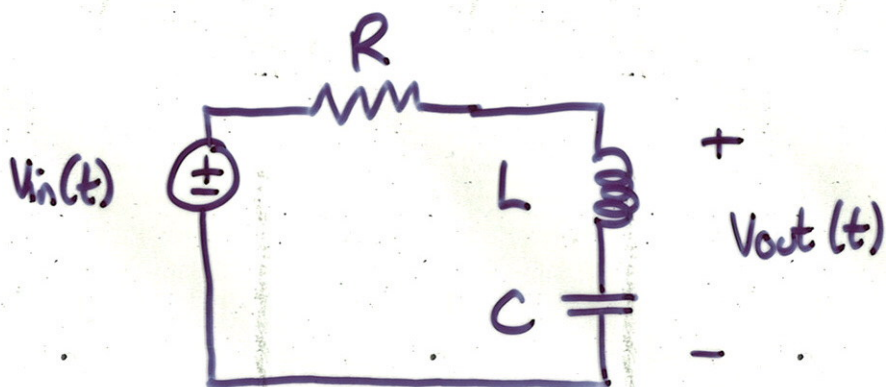

Show that this circuit has a band stop characteristic

Hint: First show that

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{LC} - \omega^2}{\frac{1}{LC} - \omega^2 + j\omega R/L}$$