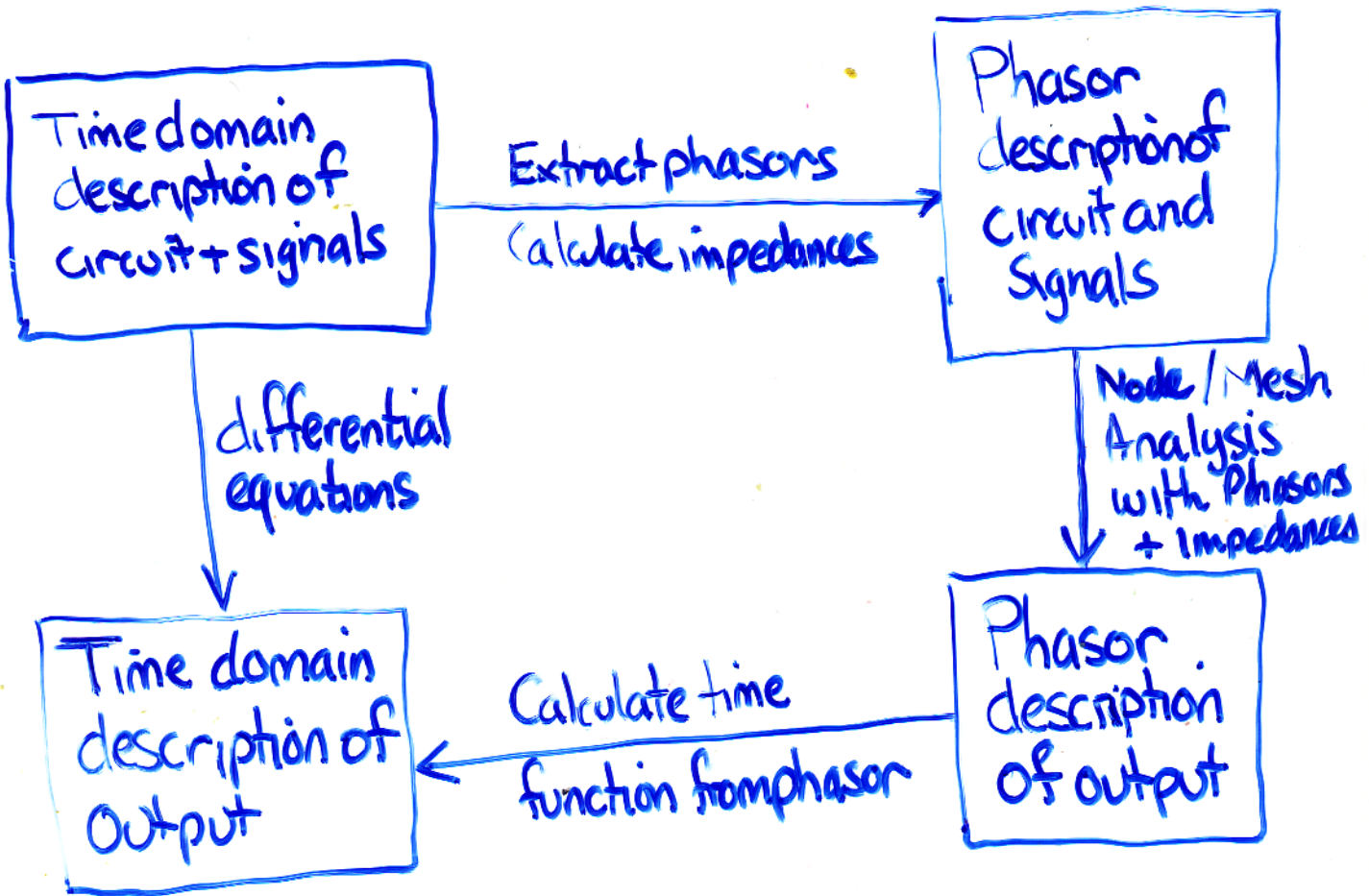


Simplified Analysis of Linear Circuits with Sinusoidal inputs in steady-state using phasors




Why does this work?

How do phasors allow us to avoid differential equations?

Phasor analysis examples

The following circuit is in the steady state.

Find $v_o(t)$

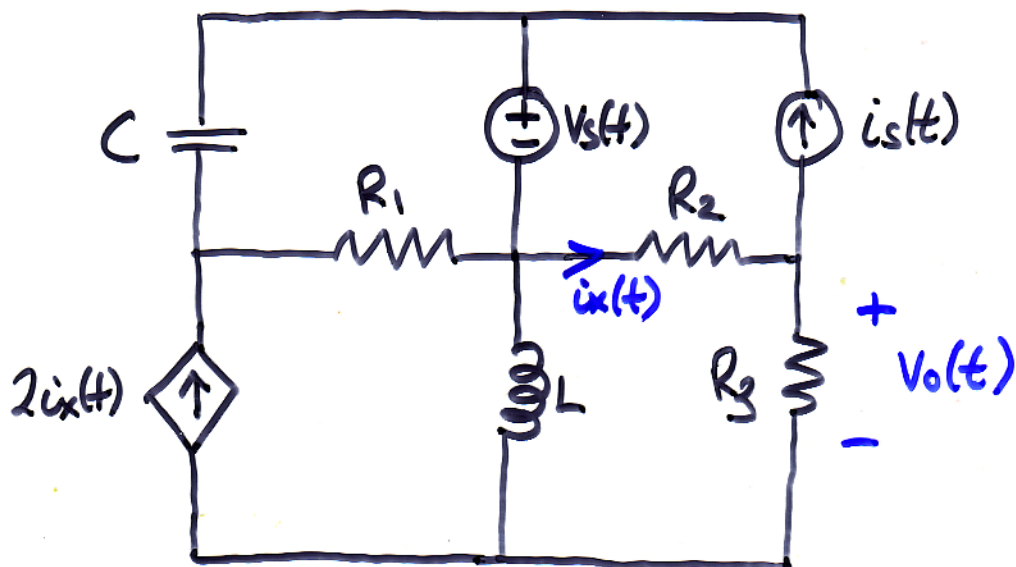

$$v_s(t) = 12 \cos(100t)$$

$$i_s(t) = 4 \cos(100t)$$

$$R_1 = R_2 = R_3 = 1 \Omega$$


$$C = 10 \text{ mF}$$

$$L = 10 \text{ mH}$$

STEP 1:

- Identify that circuit is in steady state
- Identify that all sources are sinusoidal with the same frequency, 100 rad/s^{-1}
- Therefore we can solve via phasor analysis

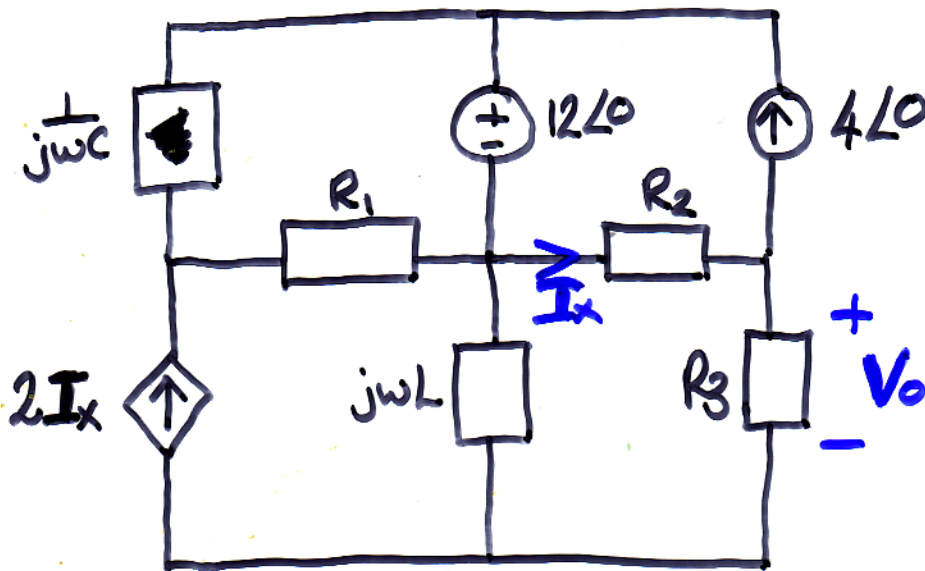STEP 2: Draw phasor equivalent circuit at 100 rad/s^{-1}




STEP 3: Solve for V_o

- Node, Mesh, Thevenin, Norton

STEP 4: Convert V_o to $v_o(t)$

STEP 3, Node analysis

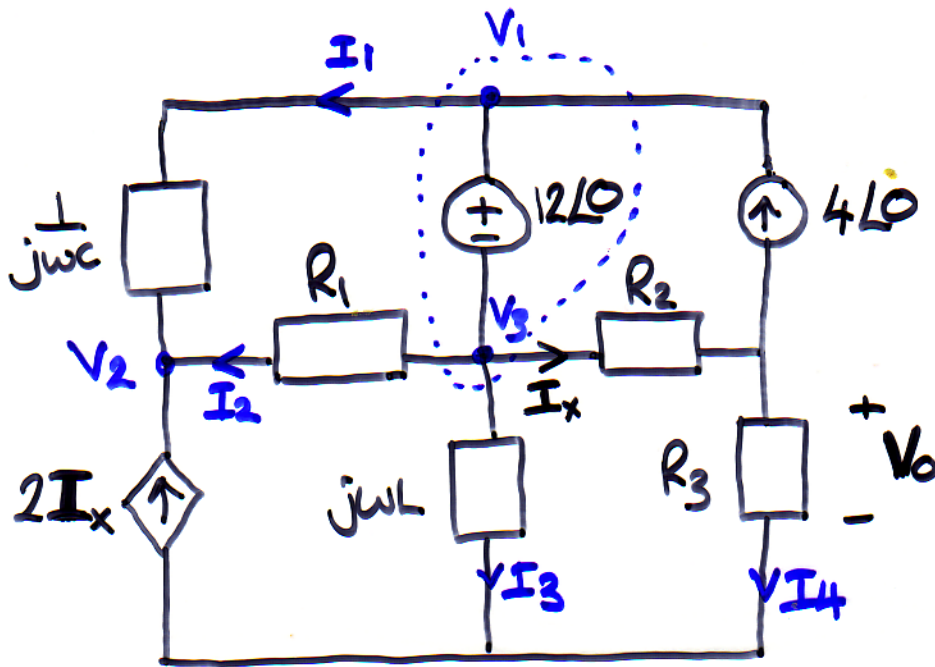

KCL at supernode:

$$I_1 + I_2 + I_x - 4L_0 = 0$$

KCL at node 2: $I_1 + I_2 + 2I_x = 0$

KCL at output node: $I_x - 4L_0 - I_4 = 0$

Inside supernode: $V_1 - V_3 = 12L_0$


Elements:

$$I_1 = \frac{V_1 - V_2}{1/jwc} = jwc(V_1 - V_2)$$

$$I_2 = (V_3 - V_2)/R_1; \quad I_4 = V_0/R_3$$

$$I_3 = \frac{V_3}{jwL}; \quad I_x = (V_3 - V_0)/R_2$$

STEP 3, MESH ANALYSIS

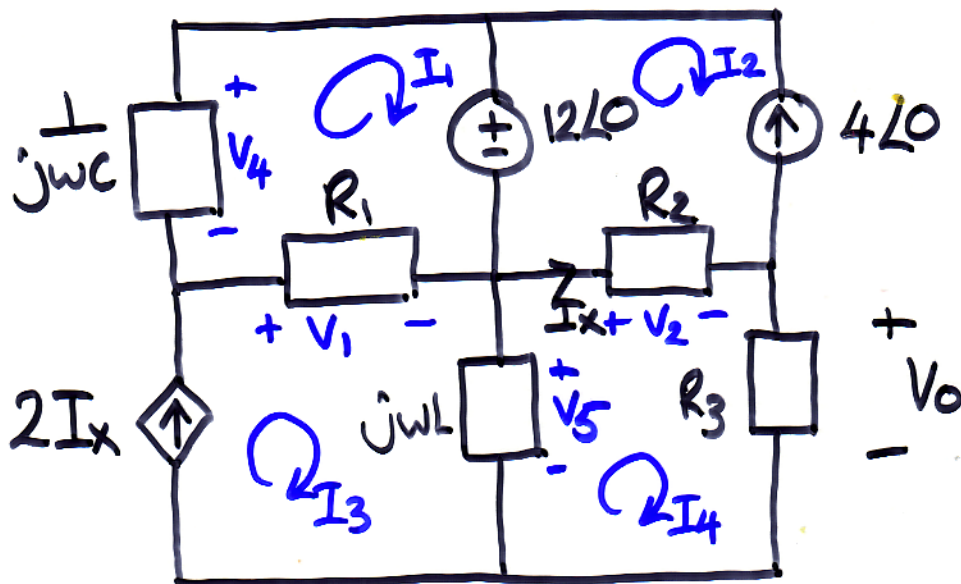

$$I_2 = -4L_0$$

$$I_3 = 2I_x \quad ; \quad I_x = I_4 - I_2$$

KVL loop 1 $-V_4 + 12L_0 - V_1 = 0$

KVL loop 4 $-V_5 + V_2 + V_0 = 0$

Elements

$$V_1 = R_1(I_3 - I_1)$$

$$V_2 = R_2(I_4 - I_2)$$

$$V_0 = R_3 I_4$$

$$V_4 = -\frac{1}{jwc} I_1$$

$$V_5 = jwL(I_3 - I_4)$$

STEP 3, solving equations

yields

$$V_0 = 4 \angle 143.13^\circ$$


STEP 4, convert back to time domain

$$v_0(t) = 4 \cos(100t + \blacksquare 143.13^\circ)$$

SUPER POSITION

- * When the circuit contains sources with more than one frequency, we must use superposition
- * However, superposition applies only to the time domain signals, we cannot superpose the phasors if they apply to signals with different frequencies
- * For circuits with sources of more than one frequency, we must.
 1. Collect sources into groups with same frequency
 2. Use phasor analysis for each group alone
 3. Calculate time responses for each group alone
 4. Add time responses.

EXAMPLE:

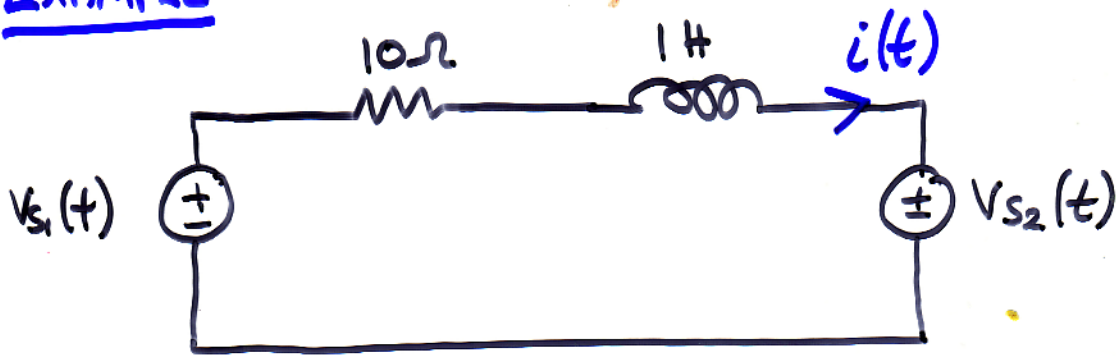


The above circuit is in the steady state.

Find $i(t)$, when $V_{s_1}(t) = 100 \cos(10t)$


$$V_{s_2}(t) = 50 \cos(20t - 10^\circ)$$

- STEP 1**
- I identify that the circuit is in the steady-state
 - I identify that there are two sinusoidal sources of different frequencies
- ⇒ Solve via superposition in time domain
- For each frequency use phasor analysis.

For the 10 rad s^{-1} source:

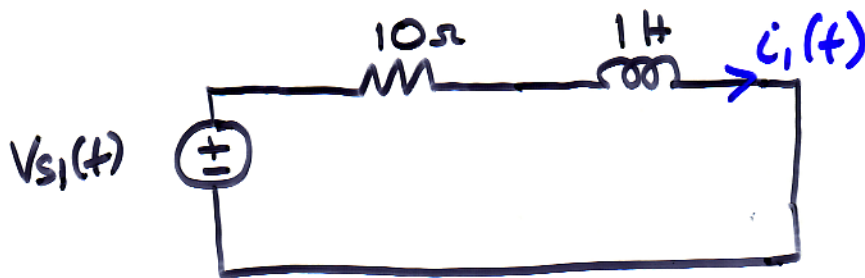


Phasor domain equivalent

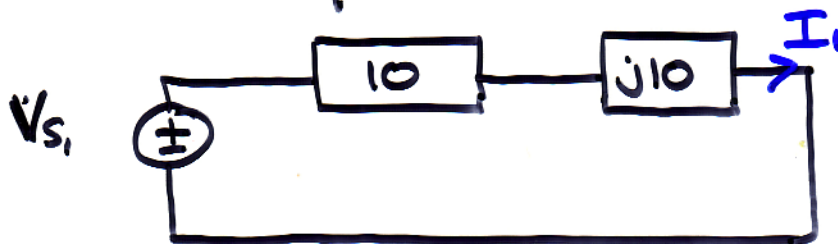


$$I_1 = \frac{V_{s1}}{10 + j10} = \frac{100 \angle 0}{10 + j10} = 7.07 \angle -45^\circ$$

$$\Rightarrow i_1(t) = 7.07 \cos(10t - 45^\circ)$$

For the 20 rad s^{-1} source

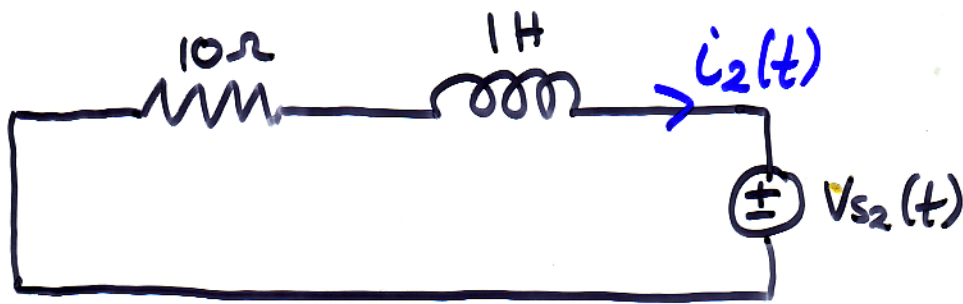

Phasor domain equivalent

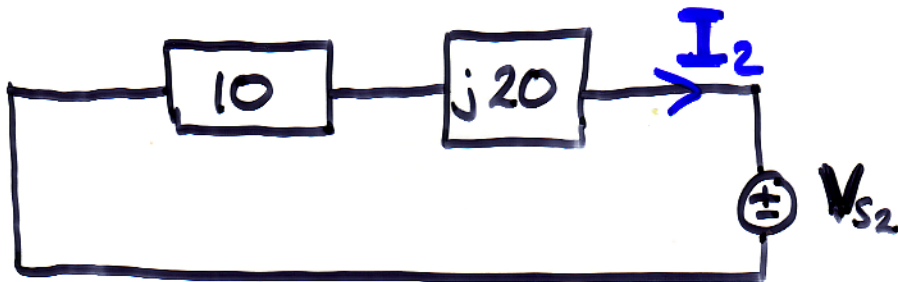


$$I_2 = \frac{-V_{s2}}{10 + j20} = \frac{-50 \angle -10^\circ}{10 + j20} = 2.24 \angle 106.6^\circ$$

$$\Rightarrow i_2(t) = 2.24 \cos(20t + 106.6^\circ)$$

Final answer

$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ &= 7.07 \cos(10t - 45^\circ) + 2.24 \cos(20t + 106.6^\circ) \end{aligned}$$

EXAMPLE

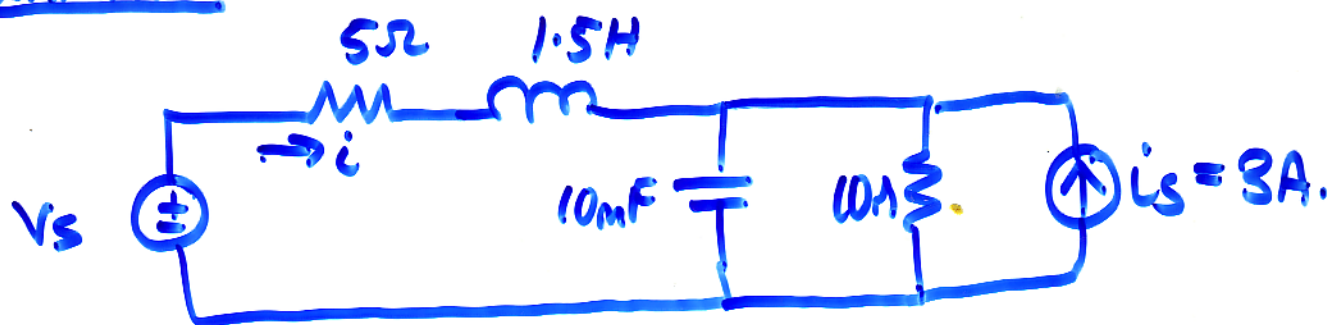

$$V_s = 10 \cos 10t.$$

Find $i(t)$.

Step 1 - look at V_s alone.

$$\underline{V}_s = 10$$

using phasor analysis, we find that

$$\underline{I}_1 = \frac{10}{\sqrt{200}} e^{-j45^\circ}$$

where \underline{I}_1 is the component of \underline{I} , due to \underline{V}_s

$$\text{Hence } i_1(t) \approx 0.71 \cos(10t - 45^\circ)$$

Step 2 - I_s alone

$$\underline{I}_s = 3, \text{ actually this is DC!}$$

$$\text{can find that } \underline{I}_2 = -2. \Rightarrow i_2(t) = -2$$

Step 3 - Add time domain

$$i(t) = i_1(t) + i_2(t) = 0.71 \cos(10t - 45^\circ) - 2 \text{ A.}$$