
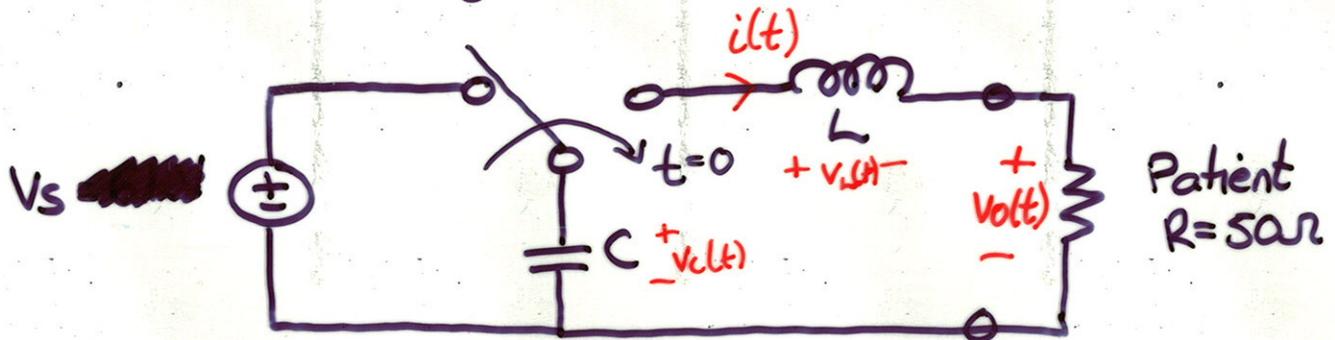


BUILDING A DEFIBRILLATOR

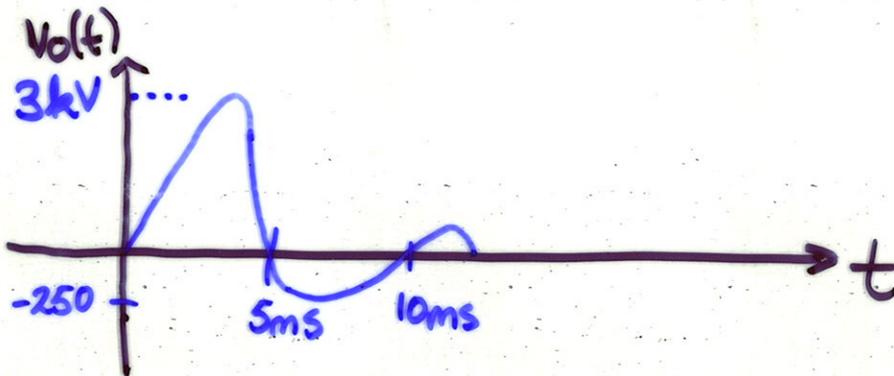~~Desired~~
Circuit topology (Lown defibrillator)




Desired response



Design L and C so that this is well approximated

This will also require design of V_s

After the switch

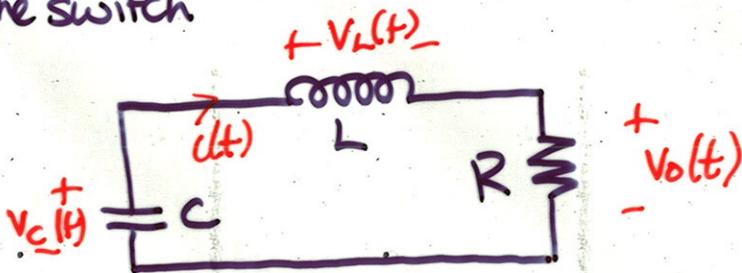

KVL $-v_C(t) + v_L(t) + v_R(t) = 0$

$$-v_C(t) + \frac{1}{C} \int_0^t i(x) dx + L \frac{di(t)}{dt} + Ri(t) = 0$$

Differentiate and divide by L.

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

We need an underdamped circuit, i.e., $\zeta < 1$

$$\Rightarrow \frac{R/L}{2\sqrt{1/LC}} < 1$$

$$\Rightarrow C < 4L/R^2$$

For an underdamped circuit, with no source.

$$i(t) = A_1 e^{-\sigma t} \cos(\omega_d t) + A_2 e^{-\sigma t} \sin(\omega_d t)$$

where

$$\omega_d = \omega_0 \sqrt{1 - \zeta^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\sigma = \zeta \omega_0 = \frac{R}{2L}$$

Since in this circuit, the inductor current at $t=0^-$ is zero, this means that $i(0^+) = 0$

$$\text{Hence } A_1 = 0$$

Therefore, this circuit has a response

$$i(t) = A_2 e^{-\sigma t} \sin(\omega_d t)$$

and hence

$$v(t) = R A_2 e^{-\sigma t} \sin(\omega_d t)$$

- what should ω_d be?

Period desired is 10ms

$$\Rightarrow \omega_d = \frac{2\pi}{10 \times 10^{-3}}$$

$$\Rightarrow \omega_0 \sqrt{1 - \zeta^2} = 200\pi \quad \textcircled{A}$$

- what should σ be?

Evaluate where $\sin(\omega_d t) = \pm 1$

That is, $t = T/4$ and $t = 3T/4$

From expression:
$$\frac{V_o(T/4)}{-V_o(3T/4)} = \frac{RA_2 e^{-\sigma T/4}}{RA_2 e^{-\sigma 3T/4}} = e^{\sigma T/2}$$

From desired: $V_o(T/4) = 3000$; $V_o(3T/4) = -250$

$$\Rightarrow e^{\sigma T/2} = \frac{3000}{250} = 12$$

$$\Rightarrow \zeta \omega_0 = 497.0 \quad \textcircled{B}$$

From (B) we have

$$\gamma_{wo} = \frac{R}{2L} = 497.0$$

Since $R = 50 \Omega$, we have

$$L = 50.3 \text{ mH}$$

From (A) we have

$$\omega_0^2 - (\omega_d)^2 = (200\pi)^2$$

$$\Rightarrow \frac{1}{LC} = (200\pi)^2 + (497.0)^2$$

Hence

$$C = 31.0 \mu\text{F}$$

Sanity check: Is circuit underdamped?

ie., is $C < 4L/R^2$?

$$C = 31.0 \times 10^{-6}$$

$$4L/R^2 = 80.5 \times 10^{-6}$$

We still have to design V_s

To do so, we need to find the required value of A_2

Requirement is


$$V_o(T/4) = 3000$$

$$V_o(t) = RA_2 e^{-\sigma t} \sin(\omega t)$$

$$\Rightarrow \text{we require } RA_2 e^{-\sigma T/4} = 3000$$

$$\Rightarrow A_2 = 207.86$$

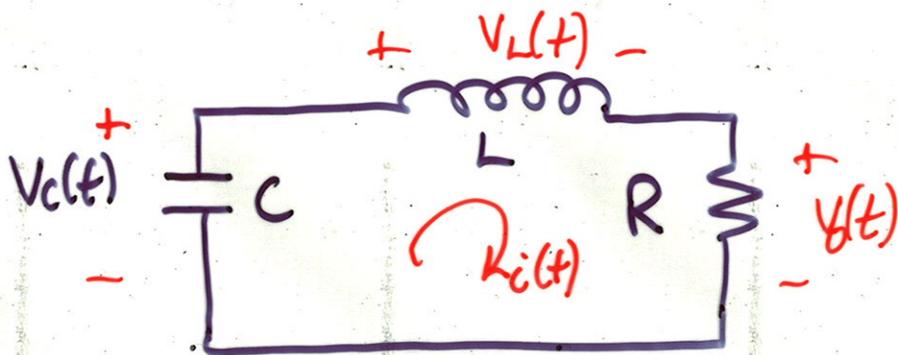Now, how to choose V_s such that $A_2 = 207.86$?



$$i(t) = A_2 e^{-\sigma t} \sin(\omega t)$$

$$V_L(t) = L \frac{di(t)}{dt}$$

$$= LA_2 \left[(-\sigma e^{-\sigma t}) \sin(\omega t) \right.$$

$$\left. + e^{-\sigma t} \omega \cos(\omega t) \right]$$

What happens at $t=0$?

$$i(0) = 0 \Rightarrow V_r(t)|_{t=0} = 0$$

$$\Rightarrow \text{at } t=0 \quad \cancel{V_r} = V_L(t)|_{t=0} = V_c(t)|_{t=0}$$

$$\text{but } V_c(t)|_{t=0} = V_s$$

Therefore, we can find the required value for V_s by solving

$$V_s = V_L(0)$$

$$= LA_2 \omega d$$

$$= 50.3 \times 10^{-3} \times 207.86 \times 200\pi$$

$$= 6.569 \text{ kV}$$