
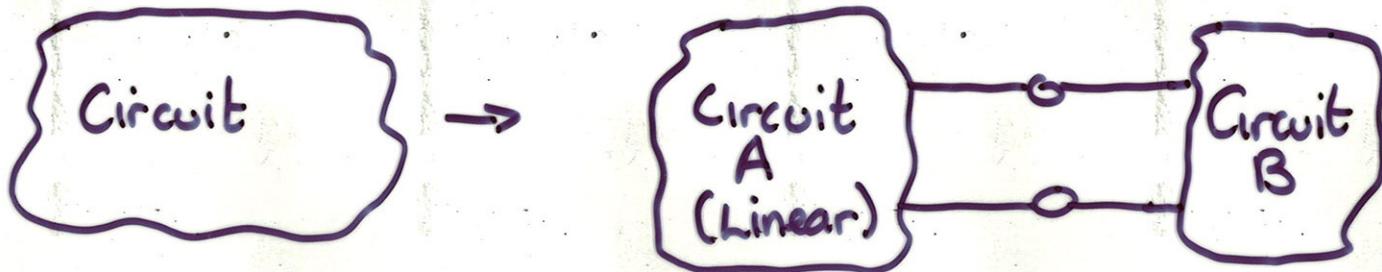

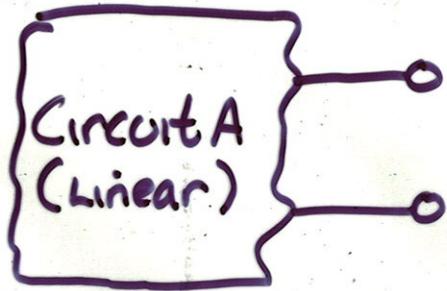
## THEVENIN & NORTON EQUIVALENTS

- a structured "divide and conquer" approach
- Partition the circuit



- We would like to build a simplified model for circuit A.
  - Very useful if you need to solve several circuits in which A is the same, but B changes
- Example: A models source & distribution network  
B models the load.




We want a model for Circuit A that is

- Simple
- Indistinguishable from Circuit A from the perspective of the terminals

How to do this?

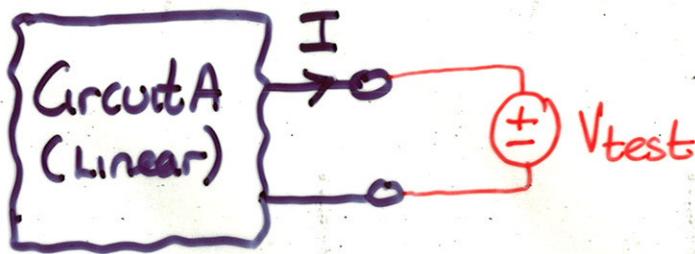- Apply a test voltage
- Apply superposition
- Interpret result in circuit form




By superposition:  $I = I_{\text{test}} + I_{\text{sc}}$

$I_{\text{test}}$ : current due to  $V_{\text{test}}$  alone; i.e., all independent sources in Circuit A turned off

$I_{\text{sc}}$ : current due to ~~not~~ sources in Circuit A alone; i.e.,  $V_{\text{test}}$  turned off; i.e.,  $V_{\text{test}}$  replaced by short circuit

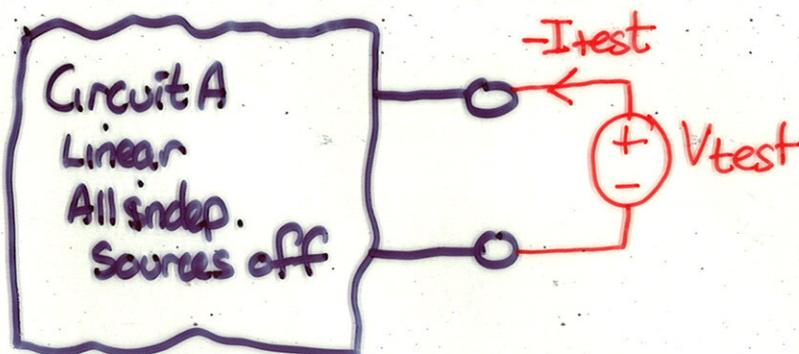What is  $\frac{V_{\text{test}}}{-I_{\text{test}}}$  ?



This is the equivalent resistance of the circuit  
Called  $R_{\text{TH}}$

$$\Rightarrow I = -\frac{V_{\text{test}}}{R_{\text{TH}}} + I_{\text{sc}}$$

Now consider the case in which  $V_{test} = R_{TH} I_{sc}$

$$\Rightarrow I = 0$$

$\Rightarrow$  terminals act like an open circuit


Let's call  $R_{TH} I_{sc} = V_{oc}$

$$\Rightarrow I = -\frac{V_{test}}{R_{TH}} + \frac{V_{oc}}{R_{TH}}$$

Alternatively,  $-V_{oc} + R_{TH}I + V_{test} = 0$

What is the circuit realization of that equation?


Previously

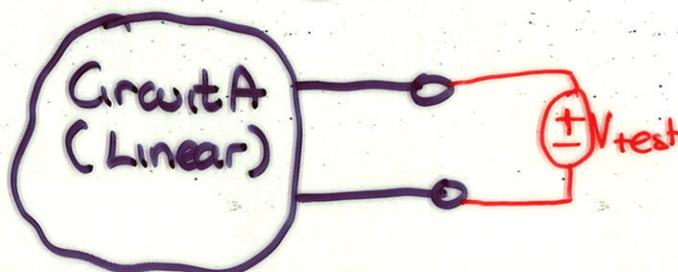

Now



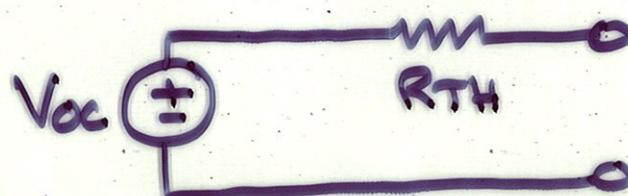Hence, the Thevenin equivalent of Circuit A is





Circuit B cannot tell the difference between Circuit A and its Thevenin equivalent


In the previous analysis, we also had the equation

$$I = I_{sc} - \frac{V_{test}}{\sum R_{TH}}$$

What is the circuit realization?

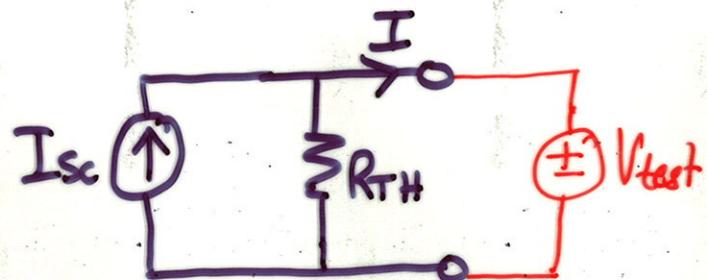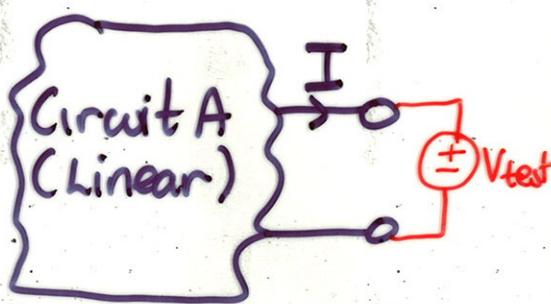

Hence Norton equivalent of Circuit A.

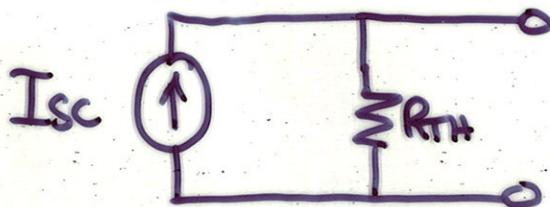

Circuit B cannot tell the difference between Circuit A, the Thevenin equiv and the Norton equiv.

From the perspective of Circuit B,  
Thevenin & Norton circuits are equivalent



Are they equivalent in a more general setting?

## CIRCUIT ANALYSIS WITH THEV. & NORT. EQUIVS

1. Partition the ~~circuit~~ circuit into circuits A and B
  - For all dependent sources, make sure that the controlling current or voltage is in the same partition
2. Construct the Thevenin or Norton equivalent of Circuit A.
3. Analyze Circuit B


# GENERAL RECIPE FOR THEVENIN

Norton recipe is analogous

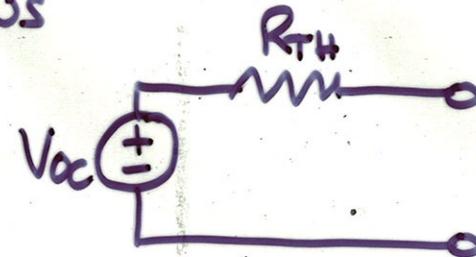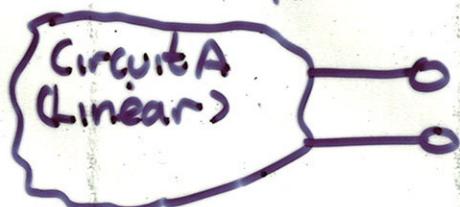


① Find  $V_{oc}$

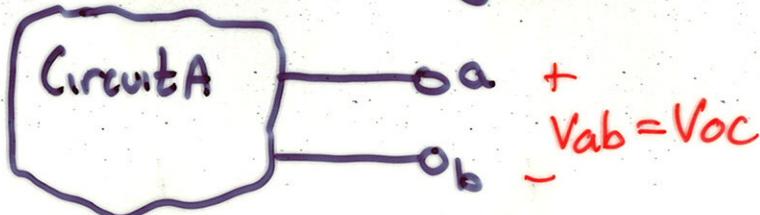That is, solve the following circuit for  $V_{ab}$ .



② Find  $I_{sc}$

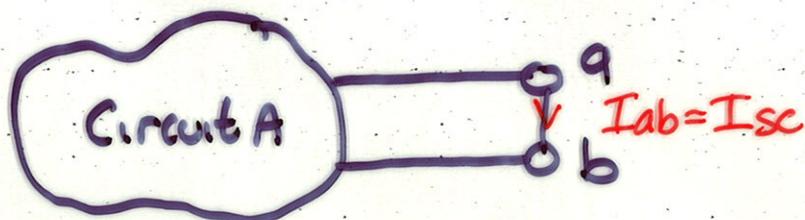
That is, solve the following circuit for  $I_{ab}$



③ Find  $\boxed{R_{Th}}$

If  $I_{sc} \neq 0$ ,  $R_{Th} = \frac{V_{oc}}{I_{sc}}$


If  $I_{sc} = 0$ , Solve

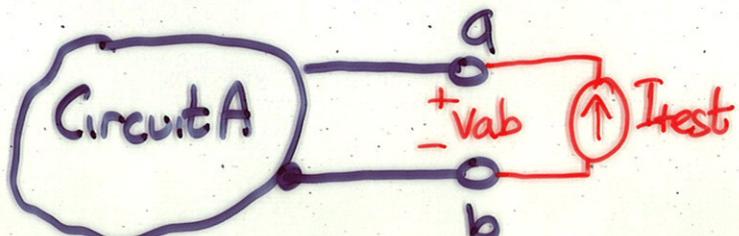

$$R_{Th} = \frac{V_{ab}}{I_{test}}$$

Example:

Find the Thevenin equivalent of.

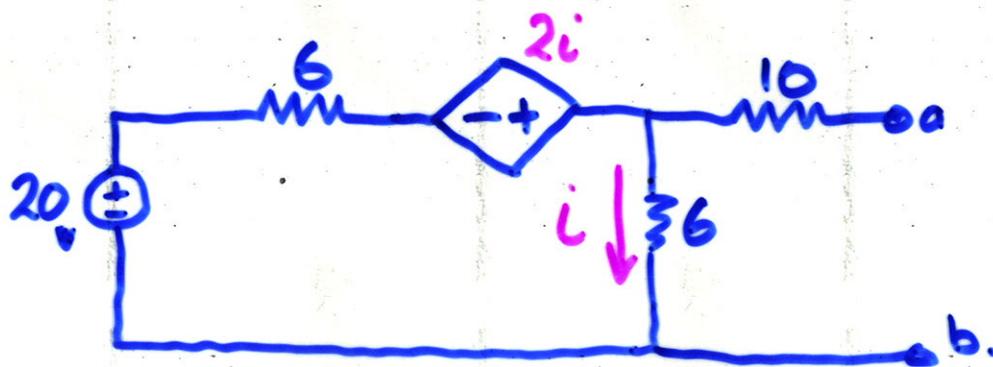

Need to find  $V_{oc}$  and  $I_{sc}$

For  $V_{oc}$ : KVL around left mesh. (no current in right mesh)

$$-20 + 6i - 2i + 6i = 0.$$


$$\Rightarrow i = 2A$$

KVL around right mesh. (no current in right mesh)

$$-6i + 10 \times 0 + V_{ab} = 0.$$

$$\Rightarrow V_{ab} = V_{oc} = 12V$$

Find  $I_{sc}$ .

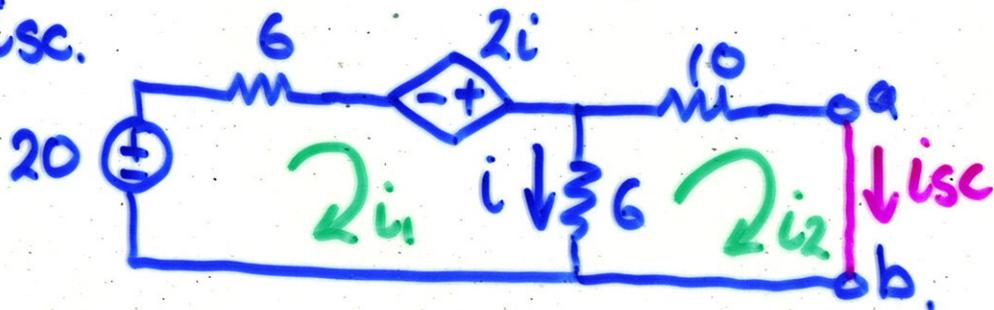

KVL on both meshes

$$-20 + 6i_1 - 2i + 6(i_1 - i_2) = 0$$

$$6(i_2 - i_1) + 10i_2 = 0$$

2 equations, 3 unknowns !!!

$$i = i_1 - i_2$$


Now can solve

$$\begin{aligned} 10i_1 - 4i_2 &= 20 \\ -6i_1 + 16i_2 &= 0 \end{aligned}$$

$$\Rightarrow i_2 = i_{SC} = 120/136 \text{ A.}$$

$$\Rightarrow R_t = \frac{V_{OC}}{i_{SC}} = \frac{12}{120/136} = 13.6 \Omega.$$

$\Rightarrow$  Thevenin equivalent

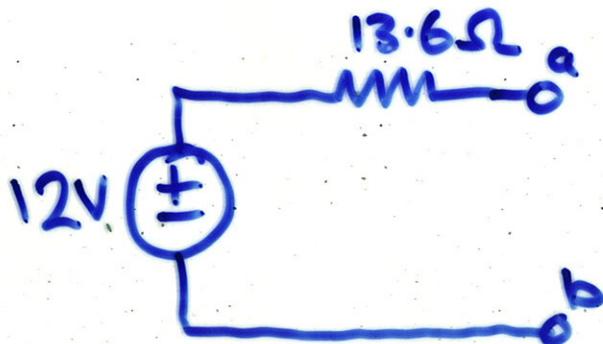

## SPECIAL RECIPE FOR THEVENIN.

### - WHEN ONLY INDEPENDENT SOURCES

① FIND  $V_{OC}$

② Turn "off" all sources

$R_{TH}$  is the equivalent resistance looking  
into the terminals

(Find this by series and parallel combinations)

### - WHEN ONLY DEPENDENT SOURCES

①  $V_{OC} = 0$ . why?

② FIND  $R_{TH}$  by the "test-based" method