

## Phasor Analysis

Since coupled inductors are often used in linear circuits with sinusoidal signals in the steady-state we would like to look at the equations in the phasor domain.

Since differentiation corresponds to multiplying by the phasor by  $j\omega$ .

$$\begin{aligned} \underline{V}_1 &= j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2 \\ \underline{V}_2 &= j\omega L_2 \underline{I}_2 + j\omega M \underline{I}_1 \end{aligned} \quad \left. \vphantom{\begin{aligned} \underline{V}_1 &= j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2 \\ \underline{V}_2 &= j\omega L_2 \underline{I}_2 + j\omega M \underline{I}_1 \end{aligned}} \right\} \text{coupled circuit 1}$$

and similarly for coupled circuit 2, except that the mutual terms subtract rather than add.

## Coupler Design.

A useful measure of the effectiveness of a coupling device is the "coupling coefficient"

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

using the formulae for  $L_1, L_2, M$ ,

$$k = \frac{C_M}{\sqrt{C_1 C_2}} \quad \text{which depends only on the magnetic + geometric structure}$$

- \* For good coupling we want  $k$  to be large.  
 i.e. we choose materials and shapes to achieve that.
- \* To assess the quality of the design, we need to know how big  $k$  can be.

~~\* We do so for the case of~~

- \* The instantaneous power absorbed by the coupled circuit is

$$\begin{aligned}
 p(t) &= v_1(t) i_1(t) + v_2(t) i_2(t) \\
 &= L_1 i_1(t) \frac{d}{dt} i_1(t) \pm M \frac{d}{dt} (i_1(t) i_2(t)) \\
 &\quad + L_2 i_2(t) \frac{d}{dt} i_2(t)
 \end{aligned}$$

+ for coupled circuit 1  
 - for coupled circuit 2

- \* The energy stored in the system is

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

- \* Since the system is passive (i.e. does not generate power)  $w(t)$  must be  $\geq 0$



Taking the worst case (coupled circuit 2), we must have

$$\frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2 \geq 0$$

This can be algebraically manipulated to.

$$\left( \sqrt{\frac{L_1}{2}} i_1 - \sqrt{\frac{L_2}{2}} i_2 \right)^2 + i_1 i_2 (\sqrt{L_1 L_2} - M) \geq 0 \quad (*)$$

This term is  $\geq 0$   
but can be zero  
in many applications

$\Rightarrow$  to ensure that  $(*)$  holds, we require

$$M \leq \sqrt{L_1 L_2}$$


Hence  $0 \leq k \leq 1$

Power transformers have  $k \rightarrow 1$

Coupled ~~radio~~ radio circuits have small  $k$ .
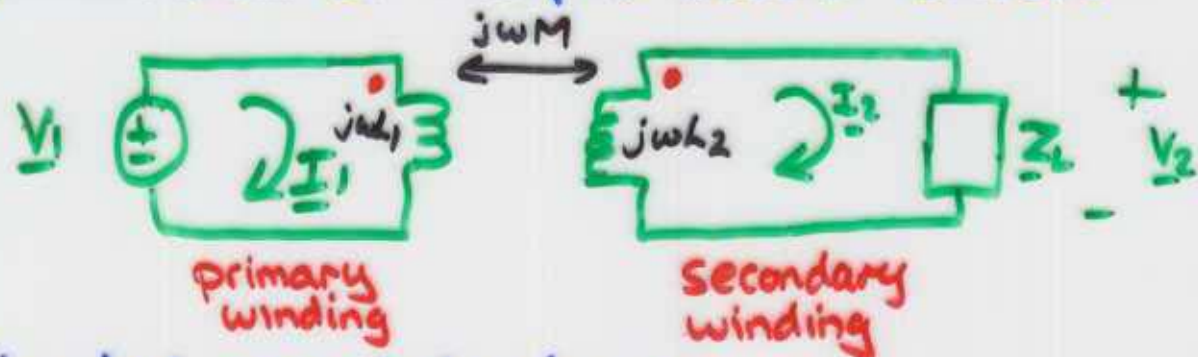
## Applications of magnetic coupling.

Consider the following "phasor domain" representation of a coupled inductor circuit



Writing KVL around the loops



$\underline{I}_1$  enters dotted terminal  
 $\underline{I}_2$  leaves dotted terminal

$$\text{Hence } \underline{I}_2 = \left[ \frac{j\omega M}{(j\omega)^2(L_1 L_2 - M^2) + j\omega L_1 Z_L} \right] \underline{V}_1$$

If the coupling coefficient  $\rightarrow 1$ , then  $L_1 L_2 \rightarrow M^2$

In that case,

$$\begin{aligned} \underline{I}_2 &= \left[ \frac{j\omega M}{j\omega L_1 Z_L} \right] \underline{V}_1 = \left( \frac{j\omega \sqrt{L_1 L_2}}{j\omega L_1 Z_L} \right) \underline{V}_1 \\ &= \frac{\sqrt{L_2}}{Z_L \sqrt{L_1}} \underline{V}_1 \end{aligned}$$

Hence 
$$\underline{V}_2 = \underline{Z}_L \underline{I}_2 = \sqrt{\frac{L_2}{L_1}} \underline{V}_1$$

Now 
$$\frac{L_2}{L_1} = \frac{C_2 N_2^2}{C_1 N_1^2}$$

If the geometry + the magnetic properties of the core are the same ~~or~~ for both coils,  $C_1 = C_2$

In that case.

$$\underline{V}_2 = n \underline{V}_1 \quad \textcircled{1}$$

where  $n = \frac{N_2}{N_1}$  is the "turns ratio"

$$\text{Similarly, } \underline{I}_1 = -n \underline{I}_2 \quad \textcircled{2}$$

Equations  $\textcircled{1}$  and  $\textcircled{2}$  describe the operation of an ideal transformer, which we now study in more detail.