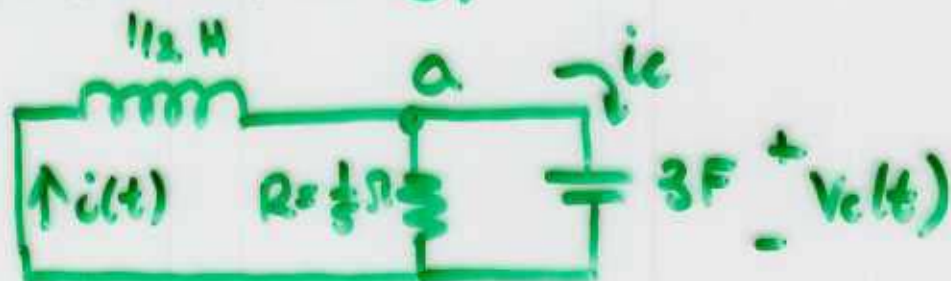


Using Laplace Transforms for Circuit Analysis

We will look at two methods.


- ① Write differential equations for the circuit, then solve using transforms
- ② Develop notions of impedance in "s-domain" to avoid having to write differential equations.

An example of method ①.



Find $v_c(t)$, $t \geq 0$, if $v_c(0) = 12\text{ V}$
and $i(0) = 60\text{ A}$

KVL for left mesh

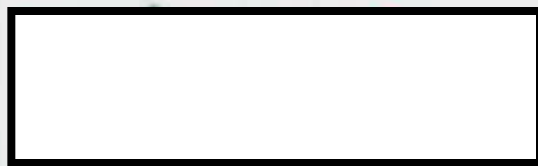

①

KCL, node a.



$$\Rightarrow C \frac{dV_c}{dt} + \frac{V_c}{R} - i = 0 \quad \text{②}$$

Take Laplace transforms of ① and ②.

$$L[sI(s) - i(0)] + V_c(s) = 0 \quad \text{③}$$

$$C[sV_c(s) - V_c(0)] + \frac{V_c(s)}{R} - I(s) = 0 \quad \text{④}$$

③ + ④ are two linear equations in two unknowns, $V_c(s)$ and $I(s)$

Solve for $V_c(s)$

$$V_c(s) = \frac{36s + 60}{3(s + \frac{2}{3})(s + 1)}$$

$$= \frac{36}{s + \frac{2}{3}} - \frac{24}{s + 1}$$

$$\Rightarrow V_c(t) = 36e^{-2t/3} - 24e^{-t}, \quad t \geq 0.$$

Method 2 - use impedance and initial conditions

* We have seen how useful the concept of impedance was for steady-state analysis of sinusoidal signals

* Now we want to do the same for general signals

+ Resistor $v(t) = R i(t)$
 $\Rightarrow V(s) = R I(s)$ $\left\{ \begin{array}{l} \text{take Laplace} \\ \text{transform of both} \\ \text{sides} \end{array} \right.$

* Suggests a notion of impedance in the "s-domain"

* Definition

If the initial current through an element and voltage across it are zero, the impedance is defined to be

$$Z(s) = \frac{V(s)}{I(s)}$$

In the case of the resistor, there is no initial condition to set.

Capacitor

$$v_c(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v_c(0) u(t)$$


Take Laplace transforms of both sides

$$V_c(s) = \frac{1}{Cs} I(s) + \frac{v_c(0)}{s}$$

⇒ Impedance is $\frac{1}{Cs}$


⇒ Equivalent models.

Time Domain

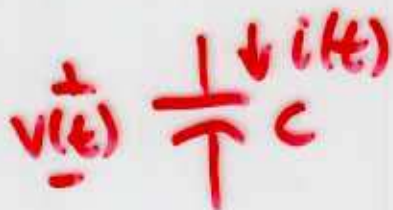

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v_c(0)$$

"s-domain"

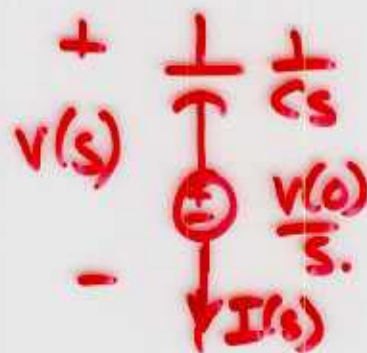


$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$

Since $V(s) = \frac{1}{Cs} I(s) + \frac{V(0)}{s}$

$\Rightarrow I(s) = (sV(s) - V(0))$

\Rightarrow Third equiv. model.

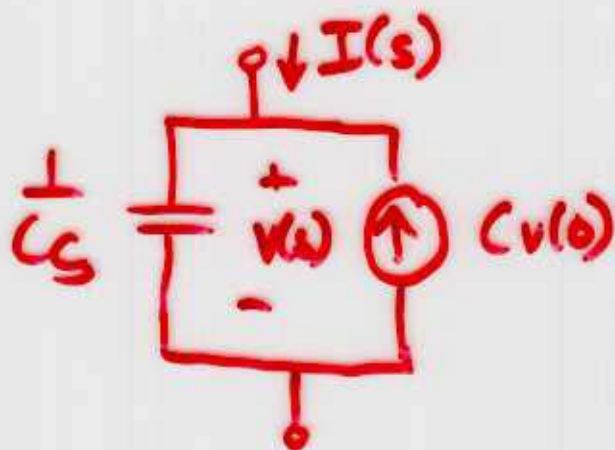

~~#~~

Now do a similar thing for inductors

$$v(t) = L \frac{di(t)}{dt}$$

Take Laplace transforms.

$$V(s) = LsI(s) - Li(0)$$

\Rightarrow Impedance of inductor is $\frac{V(s)}{I(s)}$ with
Zero initial condition = Ls

Equivalently,

$$I(s) = \frac{1}{Ls} V(s) + \frac{i(0)}{s}$$



Hence three equivalent models.

Time domain



$$v(t) = L \frac{di(t)}{dt}$$

"s-domain"

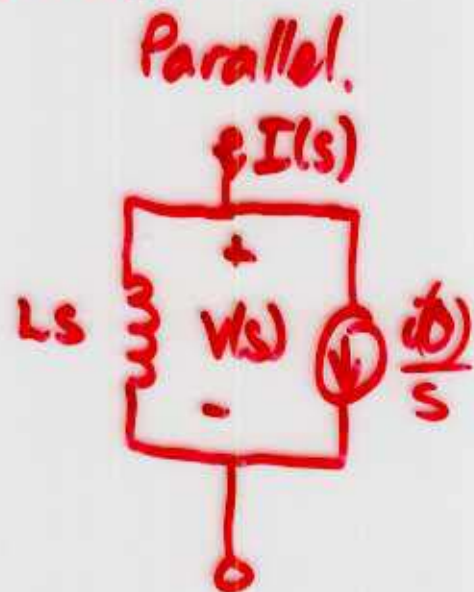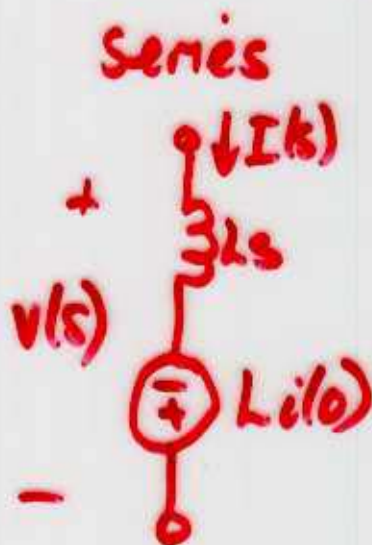

$$v(s) = LsI(s) - Li(0)$$

See also Table 14.8-1