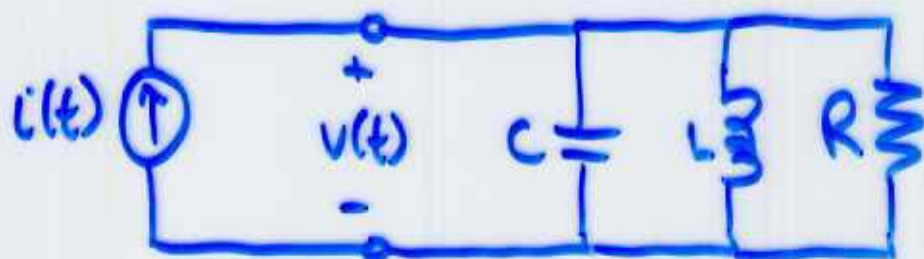


RESONANT CIRCUITS.

Consider the following circuit



where

$$i(t) = A \cos \omega t.$$

Since the circuit is linear

$$v(t) = B \cos(\omega t + \theta)$$

and the input impedance is $Z = \frac{B}{A} e^{j\theta}$

In this case,

$Z =$



$$= \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}$$

(impedances in parallel)

$$e^{-j \tan^{-1} R(\omega C - \frac{1}{\omega L})}$$

what do we observe?

① First of all,
Reactance = 0 when



② Furthermore, magnitude of impedance is a maximum at this point


③ The ω for which $\omega C - \frac{1}{\omega L} = 0$
is $\omega_0 = \frac{1}{\sqrt{LC}}$

④ For $\omega < \omega_0$, phase of Z is positive
 \Rightarrow reactance is inductive
For $\omega > \omega_0$, phase of Z is negative
 \Rightarrow reactance is capacitive

The formula for Z is accurate but inconvenient.
We can rewrite it as.

$$Z = \frac{R_1}{1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

where

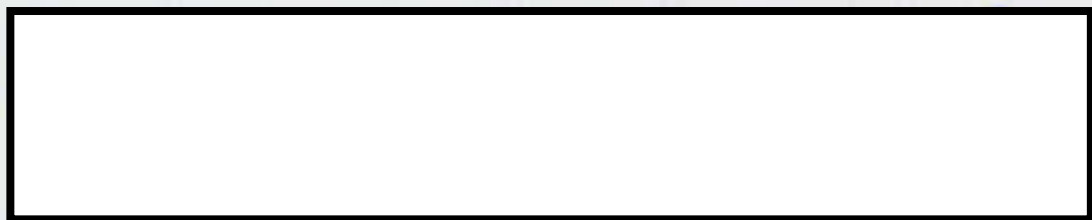

These three parameters characterise the circuit in terms of.

ω_0 = resonant frequency = $\left\{ \begin{array}{l} \text{freq. where} \\ \text{reactance} = 0 \end{array} \right.$

R_1 = maximum impedance

Q = quality factor, measures the rate at which $|z(\omega)|$ decreases from the max at $\omega = \omega_0$

larger $Q \Rightarrow$ faster decay

* An important property of resonant circuits is the bandwidth.

* We will define bandwidth to be $\omega_2 - \omega_1$, where ω_1, ω_2 are the two frequencies where

$$|Z(\omega)| = \frac{1}{\sqrt{2}} |Z(\omega_0)| = \frac{k}{\sqrt{2}} \quad (*)$$

* Here we assume that $\omega_1 < \omega_2$

* How do we find ω_1, ω_2 ? Direct solution of (*)
Find ω such that

$$\frac{k}{\sqrt{2}} = \frac{k}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

$$\Leftrightarrow 1 = Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2$$

$$\Leftrightarrow \pm 1 = Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

$$\Leftrightarrow \omega^2 \pm \frac{\omega_0 \omega}{Q} - \omega_0^2 = 0$$

This equation has 4 solutions but only 2 are > 0 .

$$\omega_{1,2} = \pm \frac{\omega_0}{2Q} + \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 + \omega_0^2}$$

Therefore $BW = \omega_2 - \omega_1 = \frac{\omega_0}{Q} = \frac{1}{RC}$


\Rightarrow when Q is larger, then BW is smaller.

Sometimes $1/Q$ is called the relative bandwidth, because

$$\frac{1}{Q} = \frac{BW}{\omega_0} = \frac{\text{bandwidth}}{\text{centre frequency}}$$

We have seen that for a parallel RLC circuit, the impedance is a maximum at the resonant frequency, ω_0 , and the rate at which the impedance decays is measured by the quality factor Q .

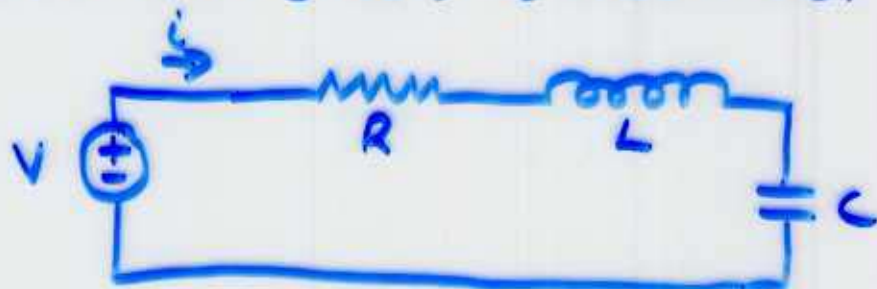A dual relationship for the admittance of a series RLC circuit is also true.



Prove for yourself:

$$Y = \frac{k}{1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

where $\omega_0 = \frac{1}{\sqrt{LC}}$, $k = \frac{1}{R}$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}, \quad BW = \frac{R}{L}$$

Now $k = \text{max admittance} \Rightarrow \text{min impedance}$
 occurs at $\omega = \omega_0$
 admittance decreases away from $\omega_0 \Rightarrow$ impedance incr. away from ω_0 .