

1. Given the network in Fig. 1,

(a) find the equations for  $V_a(t)$  and  $V_b(t)$ .

(b) find the equations for  $V_c(t)$  and  $V_d(t)$ .

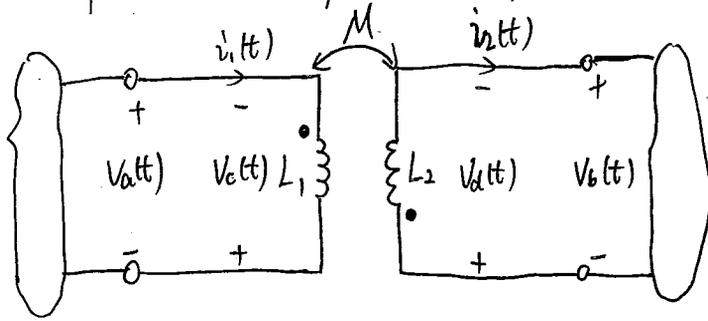


Fig. 1

Solution:

$$(a) \quad V_a(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_b(t) = -M \frac{di_1}{dt} - L_2 \frac{di_2}{dt}$$

$$(b) \quad V_c(t) = -V_a(t)$$

$$= -L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_d(t) = -V_b(t)$$

$$= M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

2. Find  $\bar{V}_0$  in the network in Fig. 2

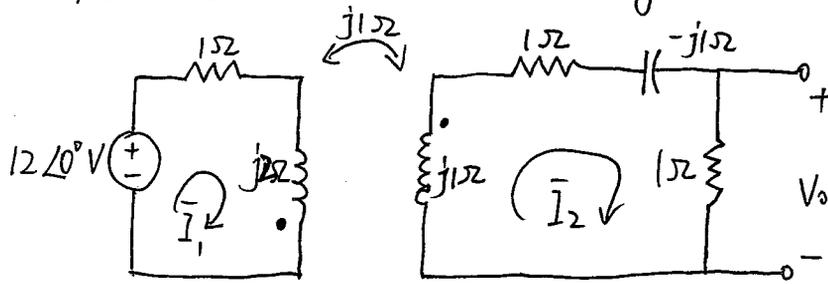


Fig. 2

Solution :

KVL for left network :

$$(1+j2)\bar{I}_1 + j1\bar{I}_2 = 12\angle 0^\circ$$

KVL for right network :

$$j1\bar{I}_1 + 3\bar{I}_2 = 0$$

$$\Rightarrow \bar{I}_1 = 5\angle -56.31^\circ \text{ A}$$

$$\bar{I}_2 = 1.66\angle -146.31^\circ \text{ A}$$

$$\bar{V}_0 = 2\bar{I}_2$$

$$= 2(1.66\angle -146.31^\circ)$$

$$= 3.32\angle -146.31^\circ$$

3. Find  $\bar{V}_0$  in the network in Fig. 3

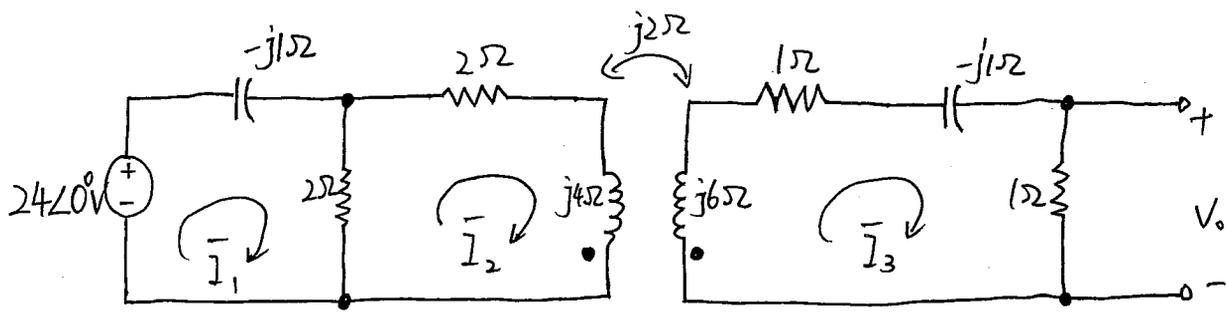


Fig. 3

Solution:

$$\text{KVL: } (2-j1)\bar{I}_1 - 2\bar{I}_2 = 24\angle 0^\circ$$

$$\text{KVL: } 2(\bar{I}_2 - \bar{I}_1) + 2\bar{I}_2 + j4\bar{I}_2 - j2\bar{I}_3 = 0$$

$$\text{KVL: } j6\bar{I}_3 - j2\bar{I}_2 + (2-j1)\bar{I}_3 = 0$$

$$\Rightarrow \bar{I}_1 = 15.82 \angle 21.14^\circ \text{ A}$$

$$\bar{I}_2 = 5.85 \angle -16.61^\circ \text{ A}$$

$$\bar{I}_3 = 2.17 \angle 5.19^\circ \text{ A}$$

$$\begin{aligned} \bar{V}_0 &= 1(\bar{I}_3) \\ &= 2.17 \angle 5.19^\circ \text{ V} \end{aligned}$$

4. Find  $\bar{V}_0$  in the network in Fig. 4

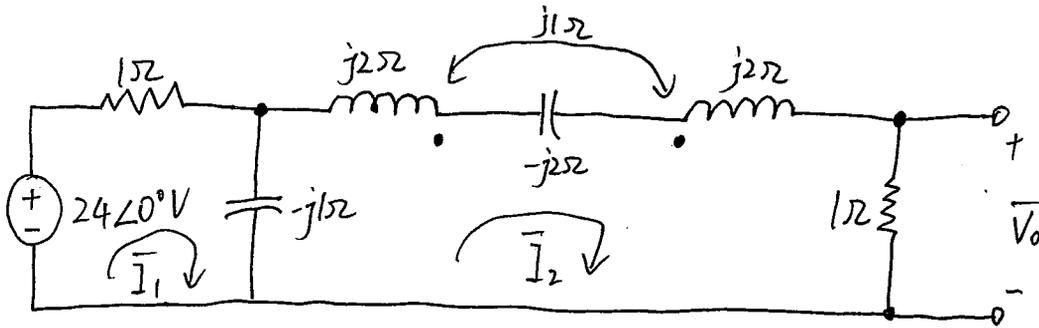


Fig. 4

Solution:

$$\text{kVL: } 1 \cdot \bar{I}_1 + (-j1) \cdot (\bar{I}_1 - \bar{I}_2) = 24 \angle 0^\circ$$

$$\text{kVL: } (-j1)(\bar{I}_2 - \bar{I}_1) + (j2 + j2 - j2 + 1)\bar{I}_2 - j1\bar{I}_2 - j1\bar{I}_2 = 0$$

$$\Rightarrow (1 - j1)\bar{I}_1 + j1\bar{I}_2 = 24 \angle 0^\circ$$

$$j1\bar{I}_1 + (1 - j1)\bar{I}_2 = 0$$

$$\Rightarrow \bar{I}_1 = 15.18 \angle 18.43^\circ \text{ A}$$

$$\bar{I}_2 = 10.73 \angle -26.57^\circ \text{ A}$$

$$\bar{V}_0 = 1 \cdot (\bar{I}_2)$$

$$= 10.73 \angle -26.57^\circ \text{ V}$$

5. Find  $V_0$  in the network in Fig. 5


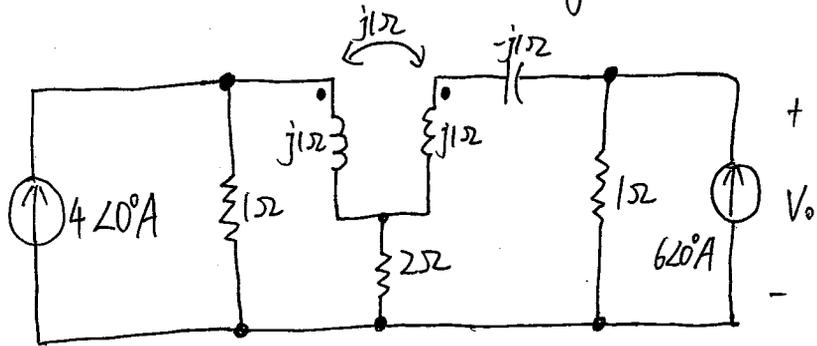


Fig. 5

Solution :

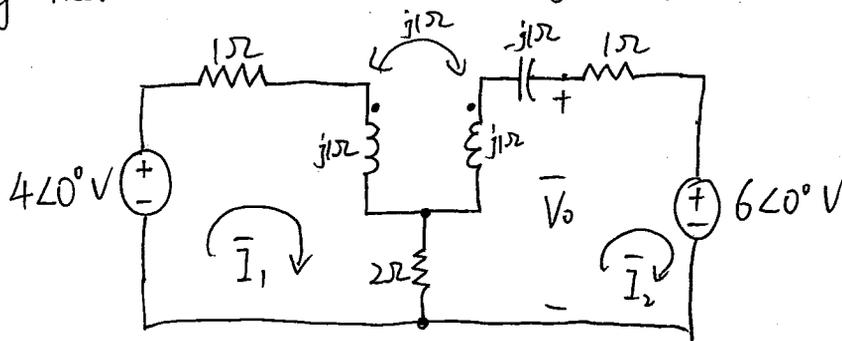By Thevenin's theorem, we get equivalent ~~circ~~ circuit.



$$\text{KVL : } (3+j1)\bar{I}_1 - (2+j1)\bar{I}_2 = 4\angle 0^\circ$$

$$\text{KVL : } -(2+j1)\bar{I}_1 + 3\bar{I}_2 = -6\angle 0^\circ$$

$$\Rightarrow \bar{I}_1 = 0.986 \angle -80.54^\circ \text{ A}$$

$$\bar{I}_2 = 1.68 \angle -159.23^\circ \text{ A}$$

$$\bar{V}_0 = (1\bar{I}_2) + 6\angle 0^\circ$$

$$= 1.68 \angle -159.23^\circ + 6\angle 0^\circ$$

$$= 4.47 \angle -7.66^\circ \text{ V}$$

6. Determine the input impedance  $Z_{in}$  of the circuit in Fig. 6


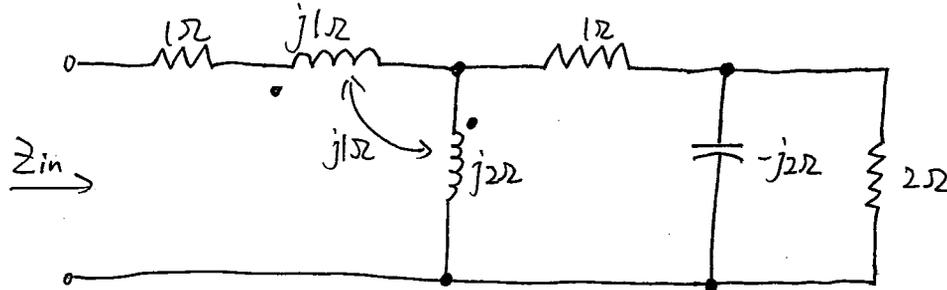


Fig. 6

Solution:

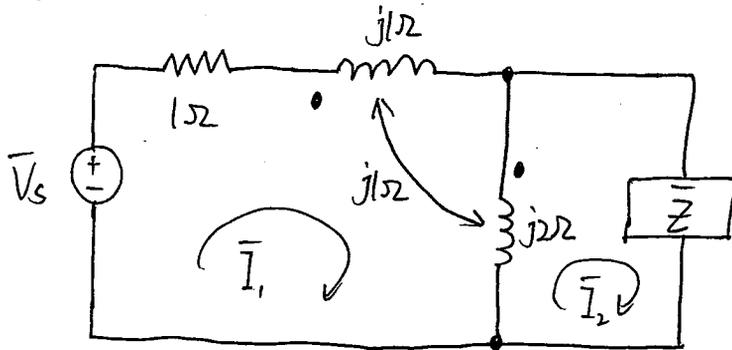

$$\text{Let } \bar{V}_s = 1 \angle 0^\circ \text{ V}$$

$$\bar{Z}_{in} = \frac{\bar{V}_s}{\bar{I}_1}$$

$$\bar{Z}_{in} = 1 + \frac{2(-j2)}{2-j2} = 1 - j1.52$$

$$\text{KVL: } (1+j3)\bar{I}_1 - j2\bar{I}_2 + j1\bar{I}_1 + j1(\bar{I}_1 - \bar{I}_2) = \bar{V}_s$$

$$(1+j5)\bar{I}_1 - j3\bar{I}_2 = 1 \angle 0^\circ$$

$$\text{KVL: } -j2\bar{I}_1 + (\bar{Z} + j2)\bar{I}_2 - j1\bar{I}_1 = 0$$

$$-j3\bar{I}_1 + (2+j1)\bar{I}_2 = 0$$

$$\Rightarrow \bar{I}_1 = 0.178 \angle -34.82^\circ \text{ A}$$

$$\bar{I}_2 = 0.24 \angle 28.61^\circ \text{ A}$$

$$\begin{aligned}\bar{Z}_{in} &= \frac{\bar{V}_s}{\bar{I}_1} \\ &= \frac{1 \angle 0^\circ}{0.178 \angle -34.82^\circ} \\ &= 4.61 + j3.21 \Omega\end{aligned}$$

7. The currents in the network in Fig. 7 are known to be  $i_1(t) = 10 \cos(377t - 30^\circ)$  mA and  $i_2(t) = 20 \cos(377t - 45^\circ)$  mA. The inductances are  $L_1 = 2$  H,  $L_2 = 2$  H, and  $k = 0.8$ . Determine  $v_1(t)$  and  $v_2(t)$ .


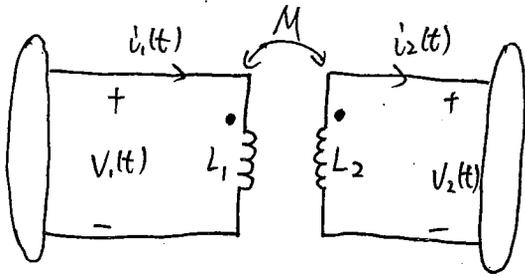


Fig. 7

Solution:

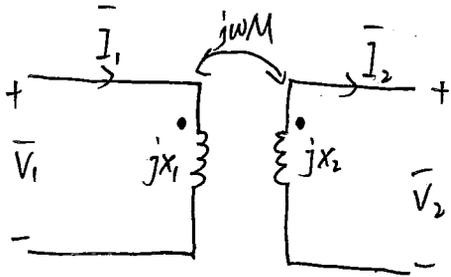

$$\text{KVL: } jX_1 \bar{I}_1 - jwM \bar{I}_2 = \bar{V}_1$$

$$\text{KVL: } -jwM \bar{I}_1 + jX_2 \bar{I}_2 = -\bar{V}_2$$

$$X_1 = \omega L_1 = 377 \times 2 \\ = 754 \Omega$$

$$X_2 = \omega L_2 = 377 \times 2 = 754 \Omega$$

$$M = k \sqrt{L_1 L_2} \\ = 0.8 \sqrt{2 \times 2} = 1.6 \text{ H}$$

$$\omega M = 377 \times 1.6 = 603.2 \Omega$$

$$\bar{I}_1 = 10 \angle -30^\circ \text{ mA}$$

$$\bar{I}_2 = 20 \angle -45^\circ \text{ mA}$$

$$\begin{aligned}\bar{V}_1 &= j(754) \cdot (10 \text{ m} \angle -30^\circ) - j(603.2) (20 \text{ m} \angle -45^\circ) \\ &= 5.16 \angle -157.2^\circ \text{ V}\end{aligned}$$

$$\begin{aligned}\bar{V}_2 &= -[-j(603.2) (10 \text{ m} \angle -30^\circ) + j754 (20 \text{ m} \angle -45^\circ)] \\ &= 9.38 \angle -144.58^\circ \text{ V}\end{aligned}$$

$$v_1(t) = 5.16 \cos(377t - 157.2^\circ) \text{ V}$$

$$v_2(t) = 9.38 \cos(377t - 144.58^\circ) \text{ V}$$

8. Determine the energy stored in the coupled inductors in the ~~the~~ circuit in Fig. 7 at  $t = 1\text{ms}$

Solution:

$$w(t) = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) - M i_1(t) i_2(t)$$

$$i_1(t) = 10 \cos(377t - 30^\circ) \text{ mA}$$

$$i_2(t) = 20 \cos(377t - 45^\circ) \text{ mA}$$

$$L_1 = 2\text{H}, \quad L_2 = 2\text{H}, \quad k = 0.8, \quad M = 1.6\text{H}$$

$$\text{at } t = 1\text{ms}$$

$$i_1(1\text{ms}) = 9.89 \text{ mA}$$

$$i_2(1\text{ms}) = 18.4 \text{ mA}$$

$$\begin{aligned} w(1\text{ms}) &= \frac{1}{2} \times 2 \times (9.89 \text{ m})^2 + \frac{1}{2} \times 2 \times (18.4 \text{ m})^2 - 1.6 \times (9.89 \text{ m}) \times (18.4 \text{ m}) \\ &= 145.2 \mu\text{J} \end{aligned}$$

9. Determine  $\bar{I}_1$ ,  $\bar{I}_2$ ,  $\bar{V}_1$  and  $\bar{V}_2$  in the network in Fig. 9

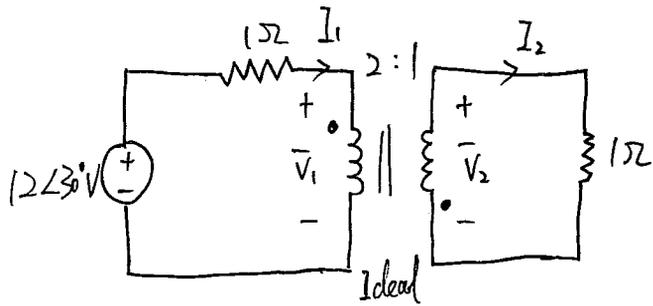


Fig. 9

Solution :

$$1. \bar{I}_1 + \bar{V}_1 = 12 \angle 30^\circ$$

$$\bar{V}_2 = 1 \cdot \bar{I}_1$$

$$-\bar{V}_1 = 2\bar{V}_2$$

$$2\bar{I}_1 = -\bar{I}_2$$

$$\bar{I}_1 - 2\bar{V}_2 = 12 \angle 30^\circ$$

$$\bar{I}_1 - 2\bar{I}_2 = 12 \angle 30^\circ$$

$$\bar{I}_1 - 2(-2\bar{I}_1) = 12 \angle 30^\circ$$

$$5\bar{I}_1 = 12 \angle 30^\circ$$

$$\bar{I}_1 = 2.4 \angle 30^\circ \text{ A}$$

$$\bar{I}_2 = -2 \times (2.4 \angle 30^\circ) = 4.8 \angle -150^\circ \text{ A}$$

$$\bar{V}_2 = 1 \times 4.8 \angle -150^\circ = 4.8 \angle -150^\circ \text{ A}$$

$$\bar{V}_1 = -2(4.8 \angle -150^\circ) = 9.6 \angle 30^\circ \text{ A}$$

10. Determine the input impedance seen by the source in the circuit in Fig. 10


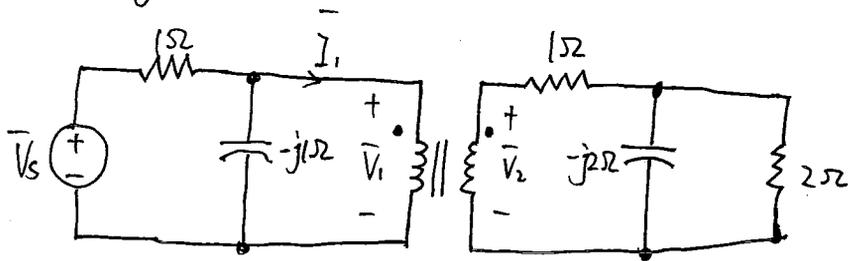


Fig. 10

Solution:

Equivalent circuit:

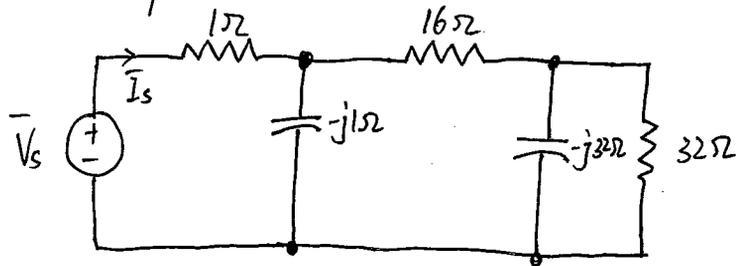

$$\bar{Z}_{in} = \frac{\bar{V}_s}{\bar{I}_s}$$

$$\bar{Z}_{in} = \{ [(32 \parallel -j32) + 16] \parallel -j1 \} + 1$$

$$= \left\{ \left[ \frac{32 \cdot (-j32)}{32 - j32} + 16 \right] \parallel -j1 \right\} + 1$$

$$= [(32 - j16) \parallel -j1] + 1$$

$$= \frac{(32 - j16)(-j1)}{32 - j16 - j1} + 1$$

$$= 1.42 \angle -43.94^\circ \Omega$$

11. Determine  $\bar{I}_s$  in the circuit in Fig. 11


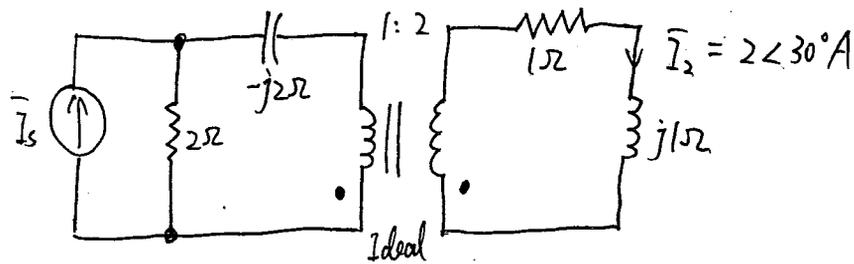


Fig. 11

Solution :

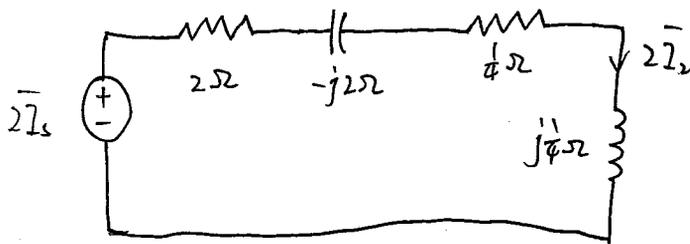Using impedance reflection and source transformation



$$\text{KVL: } (2 - j2 + \frac{1}{4} + j\frac{1}{4}) 2\bar{I}_2 = 2\bar{I}_s$$

$$\bar{I}_s = (2 - j2 + \frac{1}{4} + j\frac{1}{4}) (2\angle 30^\circ)$$

$$= 5.7\angle -7.87^\circ \text{ A}$$