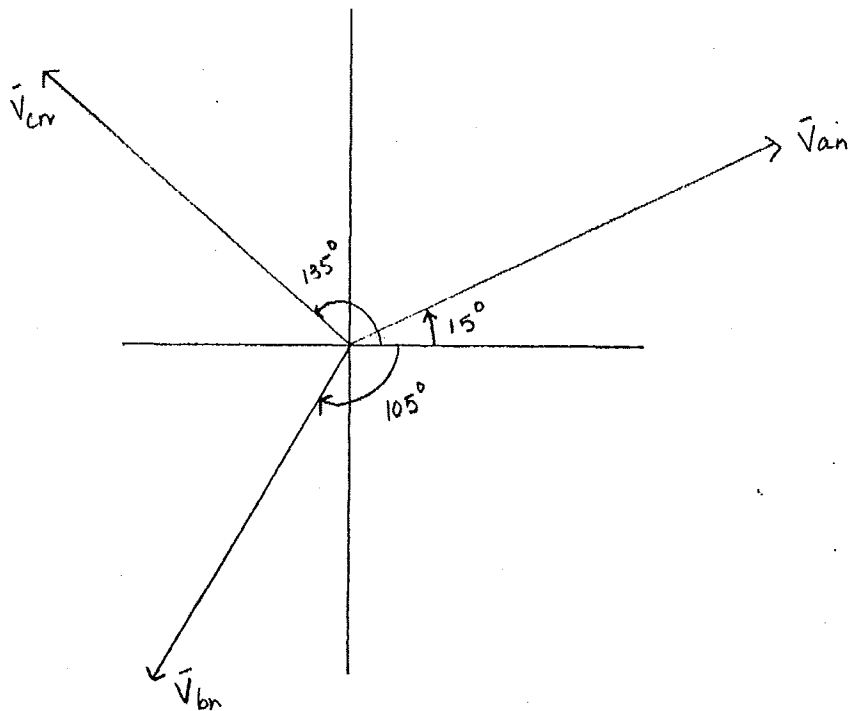


1. Sketch a phasor representation of an abc-sequence balanced three-phase Y-connected source, including V_{an} , V_{bn} , and V_{cn} if $V_{an} = 120 \angle 15^\circ \text{ Vrms}$

Solution: $\bar{V}_{an} = 120 \angle 15^\circ \text{ Vrms}$

$$\bar{V}_{bn} = 120 \angle -105^\circ \text{ Vrms}$$

$$\bar{V}_{cn} = 120 \angle 135^\circ \text{ Vrms}$$



2. Sketch a phasor representation of a balanced three-phase system containing both phase voltages and line voltages if $V_{ab} = 208 \angle 60^\circ \text{ V}_{\text{rms}}$. Label all phasors and assume an abc-phase sequence.

Solution: $\bar{V}_{ab} = 208 \angle 60^\circ \text{ V}_{\text{rms}}$

$$\bar{V}_{an} = \frac{208}{\sqrt{3}} \angle 60^\circ - 30^\circ = 120 \angle 30^\circ \text{ V}_{\text{rms}}$$


$$\bar{V}_{ba} = \bar{V}_{an} - \bar{V}_{ab} = 120 \angle 30^\circ - 208 \angle 60^\circ$$

$$\bar{V}_{bn} = 120 \angle -90^\circ \text{ V}_{\text{rms}}$$


$$\bar{V}_{cn} = 120 \angle 150^\circ \text{ V}_{\text{rms}}$$

$$\bar{V}_{bc} = 208 \angle -60^\circ \text{ V}_{\text{rms}}$$
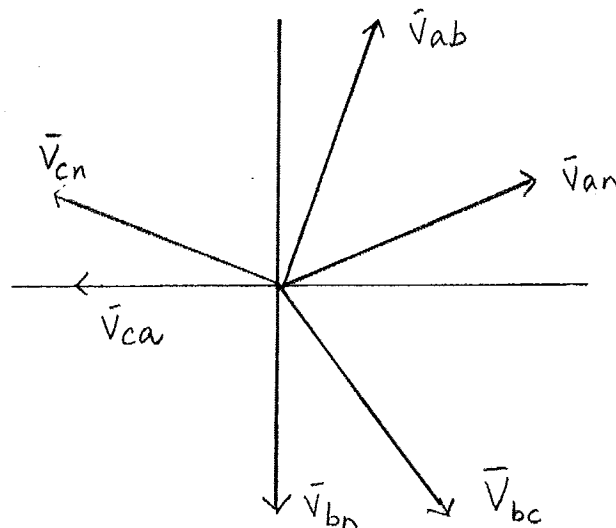
$$\bar{V}_{ca} = 208 \angle 180^\circ \text{ V}_{\text{rms}}$$



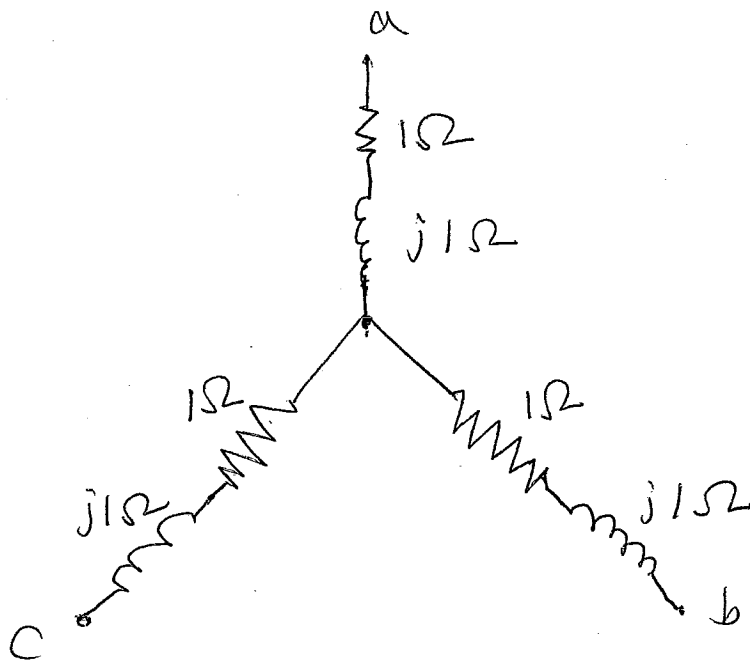3. Find the equivalent impedances Z_{ab} , Z_{bc} , Z_{ca} .



Solution:


$$Z_{an} = Z_{bn} = Z_{cn} = 1 + j \cdot 1\Omega = Z_Y$$

$$Z_{\Delta} = 3 Z_Y = 3(1 + j1)$$

$$\bar{Z}_{\Delta} = 3 + j3\Omega$$

$$\bar{Z}_{ab} = \bar{Z}_{bc} = \bar{Z}_{ca} = 3 + j3\Omega$$

4. Find the equivalent Z of the network.

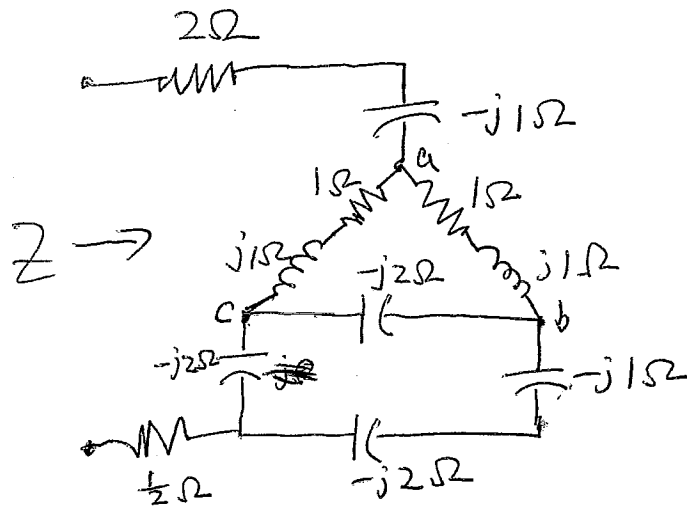


Solution: $Z_1 = 1 + j1\Omega$, $Z_2 = 1 - j1\Omega$, $Z_3 = -j2\Omega$.

$$Z_a = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2 + Z_3} = j1\Omega$$

$$Z_b = \frac{Z_1 \cdot Z_3}{Z_1 + Z_2 + Z_3} = 1 - j1\Omega$$
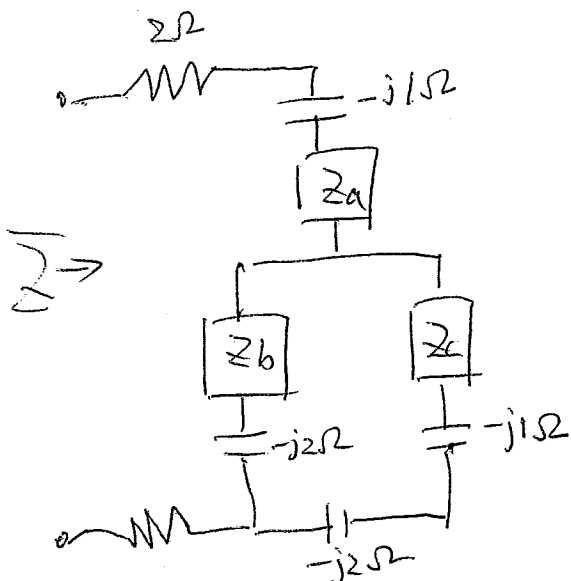
$$Z_c = \frac{Z_2 \cdot Z_3}{Z_1 + Z_2 + Z_3} = 1 - j1\Omega$$



$$Z = \left\{ (Z_c - j3) // (Z_b - j2) \right\} + Z_a + \frac{1}{2} - j1 + 2$$

$$= \frac{(1 - j1 - j3)(1 - j1 - j2)}{1 - j1 - j3 + 1 - j1 - j2} + j1 + \frac{1}{2} - j1 + 2$$

$$= 3 - j1.717$$

$$= 3.46 \angle -29.7^\circ$$


(4)

5. A positive-sequence balanced three-phase wye-connected source supplies power to a balanced wye-connected load. The magnitude of the line voltages is 208 Vrms. If the load impedance per phase is $36 + j12 \Omega$, determine the line currents if $\angle V_{an} = 0^\circ$.

Solution: $|V_{line}| = 208 \text{ V rms}$,

$$|V_{an}| = \frac{|V_{line}|}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120 \text{ V rms}$$
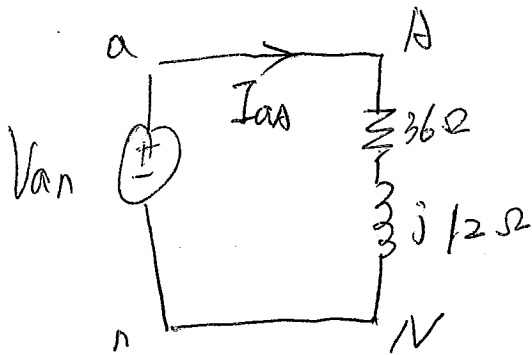
$$I_{aA} = \frac{V_{an}}{Z_{load}} = \frac{120 \angle 0^\circ}{36 + j12} = 3.16 \angle -18.43^\circ \text{ A}$$



$$I_{bB} = 3.16 \angle +38.43^\circ \text{ A}$$


$$I_{cC} = 3.16 \angle 101.57^\circ \text{ A}$$

6. A positive-sequence balanced three-phase wye-connected source with a phase voltage of 120 V rms supplies power to a balanced wye-connected load. The per phase load impedance is $40 + j10 \Omega$. Determine the line currents in the circuit if $\angle V_{an} = 0^\circ$.

Solution. $|\bar{V}_{an}| = 120 \text{ V rms}$

$$\bar{Z}_{\text{load}} = 40 + j10 \Omega$$

$$\angle \bar{V}_{an} = 0^\circ$$

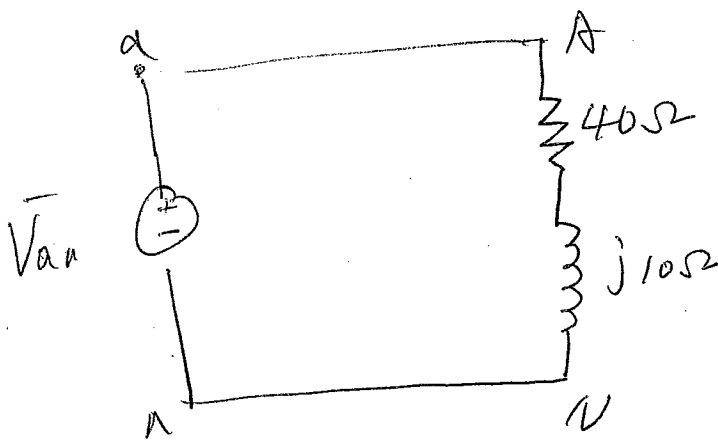

$$I_{\text{an}} = \frac{120 \angle 0^\circ}{40 + j10} = 2.91 \angle -14^\circ \text{ A}$$


$$I_{\text{bn}} = 2.91 \angle -134^\circ \text{ A}$$

$$I_{\text{cn}} = 2.91 \angle 106^\circ \text{ A}$$

(D)

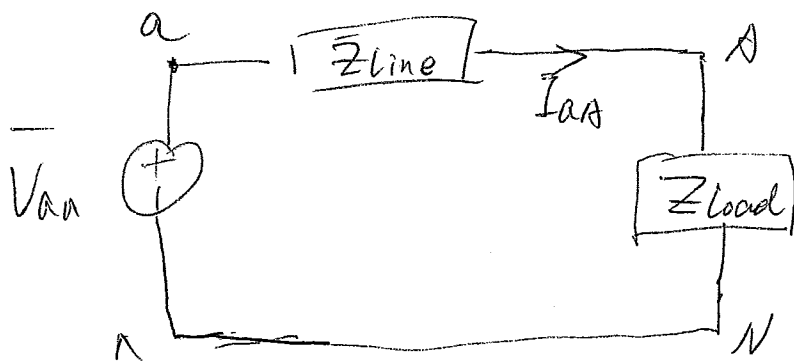7. An abc-sequence balanced three-phase wye-connected source supplies power to a balanced wye-connected load. The line impedance per phase is $1 + j5 \Omega$, and the load impedance per phase is $25 + j25 \Omega$. If the source line voltage is $208 \angle 0^\circ$ Vrms, find the line currents.

Solution: $V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ = 120 \angle -30^\circ$ Vrms.



$$I_{AA} = \frac{V_{an}}{Z_{line} + Z_{load}} = \frac{120 \angle -30^\circ}{1 + j5 + 25 + j25} = 3.02 \angle -79.1^\circ \text{ A}$$

$$I_{bB} = 3.02 \angle -199.1^\circ \text{ A}$$


$$I_{cC} = 3.02 \angle 40.9^\circ \text{ A}$$

8. In a balanced three-phase system, the abc-phase sequence source is delta connected and $V_{ab} = 120 \angle 30^\circ \text{ V rms}$. The load consists of two balanced wyes with phase impedances of $10 + j1 \Omega$ and $20 + j5 \Omega$. If the line impedance is 0, find the line currents and the load phase voltage.

Solution: $\bar{V}_{ab} = 120 \angle 30^\circ \text{ V rms}$

$$Z_1 = 10 + j1 \Omega, \quad Z_2 = 20 + j5 \Omega, \quad Z_{\text{line}} = 0 \Omega$$
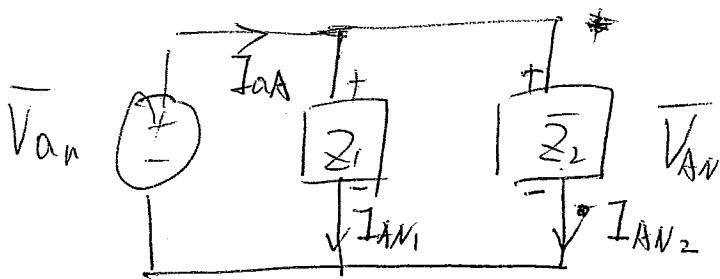
$$V_{an} = \frac{120}{\sqrt{3}} \angle 30^\circ - 30^\circ = 69.28 \angle 0^\circ \text{ V rms} = V_{AN}$$



$$I_{AB} = 10.23 \angle -128.44^\circ \text{ Arms}$$

$$I_{CB} = 10.23 \angle -111.56^\circ \text{ Arms}$$

$$I_{AN1} = \frac{V_{an}}{Z_1} = \frac{69.28 \angle 0^\circ}{10 + j1} = 6.89 \angle -5.71^\circ \text{ A}$$

$$I_{AN2} = \frac{V_{an}}{Z_2} = \frac{69.28 \angle 0^\circ}{20 + j5} = 3.36 \angle -14.04^\circ \text{ A} \quad \text{cont}$$

$$I_{AA} = I_{AN1} + I_{AN2} = 6.89 \angle -5.71^\circ + 3.36 \angle -14.04^\circ \text{ A} = 10.23 \angle -8.44^\circ \text{ Arms}$$

9. The magnitude of the complex power (apparent power) supplied by a three-phase balanced wye-wye system is 3600 VA. The line voltage is 208 V rms. If the line impedance is negligible and the power factor angle of the load is 25° , determine the load impedance.

Solution $|\overline{S}_{3-\phi}| = 3600 \text{ VA}$

$$|\overline{V}_L| = 208 \text{ V rms}$$

$$\text{PF} = \cos 25^\circ = 0.906$$

$$S_{3-\phi} = 3600 \angle 25^\circ \text{ VA}$$

$$|\overline{V}_{an}| = \frac{208}{\sqrt{3}} = 120 \text{ V rms}$$


$$|\overline{S}_{3-\phi}| = 3 |\overline{V}_{an}| |\overline{I}_{aA}| \angle \theta_{V_{an}} - \theta_{I_{aA}}$$

$$I_{aA} = \frac{S_{3-\phi}}{3 V_{an} \angle \theta_{zL}} = \frac{3600 \angle 25^\circ}{3 (120) \angle 25^\circ} = 10 \text{ A rms}$$

$$Z_{\text{load}} = \frac{120 \angle 25^\circ}{10} = 12 \angle 25^\circ \Omega.$$

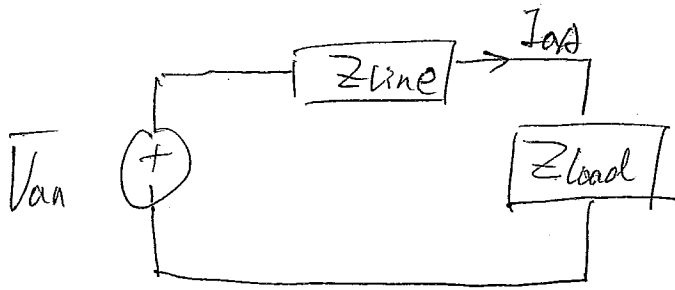10. An abc-sequence wye-connected source having a phase-a voltage of $120\angle 0^\circ$ V rms is attached to a wye-connected load having a per-phase impedance of $100\angle 70^\circ \Omega$. If the line impedance is $1\angle 20^\circ \Omega$, determine the total complex power produced by the voltage sources and the real and reactive power dissipated by the load.

Solution: $\bar{V}_{an} = 120\angle 0^\circ$ V rms, $\bar{Z}_{load} = 100\angle 70^\circ \Omega$, $\bar{Z}_{line} = 1\angle 20^\circ \Omega$.



$$\bar{I}_{AA} = \frac{120\angle 0^\circ}{1\angle 20^\circ + 100\angle 70^\circ} = 1.19\angle -69.6^\circ \text{ A}$$

$$\begin{aligned} \bar{S}_{3-\phi} &= 3 \bar{V}_{an} \cdot \bar{I}_{AA}^* = 3(120\angle 0^\circ) \cdot (1.19\angle 69.6^\circ) \\ &= 428.4\angle 69.6^\circ \text{ VA} \end{aligned}$$

$$\begin{aligned} S_{L3-\phi} &= 3 \bar{I}_{AA}^2 \cdot \bar{Z}_{load} = 3(1.19)^2 (100\angle 70^\circ) \\ &= 145.3 + j 399.21 \text{ VA} \end{aligned}$$

$$P_{L3-\phi} = 145.3 \text{ W}$$