
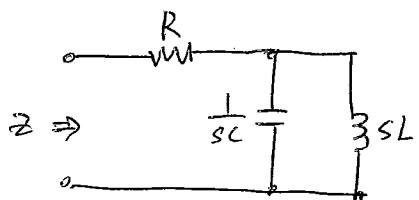



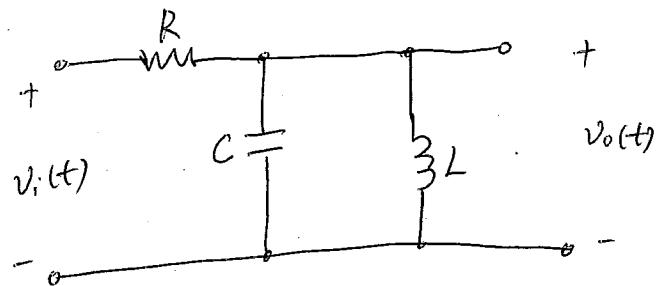
Q1. Determine the driving point impedance at the input terminals of the following network as a function of s .



$$Z = R + \frac{1}{sC} // sL = R + \frac{sL \cdot \frac{1}{sC}}{sL + \frac{1}{sC}} = R + \frac{sL}{s^2 LC + 1}$$



$$= \frac{s^2 LCR + sL + R}{s^2 LC + 1}$$

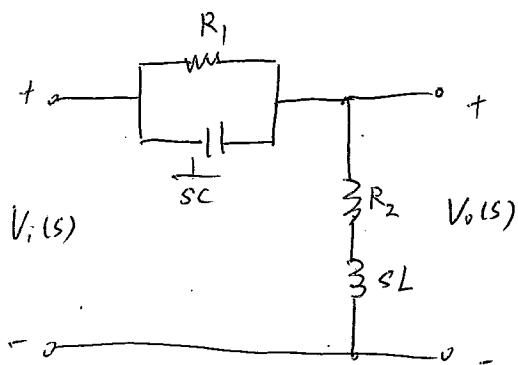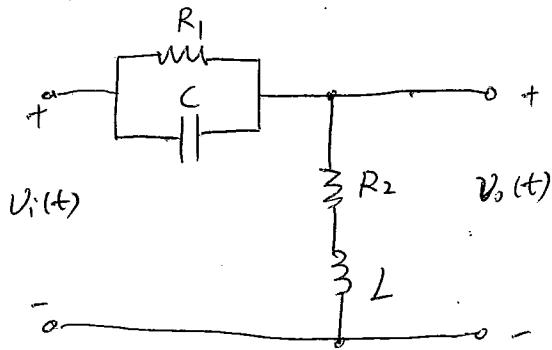Q2. Determine the voltage transfer function $V_o(s) / V_i(s)$ as function of s for the following network.





$$\begin{aligned}
 \frac{V_o(s)}{V_i(s)} &= \frac{R_2 + sL}{R_2 + sL + R_1 \parallel \frac{1}{sC}} = \frac{R_2 + sL}{R_2 + sL + \frac{R_1 \cdot \frac{1}{sC}}{R_1 + \frac{1}{sC}}} = \frac{R_2 + sL}{R_2 + sL + \frac{R_1}{R_1 s C + 1}} \\
 &= \frac{(R_2 + sL)(sR_1 C + 1)}{(R_2 + sL)(sR_1 C + 1) + R_1} = \frac{s^2 R_1 C L + s R_1 R_2 C + s L + R_2}{s^2 R_1 L C + s R_1 R_2 C + s L + R_2 + R_1} \\
 &= \frac{s^2 + s \left[\frac{R_2}{L} + \frac{1}{R_1 C} \right] + \frac{R_2}{R_1 L C}}{s^2 + s \left\{ \frac{R_2}{L} + \frac{1}{R_1 C} \right\} + \frac{R_1 + R_2}{R_1 L C}}
 \end{aligned}$$

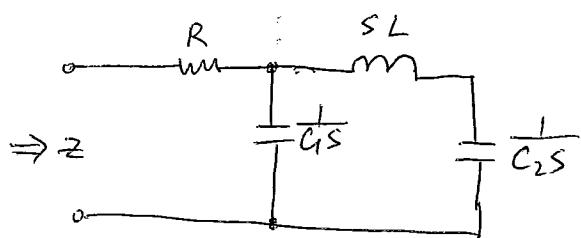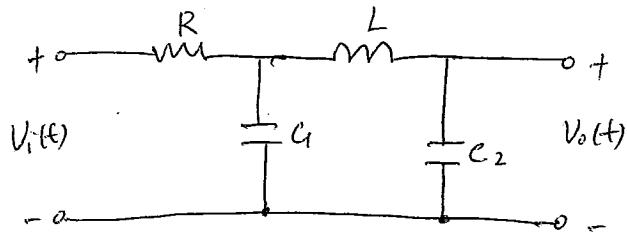Q3. Determine the driving point impedance at the input terminals of the following network as a function of s .



$$\begin{aligned}
 Z &= R + \frac{1}{C_1 s} \parallel (sL + \frac{1}{C_2 s}) = R + \frac{\frac{1}{sC_1} \cdot (sL + \frac{1}{sC_2})}{\frac{1}{sC_1} + sL + \frac{1}{sC_2}} \\
 &= R + \frac{sL + \frac{1}{sC_2}}{1 + s^2 LC_1 + \frac{C_1}{C_2}} = R + \frac{s^2 + \frac{1}{LC_2}}{s \left[s^2 C_1 + \frac{1}{L} + \frac{C_1}{C_2 L} \right]} = R + \frac{s^2 + \frac{1}{LC_2}}{s C_1 \left[s^2 + \frac{1}{LC_1} + \frac{1}{LC_2} \right]} \\
 &= R + \frac{s^2 + \frac{1}{LC_2}}{s C_1 \left(s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right)} = \frac{R s C_1 \left(s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right) + s^2 + \frac{1}{LC_2}}{s C_1 \left(s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right)} \\
 &= \frac{R \left(s^3 + s \cdot \frac{C_1 + C_2}{LC_1 C_2} + s^2 \cdot \frac{1}{RC_1} + \frac{1}{LC_2 RC_1} \right)}{s \left(s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right)} \\
 &= \frac{R \left(s^3 + \frac{1}{RC_1} s^2 + \frac{C_1 + C_2}{LC_1 C_2} s + \frac{1}{RLC_1 C_2} \right)}{s \left(s^2 + \frac{C_1 + C_2}{LC_1 C_2} \right)}
 \end{aligned}$$

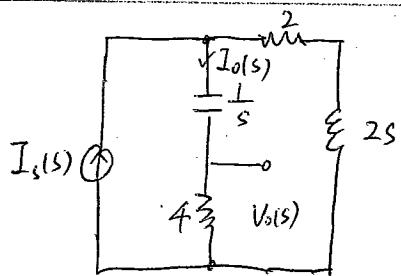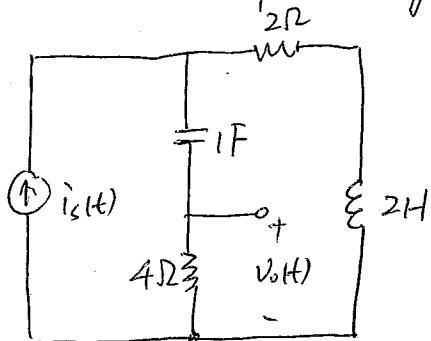Q4. Find the transfer impedance $V_o(s) / I_s(s)$ for the network shown in the following figure.





$$\text{Let } z_1 = 4 + \frac{1}{s} = \frac{4s+1}{s} \Omega$$

$$z_2 = 2 + 2s$$

$$\frac{I_o}{I_s} = \frac{z_2}{z_1 + z_2} = \frac{2+2s}{2+2s + \frac{4s+1}{s}} = \frac{2s(s+1)}{2s^2 + 6s + 1}$$


$$\frac{V_o(s)}{I_s(s)} = \frac{I_o(s) \cdot 4}{I_s(s)} = \frac{8s(s+1)}{2s^2 + 6s + 1}$$

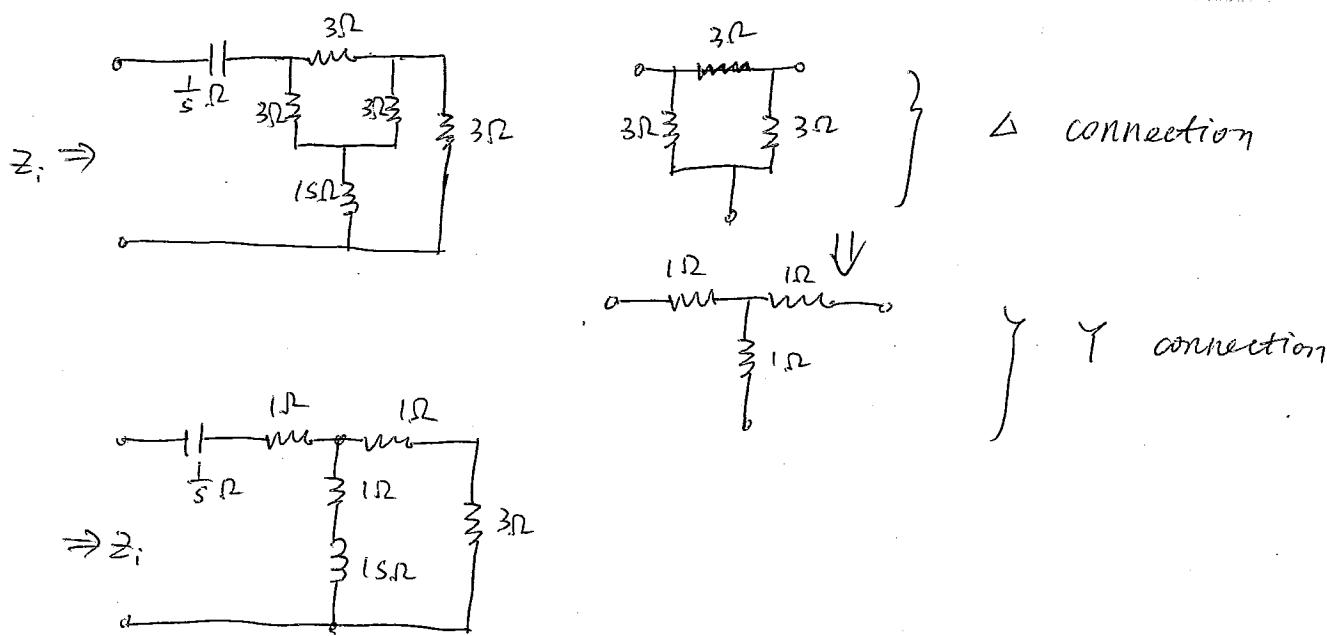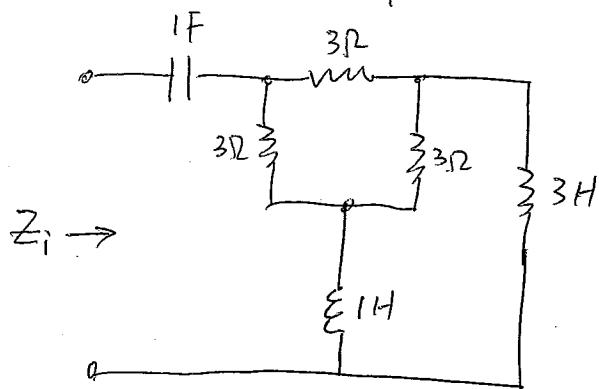Q5. Find the driving point impedance at the input terminals of the circuit. as a function of s .



$$\begin{aligned}
 Z_i &= \frac{1}{s} + 1 + (1+1s) // (1+3) = 1 + \frac{1}{s} + \frac{4 \times (1+s)}{4+1+s} = 1 + \frac{1}{s} + \frac{4(s+1)}{s+5} \\
 &= \frac{s^2 + 5s + s + 5 + 4s^2 + 4s}{s(s+5)} = \frac{5s^2 + 10s + 5}{s(s+5)} = \frac{s(s^2 + 2s + 1)}{s(s+5)} \Omega
 \end{aligned}$$

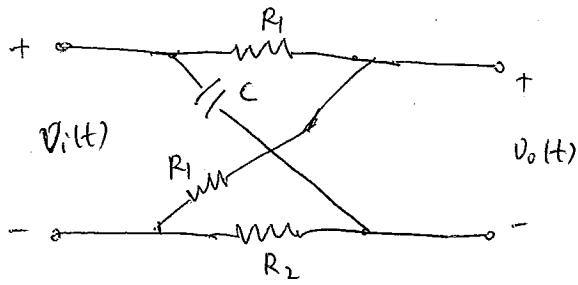Q6. Determine the voltage transfer function $\frac{V_o(s)}{V_I(s)}$



Circuit diagram with node voltages V₁ and V₂ defined. A capacitor C is shown between V₁ and ground.



$$V_1 = V_I \cdot \frac{R_1}{R_1 + R_1} = \frac{V_I}{2}$$

$$V_2 = V_I \cdot \frac{R_2}{R_2 + \frac{1}{sC}} = \frac{sR_2 C}{sR_2 C + 1} \cdot V_I$$

$$V_o = V_1 - V_2 = \frac{1}{2}V_I - \frac{sR_2 C}{sR_2 C + 1}V_I = V_I \frac{sR_2 C + 1 - 2sR_2 C}{2(sR_2 C + 1)}$$

$$\frac{V_o(s)}{V_I(s)} = \frac{1}{2} \cdot \frac{1 - sR_2 C}{1 + sR_2 C}$$

Q7. Find $\frac{V_o(s)}{V_s(s)}$

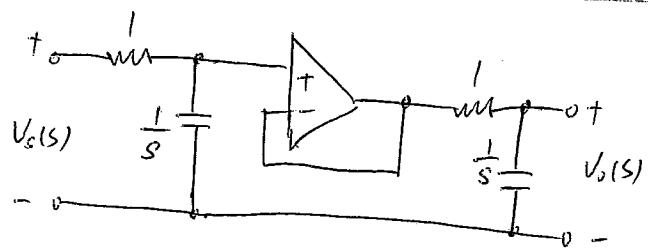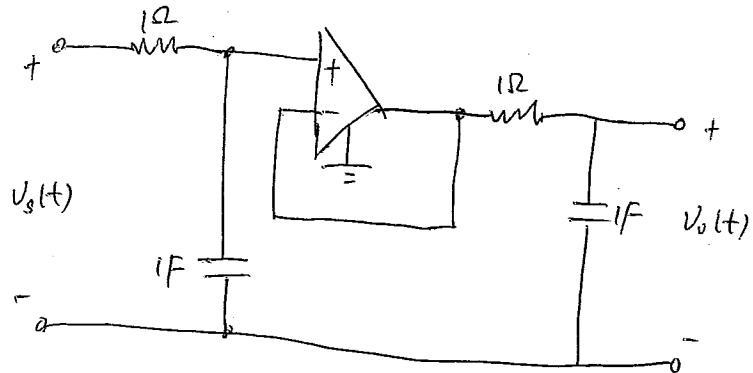

$$\frac{V_+(s)}{V_s(s)} = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$



$$V_- = V_+ = \frac{1}{s+1} \cdot V_s$$

$$\frac{V_o}{V_-} = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$

$$V_o = \frac{1}{s+1} V_- = \frac{1}{(s+1)^2} V_s$$

$$\therefore \frac{V_o}{V_s} = \frac{1}{(s+1)^2}$$

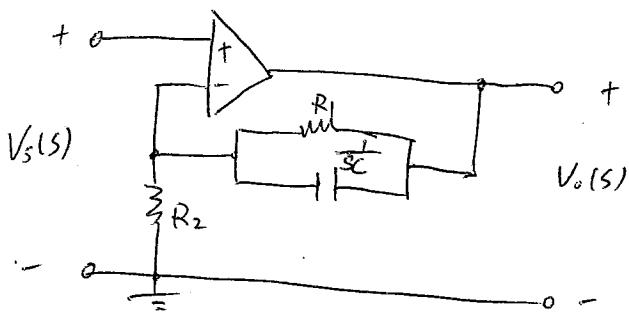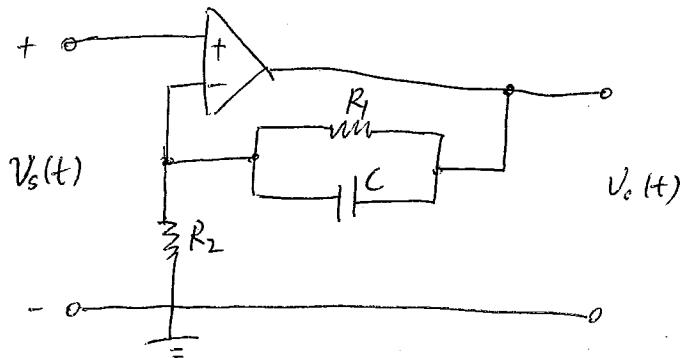
Q8. Find the transfer function $\frac{V_o(s)}{V_s(s)}$



$$V = V_+ = V_s(s)$$

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{R_2 + R_1 || \frac{1}{sC}}{R_2} = 1 + \frac{R_1 \cdot \frac{1}{sC}}{R_2 \cdot (R_1 + \frac{1}{sC})} = 1 + \frac{R_1}{R_2(R_1 s C + 1)} \\ &= \frac{s R_1 R_2 C + R_2 + R_1}{s R_1 R_2 C + R_2} = \frac{s + \frac{R_1 + R_2}{R_1 R_2 C}}{s + \frac{1}{R_1 C}} \end{aligned}$$

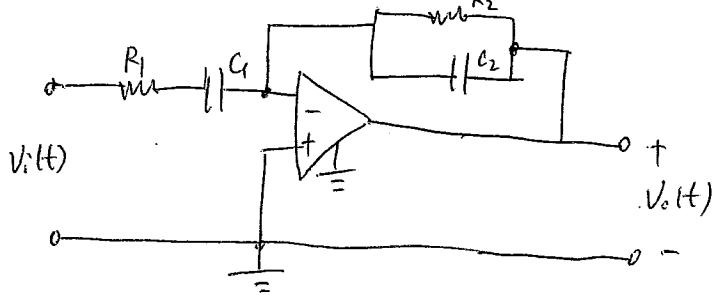Q9. Determine the voltage transfer function $\frac{V_o(s)}{V_i(s)}$




$$\text{Let } Z_1 = R_1 + \frac{1}{sC_1} = \frac{sR_1C_1 + 1}{sC_1}$$

$$Z_2 = R_2 // \frac{1}{sC_2} = \frac{\frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{sC_2 R_2 + 1}$$

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2}{Z_1} = -\frac{R_2}{sC_2 R_2 + 1} - \frac{sC_1}{sR_1 C_1 + 1}$$

$$= -\frac{sR_2 C_1}{(sC_2 R_2 + 1)(sR_1 C_1 + 1)}$$

Q10 Find $\frac{V_o(s)}{V_i(s)}$

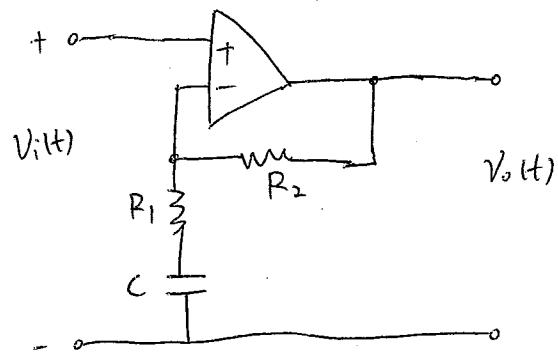

$$V_- = V_+ = V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 + R_1 + \frac{1}{sC}}{R_1 + \frac{1}{sC}} = \frac{s(R_1 + R_2)C + 1}{sR_1C + 1}$$

Q11, sketch the magnitude characteristic of Bode Plot for the transfer function $G(j\omega) = \frac{10(j\omega+2)(j\omega+100)}{j\omega(-\omega^2+4j\omega+100)}$

$$\begin{aligned} G(j\omega) &= \frac{(10(j\omega+2))(j\omega+100)}{j\omega(-\omega^2+4j\omega+100)} \\ &= 10 \frac{2(j\omega/2+1) \cdot 100(j\omega/100+1)}{j\omega \cdot 100 \cdot (-\frac{\omega^2}{100} + \frac{4j\omega}{100} + 1)} \\ &= \frac{20(j\omega/2+1)(j\omega/100+1)}{j\omega(1 - \frac{\omega^2}{100} + \frac{4j\omega}{100} + 1)} \end{aligned}$$

$$K_0 = 20$$

First order pole at origin.

two simple zeros : $\omega_1 = 2 \text{ rad/s}$, $\omega_2 = 100 \text{ rad/s}$



quadratic poles at : $\omega_3 = 10 \text{ rad/s}$, $\zeta_3 = 0.2$

$$-\frac{\omega^2}{100} + \frac{4j\omega}{100} + 1 = \left(\frac{j\omega}{100}\right)^2 + \frac{4j\omega}{100} + 1$$

standard form : $(j\omega\tau_3)^2 + 2\zeta_3 j\omega\tau_3 + 1$

$$\tau_3^2 = 100 \Rightarrow \tau_3 = \frac{1}{10} \quad \omega_3 = \frac{1}{\tau_3} = 10 \text{ rad/s}$$
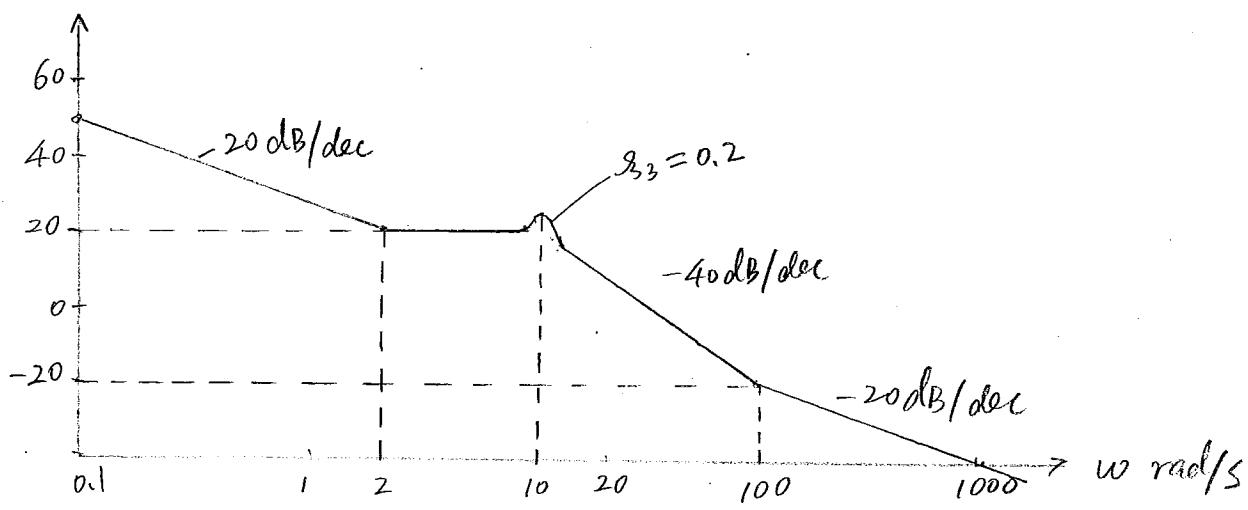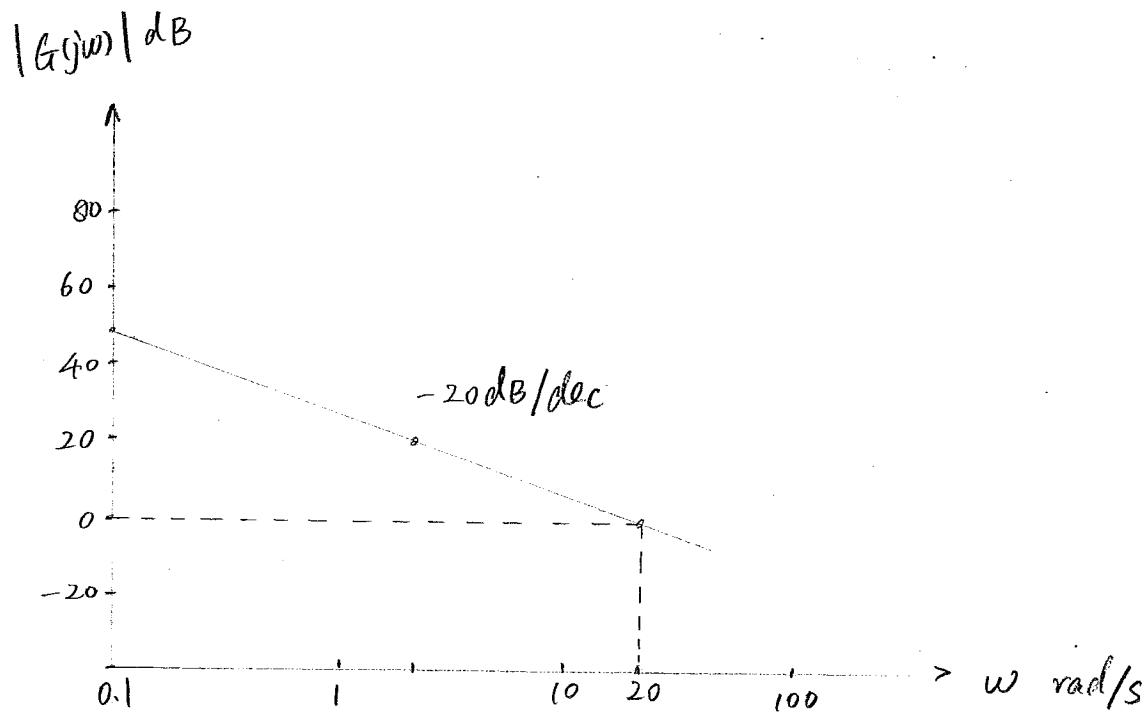
$$2\zeta_3 \frac{1}{10} = \frac{4}{100} \Rightarrow \zeta_3 = 0.2$$



Q12. Find $H(j\omega)$ if its amplitude characteristic is shown in Fig. 2.

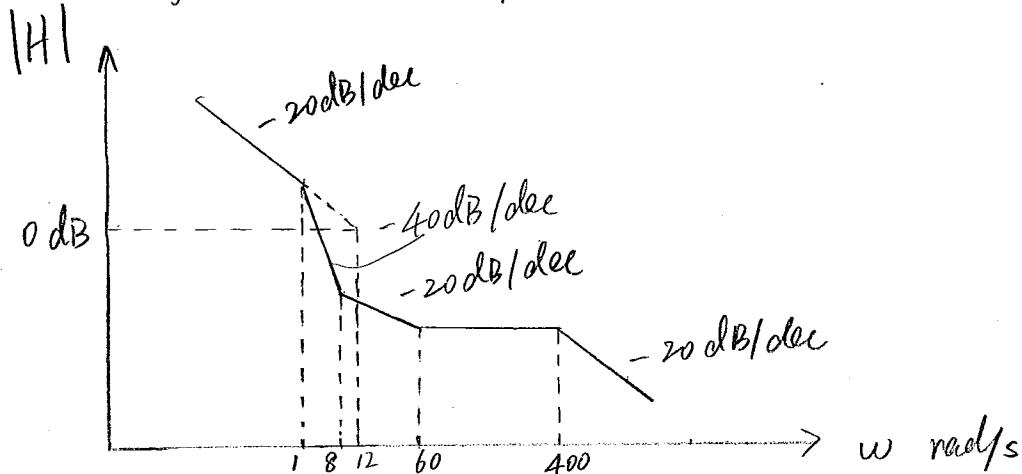


Figure. 2.

First order pole at origin

Simple poles : $\omega_1 = 1 \text{ rad/s}$, $\omega_2 = 400 \text{ rad/s}$

Simple zeros : $\omega_3 = 8 \text{ rad/s}$, $\omega_4 = 60 \text{ rad/s}$

$$\begin{aligned}
 H(j\omega) &= \frac{12}{j\omega} \cdot \frac{1}{j\omega+1} \cdot \left(\frac{j\omega}{8} + 1\right) \cdot \left(\frac{j\omega}{60} + 1\right) \cdot \frac{1}{\left(\frac{j\omega}{400} + 1\right)} \\
 &= 12 \times \frac{1}{8} \times \frac{1}{60} \times \frac{1}{400} \cdot \frac{(j\omega+8)(j\omega+6)}{j\omega(j\omega+1)(j\omega+400)} \\
 &= 10 \cdot \frac{(j\omega+8)(j\omega+6)}{j\omega(j\omega+1)(j\omega+400)}
 \end{aligned}$$

Q13. Given the network in Fig 3., sketch the magnitude characteristic of the transfer function

$$G_V(j\omega) = \frac{V_o}{V_i} (j\omega)$$

Identify the type of filter

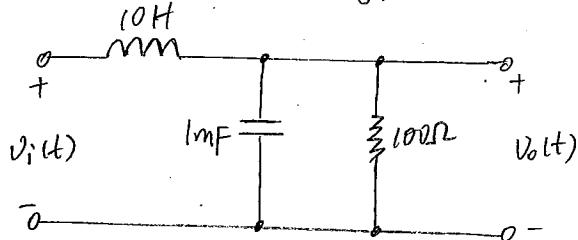


Figure 3


$$\begin{array}{ccc}
 \text{+j}10\omega\text{H} & & \\
 +-----|-----+ & & \\
 \text{V}_i & -j\frac{1000}{\omega}\text{F} & \text{V}_o \\
 | & & | \\
 \text{-} & & \text{-}
 \end{array}
 \quad
 \begin{aligned}
 j\omega L &= j10\omega \text{H} \\
 \frac{1}{j\omega C} &= \frac{1}{j10^{-3}\omega} = -j\frac{1000}{\omega} \text{F}
 \end{aligned}$$

$$\begin{aligned}
 Z_{II} &= -j\frac{1000}{\omega} \parallel 100 = \frac{-j\frac{1000}{\omega} \times 100}{-j\frac{1000}{\omega} + 100} = \frac{-j\frac{1000}{\omega}}{-j\frac{10}{\omega} + 1} = \frac{-j\frac{1000}{\omega}}{-j10 + \omega} \\
 &= \frac{100}{10 + j\omega}
 \end{aligned}$$

$$\frac{V_o}{V_i} = \frac{Z_{II}}{Z_{II} + j10\omega} = \frac{\frac{100}{10 + j\omega}}{\frac{1000}{10 + j\omega} + j10\omega} = \frac{10^3}{10^3 + j10\omega(10 + j\omega)} = \frac{100}{100 - \omega^2 + j10\omega}$$

$$\frac{V_o}{V_i} = \frac{100}{(\omega)^2 + j\omega(10 + 100)} = \frac{1}{\frac{(\omega)^2}{100} + \frac{j\omega}{10} + 1}$$

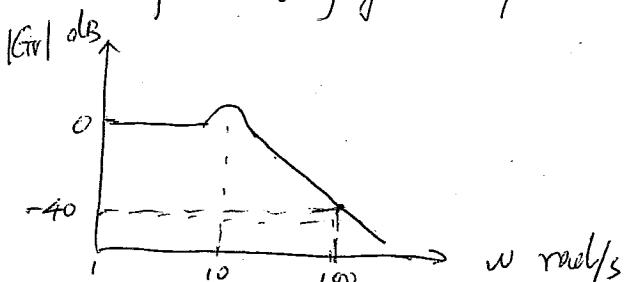
Complex conjugate poles : $\tau = \frac{1}{10}$ $\frac{10}{100} = 2\% \tau \Rightarrow \xi = 0.5$



lowpass filter

Resonant Circuit

Series Resonance

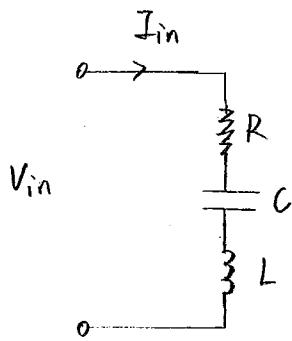

$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$\text{Resonance frequency : } \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\min |Z(j\omega)| = Z(j\omega_0) = R$$

Quality factor:

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}} = 2\pi \frac{E \text{ stored in } C, L}{E \text{ dissipated on } R}$$

$$\text{Bandwidth : } BW = \omega_{HI} - \omega_{LO} = \frac{\omega_0}{Q}$$

Parallel Resonance

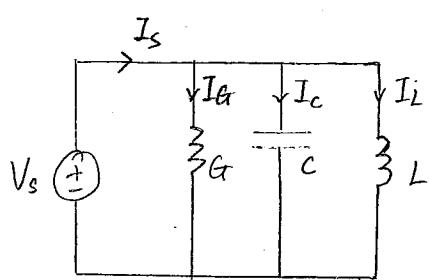

$$Y(j\omega) = G + j\omega C + \frac{1}{j\omega L}$$

$$\text{Resonance frequency : } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{R}{\omega_0 L} = \frac{1}{G \omega_0 L} = R \omega_0 C = \frac{\omega_0 C}{G}$$

$$Y(j\omega_0) = G$$

$$BW = \frac{\omega_0}{Q}$$

Q14. A series RLC circuit resonates at 1000 rad/s. If $C = 20 \mu F$, and it is known that the impedance at resonance is 2.4Ω , compute the value of L , the Q of the circuit, and the bandwidth.

$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$\omega_0 = 1000 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



$$L = \frac{1}{\omega_0^2 C} = \frac{1}{1000^2 \times 20 \times 10^{-6}} = \frac{1}{20} = 50 \text{ mH}$$

$$Z(j\omega_0) = R = 2.4 \Omega$$

$$Q = \frac{\omega_0 L}{R} = \frac{1000 \times 50 \times 10^3}{2.4} \approx 20.83$$

$$BW = \frac{\omega_0}{Q} = \frac{1000}{20.83} \approx 48.01 \text{ rad/s.}$$

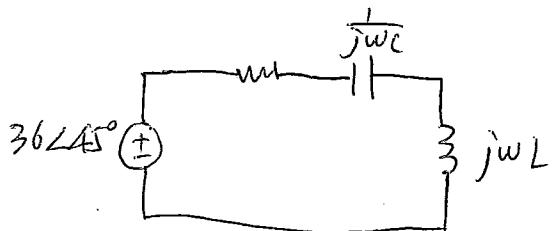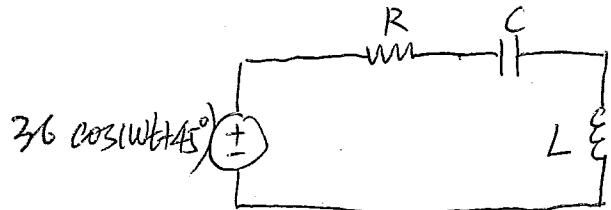Q15. In the network, the inductor value is 10mH , and the circuit is driven by a variable-frequency source. If the magnitude of the current at resonance is 12A , $\omega_0 = 1000 \text{ rad/s}$, and $L = 10\text{mH}$, find c , Q and the bandwidth of the circuit.



$$Z = R + \frac{1}{j\omega C} + j\omega L = R + j(\omega L - \frac{1}{\omega C})$$

$$\text{at resonance } Z = R = \frac{36}{12} = 3\Omega$$


$$Q = \frac{\omega_0 L}{R} = \frac{10^3 \times 10 \times 10^{-3}}{3} = \frac{10}{3} \approx 3.33$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(10^3)^2 \cdot (10 \times 10^{-3})} = \frac{1}{10^4} = 100 \mu\text{F}$$

$$BW = \frac{\omega_0}{Q} = \frac{10^3}{\frac{10}{3}} = 300 \text{ rad/s}$$

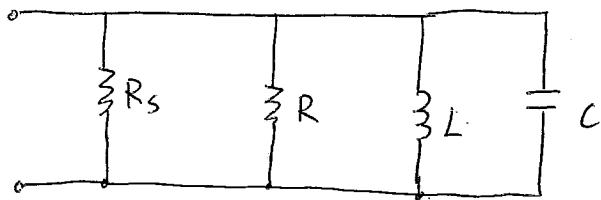Q16. Consider the network, if $R = 1\text{ k}\Omega$, $L = 20\text{ mH}$, $C = 50\text{ }\mu\text{F}$, and $R_s = \infty$, determine the resonance frequency ω_0 and Q of the network, and the ~~bandwidth~~ bandwidth of the network. What impact does an R_s of $10\text{ k}\Omega$ have on the quantities determined?



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 50 \times 10^{-6}}} = 10^3 \text{ rad/s}$$

If $R_s = \infty$,

$$Q = \omega_0 R C = 10^3 \times 10^3 \times 50 \times 10^{-6} = 50$$

$$BW = \frac{\omega_0}{Q} = \frac{1000}{50} = 20 \text{ rad/s}$$


When $R_s = 10\text{ k}\Omega$

$$R_{eq} = R_s // R = 10\text{ k}\Omega // 1\text{ k}\Omega = \frac{10 \times 1}{10 + 1} = \frac{10}{11} \text{ k}\Omega \approx 909\text{ }\Omega$$

$$Q = \omega_0 R_{eq} C = 10^3 \times 909 \times 50 \times 10^{-6} = 45.45$$

$$BW = \frac{\omega_0}{Q} = \frac{1000}{45.45} = 22 \text{ rad/s}$$

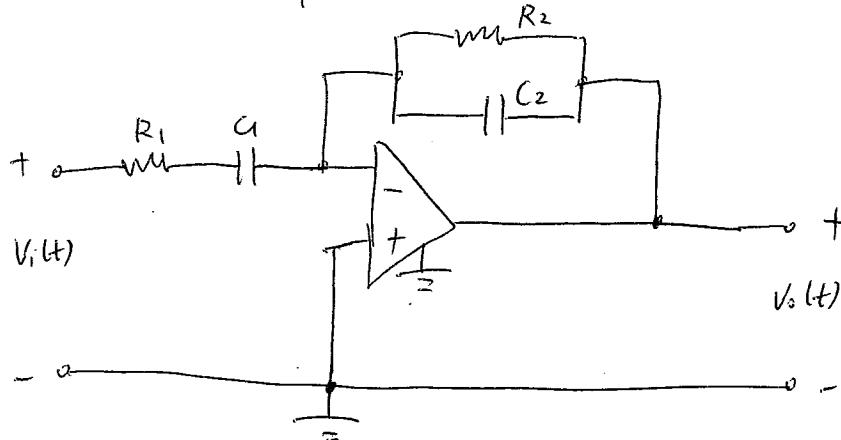Q17. Determine the voltage transfer function and its magnitude characteristic for the network and identify the filter properties.



(See Q9)

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1+j\omega C_1 R_1}{j\omega C_1} \quad Z_2 = R_2 || \frac{1}{j\omega C_2} = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1+j\omega C_2 R_2}$$


$$\begin{aligned} G_V(j\omega) &= \frac{V_o}{V_i} = - \frac{Z_2}{Z_1} = - \frac{R_2}{(1+j\omega C_2 R_2)} \cdot \frac{j\omega C_1}{(1+j\omega C_1 R_1)} \\ &= - \frac{j\omega C_1 R_2}{(j\omega C_1 R_1 + 1)(j\omega C_2 R_2 + 1)} \end{aligned}$$

zero at origin


$$\text{poles : } \omega_1 = \frac{1}{R_1 C_1} \quad \omega_2 = \frac{1}{R_2 C_2}$$

$$\left| G_V(j\omega) \right|_{\omega \rightarrow 0} \rightarrow 0 \quad \left| G_V(j\omega) \right|_{\omega \rightarrow \infty} \rightarrow 0, \quad \left| G_V(j\omega) \right|_{0 < \omega < \omega_0} > 0$$

The filter is a bandpass filter.

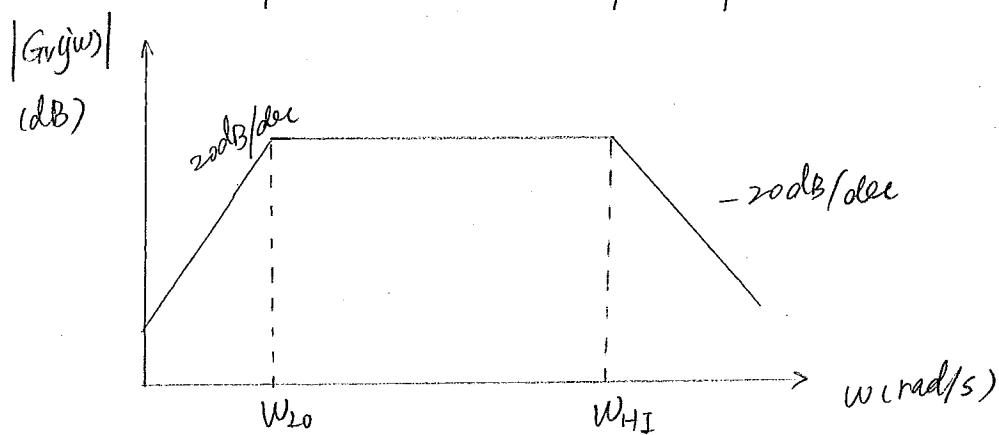

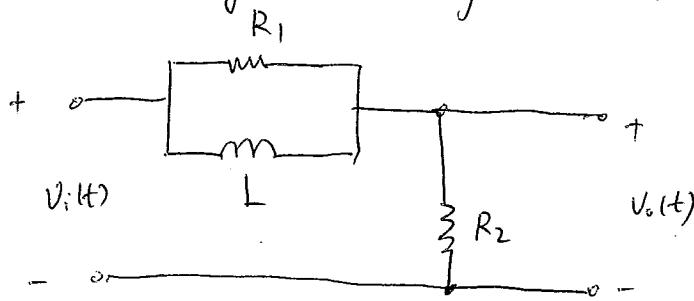
Q18. Determine what type of filter the network represents by determining the voltage transfer function.




$$\begin{aligned}
 G_V(j\omega) &= \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_2}{R_2 + R_1 || j\omega L} = \frac{R_2}{R_2 + \frac{R_1 \cdot j\omega L}{R_1 + j\omega L}} \\
 &= \frac{R_1 R_2 + j\omega R_2 L}{R_1 R_2 + j\omega R_2 L + j\omega R_1 L} \\
 &= \frac{R_2 (R_1 + j\omega L)}{R_1 R_2 + j\omega L (R_1 + R_2)} \\
 &= \frac{R_2}{R_1 + R_2} \cdot \frac{j\omega + \frac{R_1}{L}}{j\omega + \frac{R_1 R_2}{(R_1 + R_2)L}}
 \end{aligned}$$

$$G_V(j0) = 1 \quad G_V(j\infty) = \frac{R_2}{R_1 + R_2} < 1$$

The filter is a lowpass filter

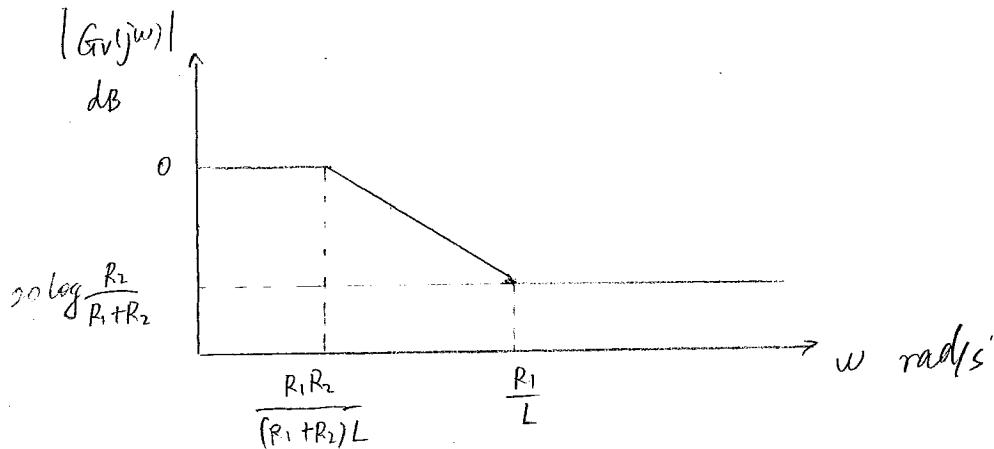

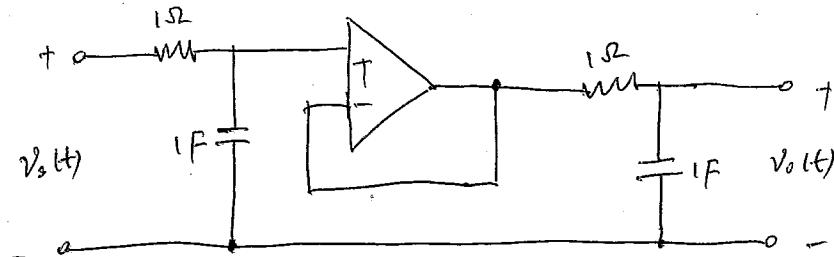Q19. Given the network in the following figure, and employing the voltage follower analyzed in chapter 4, determine the voltage transfer function and its magnitude characteristic. What type of filter does the network represent?




(See Q7)


$$G_V(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = \frac{1}{(1+j\omega)^2}$$

second order pole at 1 rad/s

The filter is a lowpass filter.

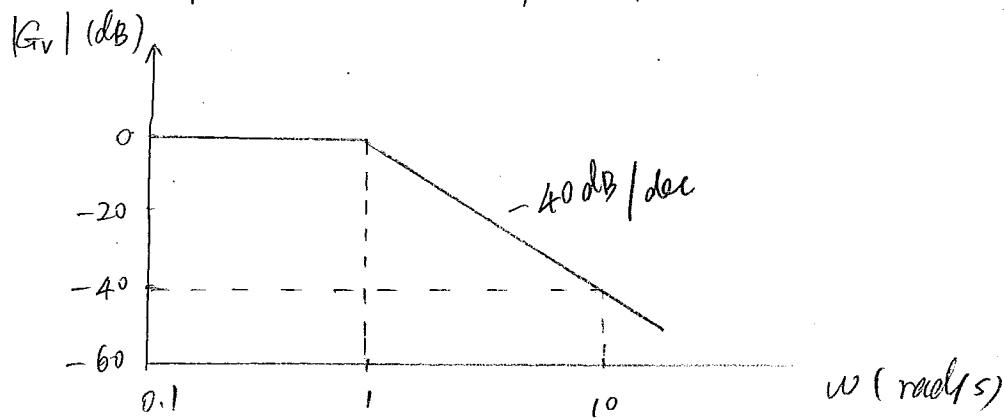

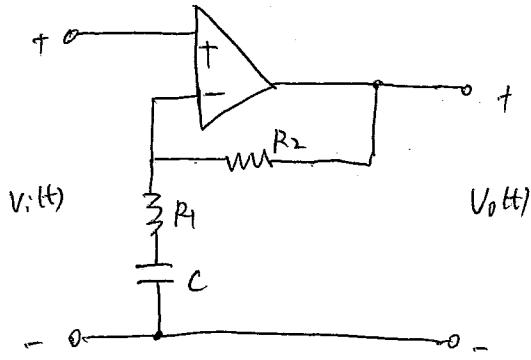Q20. Given the network, find the transfer function $\frac{V_o}{V_i}(j\omega)$ and determine what type of filter the network represents.




(See Q10)

$$G_V(j\omega) = \frac{V_o}{V_i}(j\omega) = \frac{1 + j\omega C(R_1 + R_2)}{1 + j\omega CR_1}$$


First order simple zero : $\omega_1 = \frac{1}{C(R_1 + R_2)}$

First order simple pole : $\omega_2 = \frac{1}{CR_1}$

$$|G_V(j0)| = 1 \quad |G_V(j\infty)| = \frac{R_1 + R_2}{R_1} > 1 \quad \text{High pass filter}$$

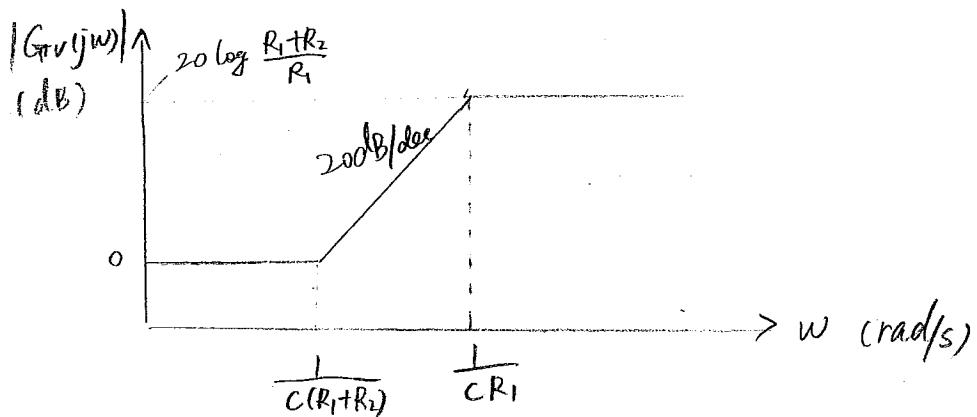

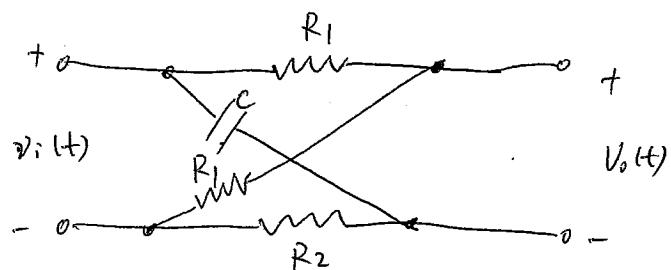Q21. Determine what type of filter this network represents by determining the voltage transfer function.



(see Q6)


$$G_V(j\omega) = \frac{1}{2} \left[\frac{1-j\omega R_2 C}{1+j\omega R_2 C} \right]$$

$$|G_V(j\omega)| = \frac{1}{2} \sqrt{\frac{1+\omega^2 R_2^2 C^2}{1+\omega^2 R_2^2 C^2}} = \frac{1}{2}$$

$|G_V(j\omega)|$ is independent of ω .

The filter is an allpass filter.

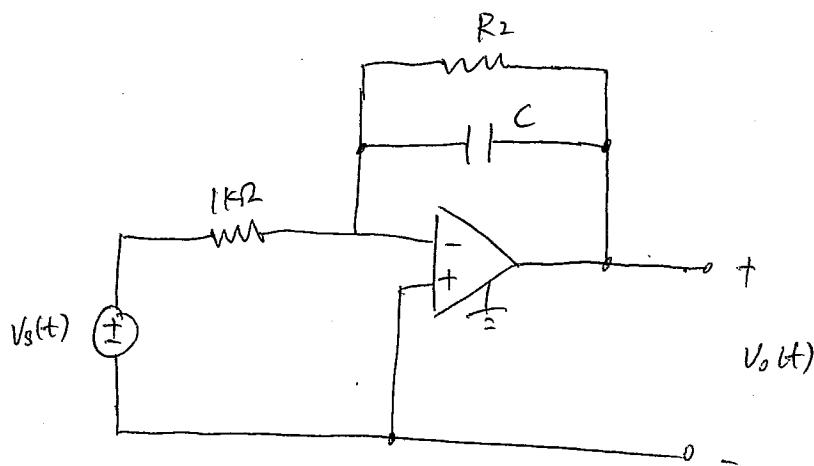Q22. For the low-pass active filter in the following figure, choose R_2 and C such that $H_0 = -7$ and $f_c = 10 \text{ kHz}$



$$\text{Let } Z_1 = 1 \text{ k}\Omega$$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C} = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1}$$

$$H(j\omega) = - \frac{Z_2}{Z_1} = - \frac{R_2}{(j\omega C R_2 + 1) \cdot 10^3}$$

$$= - \frac{1}{10^3 C} \cdot \frac{1}{j\omega + \frac{1}{R_2 C}}$$

$$H_0 = - \frac{R_2 C}{10^3 C} = -7 \Rightarrow R_2 = 7 \text{ k}\Omega$$

$$\omega_0 = \frac{1}{R_2 C} = 2\pi f_c = 2\pi \times 10^3 \times 10$$

$$C = \frac{1}{R_2 \cdot 2\pi \times 10^3 \times 10} = \frac{1}{2\pi \times 10^3 \times 7 \times 10^3 \times 10} \approx 2.27 \text{ nF}$$