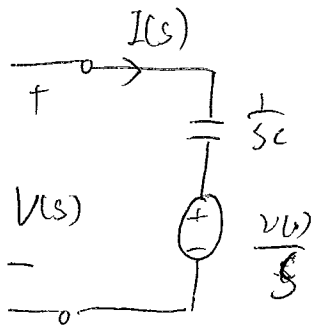




\xleftrightarrow{S}




$$i(t) = C \frac{dv(t)}{dt}$$

$$\Leftrightarrow I(s) = C (sV(s) - v(0))$$
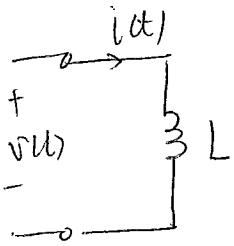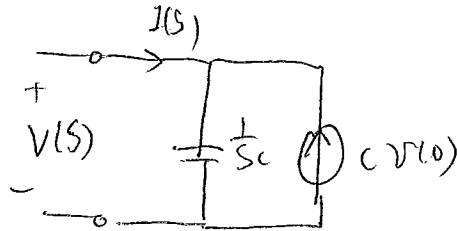
$$V(s) = \frac{1}{sC} I(s) + \frac{v(0)}{s}$$




\xleftrightarrow{S}

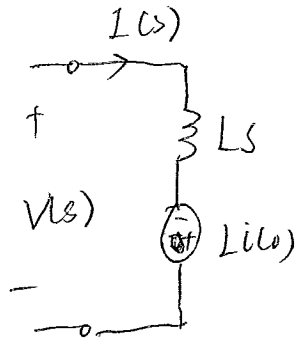


$$v(t) = L \frac{di(t)}{dt}$$

$$\Leftrightarrow V(s) = L (sI(s) - i(0))$$


$$= sL I(s) - L i(0)$$

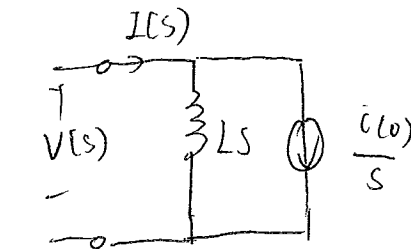

nodal analysis:

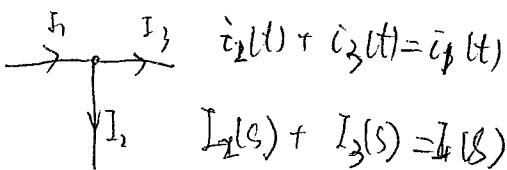

Loop analysis:



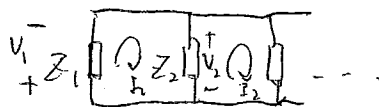


$$V_1 + V_2 = 0$$


$$I_1 Z_1 + (I_1 - I_2) V_2 = 0$$

$$I_2 (Z_1 + Z_2) - I_1 V_2 = 0$$


Thevenin's:

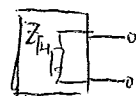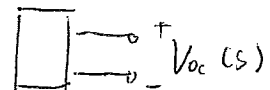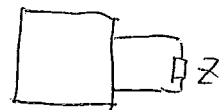

Q1: Find the input impedance $Z(s)$

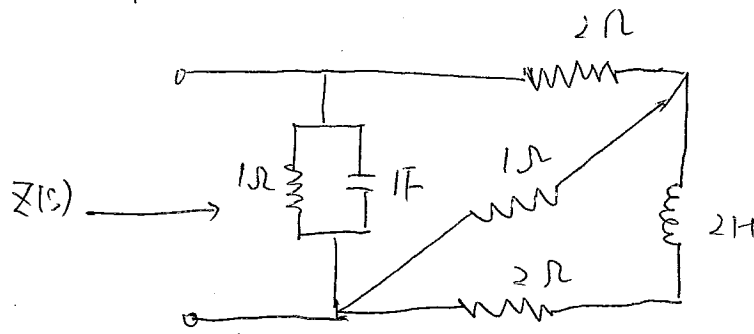


Sol:

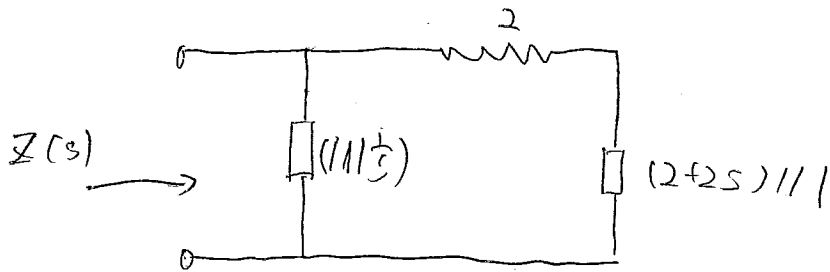


$$Z(s) = (1 \parallel \frac{1}{s}) \parallel [2 + (2 + 2s) \parallel 1]$$

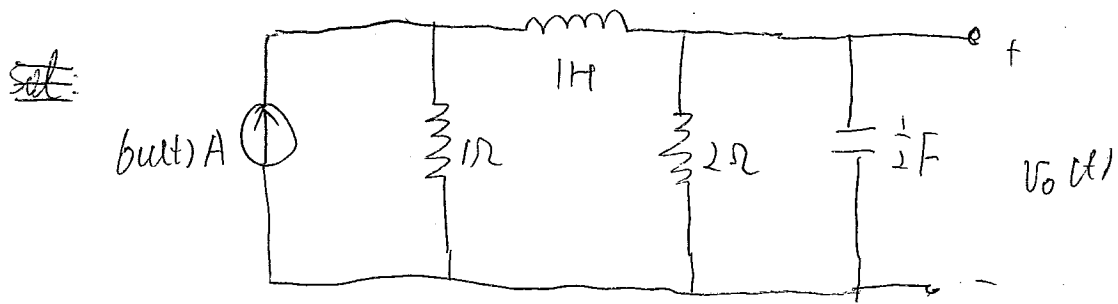Q2: Determine the value of the output voltage as $t \rightarrow \infty$



sol: For $t > 0$, the input is DC, all voltages and currents will become DC as well, so $V_c \rightarrow 0$ and $i_L \rightarrow 0$ as $t \rightarrow \infty$.

When $t \rightarrow \infty$,

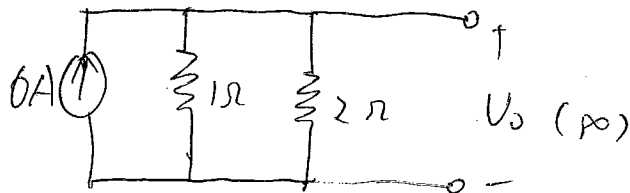


$$V_o(\infty) = 6 \cdot (1/12)$$


$$= 6 \cdot \frac{2}{1+2}$$

$$= 4V$$

Q3: find $i_1(t)$, $t > 0$.

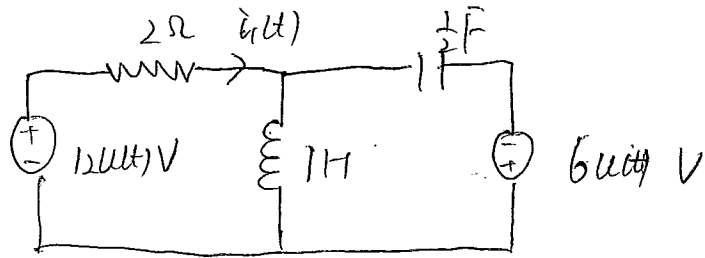

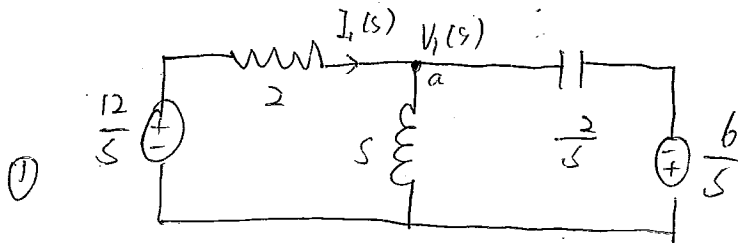sol: Because of zero initial conditions, for $t > 0$



② KCL at a:
$$\frac{\frac{12}{s} - V_1(s)}{2} = \frac{V_1(s)}{s} + \frac{V_1(s) + \frac{6}{s}}{\frac{1}{s}}$$

$$V_1(s) = \frac{6(2-s)}{s^2 + s + 2}$$

③
$$I_1(s) = \frac{\frac{12}{s} - V_1(s)}{2} = \frac{3(3s^2 + 4)}{s(s^2 + s + 2)}$$


④
$$I_1(s) = \frac{A}{s} + \frac{B}{s + \frac{1}{2} - j\frac{\sqrt{7}}{2}} + \frac{B^*}{s + \frac{1}{2} + j\frac{\sqrt{7}}{2}}$$

⑤
$$A = I_1(s) \Big|_{s=0} = \frac{12}{2} = 6$$


$$B = I_1(s) (s + \frac{1}{2} - j\frac{\sqrt{7}}{2}) \Big|_{s = -\frac{1}{2} + j\frac{\sqrt{7}}{2}} = 3.21 \angle 62.1^\circ$$

⑥
$$i_1(t) = [6 + 6.42 e^{-\frac{t}{2}} \cos(\frac{\sqrt{7}}{2}t + 62.1^\circ)] u(t) \text{ A}$$

Q4: find $i_o(t)$, $t > 0$.

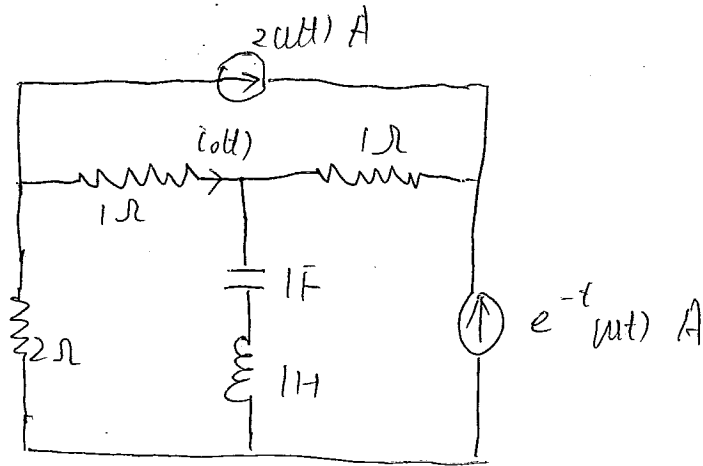

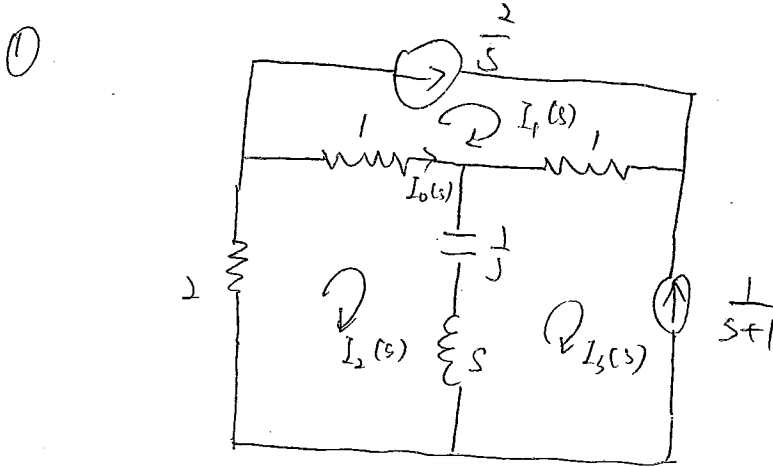sol. because of zero initial conditions, when $t > 0$.



② Loop equations: $(2+1+\frac{1}{s}+s)I_2(s) = I_1(s) + (\frac{1}{s}+s)I_3(s)$


Also: $I_1(s) = \frac{2}{s}$, $I_3(s) = -\frac{1}{s+1}$, $I_o(s) = I_2(s) - I_1(s)$

③ $\Rightarrow I_o(s) = \frac{-3s^3 + 6s^2 + 7s + 2}{s(s+1)(s+0.382)(s+2.62)}$

④ $I_o(s) = \frac{-2}{s} + \frac{2}{s+1} + \frac{0.065}{s+0.382} - \frac{3.06}{s+2.62}$


⑤ $i_o(t) = [-2 + 2e^{-t} + 0.065e^{-0.382t} - 3.06e^{-2.62t}] u(t) \text{ A}$

Q5: find $v_o(t)$, $t > 0$

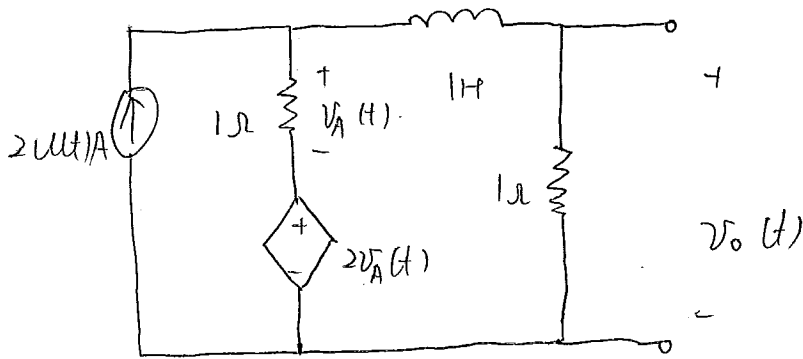


Sol: Zero initial conditions.

Using Thevenin's theorem.

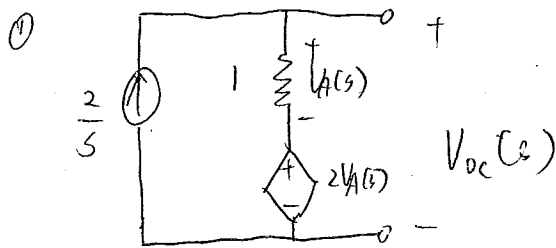


$$v_A(s) = \frac{2}{s} - 1$$

$$V_{OC}(s) = 3v_A(s) = \frac{6}{s}$$

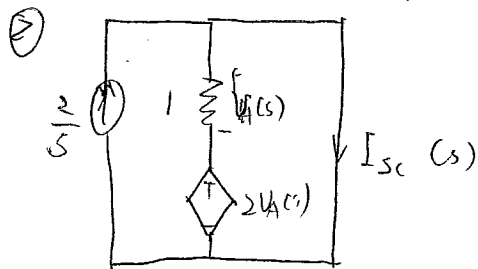

$$I_{SC}(s) = \frac{2}{s}$$
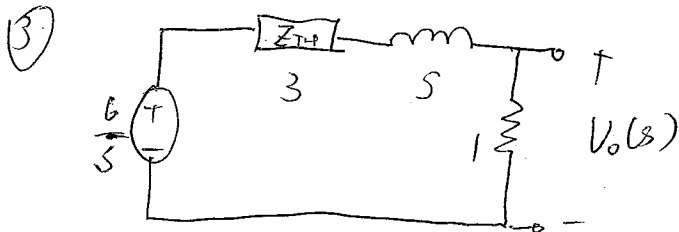
$$Z_{TH}(s) = \frac{V_{OC}(s)}{I_{SC}(s)} = 3$$



④

$$v_o(s) = \frac{1}{4+s} \times \frac{6}{s}$$


⑤

$$v_o(s) = \frac{3}{s} - \frac{3}{s+4}$$


⑥

$$v_o(t) = 1.5 (1 - e^{-4t}) u(t) \text{ V}$$

Q6: find $i_o(t)$, $t > 0$

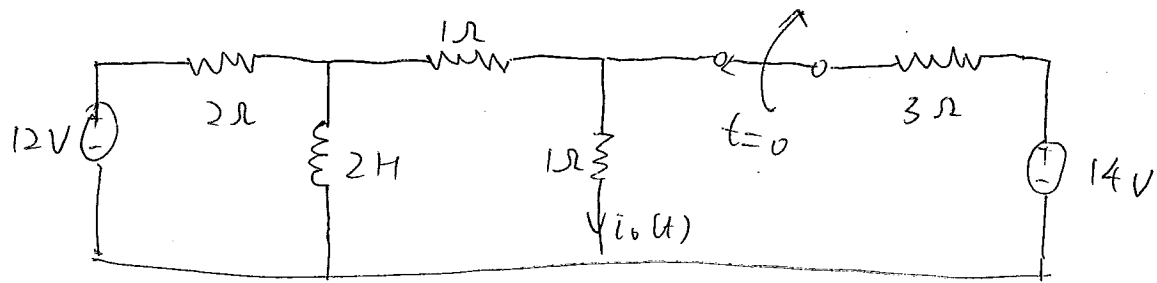

Sol: ① when $t = 0^-$

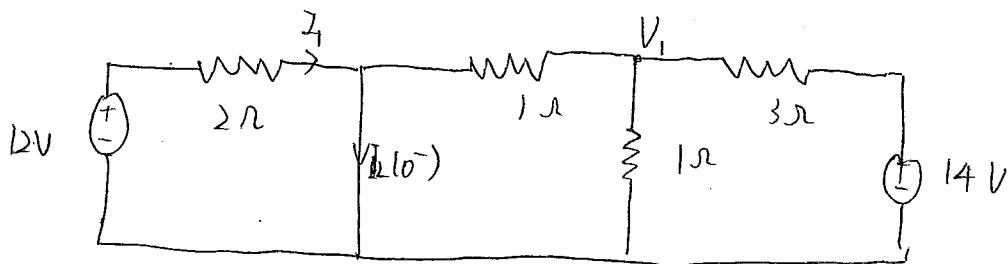


$$1) I_1 = \frac{12V}{2\Omega} = 6A$$

$$2) \frac{14 - V_1}{3} = \frac{V_1}{1} + \frac{V_1}{1} \Rightarrow V_1 = 2V$$

$$3) I_o(0^-) = I_1 + \frac{V_1}{1} = 8A$$

② when $t > 0$:

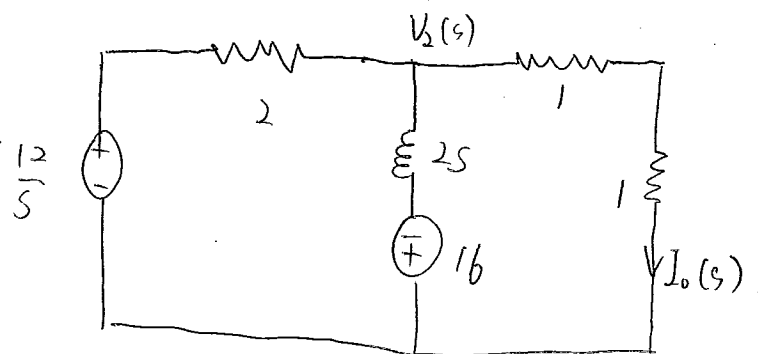

$$1) \text{KCL at } V_2: \frac{\frac{12}{5} - V_2(s)}{2} = I_o(s) + \frac{V_2(s) + 16}{25}$$


$$2) \text{Also: } V_2(s) = 2I_o(s)$$

Q6:


$$3) \quad I_0(s) = \frac{-8s}{s(8s+4)} = \frac{-4}{2s+1} = \frac{-2}{s+\frac{1}{2}}$$

$$4) \quad i_0(t) = -e^{-\frac{t}{2}} \text{ (A)}$$

Q7: find $v_o(t)$, $t > 0$.

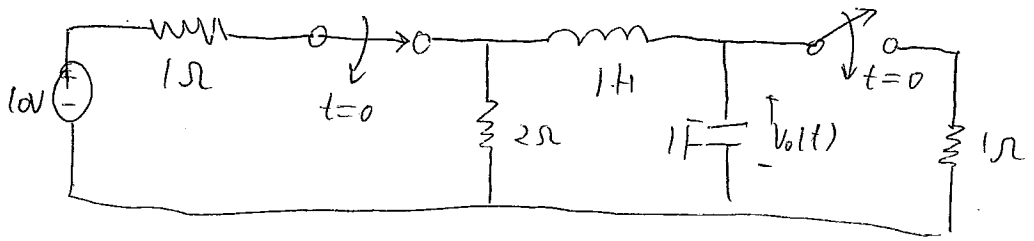


sol. ① When $t=0^-$

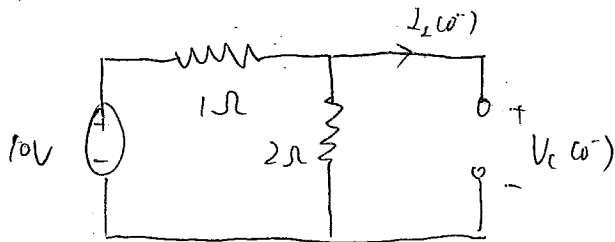

$$1) I_L(0^-) = 0 \text{ A}$$

$$2) V_C(0^-) = \frac{2}{1+2} \cdot 10 = \frac{20}{3} \text{ V}$$

② When $t > 0$,

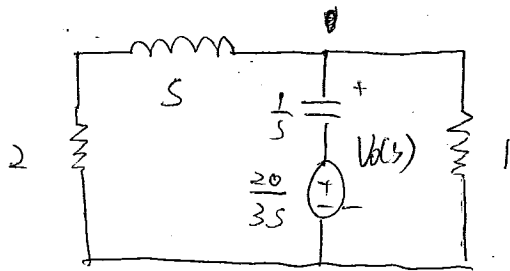

$$1) \text{KCL: } \frac{V_o(s)}{s+2} + \frac{V_o(s)}{1} + \frac{V_o(s) - \frac{20}{3s}}{\frac{1}{s}} = 0$$


$$2) V_o(s) = \frac{\frac{20}{3} (s+2)}{s^2 + 3s + 3}$$

$$3) V_o(s) = \frac{A}{s + \frac{3}{2} - j\frac{\sqrt{3}}{2}} + \frac{A^*}{s + \frac{3}{2} + j\frac{\sqrt{3}}{2}}$$


$$A = V_o(s) (s + \frac{3}{2} - j\frac{\sqrt{3}}{2}) \Big|_{s = -\frac{3}{2} + j\frac{\sqrt{3}}{2}} = 3.85 \angle -30^\circ$$

$$4) v_o(t) = [7.7 e^{-\frac{3}{2}t} \cos(\frac{\sqrt{3}}{2}t - 30^\circ)] \text{ u(t)} \text{ V}$$

Q8: find $i_o(t)$, $t > 0$.

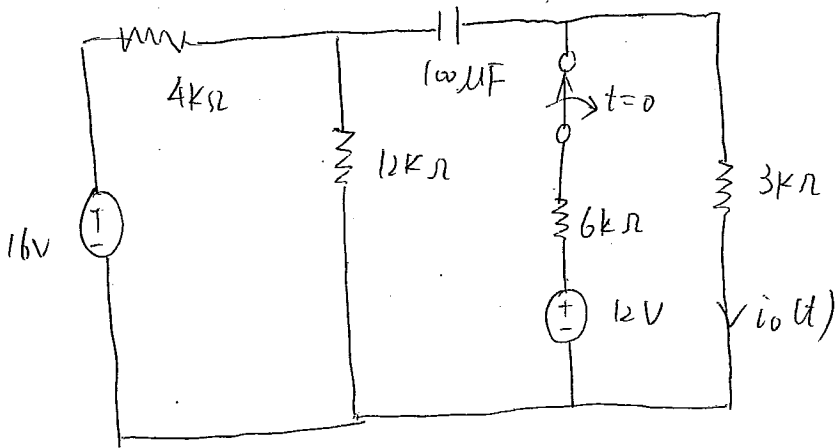

Sol. ① when $t = 0^-$

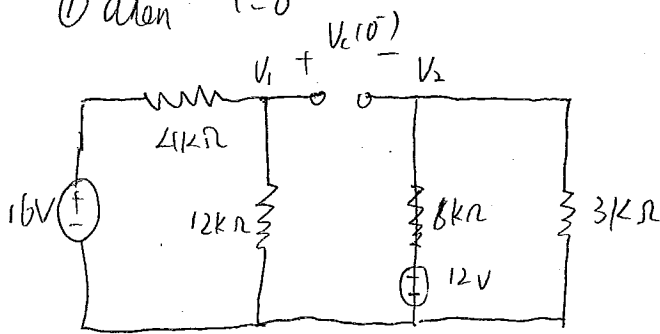


$$1) V_1 = \frac{12k}{12k+4k} \cdot 16 = 12V$$

$$V_2 = \frac{3k}{6k+3k} \cdot 12V = 4V$$

$$2) V_c(0^-) = V_1 - V_2 = 8V$$

② when $t > 0$.

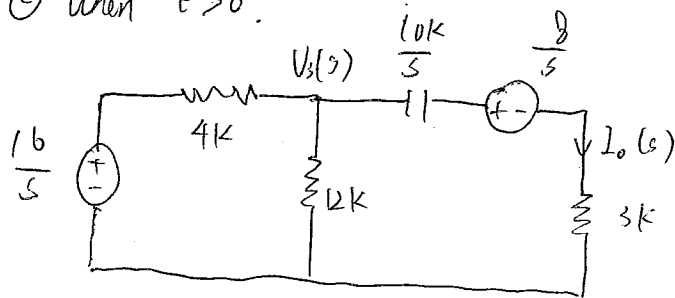



$$1) \text{KCL: } \frac{16/5 - V_3(s)}{4k} = \frac{V_3(s)}{12k} + I_o(s)$$

$$\text{Also: } V_3(s) = \frac{8}{s} + I_o(s) \cdot (3k + \frac{10k}{5})$$

$$2) I_o(s) = \frac{2/3}{s + 5/3} \text{ mA}$$

$$3) i_o(t) = \frac{2}{3} e^{-\frac{5}{3}t} \text{ (mA)}$$

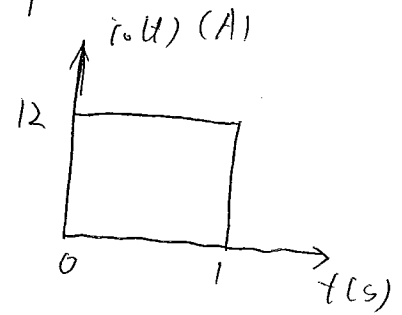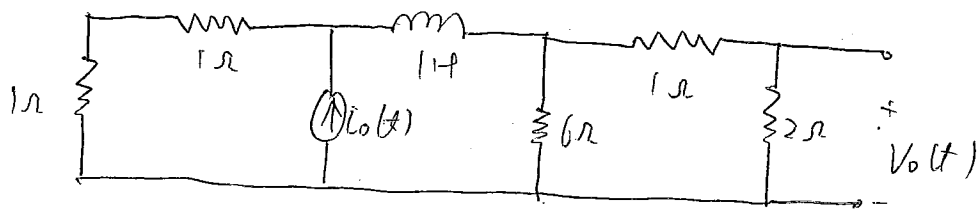
Q9: Find $V_o(t)$, $t > 0$, if the input is represented by the waveform below.



sol: 1) $i_o(t) = 12 u(t) - 12 u(t-1) A$

$$I_o(s) = \frac{12}{s} (1 - e^{-s}) A$$

2) when $t > 0$

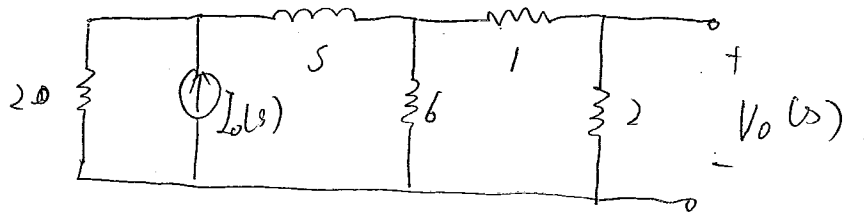


$$1) V_o(s) = \frac{2}{(s+6/13)+2} \times \frac{6}{6+3} I_o(s) \times 2$$

$$2) V_o(s) = \frac{32}{s(s+4)} (1 - e^{-s})$$

$$3) V_o(s) = \left(\frac{8}{s} - \frac{8}{s+4} \right) - \left(\frac{8}{s} - \frac{8}{s+4} \right) e^{-s}$$


$$4) V_o(t) = (8 - 8e^{-4t}) u(t) - [8 - 8e^{-4(t-1)}] u(t-1) V.$$

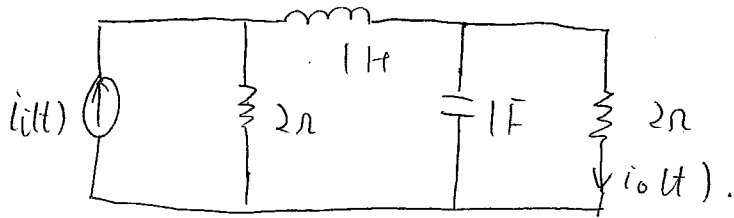Q.10: Determine the transfer function $I_o(s) / I_i(s)$.



Sol:
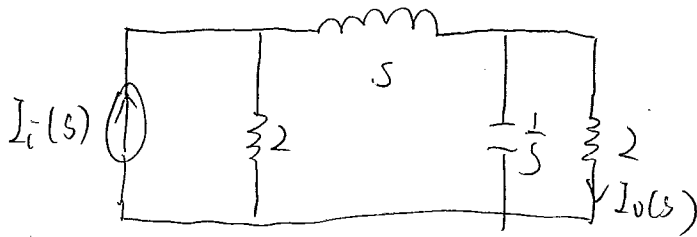
$$I_o(s) = \frac{2}{2 + (s + \frac{1}{3} // 2)} \times \frac{\frac{1}{3}}{2 + \frac{1}{3}} \times I_i(s)$$



$$\frac{I_o(s)}{I_i(s)} = \frac{1}{s^2 + \frac{5}{2}s + 2}$$

Q11 Transfer function:

$$G(s) = \frac{100s}{s^2 + 13s + 40}$$

Determine the damping ratio, the undamped frequency, and the type of response that will be exhibited by the network.

Sol: Characteristic equation:

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

ζ : damping ratio, ω_0 : undamped frequency

$\zeta > 1$: overdamped, $\zeta < 1$: underdamped, $\zeta = 1$: critically damped.

In this problem,


1) $s^2 + 13s + 40 = 0$

2) $\omega_0 = \sqrt{40}$ rad/s,


3) $2\zeta\omega_0 = 13 \Rightarrow \zeta = \frac{13}{2\sqrt{40}} = 1.03$

4) $\zeta > 1$, the system is overdamped.

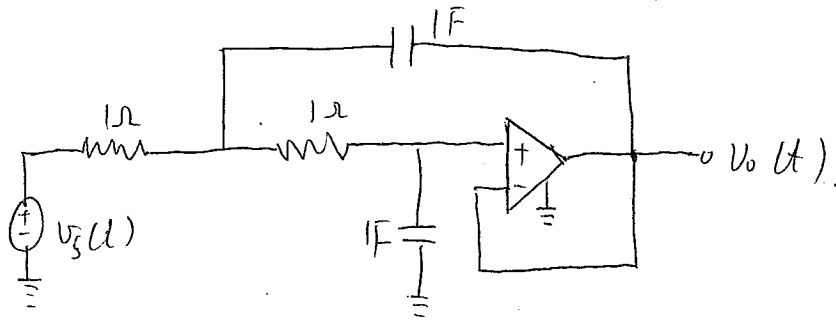Q2. Find the transfer function. If the step function is applied to the network, will the response be overdamped, underdamped, or critically damped?



Sol: In s-domain,

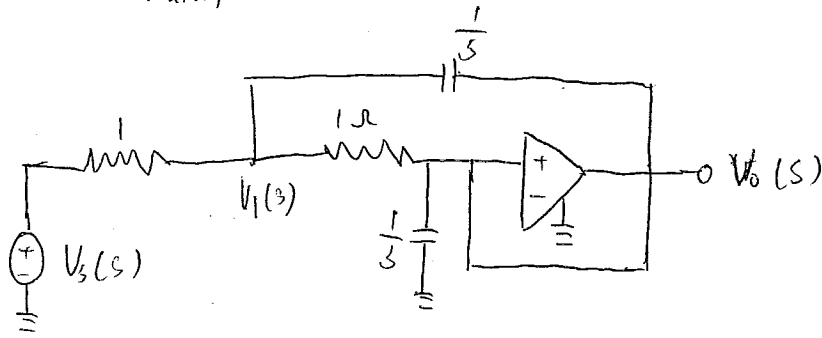

$$1) \quad \frac{v_s(s) - v_1(s)}{1} = \frac{v_1(s) - v_o(s)}{\frac{1}{s}} + \frac{v_1(s)}{1 + \frac{1}{s}}$$

$$\left\{ \begin{array}{l} \frac{v_1(s)}{1 + \frac{1}{s}} = \frac{v_o(s)}{\frac{1}{s}} \end{array} \right.$$

$$2) \quad \frac{v_o(s)}{v_s(s)} = \frac{1}{(s+1)^2}$$


$$3) \quad s^2 + 2s + 1 = 0$$

$$\omega_0 = 1 \text{ rad/s}$$


$$2\zeta\omega_0 = 2 \Rightarrow \zeta = 1$$

The system is critically damped.

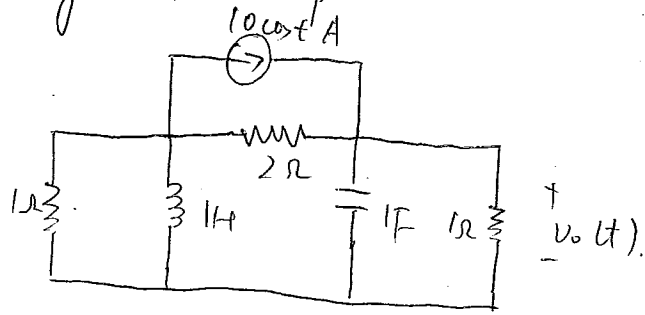Q13: Find the steady-state response $v_o(t)$.



Sol: Source change:

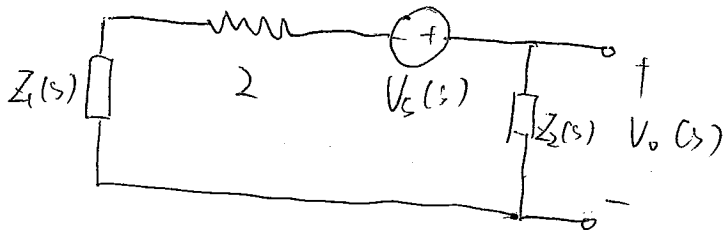

$$1) Z_1(s) = 1/s = \frac{1}{s}, \quad Z_2(s) = 1/s = \frac{1}{s+1}$$

$$2) V_s(s) = 20 \angle 0^\circ \text{ V}$$

$$3) V_o(s) = \frac{Z_2(s)}{Z_1(s) + 2 + Z_2(s)} V_s(s)$$

$$4) V_o(s) = \frac{1/3}{1+s} V_s(s)$$


5) In steady-state, let $s = j\omega$

$$V_o(s) = \frac{1/3}{1+j\omega} \cdot 20 \angle 0^\circ$$


$$= 4.71 \angle -45^\circ \text{ V}$$

$$6) V_{os}(t) = 4.71 \cos(t - 45^\circ) \text{ V}$$

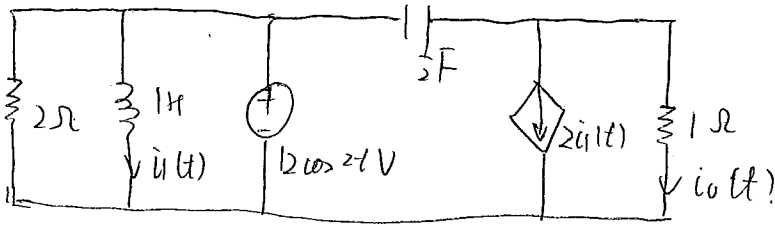Q(4): Determine the steady-state response $i_o(t)$.



Sol: In s -domain:

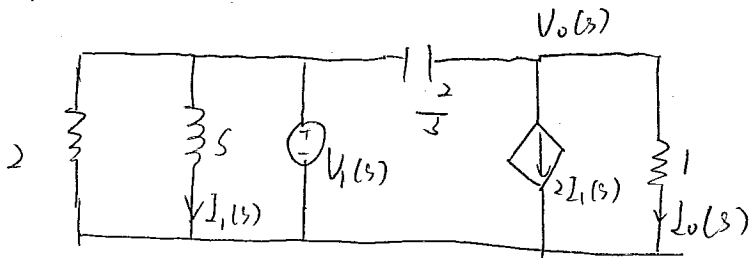

$$V_1(s) = 12 \angle 0^\circ \text{ V}$$

$$1) I_1(s) = \frac{V_1(s)}{s}, \quad I_o(s) = \frac{V_o(s)}{1}$$

$$\text{KCL: } \frac{V_o(s) - V_1(s)}{\frac{2}{s}} + 2I_1(s) + \frac{V_o(s)}{1}$$

$$2) I_o(s) = \frac{s-2}{s} V_1(s)$$

3) In steady state, let $s = j2$.

$$I_o(s) = \frac{j2-2}{j2} \cdot 12 \angle 0^\circ$$

$$= 16.97 \angle 45^\circ \text{ A}$$

$$4) i_{oss}(t) = 16.97 \cos(2t + 45^\circ) \text{ A}$$