
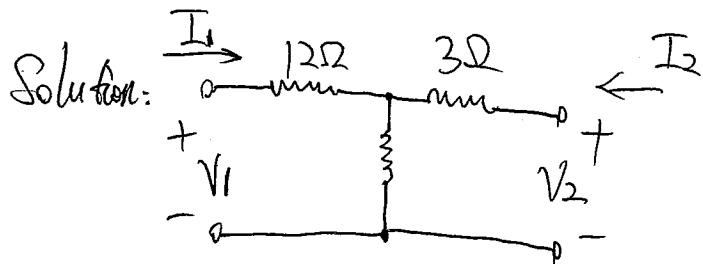


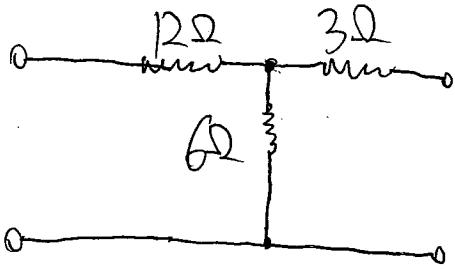Q1. Find the  $\Upsilon$  parameters for the two-port network shown below.




$$Y_{11} = I_1 / V_1 \Big|_{V_2=0} = \frac{1}{12 + (6//3)} = \frac{1}{14} S.$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{3 + (2//6)} = \frac{1}{7} S$$

$$Y_{12} = -\frac{I_1}{V_2} \Big|_{V_1=0} = \left[ -\frac{12//6}{(12//6) + 3} \right] \left( -\frac{1}{12} \right) = -\frac{1}{21} S$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \left[ -\frac{3//6}{(3//6) + 12} \right] \left( -\frac{1}{3} \right) = -\frac{1}{21} S$$

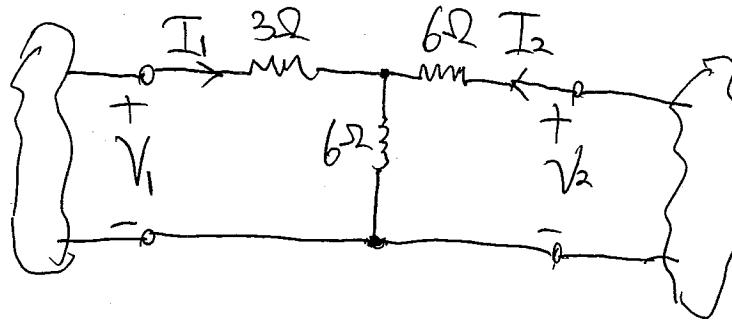Q2. Determine the  $\Upsilon$  parameters for the network.




$$\text{Solution: } \Upsilon_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{3 + (6//6)} = \frac{1}{6} \text{ S.}$$

$$\Upsilon_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{6 + (6//3)} = \frac{1}{8} \text{ S}$$

$$\Upsilon_{12} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{6//6}{(6//6) + 3} \left(-\frac{1}{6}\right) = -\frac{1}{12} \text{ S.}$$

$$\Upsilon_{21} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{3//6}{(3//6) + 6} \left(-\frac{1}{3}\right) = -\frac{1}{12} \text{ S.}$$

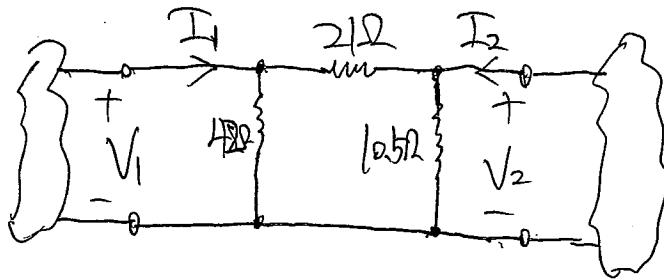Q3. Find the  $\mathbf{Z}$  parameters for the two-port network.




$$\text{So } Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 4\Omega \parallel (2 + 1.5) = 1.8\Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 1.5\Omega \parallel (2 + 4\Omega) = 0.9\Omega$$


$$Z_{12} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{4\Omega}{4\Omega + 2 + 1.5} (1.5) = 6\Omega$$

$$Z_{21} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{1.5}{1.5 + 2 + 4\Omega} (4\Omega) = 6\Omega$$

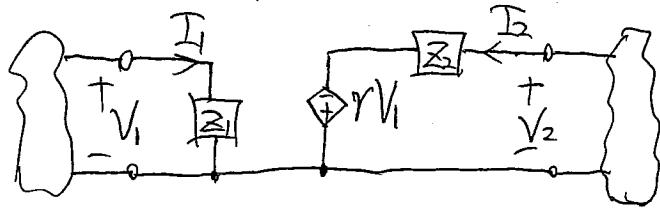Q4. Find the  $\Sigma$  parameters for the network.



Solution:

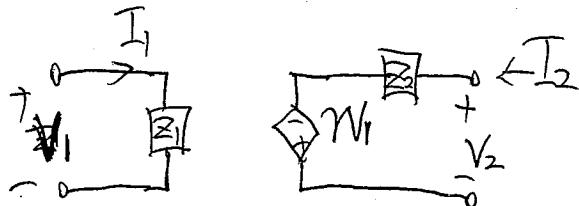


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = Z_1$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_2$$

$$Z_{12} = \frac{V_2}{I_1} \Big|_{I_2=0} = -\frac{rV_1}{V_1/Z_1} = -rZ_1$$

$$Z_{21} = \frac{V_1}{I_2} \Big|_{I_1=0} = 0$$

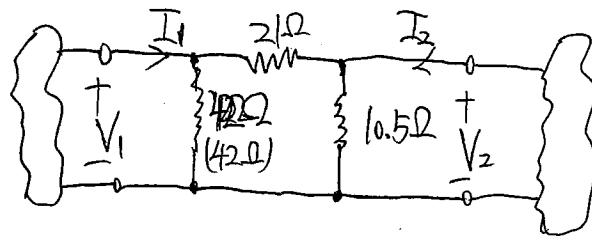Q5. Compute the hybrid parameters for the network.



Solution:

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = R_1 // R_2 = 14\Omega$$


$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = - \frac{R_1}{R_1 + R_2} = -\frac{2}{3}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{R_1}{R_1 + R_2} = \frac{2}{3}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{1}{R_3 // (R_1 + R_2)} = \frac{1}{9} S.$$



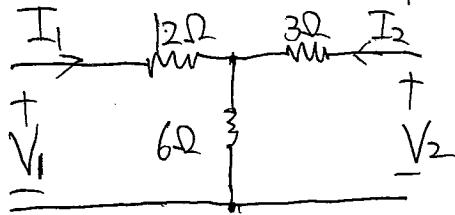Q7. Find the transmission parameters for the network.




$$\text{Solution: } A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow V_2 = \frac{6}{18} V_1 \Rightarrow A = 3$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \Rightarrow -I_2 = \frac{(3/6)V_1}{V_2 + (3/6)} \quad (1) \Rightarrow B = 2\Omega$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{1}{6} S.$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} \Rightarrow -I_2 = I_1 \left( \frac{6}{6+3} \right) \Rightarrow D = \frac{3}{2}$$

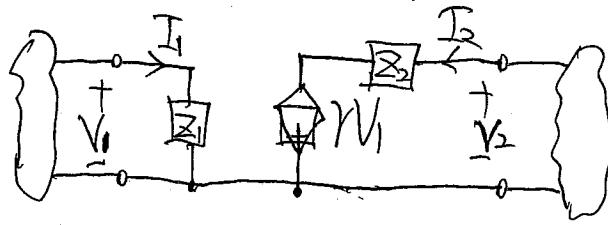Q8. Find the ABCD parameters for the circuit.



$$\text{Solution: } A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow V_2 = -rV_1 \Rightarrow A = -\frac{1}{r}$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \Rightarrow I_2 = \frac{rV_1}{Z_2} \Rightarrow B = -\frac{Z_2}{r}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \Rightarrow V_2 = -rV_1, V_1 = I_1 Z_1 \Rightarrow C = -\frac{1}{rZ_1}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} \Rightarrow I_2 = \frac{M_1}{Z_2}, I_1 = \frac{V_1}{Z_1} \Rightarrow D = -\frac{Z_2}{rZ_1}$$

Q9. Following are the hybrid parameters for a network.

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{5} & \frac{2}{5} \\ -\frac{2}{5} & \frac{1}{5} \end{bmatrix}$$

Determine the Y parameters for the network.

Solution:  $* y_{11} = \frac{1}{h_{11}} = \frac{5}{11} s.$

$$* y_{12} = -\frac{h_{12}}{h_{11}} = -\frac{2}{11} s.$$

$$* y_{21} = \frac{h_{21}}{h_{11}} = -\frac{2}{11} s.$$

$$y_{22} = \frac{\Delta_4}{h_{11}}, \quad \Delta_4 = \frac{11}{5} \left(\frac{1}{5}\right) - \left(-\frac{2}{5}\right) \left(\frac{2}{5}\right) = \frac{11}{25} + \frac{4}{25} = \frac{15}{25} = \frac{3}{5}$$

$$\Rightarrow * y_{22} = \frac{3}{11} s.$$

Q10. If the  $\gamma$  parameters for a Network are known to be

$$\begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{\pi} & -\frac{2}{\pi} \\ -\frac{2}{\pi} & \frac{3}{\pi} \end{bmatrix}$$

Find the  $\mathbf{z}$  parameters.

Solution:  $\Delta\gamma = \frac{5}{\pi}(\frac{3}{\pi}) - (-\frac{2}{\pi})^2 = \frac{15}{\pi^2} - \frac{4}{\pi^2} = \frac{11}{\pi^2} = \frac{1}{\pi}$


$$Z_{11} = \frac{\gamma_{22}}{\Delta\gamma} = 3\Omega$$

$$Z_{12} = -\frac{\gamma_{12}}{\Delta\gamma} = 2\Omega$$


$$Z_{21} = -\frac{\gamma_{21}}{\Delta\gamma} = 2\Omega$$

$$Z_{22} = \frac{\gamma_{11}}{\Delta\gamma} = 5\Omega$$

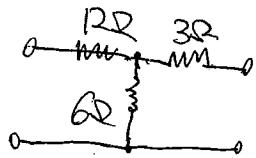Q11. Find the transmission parameters of the network in




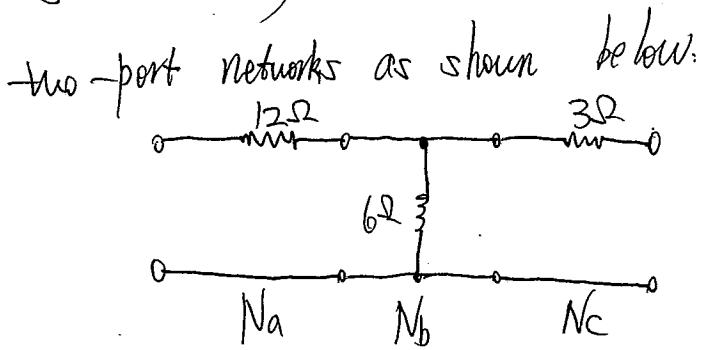by considering the circuit to be a cascade interconnection of three two-port networks as shown below:



Solution: Network consists of 3 two-ports.

Circuit A

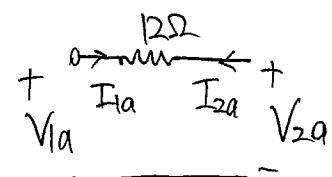


$$A_a = \frac{V_1}{V_2} \Big|_{I_2=0} = 1$$

$$B_a = \frac{V_1}{-I_2} \Big|_{V_2=0} = 12\Omega$$

$$C_a = \frac{I_1}{V_2} \Big|_{I_2=0} = 0$$

$$D_a = \frac{I_1}{-I_2} \Big|_{V_2=0} = 1$$

Circuit B

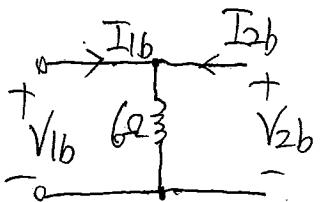


$$A_b = 1$$

$$B_b = 0 \quad (I_{2b} = \infty)$$

$$C_b = \frac{1}{6} S$$

$$D_b = 1$$

Circuit C

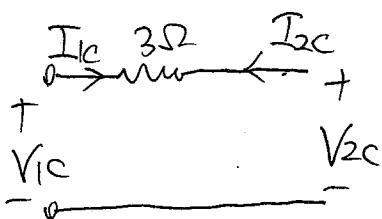

$$A_c = 1$$


$$B_c = 3\Omega$$

$$C_c = 0$$

$$D_c = 1$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 12 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{6} & 1 \end{bmatrix} \begin{bmatrix} 1 & 3 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 & 21 \\ 0 & \frac{3}{2} \end{bmatrix}$$

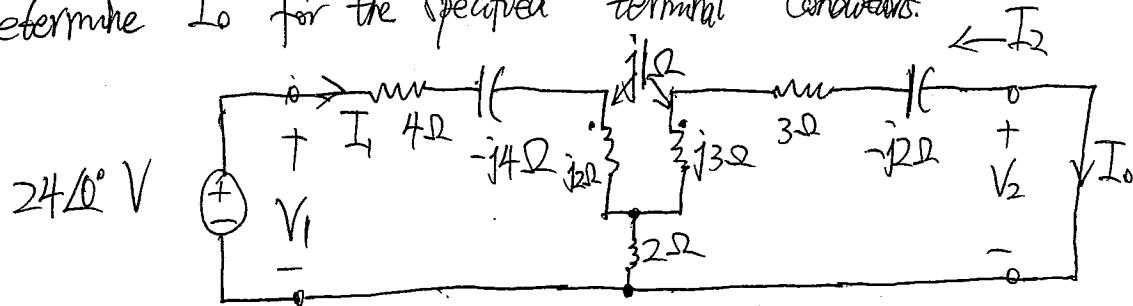Q12. Find the  $Z$  parameters for the two-port network below and then determine  $I_o$  for the specified terminal conditions.



Solution:

$$V_1 = I_1 (6 - j2) + I_2 (2 + j1)$$

$$\boxed{Z_{11} = 6 - j2 \Omega \quad Z_{12} = 2 + j1 \Omega \\ Z_{21} = 2 + j1 \Omega \quad Z_{22} = 5 + j1 \Omega}$$

$$V_2 = I_1 (2 + j1) + I_2 (5 + j1)$$

$$V_1 = 24\angle 10^\circ V$$

$$I_2 = I_o$$

$$V_2 = 0$$

$$\begin{bmatrix} 6 - j2 & 2 + j1 \\ 2 + j1 & 5 + j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 24\angle 10^\circ \\ 0 \end{bmatrix} \Rightarrow I_2 = 1.78\angle 138^\circ A$$

$$\Rightarrow I_o = 1.78\angle 42^\circ A.$$