

# Laboratory 2: Exploring the Basic Properties of Op-Amp

ELEC ENG 2CJ4: Circuits and Systems  
Instructor: Prof. Jun Chen

## 1 Objective

The objective of this lab is for you to become familiar with the basic properties of the operational amplifier circuits.

## 2 Equipment

The following equipments are used in this laboratory:

- DC voltage source with positive and negative output( $\pm 10\text{V}$ ); Oscilloscope; Function signal generator
- Resistors:  $10\text{k}\Omega \times 2$ ,  $22\text{k}\Omega \times 2$ ,  $27\text{k}\Omega \times 2$ ,  $100\text{k}\Omega \times 2$
- Op-Amp: LMC358

**LM358** Dual operational amplifier (see Figure 1) consists of two independent, high-gain frequency-compensated operational amplifiers designed to operate from a single supply or split supply over a wide range of voltages.

## 3 Pre-lab Exercises

The circuit symbol of Op-Amp is shown in Figure 2. There are two input terminals (non-inverting and inverting). The corresponding input voltages are denoted by  $v_p$  and  $v_n$ , respectively. The output voltage  $v_o$  is equal to the difference of the two input voltages multiplied by the gain  $A_v$  (which is a big number)

$$v_o = A_v \times (v_p - v_n). \quad (1)$$

# LM358

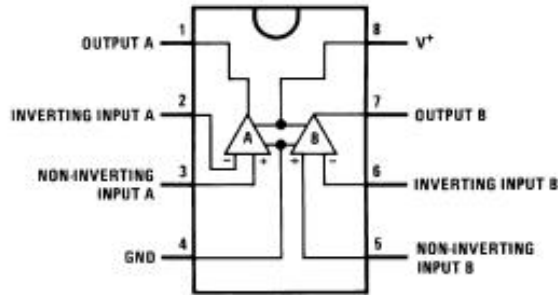


Figure 1: LM358 Dual operational amplifier

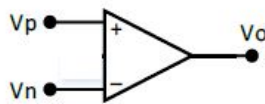


Figure 2: Circuit symbol of Op-Amp

## 3.1 Circuit Analysis

### 3.1.1 Analyze the linear active region and the saturation region

The maximum and the minimum output voltages of Op-Amp are limited by the power supplies. This is true for both open-loop, and, as you will find out in the lab, closed-loop configurations. An open-loop configuration is schematically indicated in Figure 3.

Note that the input voltage range (for the linear active region) is given by

$$\frac{-V_{cc}}{A_v} < v_p - v_n < \frac{+V_{cc}}{A_v}. \quad (2)$$

- As a result of the large amplification  $A_v$  (say  $A_v = 100000$ ), the input voltage difference ( $v_p - v_n$ ) must be very small (in order to operate in the linear active region).
- Please analyze and plot the relation between the output voltage  $v_0$  and the input voltage difference  $v_p - v_n$ , in which you should mark the linear active region and the saturation region.

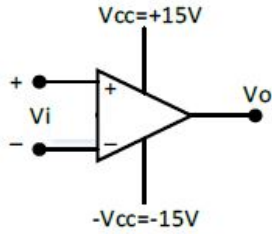


Figure 3: An open-loop configuration

### 3.1.2 Design and analyze closed-loop circuits

Here we design closed-loop Op-Amp circuits to verify the linearity and non-linearity of the operational amplifier. Question: Why not use the open-loop circuit directly?

#### a. Inverting Op-Amp Circuits

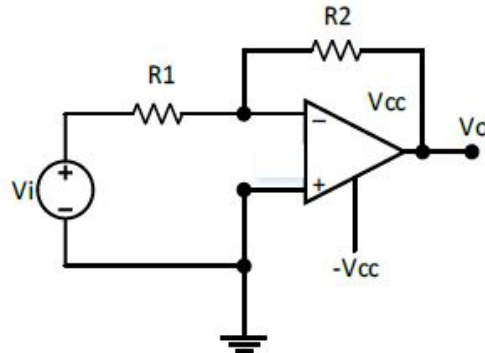


Figure 4: An inverting Op-Amp circuit

#### b. Noninverting Op-Amp Circuits

Express the gain  $A = \frac{v_o}{v_i}$  as a function of  $R_1$  and  $R_2$  for the inverting and the noninverting Op-Amp circuits shown in Figure 4 and Figure 5. Note that this closed-loop gain  $A$  is independent of the op-amp open-loop gain  $A_v$ .

## 3.2 Numerical Evaluation

There are two important facts which are useful for analyzing the Op-Amp circuits.

#### a. The input current is zero.

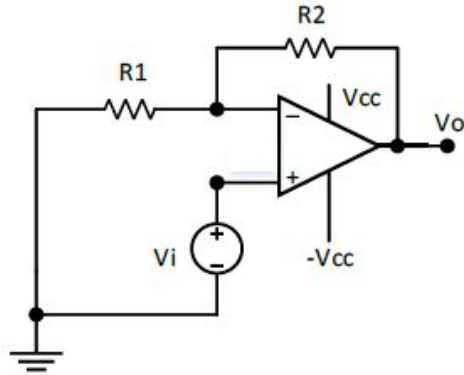


Figure 5: A noninverting Op-Amp circuit

- b. The voltage difference between the inverting and non-inverting inputs is zero (when the amplifier is used with negative feedback).
- Suppose  $R_1 = 22k\Omega$ ,  $R_2 = 100k\Omega$ ,  $V_{cc+} = +10V$ ,  $V_{cc-} = -10V$ . Determine the linear active region and the saturation region of the inverting and the noninverting Op-Amp circuits shown in Figure 4 and Figure 5.

## 4 Experiment

In this experiment, construct the Op-Amp circuits in the pre-lab. Use the square-wave output of the function generator to emulate the input signal, where you should only observe the changes of peak to peak magnitude. Suppose  $R_1 = 22k\Omega$ ,  $R_2 = 100k\Omega$ ,  $V_{cc+} = +10V$ ,  $V_{cc-} = -10V$ .

- Measure the peak to peak amplitude in scope.
- Compare it with the output of the function generator, and calculate the closed-loop gain  $A$ .
- Compare your analytical results with your experimental measures. Depict the linearly active region and the saturation region.
- Include the relevant waveforms in your report.

Repeat the above experiment for the following values:  $V_{cc+} = +5V$ ,  $V_{cc-} = -5V$ . Explain your findings.

## 5 Report

Your report should include the proposed circuits, the relevant theoretical analysis as well as the experimental results.