

# Laboratory 4: Differentiators and Integrators

ELEC ENG 2CJ4: Circuits and Systems  
Instructor: Prof. Jun Chen

## 1 Objective

You will learn how to construct differentiators and integrators using Op-Amps.

## 2 Equipment

The following equipments are used in this laboratory:

- DC voltage source with positive and negative output( $\pm 10V$ ); Oscilloscope; Function signal generator
- Resistors:  $1k\Omega \times 2$ ,  $10k\Omega \times 2$ ,  $100k\Omega \times 2$ ,  $2.2M\Omega \times 1$
- Capacitors:  $1nF(102) \times 1$ ,  $100nF(104) \times 1$
- Op-Amp LM358

## 3 Pre-lab Exercises

A simple differentiator based on the RC Op-Amp circuit can be found in Figure 1. The ideal input-output relationship for this differentiator is given by

$$v_o(t) = -RC \frac{dv_i(t)}{dt}. \quad (1)$$

A simple integrator based on the RC Op-Amp circuit can be found in Figure 2. The ideal input-output relationship for this integrator is given by

$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(x) dx + v_o(0). \quad (2)$$

### 3.1 Circuit Analysis

#### 3.1.1 Analyze the differentiator

In practice, the output of the differentiator in Figure 1 is quite sensitive to the noise perturbation, especially in the high frequency regime (Can you explain why?). For this reason, we incorporate a series resistor at the input as shown in Figure 3 (Can you explain the role of this resistor).

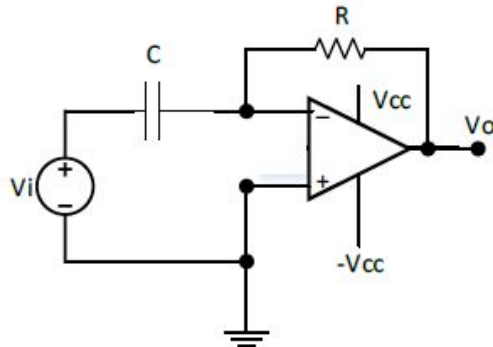


Figure 1: A simple differentiator based on the RC Op-Amp circuit

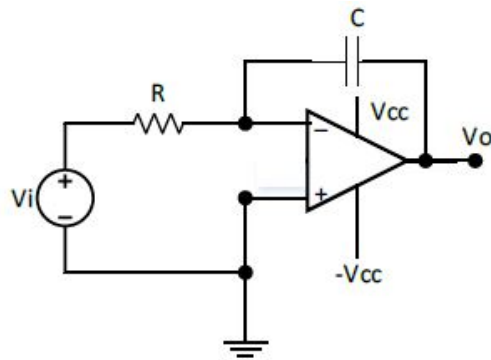


Figure 2: A simple integrator based on the RC Op-Amp circuit

- Assume  $R_1 = 10K\Omega$ ,  $R_2 = 1K\Omega$ ,  $C_1 = 1nF(102)$ ,  $V_{cc+} = +10V$ , and  $V_{cc-} = -10V$ . Consider two types of inputs: 1) the triangle wave, 2) the sine wave (both with frequency =  $4KHz$  and peak-to-peak amplitude =  $1V$ ). Analyze and plot the relationship between the input voltage and the output voltage.

### 3.1.2 Analyze the integrator

In practice, instead of using the integrator in Figure 2, we use the one shown in Figure 4, where a resistor paralleled to the feedback capacitor is added. The value of  $R_4$  is chosen to be large enough so that the bias current going through this branch is negligible.

- Assume  $R_3 = 10K\Omega$ ,  $R_4 = 2.2M\Omega$ ,  $C_3 = 100nF(104)$ ,  $V_{cc+} = +10V$ , and  $V_{cc-} = -10V$ . Consider two types of inputs: 1) the triangle wave, 2) the sine wave (both with frequency =  $1KHz$  and peak-to-peak amplitude =

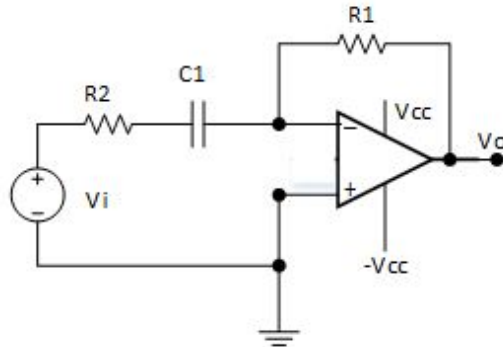


Figure 3: A practical differentiator

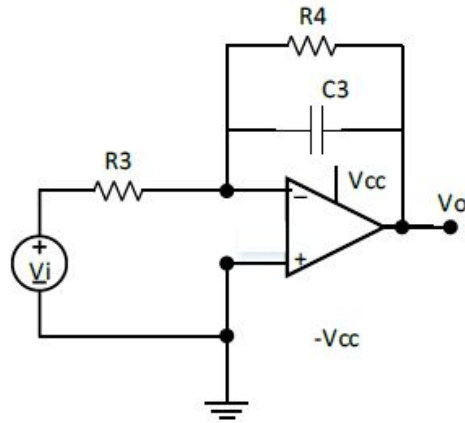


Figure 4: A practical integrator

2V). Analyze and plot the relationship between the input voltage and the output voltage.

## 4 Experiment

### 4.1 Differentiator

In this experiment, construct the differentiator in Figure 3.

- Use 1) the triangle wave, 2) the sine wave (both with frequency=  $4KHz$  and peak-to-peak amplitude=  $1V$ ) as the inputs, and measure the corresponding outputs.
- Compare your theoretical analysis with your measured responses.

- Set the frequency=  $10\text{KHz}$  or higher. Check whether the differentiator functions properly, and explain your finding.
- Set the frequency=  $10\text{Hz}$  or lower. Check whether the differentiator functions properly, and explain your finding.
- Include the relevant waveforms in your report.

## 4.2 Integrator

In this experiment, construct the integrator in Figure 4.

- Use 1) the triangle wave, 2) the sine wave (both with frequency=  $1\text{KHz}$  and peak-to-peak amplitude=  $2\text{V}$ ) as the inputs, and measure the corresponding outputs.
- Compare your theoretical analysis with your measured responses.
- Set the frequency=  $10\text{Hz}$  or lower. Check whether the integrator functions properly, and explain your finding.
- Include the relevant waveforms in your report.

## 5 Report

In your write-up, present all the relevant circuits, the theoretical and experimental results as well as your analysis.