

[3]

$$CMRR_{dB} = 20 \log_{10}(CMRR)$$

$$\therefore CMRR_{dB} = 20 \log(250000) \\ \approx 108 \text{ dB}$$

[5]

$$A_{ol} = 175000, \quad A_{cm} = 0.18, \quad CMRR_{dB} = ??$$

$$CMRR_{dB} = 20 \log\left(\frac{A_{ol}}{A_{cm}}\right) \\ = 20 \log\left(\frac{175000}{0.18}\right) = 119.76 \\ \approx 120 \text{ dB}$$

[6]

$$CMRR = 300000, \quad A_{ol} = 90000, \quad A_{cm} = ??$$


$$\therefore CMRR = \frac{A_{ol}}{A_{cm}}$$

$$\therefore A_{cm} = \frac{A_{ol}}{CMRR} = \frac{90000}{300000} = 0.3$$

12

$$V_F = B V_{out}$$

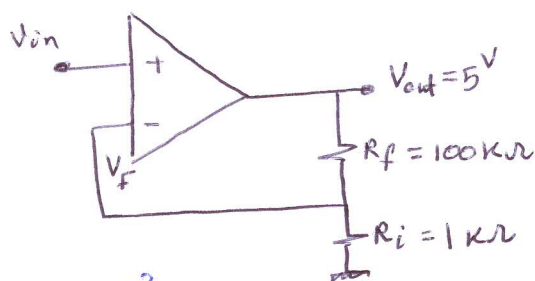
$$\therefore B = \frac{R_i}{R_i + R_f} = \frac{1k}{(100+1)k} = 9.9 \times 10^{-3}$$



$$\therefore V_F = 9.9 \times 10^{-3} \times 5$$

$$\therefore V_F = 49.5 \text{ mV}, \quad B = 9.9 \times 10^{-3}$$

13

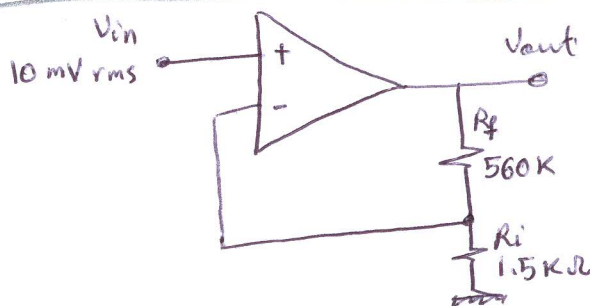

NI amplifier

$$a) A_{cl(NI)} \approx \frac{1}{B} \quad ; \quad B = \frac{R_i}{R_i + R_f} = \frac{1.5}{1.5 + 560} \approx 2.64 \times 10^{-3}$$

$$\therefore A_{cl(NI)} = 374.33$$

$$b) V_{out} = A_{cl(NI)} V_{in} = 374.33 \times 10 \text{ mV rms} = 3743.3 \text{ mV rms}$$


$$\therefore V_{out} = 3.743 \text{ V rms}$$

$$c) V_f = B V_{out} = 2.64 \times 10^{-3} \times 3.743 = 9.994 \times 10^{-3} \text{ V rms}$$

$$\therefore V_f = 9.994 \text{ mV rms}$$

14
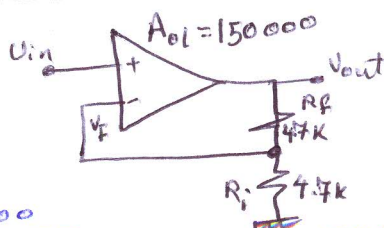
$$a) B = \frac{R_i}{R_f + R_i} = \frac{4.7}{47 + 4.7} = 90.9 \times 10^{-3}$$



$$\therefore A_{cl} = \frac{A_{ol}}{1 + B A_{ol}} = \frac{150000}{1 + (90.9 \times 10^{-3} \times 150000)} = \frac{150000}{136.36} \approx 11$$

OR

$$A_{cl} \approx \frac{1}{B} \approx 11$$

14

(3)

$$b) B = \frac{R_i}{R_i + R_f} = \frac{10 \times 10^3}{10 \times 10^3 + 1 \times 10^6} = 9.9 \times 10^{-3}$$

$$\therefore A_{cl(NI)} = \frac{A_{ol}}{1 + BA_{ol}} = \frac{100000}{1 + 9.9 \times 10^{-3} \times 100000} = \frac{100000}{991} = 100.91$$

OR

$$A_{cl(NI)} \approx \frac{1}{B} = 101$$

c)

$$B = \frac{R_i}{R_i + R_f} = \frac{4.7}{4.7 + 220} = 20.92 \times 10^{-3}$$

$$\therefore A_{cl(NI)} = \frac{A_{ol}}{1 + BA_{ol}} = \frac{200000}{1 + 20.92 \times 10^{-3} \times 200000} = \frac{200000}{4185} = 47.79$$

OR

$$A_{cl(NI)} \approx \frac{1}{B} = 47.8$$

d)

$$B = \frac{R_i}{R_i + R_f} = \frac{1}{1 + 22} = 43.48 \times 10^{-3}$$


$$A_{cl} = \frac{A_{ol}}{1 + BA_{ol}} = \frac{185000}{1 + 43.48 \times 10^{-3} \times 185000} = \frac{185000}{8044.8} = 22.996$$

OR

$$A_{cl} \approx \frac{1}{B} = 22.999 \approx 23$$

16

a)

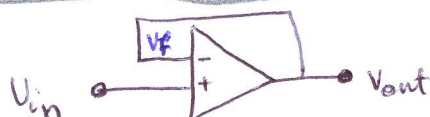

Voltage Follower

$$V_f = V_{out} \quad \therefore B = 1$$

$$\therefore V_{out} = A_{ol}(V_{in} - V_f) \\ = A_{ol}(V_{in} - V_{out})$$

$$\therefore V_{out}(1 + A_{ol}) = A_{ol} V_{in}$$

$$\therefore A_{cl(VF)} = \frac{V_{out}}{V_{in}} = \frac{A_{ol}}{1 + A_{ol}}$$


$$\therefore A_{ol} \gg 1$$

$$\therefore A_{cl(VF)} \approx 1$$

$$A_{cl} = 1$$

16

b)

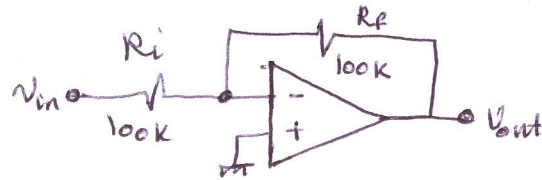

Inverting Amplifier


(4)

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

$$= -\frac{100k}{100k}$$

$$\therefore A_{cl} = -1$$

c)

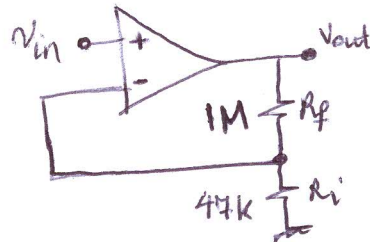

Noninverting Amplifier


$$A_{cl(NI)} = \frac{1}{B} = \frac{1}{\frac{R_i}{R_i + R_f}}$$

$$\therefore A_{cl} = \frac{R_i + R_f}{R_i} = 1 + \frac{R_f}{R_i}$$

$$\therefore A_{cl} = 1 + \frac{1 \times 10^6}{47 \times 10^3}$$

$$\therefore A_{cl} = 22.3$$

d)

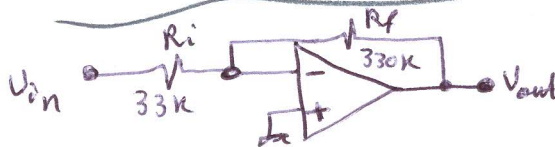

$$A_{cl(I)} = -\frac{R_f}{R_{in}}$$

$$= -\frac{330k}{33k} = -10$$

$$\therefore A_{cl} = -10$$