

# Lecture 2:Circuit Theory (1)

Ohm's law, Kirchhoff's voltage law, examples,  
Kirchhoff's current law, Mesh Analysis, Voltage  
Dividers, Current Dividers, Superposition Theorem


# Ohm's Law

Ohm's law states that the current through a conductor between two points is directly proportional to the potential difference across the two points. The constant of proportionality is the resistance



wikipedia



$$I=V/R \quad \text{or} \quad V=IR$$

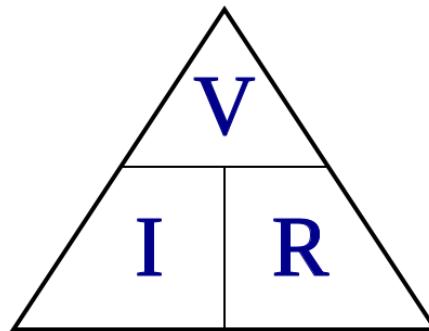

**What is the origin of this law in electromagnetics?**
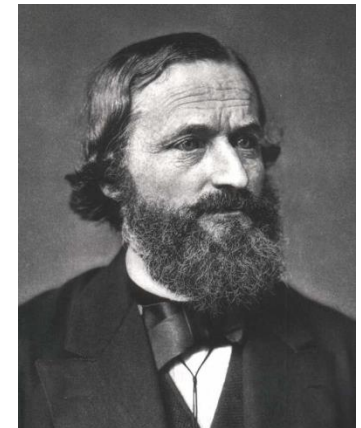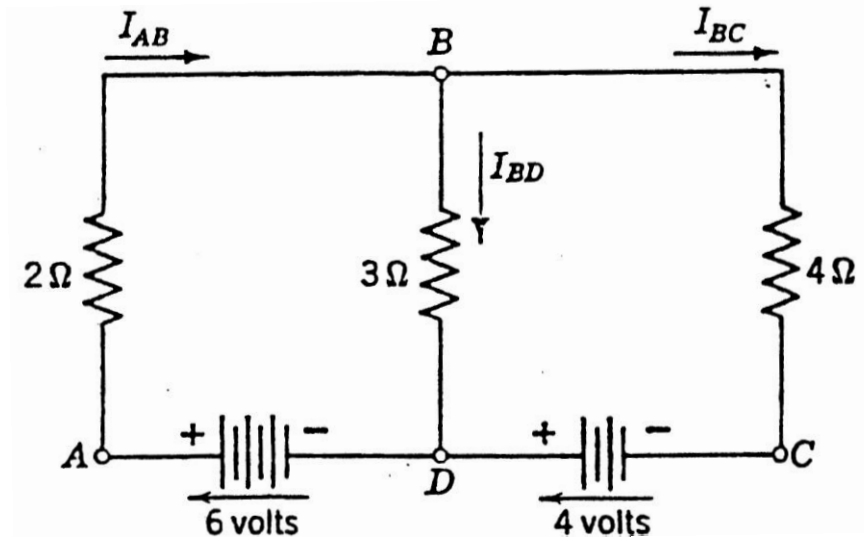
# Kirchhoff's Current Law

For any junction:  $\sum I_{\text{in}} = \sum I_{\text{out}}$



wikipedia

- For junction B:  $I_{AB} = I_{BD} + I_{BC}$
- For junction D:  $I_{BD} + I_{BC} = I_{AB}$  (dependent)
- Number of independent KCL equations =  
number of junctions – 1

**Analogy with water flow in pipes?**

# Kirchhoff's Voltage Law

For any closed loop:  $\sum \vec{V}_{\text{rise}} = 0$ ,


or  $\sum \vec{V}_{\text{rise}} = 0$

For the left-hand loop:  $6 - 2I_{AB} - 3I_{BD} = 0$

For the right-hand loop:  $4 + 3I_{BD} - 4I_{BC} = 0$

For the outer loop:  $4 + 6 - 2I_{AB} - 4I_{BC} = 0$  (dependent)

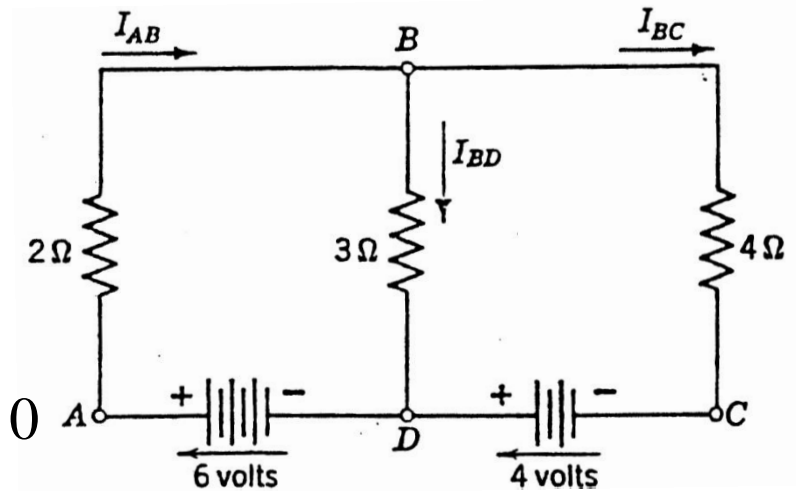A new loop equation is independent on the previous if it contains new current(s) and/or battery(s).




**origin of this law in electromagnetics?**
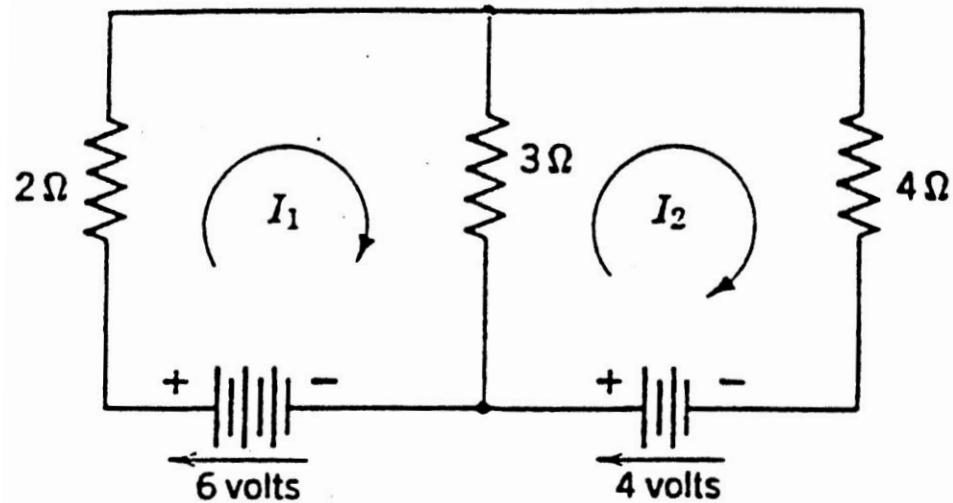
# Mesh-Current Analysis

every loop is assigned one current flowing in the clockwise directions

Kirchhoff's voltage and current laws are then used to solve for these currents



Writing Kirchhoff's voltage laws:

$$\begin{aligned} 6 - 2I_1 - 3I_1 + 3I_2 &= 0 \\ 4 + 3I_1 - 3I_2 - 4I_2 &= 0 \end{aligned} \Rightarrow \begin{bmatrix} -5 & 3 \\ 3 & -7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -6 \\ -4 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -5 & 3 \\ 3 & -7 \end{bmatrix}^{-1} \begin{bmatrix} -6 \\ -4 \end{bmatrix} = \begin{bmatrix} 2.077 \\ 1.462 \end{bmatrix} \text{ A}$$


# Voltage Divider

The voltage divider is a series combination of two resistors.

The total voltage  $V$  is divided between these resistors according to the direct ratio of their resistances:

$$I = \frac{V}{R_1 + R_2}$$

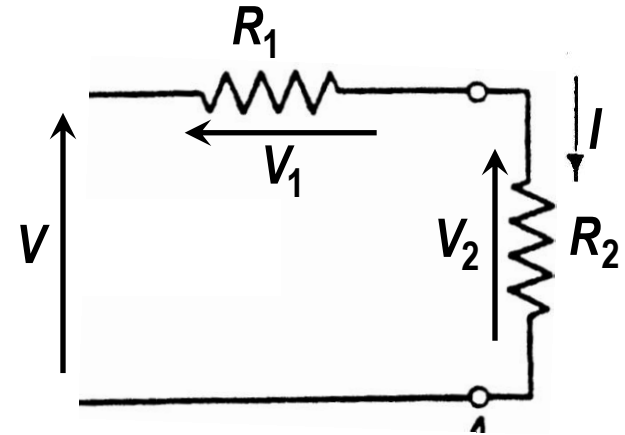
$$V_1 = I R_1 = \frac{V R_1}{R_1 + R_2}, \quad V_2 = I R_2 = \frac{V R_2}{R_1 + R_2}, \quad \frac{V_1}{V_2} = \frac{R_1}{R_2}$$


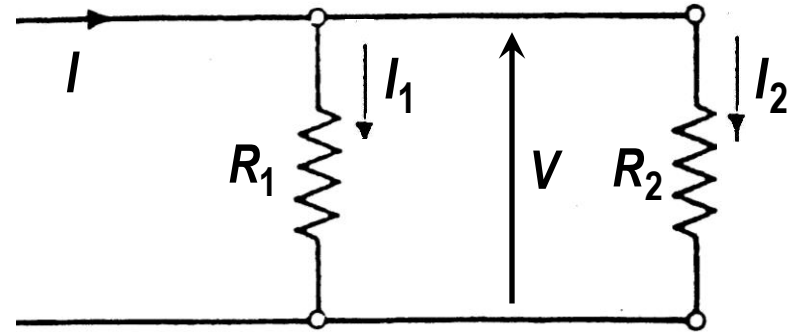
# Current Divider

The current divider is a parallel combination of two resistors.

The total current  $I$  is divided between these resistors according to the inverse ratio of their resistances:




$$V = I \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = \frac{I R_2}{R_1 + R_2}, \quad I_2 = \frac{V}{R_2} = \frac{I R_1}{R_1 + R_2}, \quad \frac{I_1}{I_2} = \frac{R_2}{R_1}$$
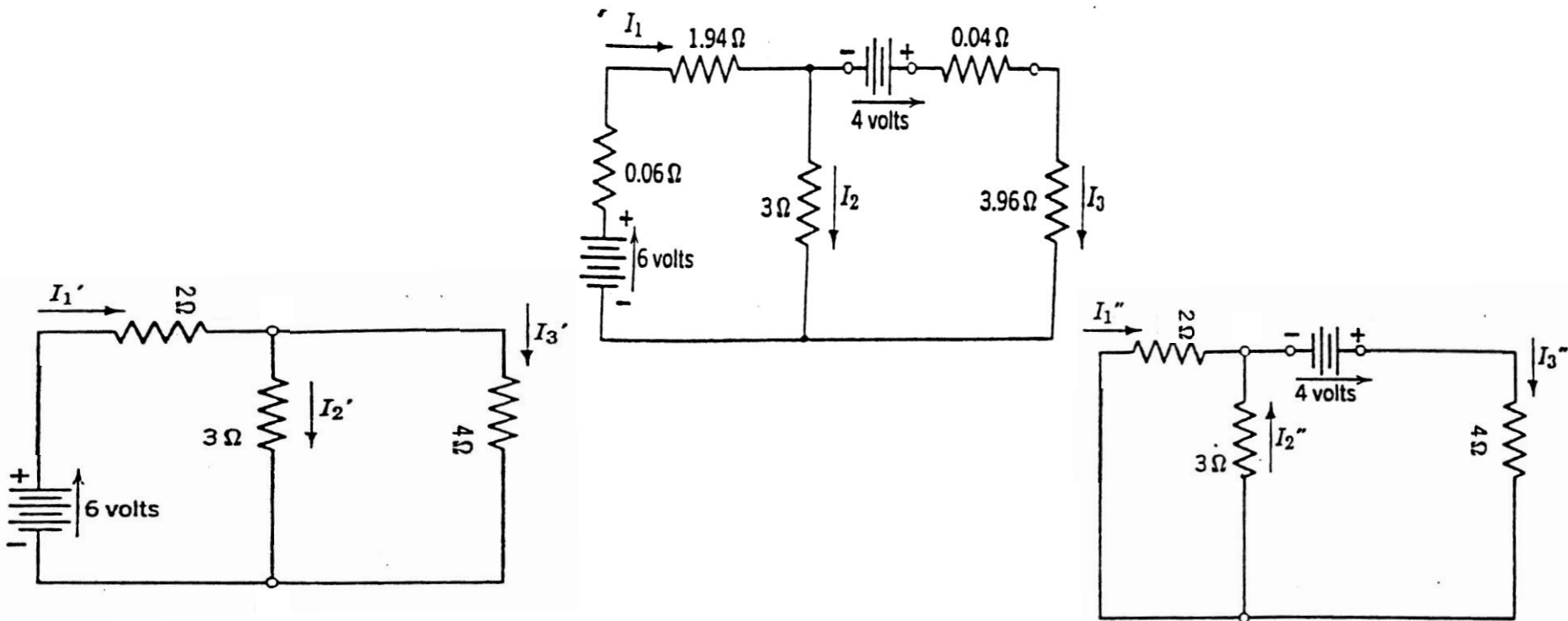
# Superposition Theorem

A circuit which contains more than one voltage source can be considered as the superposition of a number of circuits, each has only one voltage source only, while the rest of the voltage sources are replaced by short circuits.





# Superposition (Cont'd)

## Original Circuit

This circuit has been solved using Kirchhoff's laws:

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2.077 \\ 0.615 \\ 1.462 \end{bmatrix} \text{ A}$$

## First Sub-Circuit

$$I'_1 = \frac{6}{2 + (3 \parallel 4)} = 1.615 \text{ A}$$

$$I'_2 = I'_1 \frac{4}{3 + 4} = 0.923 \text{ A}$$

$$I'_3 = I'_1 - I'_2 = 0.692 \text{ A}$$

## Second Sub-Circuit

$$I''_3 = \frac{4}{4 + (3 \parallel 2)} = 0.769 \text{ A}$$

$$I''_2 = I''_3 \frac{2}{3 + 2} = 0.308 \text{ A}$$

$$I''_1 = I''_3 - I''_2 = 0.461 \text{ A}$$

$$I_1 = I'_1 + I''_1 = 1.615 + 0.461 = 2.076 \text{ A}$$

$$I_2 = I'_2 - I''_2 = 0.923 - 0.308 = 0.615 \text{ A}$$

$$I_3 = I'_3 + I''_3 = 0.692 + 0.769 = 1.461 \text{ A}$$