

Lecture 25: Bipolar Junction Transistors (2)

Load Line Analysis, Operating Regions,
Examples

Load Line Analysis


The DC operating point (Q-point) of the BJT is the point of intersection between the two relations.

The cutoff point is the intersection of the DC load line with $I_B = 0$ curve (horizontal axis).

At this point:

$$I_{B(\text{cutoff})} = 0, \quad I_{C(\text{cutoff})} = 0,$$

$$V_{CE(\text{cutoff})} = V_{CC}$$

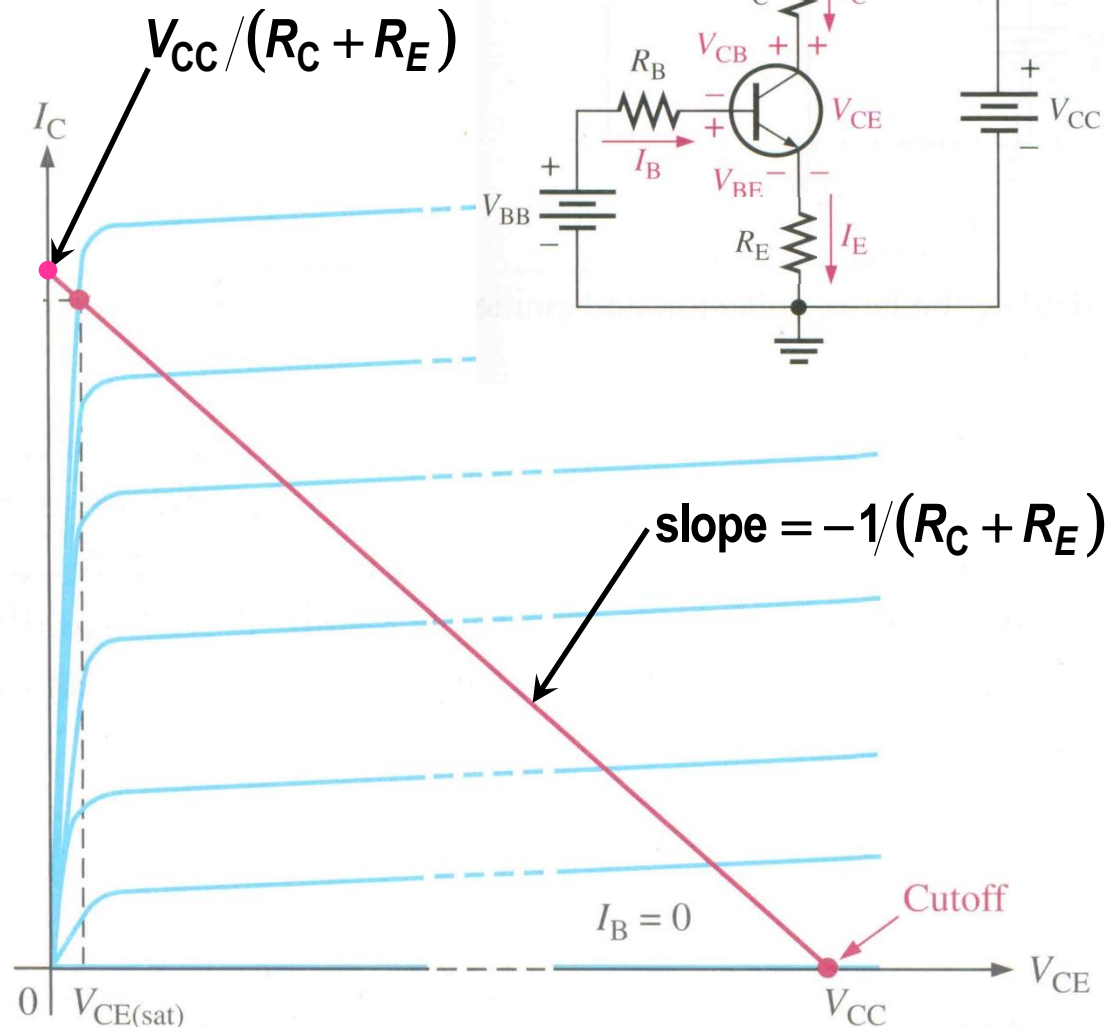


Saturation

At the saturation point, several collector characteristic curves, with $I_B \geq I_{B(\text{sat})}$, intersect with the DC load line. At this point I_C and V_{CE} are fixed:

$$V_{CE} = V_{CE(\text{sat})} \leq 0.7 \text{ V}$$

$$I_C = I_{C(\text{sat})} = (V_{CC} - V_{CE(\text{sat})}) / (R_C + R_E) \\ \cong V_{CC} / (R_C + R_E)$$
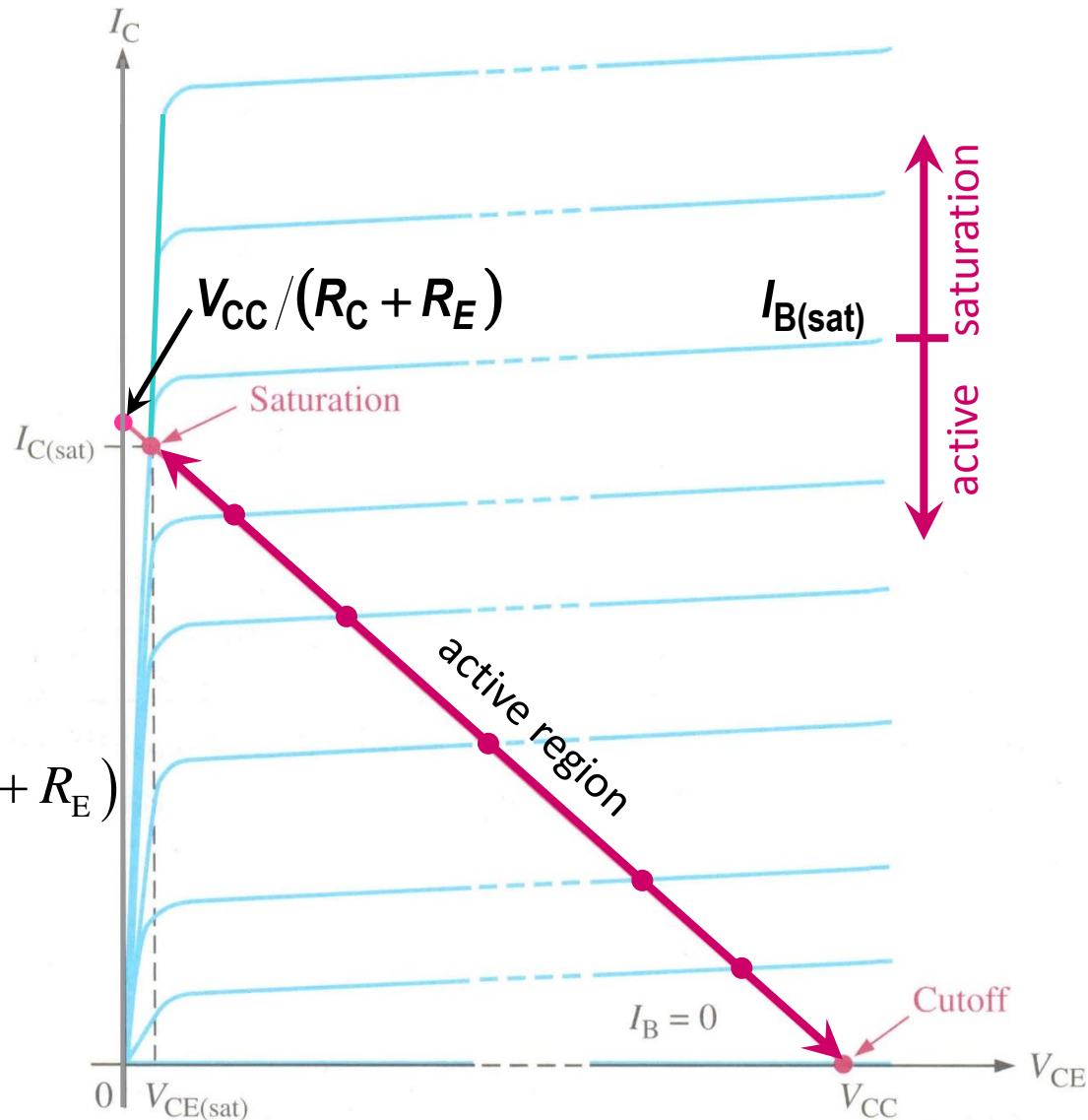
$$I_B \geq I_{B(\text{sat})} = I_{C(\text{sat})} / \beta_{DC}$$




Active Region

The active region of the transistor operation, is the region along the DC load line between cutoff and saturation points:

$$I_B \leq I_{B(\text{sat})} = I_{C(\text{sat})} / \beta_{\text{DC}}$$

$$I_C = \beta_{\text{DC}} I_B$$

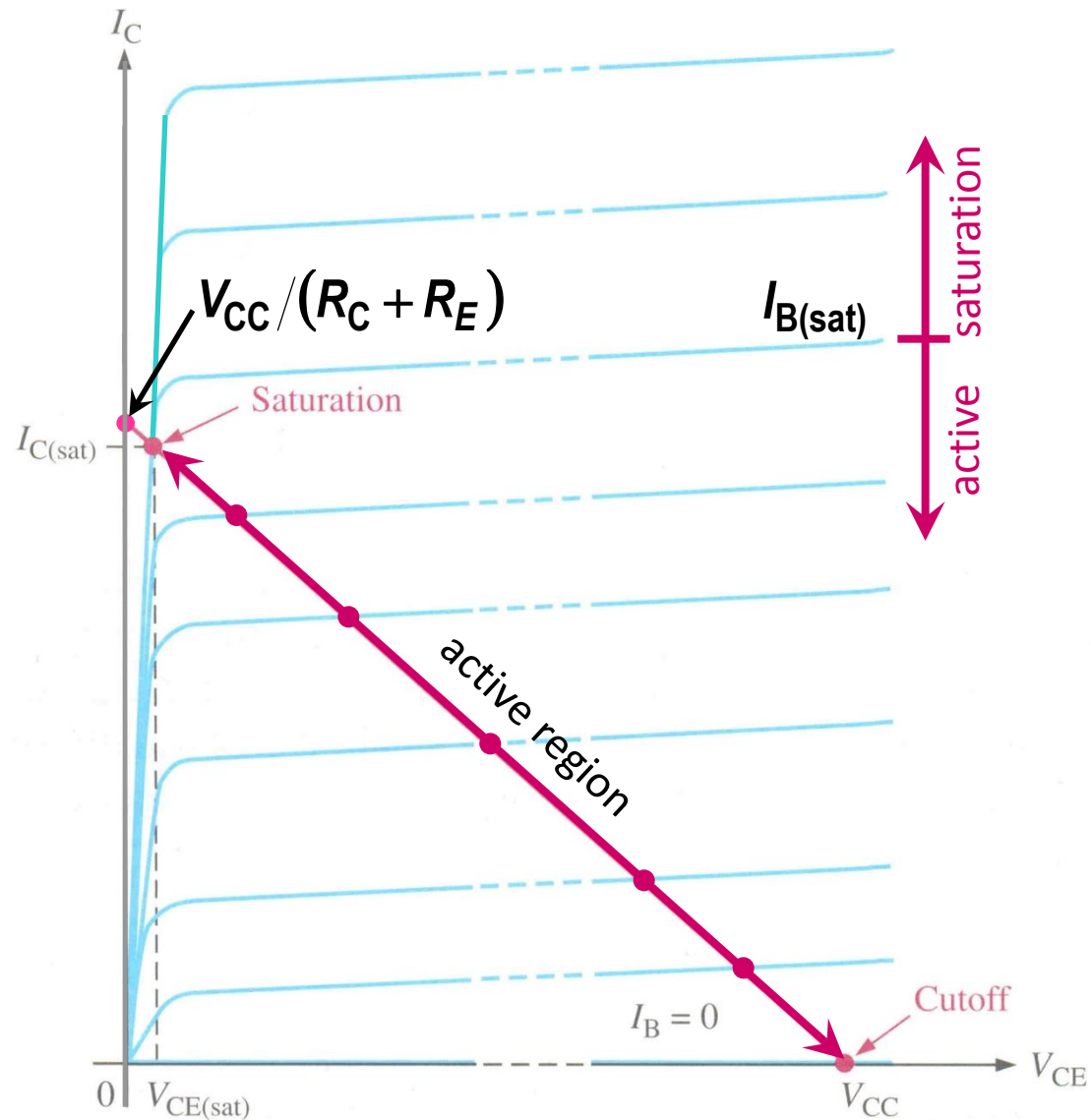
$$V_{\text{CE}} = V_{\text{CC}} - I_C (R_C + R_E)$$



Regions of Operations

<i>Attribute</i>	<i>Cutoff</i>	<i>Active</i>	<i>Saturation</i>
<i>BE Junction</i>	RB	FB	FB
<i>BC Junction</i>	RB	RB	FB
<i>I_B</i>	0	$\leq I_{B(sat)}$	$\geq I_{B(sat)}$
<i>I_C</i>	0	$\beta_{DC} I_B$	$I_{C(sat)}$
<i>V_{CE}</i>	V_{CC}	$V_{CC} - I_C(R_C + R_E)$	$V_{CE(sat)}$
<i>Application</i>	Opened Switch	Current Amplifier	Closed Switch

Transistor as a Switch

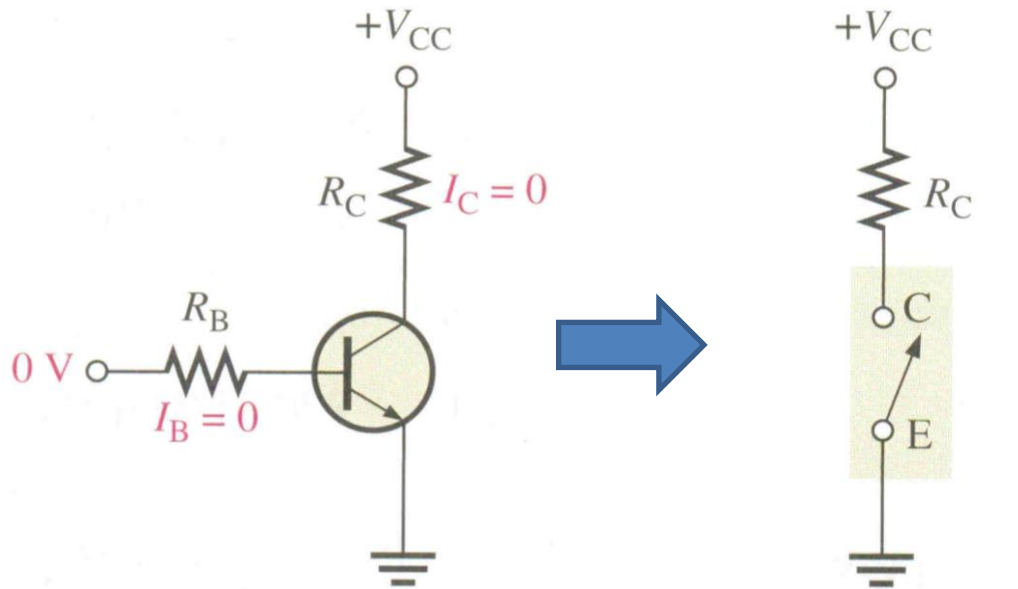

$$I_B = I_{B(\text{cutoff})} = 0$$


$$I_C = I_{C(\text{cutoff})} \cong 0$$

$$V_{CE} = V_{CE(\text{cutoff})} \cong V_{CC}$$

$$I_C = 0$$

$$V_{CE} = V_{CC}$$


Transistor as a Switch (Cont'd)

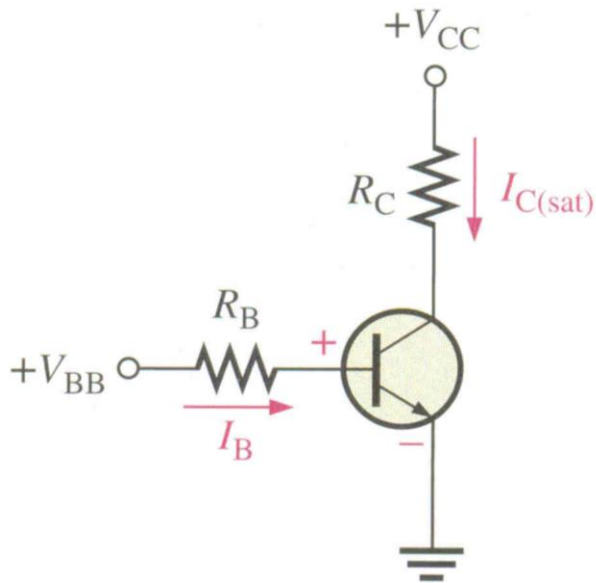

$$I_B > I_{B(sat)}$$

$$V_{CE} = V_{CE(sat)} \cong 0$$

$$I_C = I_{C(sat)} \cong V_{CC}/R_C$$

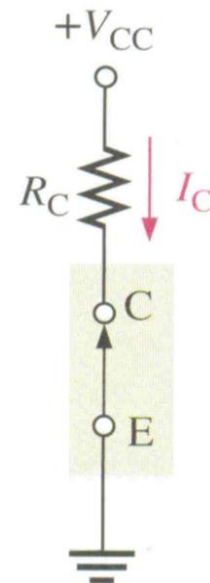

$$V_{CE} = 0$$

$$I_C = V_{CC}/R_C$$