

Lecture 5: Circuit Theory (5)

Combination of elements, resonance circuits,
filters, power in AC circuits

Combined AC Impedances

$Z \equiv$ impedance of
combined elements (Ω)


$$= \underbrace{R}_{\text{resistance } (\Omega)} + j \underbrace{X}_{\text{reactance } (\Omega)} \Rightarrow \begin{cases} \text{Resistor: } R > 0, X = 0 \\ \text{Inductor: } R = 0, X = \omega L \\ \text{Capacitor: } R = 0, X = -1/\omega C \end{cases}$$

$Y \equiv$ admittance of
combined elements ($1/\Omega$)

$$= \underbrace{G}_{\text{conductance } (1/\Omega)} + j \underbrace{B}_{\text{susceptance } (1/\Omega)} \Rightarrow \begin{cases} \text{Resistor: } G = 1/R, B = 0 \\ \text{Inductor: } G = 0, B = -1/\omega L \\ \text{Capacitor: } G = 0, B = \omega C \end{cases}$$

Series Combination
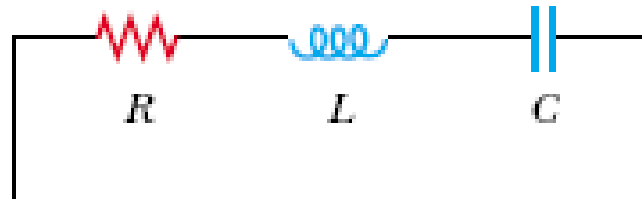
$$Z_T = Z_1 + Z_2 + \dots + Z_N, \quad Y_T = 1/Z_T$$



$$Z_T = Z_R + Z_L + Z_C = R + j\omega L + (1/j\omega C)$$

$$Y_T = \frac{1}{Z_T} = \frac{1}{R + j(\omega L - 1/\omega C)}$$


Parallel Combination

$$Y_T = Y_1 + Y_2 + \cdots + Y_N,$$

$$Z_T = 1/Y_T$$

$$Y_T = Y_R + Y_L + Y_C = (1/R) + (1/j\omega L) + j\omega C$$
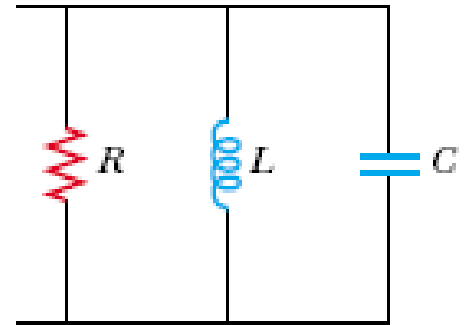
$$Z_T = \frac{1}{Y_T} = \frac{1}{(1/R) + j(\omega C - 1/\omega L)}$$



Power in AC Circuits

For DC circuits, power consumption is constant and does not change with time!

In general, $p(t) \equiv$ instantaneous power

$$= v i = V_{\max} I_{\max} \cos(\omega t + \varphi_V) \cos(\omega t + \varphi_I)$$

$$\bar{p} \equiv \text{time-average power} = \frac{1}{T} \int_0^T V_{\max} I_{\max} \cos\left(\underbrace{\omega t + \varphi_V}_{\theta_1}\right) \cos\left(\underbrace{\omega t + \varphi_I}_{\theta_2}\right) dt$$

$$= \frac{V_{\max} I_{\max}}{2T} \int_0^T \left[\cos\left(\underbrace{2\omega t + \varphi_V + \varphi_I}_{\theta_1 + \theta_2}\right) + \cos\left(\underbrace{\varphi_V - \varphi_I}_{\theta_1 - \theta_2}\right) \right] dt$$

$$= \frac{V_{\max} I_{\max}}{2T} \underbrace{\int_0^T \cos(2\omega t + \varphi_V + \varphi_I) dt}_0 + \frac{V_{\max} I_{\max}}{2T} \int_0^T \cos(\varphi_V - \varphi_I) dt$$

Power in AC Circuits (Cont'd)

$$\text{time-average power} = \frac{V_{\max} I_{\max}}{2T} \cos(\varphi_V - \varphi_I) \int_0^T dt$$

$\therefore \bar{p} \equiv$ time-average power (active power)

$$= \frac{1}{2} V_{\max} I_{\max} \underbrace{\cos(\varphi_V - \varphi_I)}_{\text{power factor}} = \underbrace{V_{\text{rms}} I_{\text{rms}}}_{\text{apparent power}} \underbrace{\cos(\varphi_V - \varphi_I)}_{\text{power factor}}$$

$$\text{power factor} \equiv \cos(\varphi_V - \varphi_I) \underset{Z=V/I}{=} \cos(\varphi_Z)$$

$$\underset{Z=R+jX}{=} \frac{R}{\sqrt{R^2 + X^2}} \quad \Rightarrow \quad 0 \leq \text{power factor} \leq 1$$

R is +
 X is \pm

What is the time-average power for resistors, capacitors, and inductors?

Alternative Expression for AC Power

The same value of time-average power can be obtained using the following formula:

$$\bar{p} \equiv \text{time-average power} = \frac{1}{2} \Re (V I^*)$$

Proof:

$$\begin{aligned} \frac{1}{2} \Re (V I^*) &= \frac{1}{2} \Re (V_{\max} e^{j\phi_V} I_{\max} e^{-j\phi_I}) \\ &= \frac{1}{2} V_{\max} I_{\max} \Re [e^{j(\phi_V - \phi_I)}] \\ &= \frac{1}{2} V_{\max} I_{\max} \cos (\phi_V - \phi_I) = \bar{p} \end{aligned}$$


Filters

The filter is a frequency-selective two-port network, which allows certain frequency band(s) to pass from input to output port, and stops other frequency band(s).

If a frequency-dependent impedance (Z) is combined with a resistor (R) in voltage divider configurations, different filters can be realized. Other frequency-selective configurations are also used.

Filters find wide applications in different applications in electrical engineering


Voltage Divider as a Filter

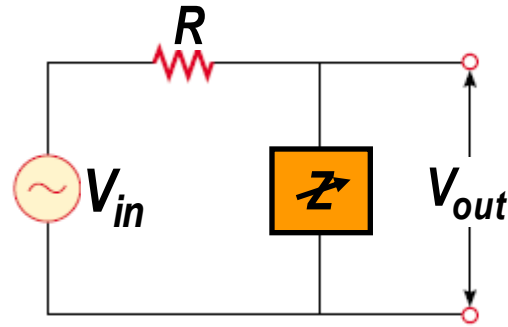

$$A_v \equiv \text{voltage gain} \equiv \frac{V_{out}}{V_{in}} = \frac{Z}{Z + R}$$

$$|A_v| = \left| \frac{Z}{Z + R} \right| = \left| \frac{1}{1 + R/Z} \right| = \frac{1}{|1 + R/Z|} \propto |Z|$$


Voltage Divider (Cont'd)

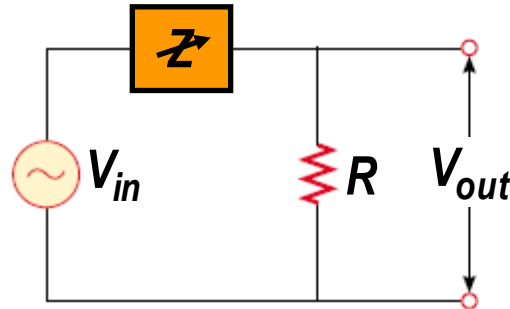



$$A_v \equiv \text{voltage gain} \equiv \frac{V_{out}}{V_{in}} = \frac{R}{R + Z}$$

$$|A_v| = \left| \frac{R}{R + Z} \right| = \left| \frac{1}{1 + Z/R} \right| = \frac{1}{|1 + Z/R|} \propto \frac{1}{|Z|}$$



Voltage Divider (Cont'd)

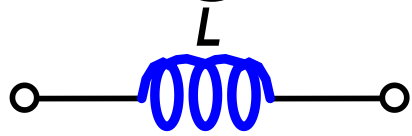



$$|Z| = \omega L = \begin{cases} 0 \text{ (s.c.)}, & \omega = 0 \\ \infty \text{ (o.c.)}, & \omega = \infty \end{cases}$$

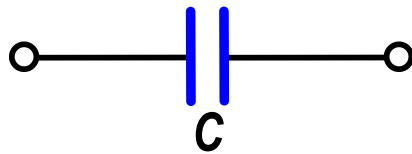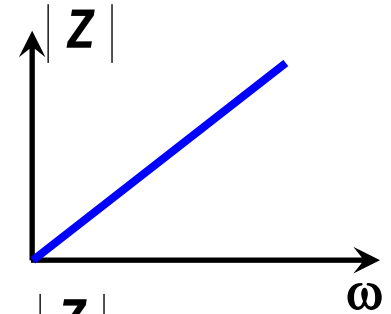

$$|Z| = \frac{1}{\omega C} = \begin{cases} \infty \text{ (o.c.)}, & \omega = 0 \\ 0 \text{ (s.c.)}, & \omega = \infty \end{cases}$$

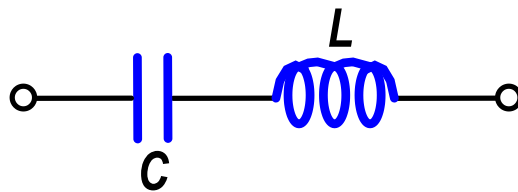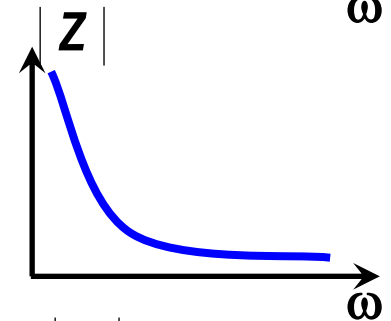

$$|Z| = \left| \omega L - \frac{1}{\omega C} \right| = \begin{cases} \infty \text{ (o.c.)}, & \omega = 0 \\ 0 \text{ (s.c.)}, & \omega = \omega_0 \\ \infty \text{ (o.c.)}, & \omega = \infty \end{cases}$$

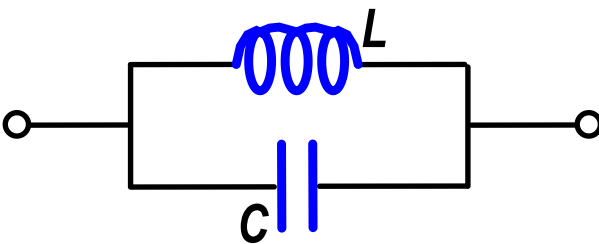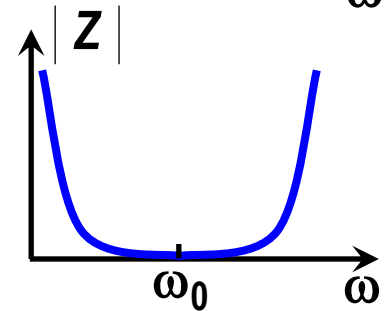

$$|Z| = \frac{1}{\left| \omega C - \frac{1}{\omega L} \right|} = \begin{cases} 0 \text{ (s.c.)}, & \omega = 0 \\ \infty \text{ (o.c.)}, & \omega = \omega_0 \\ 0 \text{ (s.c.)}, & \omega = \infty \end{cases}$$

