


Lecture 8: Diodes (2)

Half-Wave Rectifier, Full-Wave Rectifier, Diode
Clippers, Diode Clampers, Examples

Half Wave Rectifier


The rectifier is a diode circuit that converts the AC input voltage to a pulsating DC voltage.

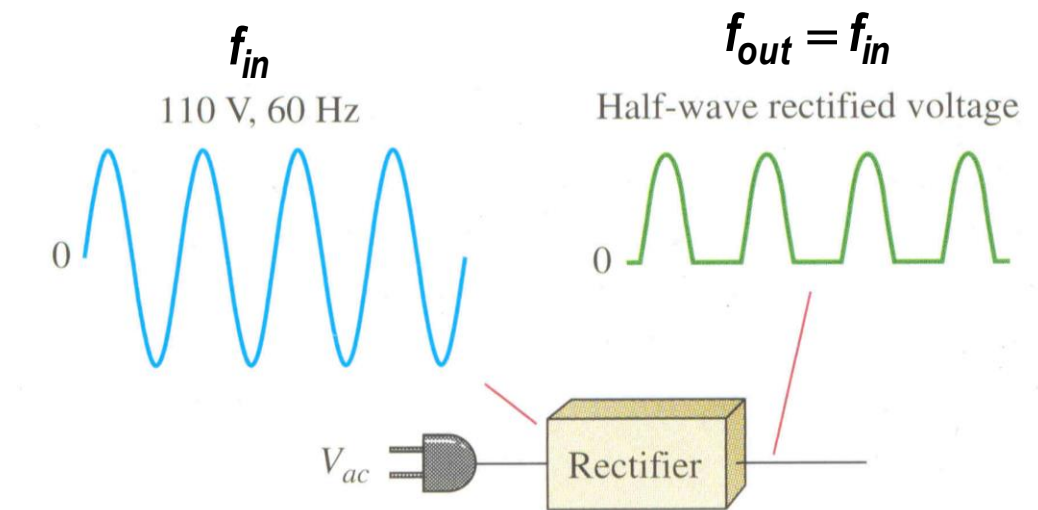It can be either a half-wave or a full-wave rectifier:



The half-wave rectifier allows unidirectional current through the load only during one-half of the input cycle.

Full-Wave Rectifier

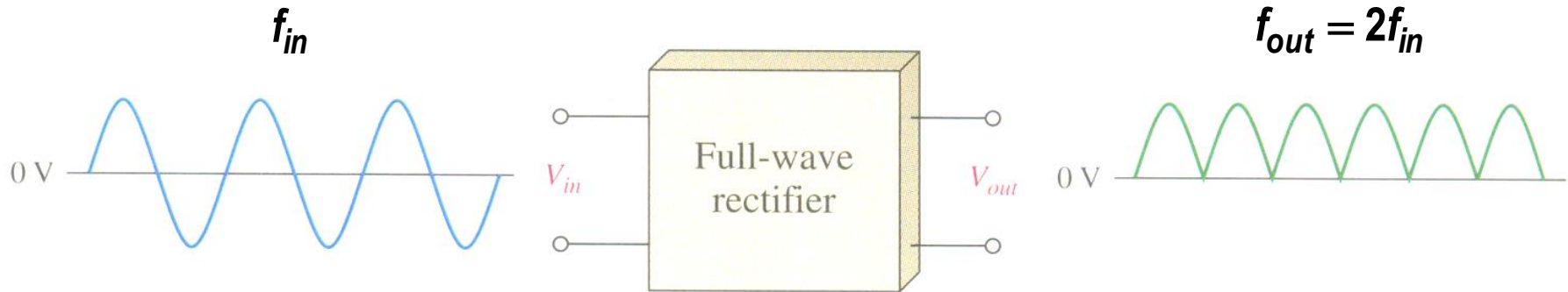

The full-wave rectifier allows unidirectional current through the load during the entire input cycle.



Half-Wave Rectifier Using Diodes

+ve Half-Cycle

The diode is forward-biased.

Current can flow through the load.

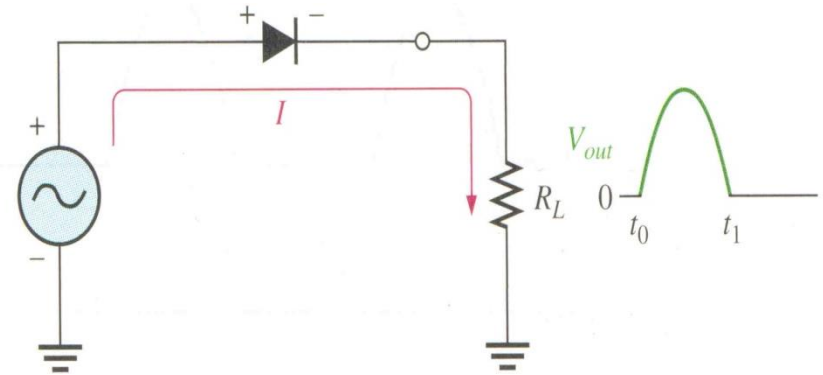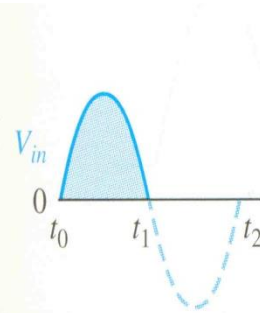The output voltage equals: $V_{out} = V_{in} - 0.7 \text{ V}$





-ve Half-Cycle

The diode is reverse-biased.


Current can't flow through the load.

The output voltage equals: $V_{out} = 0$

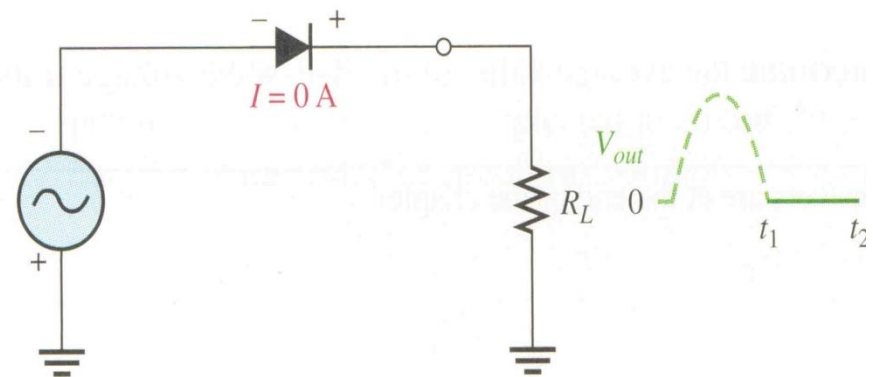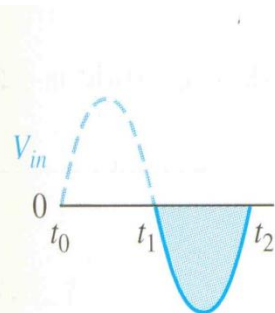

Half-Wave Rectifier (Cont'd)

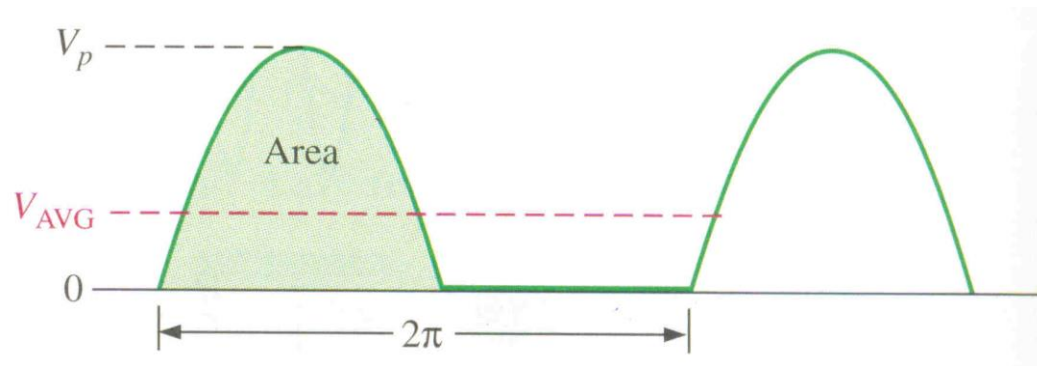The time-average value of the output voltage can be calculated as follows:




$$\begin{aligned} V_{AVG(out)} &= \frac{1}{2\pi} \int_0^{2\pi} V_{out}(\theta) d\theta && \text{Condition on peak inverse voltage?} \\ &= \frac{1}{2\pi} \left[\int_0^{\pi} V_{p(out)} \sin(\theta) d\theta + \int_{\pi}^{2\pi} 0 d\theta \right] \\ &= \frac{V_{p(out)}}{2\pi} \left[-\cos(\theta) \right]_0^{\pi} = -\frac{V_{p(out)}}{2\pi} (-1-1) \Rightarrow \therefore V_{AVG(out)} \Big|_{\text{half-wave}} = \frac{V_{p(out)}}{\pi} \end{aligned}$$

Half-Wave Rectifier (Cont'd)

Usually a transformer is used to couple the AC input voltage from the source to the rectifier


This transformer allows either stepping-up or -down of the input voltage

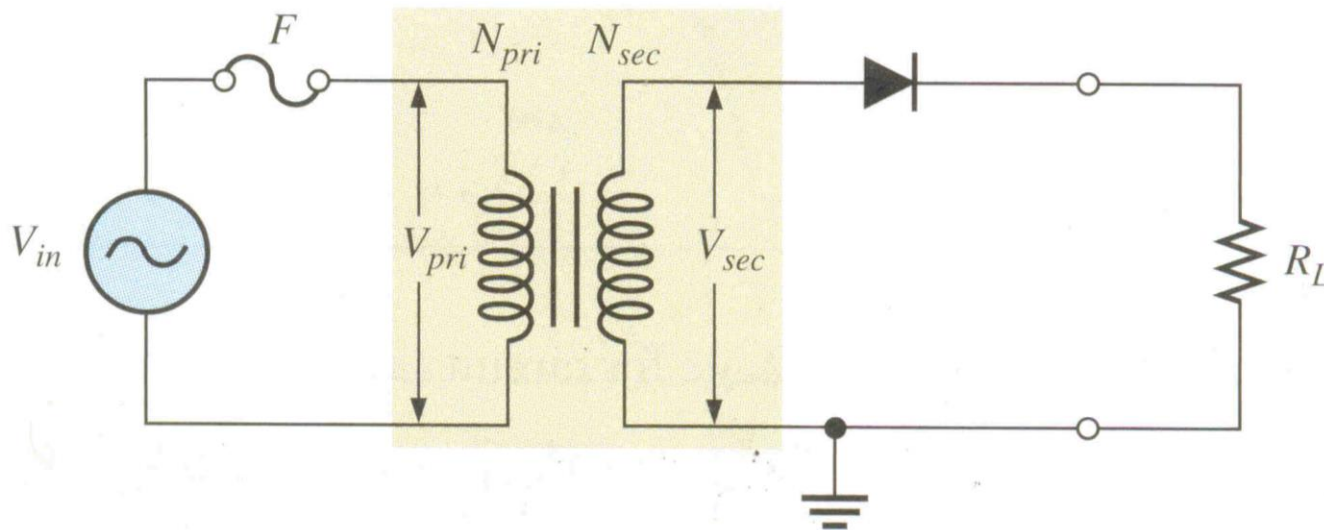The turns ratio (n) controls the voltage supplied to the rectifier, such that: $V_{sec} = n V_{pri}$, where $n \equiv \text{turns ratio} = N_{sec} / N_{pri}$



Full-Wave Bridge Rectifier

+ve Half-Cycle

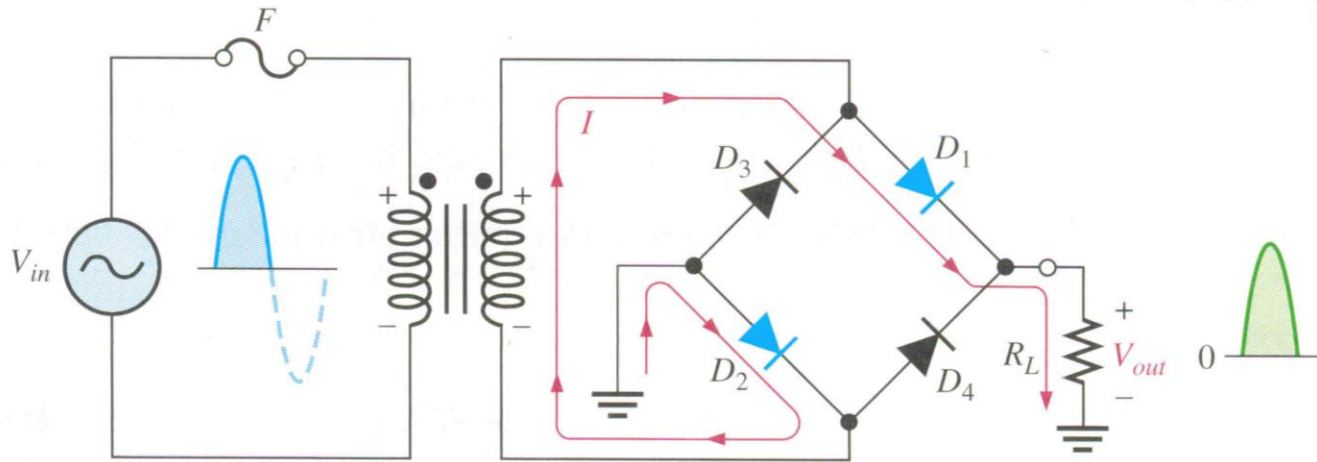


D_1 and D_2 are forward-biased, while D_3 and D_4 are reverse-biased.

Current flows in the load from node A toward ground.

Output voltage equals: $V_{out} = V_{sec} - 1.4 \text{ V}$

Full-Wave Bridge (Cont'd)

-ve Half-Cycle

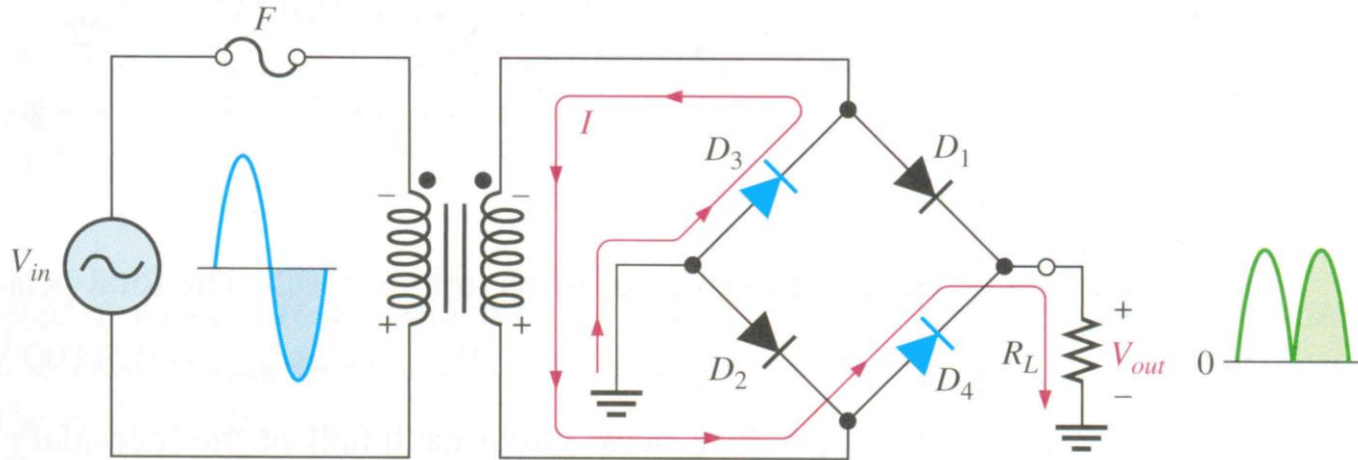


D_1 and D_2 are reverse-biased, while D_3 and D_4 are forward-biased.

Current flows in the same direction from node A toward ground.

Output voltage equals: $V_{out} = V_{sec} - 1.4 \text{ V}$

Full-Wave Bridge (Cont'd)

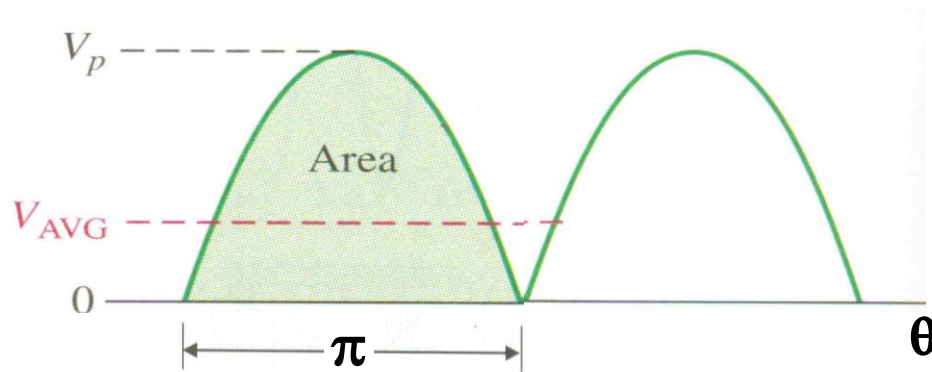

$$V_{AVG(out)} = \frac{\text{area under a complete cycle}}{\text{period of a complete cycle}}$$

$$= \frac{\text{area of the half-wave rectifier}}{\pi}$$

$$= 2 \times V_{AVG(out)} \Big|_{\text{half-wave}}$$

What is the Peak Inverse Voltage?

$$\therefore V_{AVG(out)} \Big|_{\text{full-wave}} = 2V_{p(out)} / \pi$$

Diode Limiters

The diode *limiter (clipper)* is a circuit that passes to the output port that part from the input waveform that falls either above or below certain reference level. It is very useful for protection.


D is FB, $V_D = 0.7$,

$V_{out} = 0.7$

$V_{in} \rightarrow -V_{p(in)} :$


D is RB, $I_D = 0$

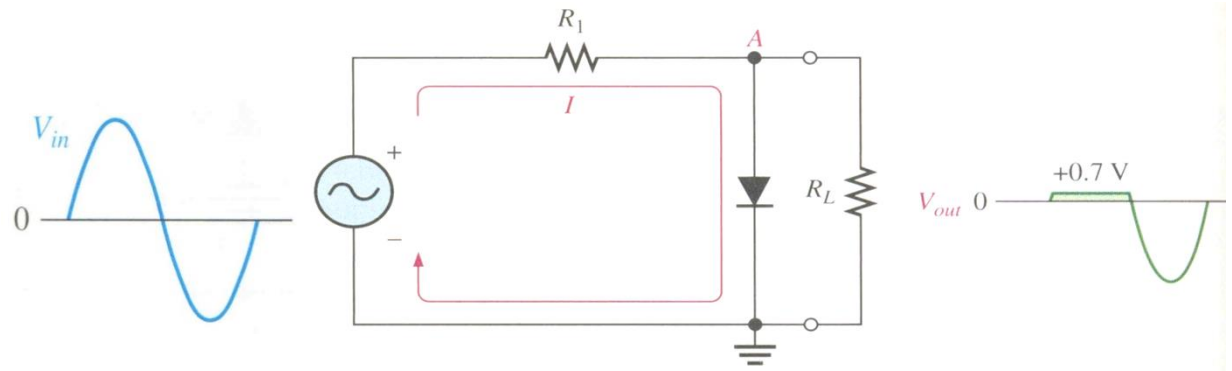$V_{out} = V_{in} R_L / (R_1 + R_L) \underset{R_1 \ll R_L}{\cong} V_{in}$



Positive Limiter

Diode Limiters (Cont'd)

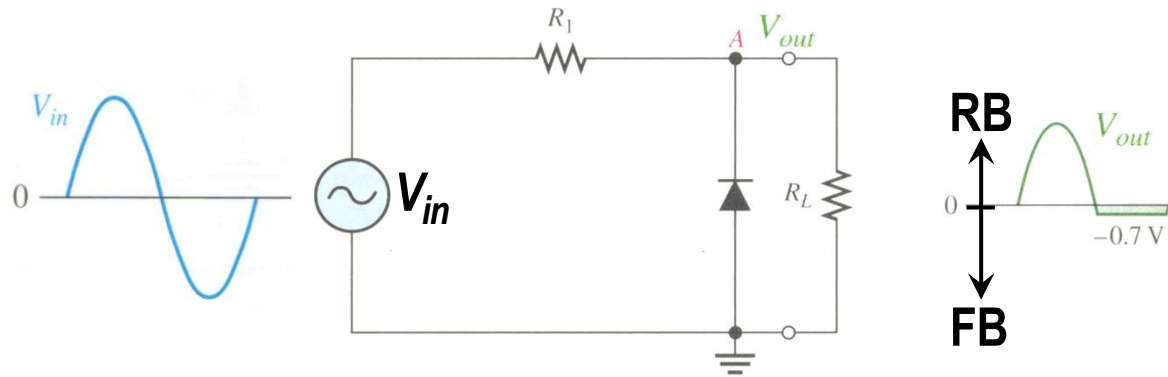

$$\underline{V_{in} \rightarrow V_{p(in)} :}$$

D is RB, $I_D = 0$

$$V_{out} = V_{in} R_L / (R_1 + R_L) \underset{R_1 \ll R_L}{\cong} V_{in}$$

Negative limiter

$$\underline{V_{in} \rightarrow -V_{p(in)} :}$$

D is FB, $V_D = 0.7$,


$$V_{out} = -0.7$$

Diode Clamper

The diode *clamper* is a circuit that adds a DC level (positive or negative) to an AC voltage.

The circuit below is a *positive* clamper which adds a +ve DC level to the input voltage.

First Quarter Cycle

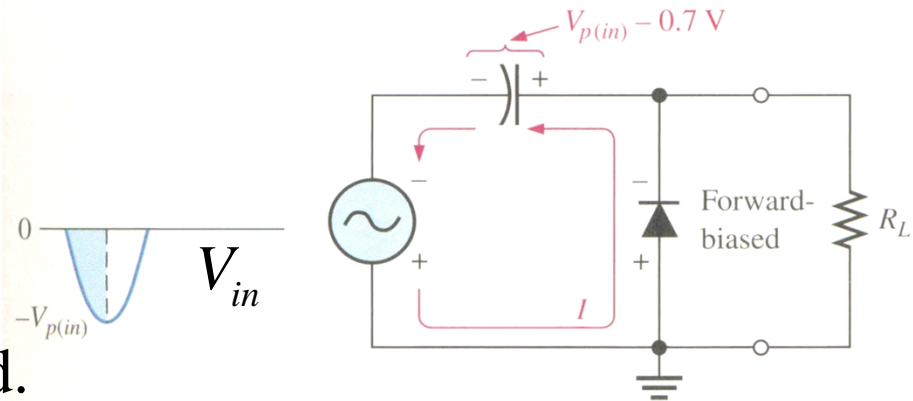


The diode is forward-biased.

$\tau = r'_d C$ is small.

The capacitor is *fastly* charging up to $V_C = V_{p(in)} - 0.7\text{V}$.

Diode Clamper (Cont'd)

Rest of Cycles

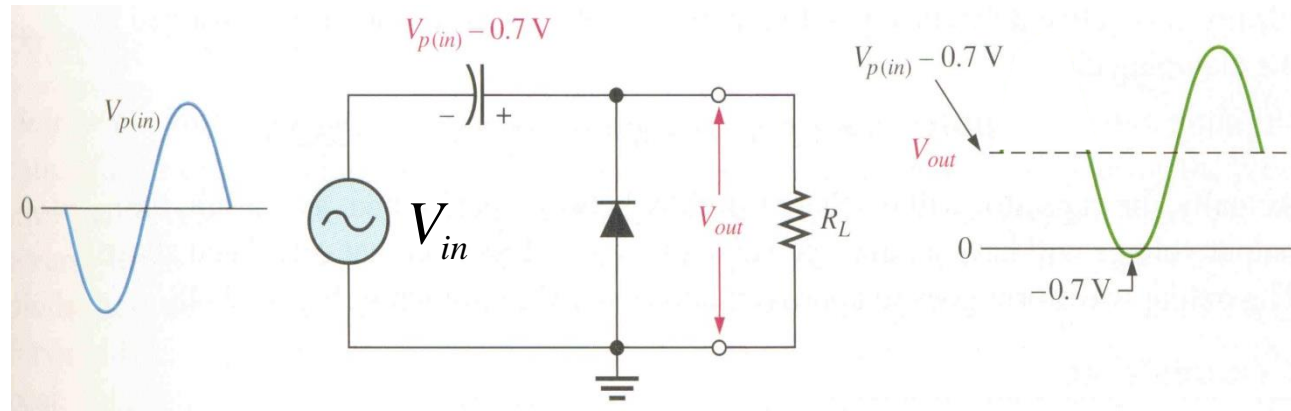

$V_{pn} = -V_{in} - V_C = -V_{in} - V_{p(in)} + 0.7 < 0.7$ Diode is reverse-biased.

The large C is discharging very slowly through R_L .

C can be considered as a battery with constant voltage of $V_C = V_{p(in)} - 0.7$.

$$V_{out} = V_{in} + V_C = V_{in} + V_{p(in)} - 0.7V.$$