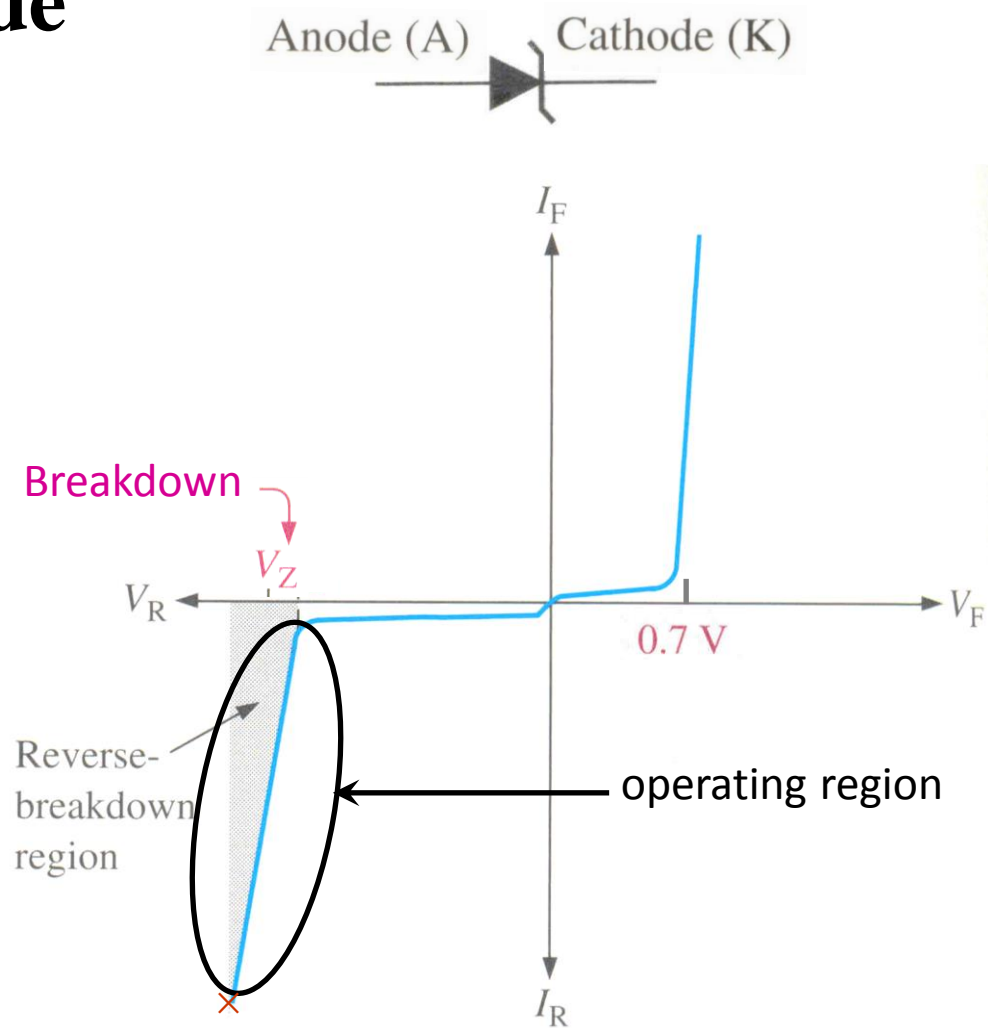


Lecture 9: Diodes (3)

Zener Diodes and their Applications, Examples

Zener Diode



Zener diode is a diode operating in the breakdown region


Zener as a Voltage Regulator

A Zener diode operating along the breakdown line acts as a voltage regulator as it maintains a nearly constant voltage across its terminals over a relatively wide range of the reverse-current ($I_{ZK} < I_Z < I_{ZM}$), where:

In addition to I_{ZK} and I_{ZM} , a Zener diode is characterized by a test point along the breakdown line. The coordinates of this point are

$I_{ZT} \equiv$ Zener test current,

$V_{ZT} \equiv$ Zener test voltage

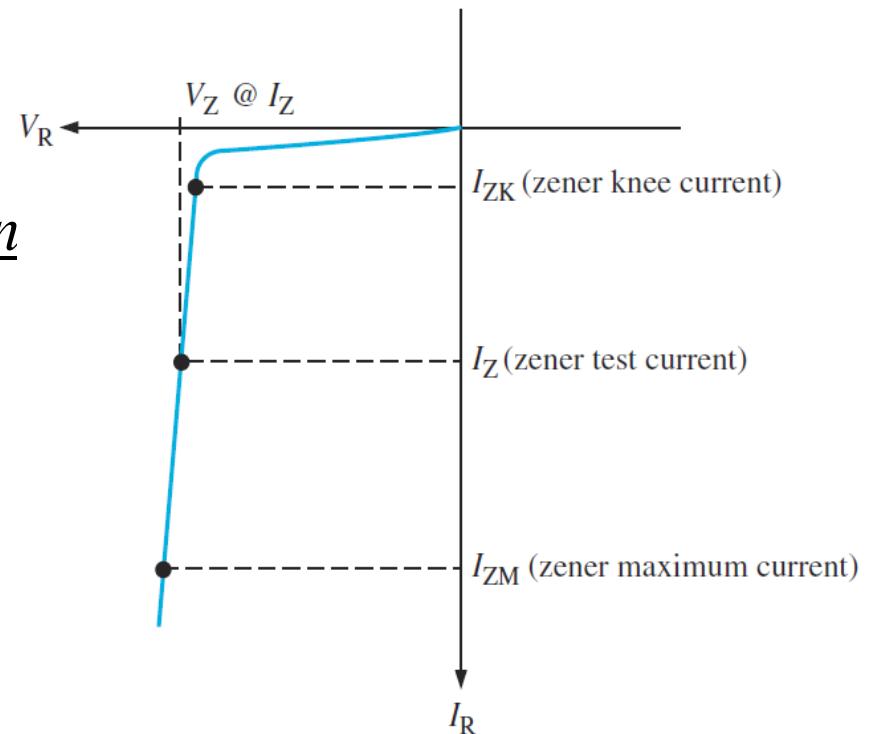


Dynamic Impedance

$Z_Z \equiv$ dynamic impedance


$$= \frac{\Delta V_Z}{\Delta I_Z}$$

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{V_{ZT} - V_{Z0}}{I_{ZT} - 0}$$

$$V_{Z0} = V_{ZT} - Z_Z I_{ZT}$$

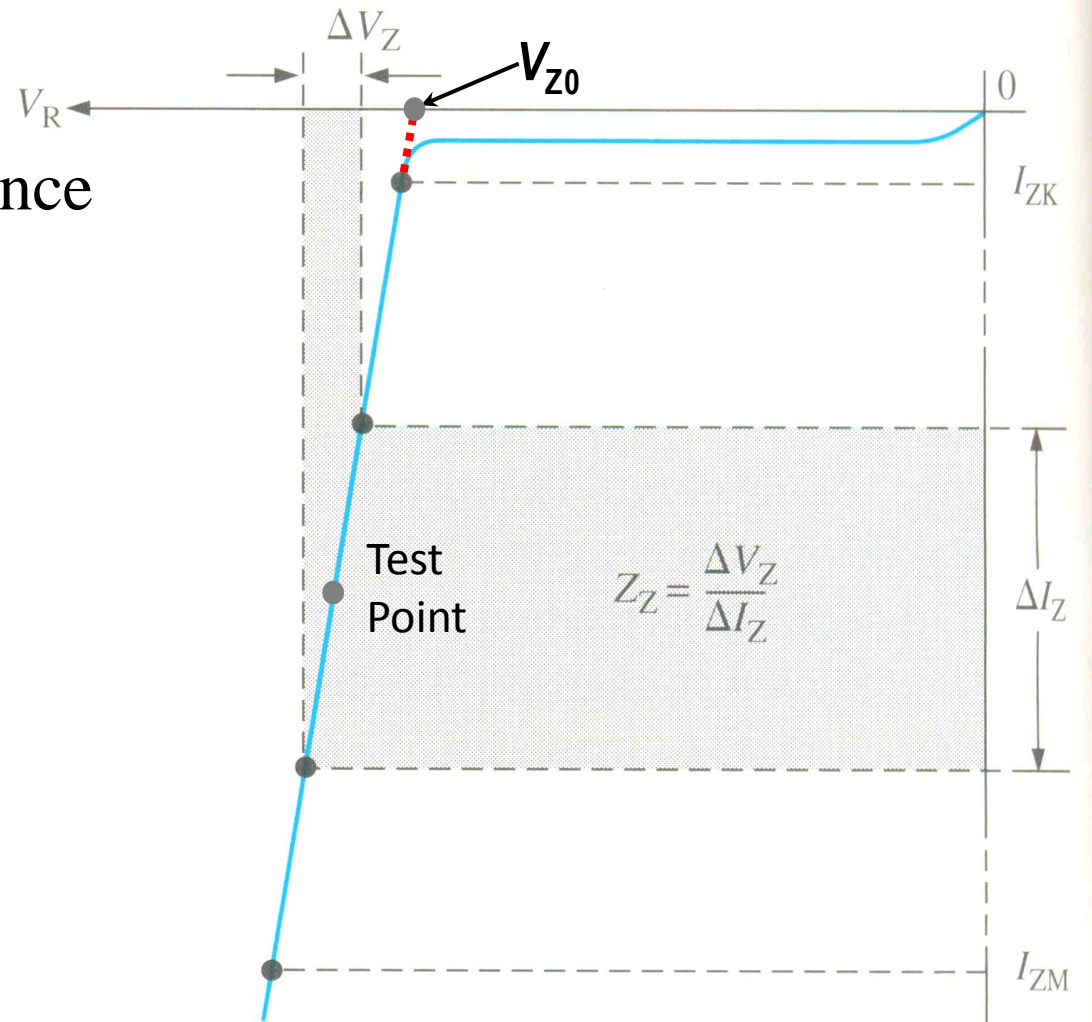


Ideal Zener Equivalent Circuit

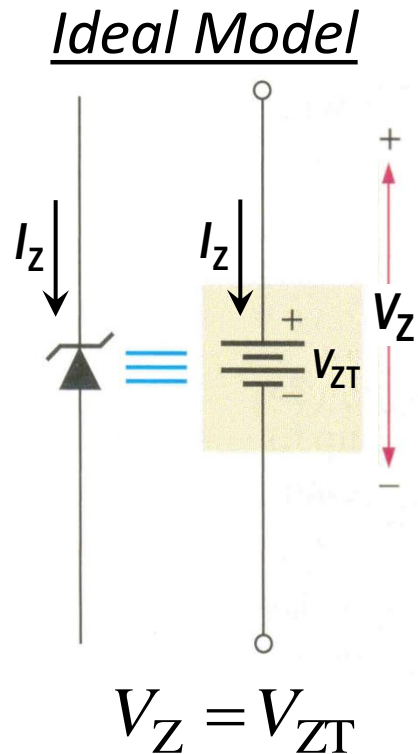

The breakdown line is approximated by an ideal vertical line located at V_{ZT}


Practical Zener Model

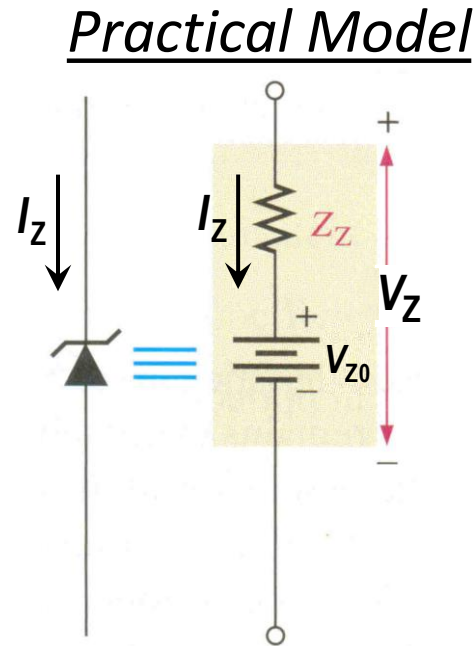

From CC Curve: $V_Z = V_{Z0} + \Delta V_Z = V_{Z0} + Z_Z \Delta I_Z$
 $= V_{Z0} + Z_Z I_Z$

From Model: $V_Z = V_{Z0} + Z_Z I_Z$


Voltage Regulation Using Zeners

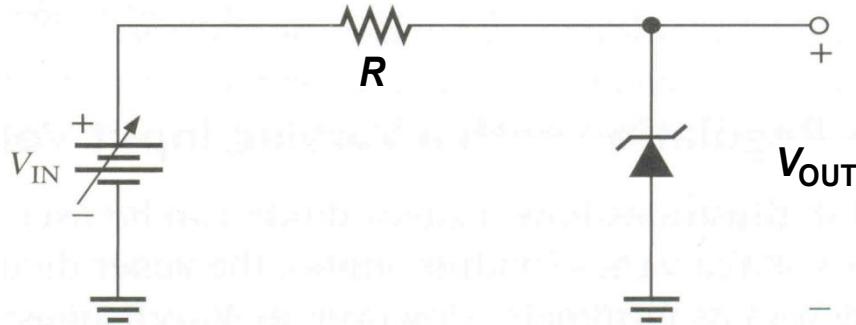

Line regulation $\equiv \Delta V_{OUT} / \Delta V_{IN}$


$$= \left[V_{OUT(max)} - V_{OUT(min)} \right] / \left[V_{IN(max)} - V_{IN(min)} \right]$$

K-Point ($I_Z = I_{ZK}$)

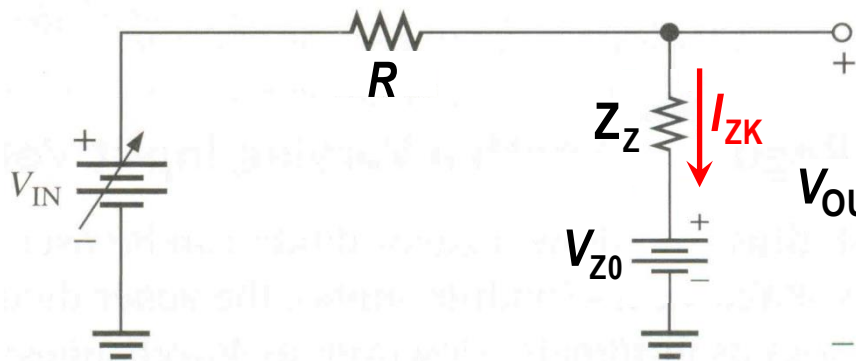

$$V_{OUT(min)} = V_{Z0} + I_{ZK} Z_Z,$$

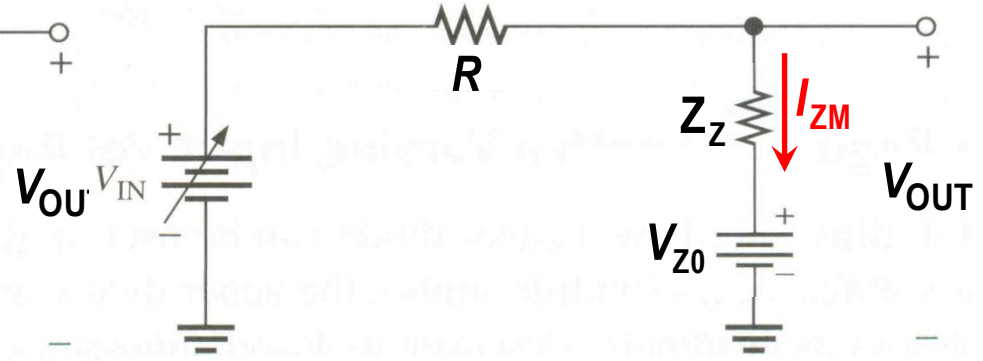
$$V_{IN(min)} = V_{OUT(min)} + I_{ZK} R$$



$$V_{OUT(max)} = V_{Z0} + I_{ZM} Z_Z,$$

$$V_{IN(max)} = V_{OUT(max)} + I_{ZM} R$$

Power Supply Regulator

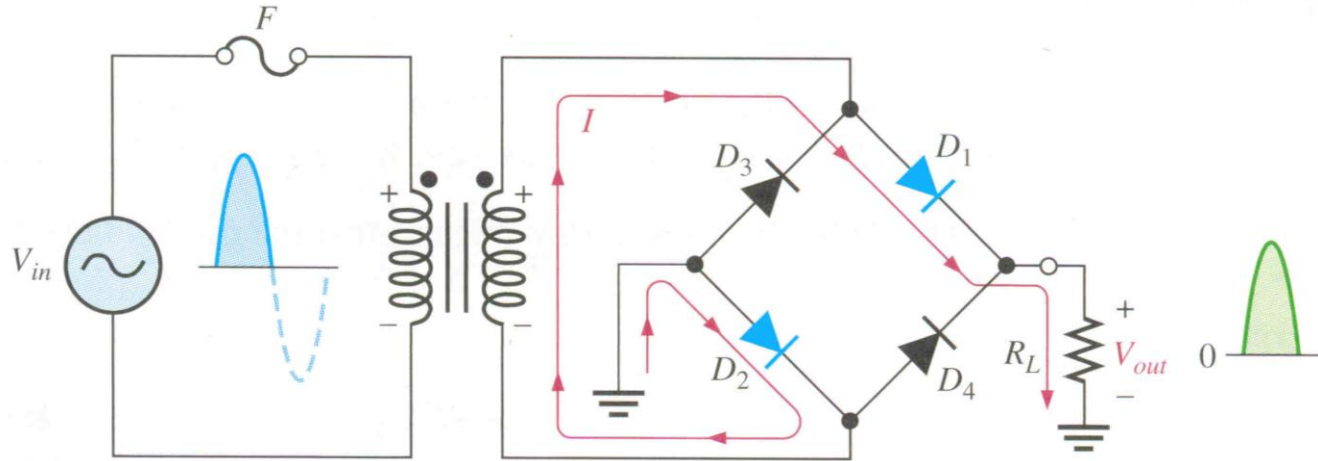

Power Supply Regulators (Cont'd)

The voltage regulator is a three terminals device, which is used to suppress the residual ripples in the output of the filter

Its simplest form is a Zener diode in series with a resistor

