

# Lecture 15:Field Effect Transistors (FETs) (1)


JFET, Characteristic Curves, Biasing, Examples

# FET

The idea for a field-effect transistor (FET) was first proposed by Julius Lilienthal, a physicist and inventor. In 1930 he was granted a U.S. patent for the device.

His ideas were later refined and developed into the FET.

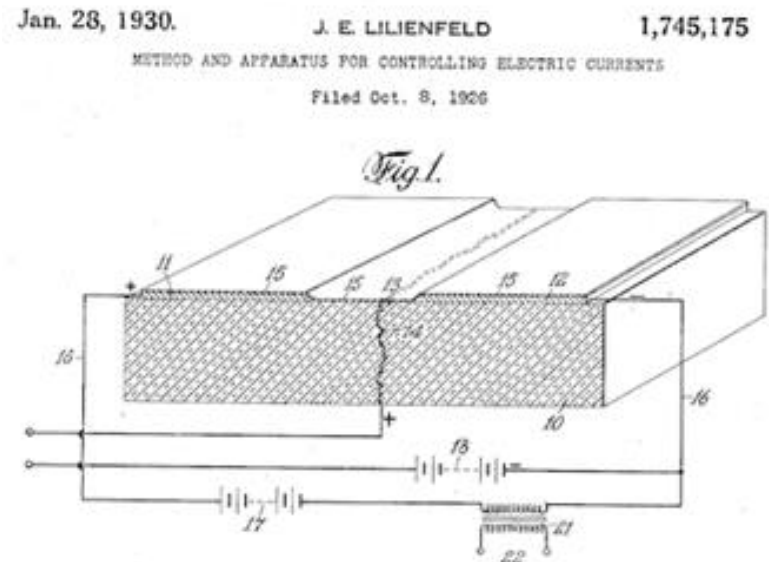
Materials were not available at the time to build his device. A practical FET was not constructed until the 1950's. Today FETs are the most widely used components in integrated circuits.



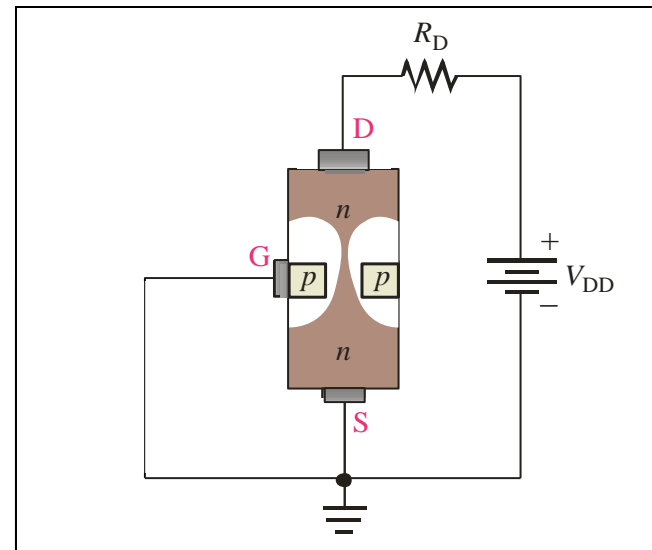
# JFET

The JFET (or Junction Field Effect Transistor) is a normally ON device. For the  $n$ -channel device illustrated, when the drain is positive with respect to the source and there is no gate-source voltage, there is current in the channel.


When a negative gate voltage is applied to the FET, the electric field causes the channel to narrow, which in turn causes current to decrease.




# JFET Operation

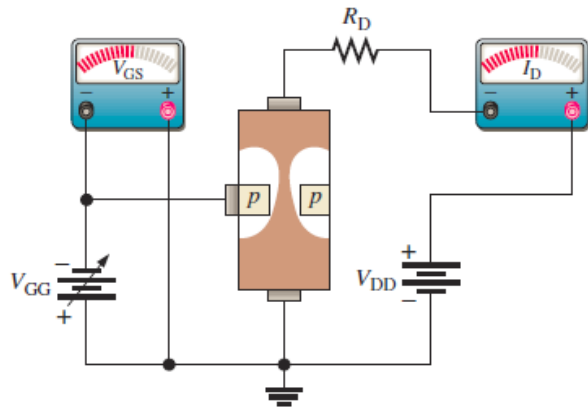

(a) JFET biased for conduction

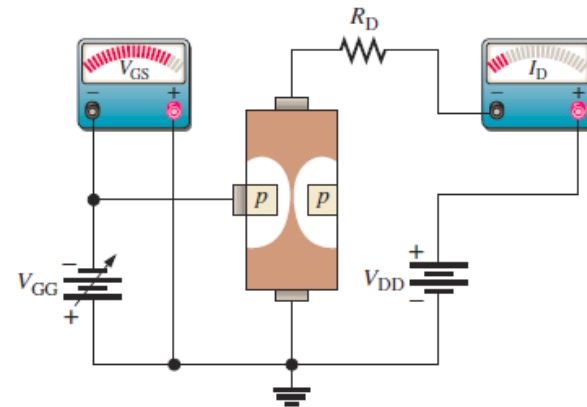

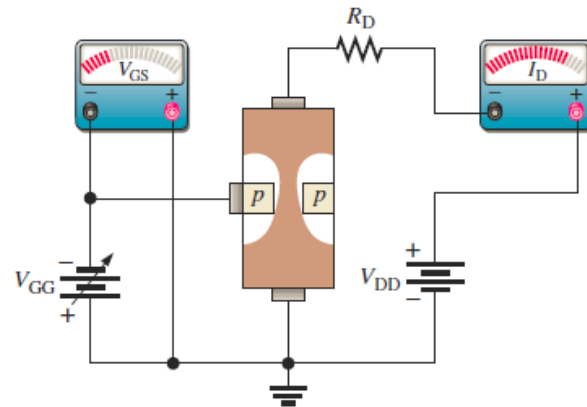(b) Greater  $V_{GS}$  narrows the channel (between the white areas) which increases the resistance of the channel and decreases  $I_D$ .




(c) Less  $V_{GS}$  widens the channel (between the white areas) which decreases the resistance of the channel and increases  $I_D$ .
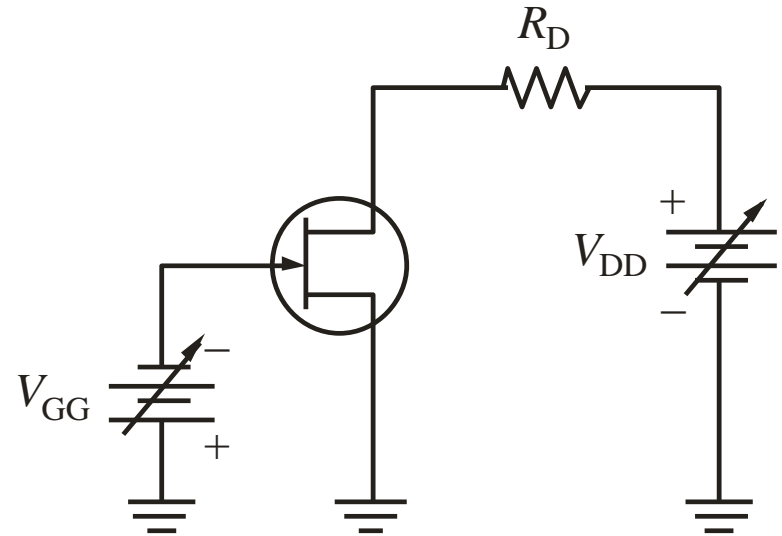
# JFET Circuit Symbol

There are two types of JFETs:  $n$ -channel and  $p$ -channel. The dc voltages are opposite polarities for each type.

The symbol for an  $n$ -channel JFET is shown, along with the proper polarities of the applied dc voltages. For an  $n$ -channel device, the gate is always operated with a negative (or zero) voltage with respect to the source.



We will focus on  $n$ -channel JFET


# Drain Characteristic Curves

There are three regions as illustrated for the case when  $V_{GS} = 0$  V.

Between  $A$  and  $B$  is the **Ohmic region**, where current and voltage are related by Ohm's law.

From  $B$  to  $C$  is the **active (or constant-current) region** where current is essentially independent of  $V_{DS}$ .

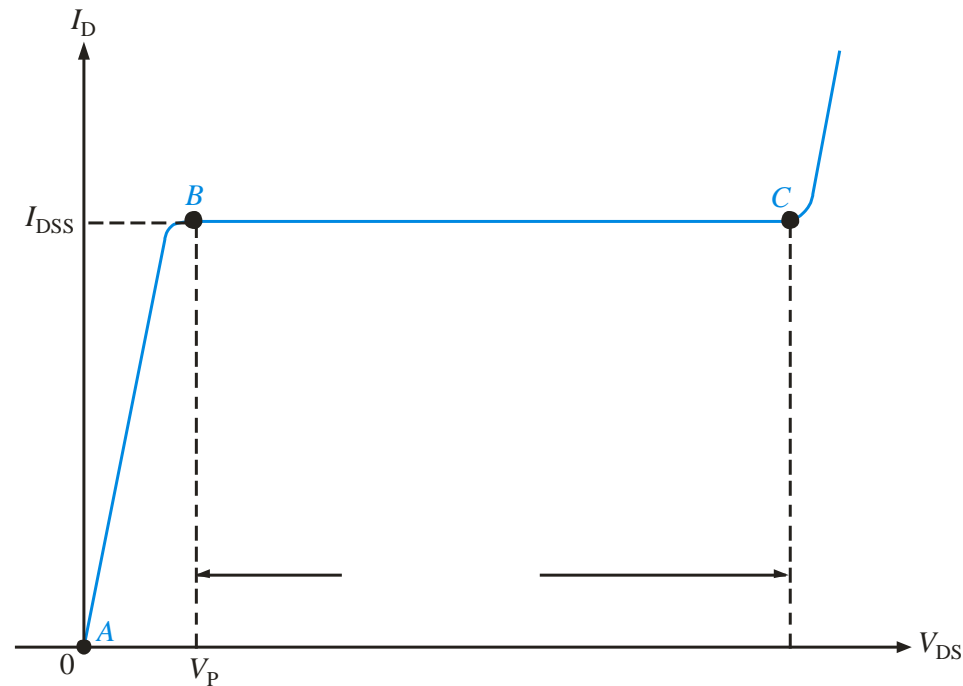
Beyond  $C$  is the breakdown region. Operation here can damage the FET.


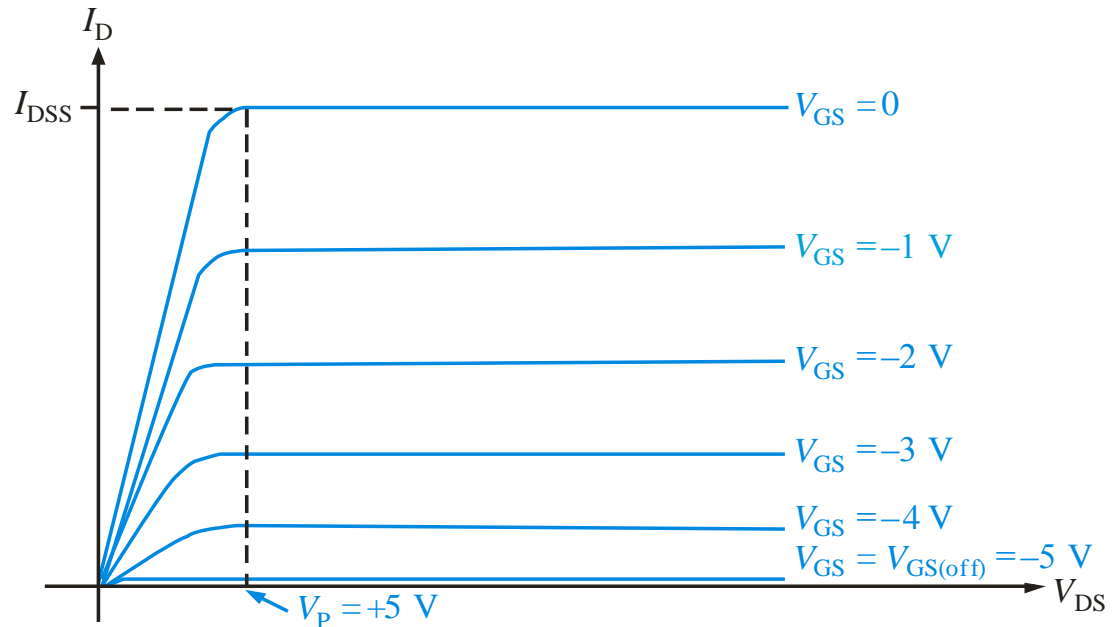
# Characteristic Curves (Cont'd)

When  $V_{GS}$  is set to different values, the relationship between  $V_{DS}$  and  $I_D$  develops a family of characteristic curves for the device.

An  $n$ -channel characteristic is illustrated here. Notice that  $V_p$  is positive and has the same magnitude as  $V_{GS(off)}$ .




# Transconductance Curve

A plot of  $V_{GS}$  to  $I_D$  is called the transfer or transconductance curve. The transfer curve is a plot of the output current ( $I_D$ ) to the input voltage ( $V_{GS}$ ).

The transfer curve is based on the equation

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

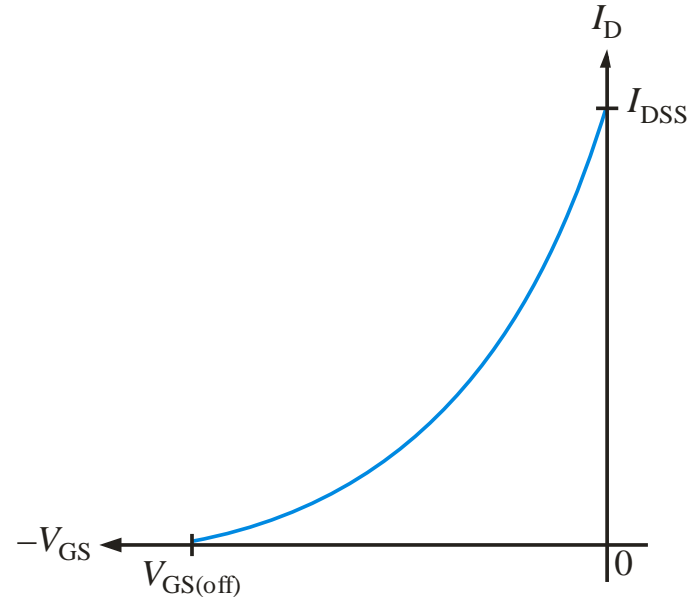By substitution, you can find other points on the curve for plotting the universal curve.





# Transconductance

The transconductance is the ratio of a change in output current ( $\Delta I_D$ ) to a change in the input voltage ( $\Delta V_{GS}$ ).


This definition is  $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$

The following approximate formula is useful for calculating  $g_m$  if you know  $g_{m0}$ .

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

The value of  $g_{m0}$  can be found from


$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

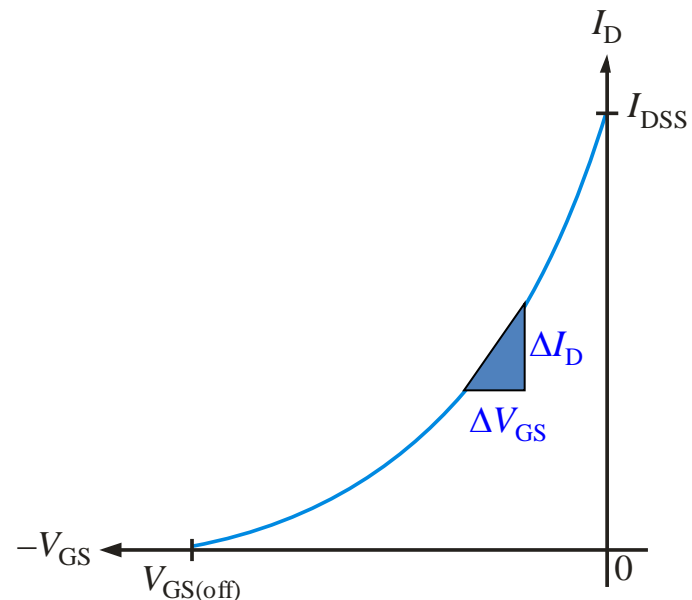
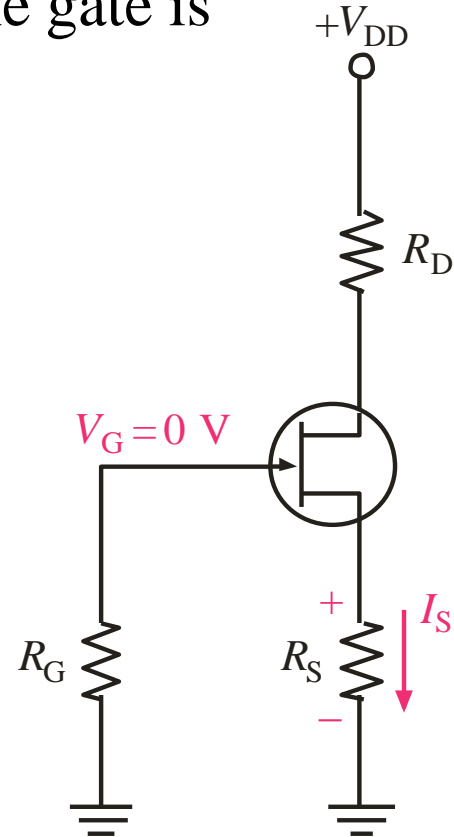
# Biasing of a JFET

Self-bias is simple and effective, so it is the most common biasing method for JFETs. With self bias, the gate is essentially at 0 V.

An  $n$ -channel JFET is illustrated. The current in  $R_S$  develops the necessary reverse bias that forces the gate to be less than the source.




# Voltage Divider Biasing

Voltage-divider biasing is a combination of a voltage-divider and a source resistor to keep the source more positive than the gate.

$V_G$  is set by the voltage-divider and is independent of  $V_S$ .  $V_S$  must be larger than  $V_G$  in order to maintain the gate at a negative voltage with respect to the source.

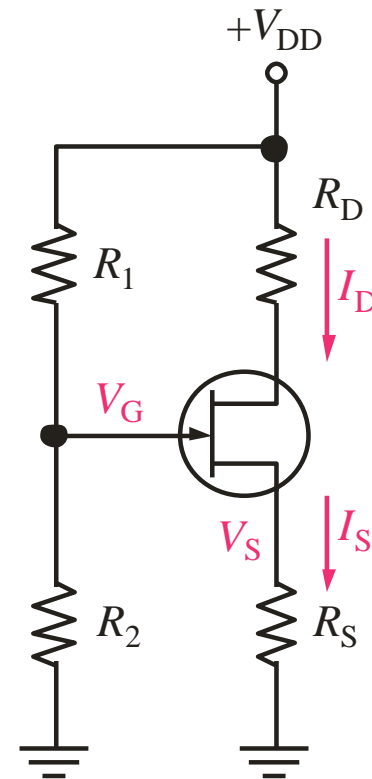Voltage-divider bias helps stabilize the bias for variations between transistors.



# Current Source Biasing

An even more stable form of bias is current-source bias. The current-source can be either a BJT or another FET. With current-source biasing, the drain current is essentially independent of  $V_{GS}$ .

In this circuit  $Q_2$  serves as a current source for  $Q_1$ . An advantage to this particular circuit is that the output can be adjusted (using  $R_{S2}$ ) for 0 V DC.

