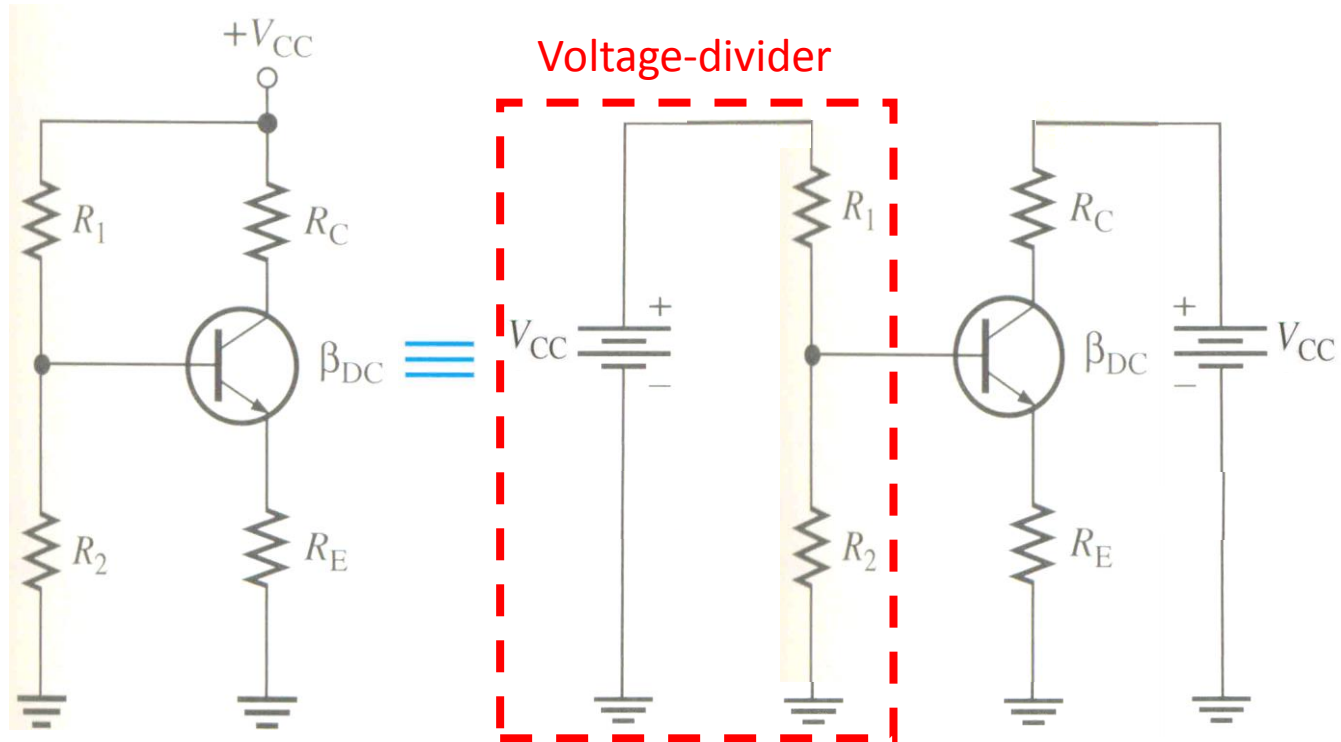



Lecture 26: Bipolar Junction Transistors (3)

Different Bias Networks, BJT as an Amplifier,
Examples

Voltage Divider Bias



Voltage Divider Bias

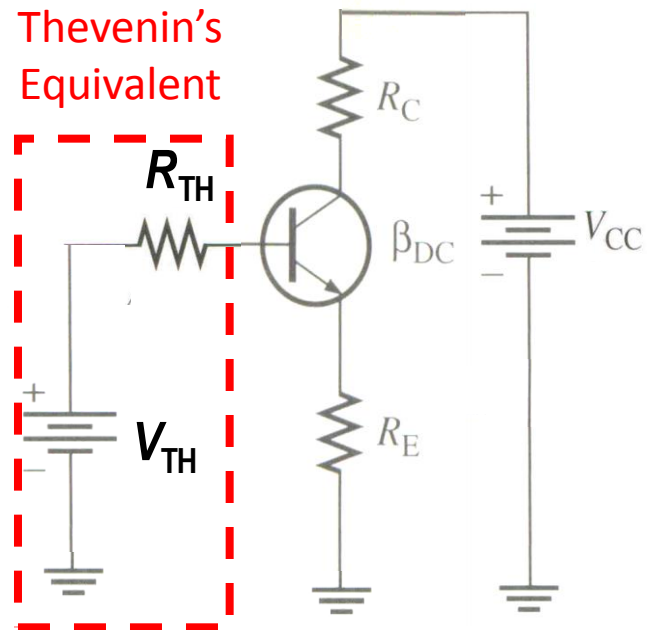


$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}, \quad R_{TH} = R_1 \parallel R_2$$

Voltage Divider (Cont'd)

$$V_{TH} = I_E R_E + V_{BE} + I_B R_{TH}$$
$$\cong I_C R_E + V_{BE} + I_C R_{TH} / \beta_{DC}$$

$$\therefore I_C = \frac{V_{TH} - V_{BE}}{R_E + R_{TH} / \beta_{DC}},$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

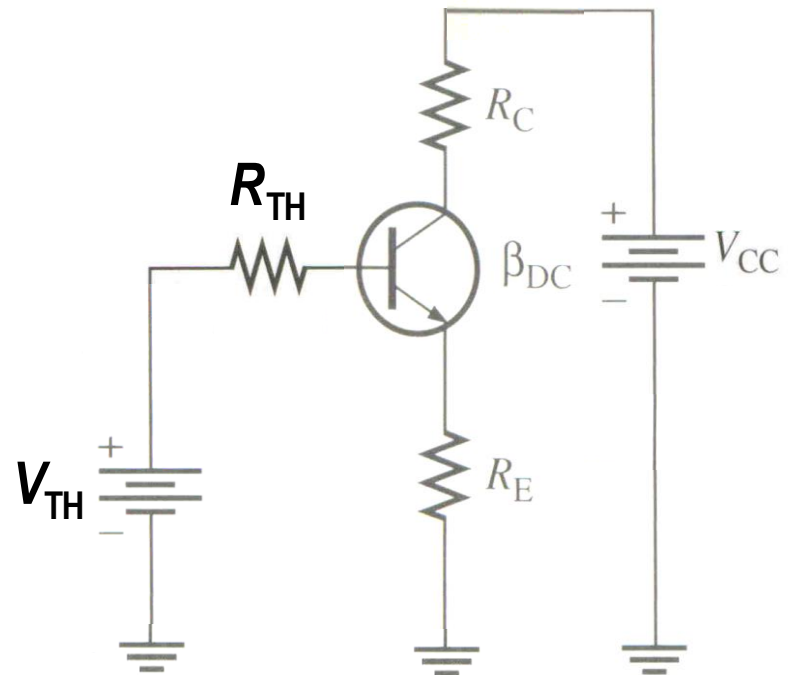


Base Bias

$$V_{CC} = V_{BE} + I_B R_B = V_{BE} + \frac{I_C}{\beta_{DC}} R_B$$
$$\therefore I_C = \frac{V_{CC} - V_{BE}}{R_B / \beta_{DC}} = \beta_{DC} \frac{V_{CC} - V_{BE}}{R_B},$$

$$V_{CE} = V_{CC} - I_C R_C$$

This circuit is used often as a switch

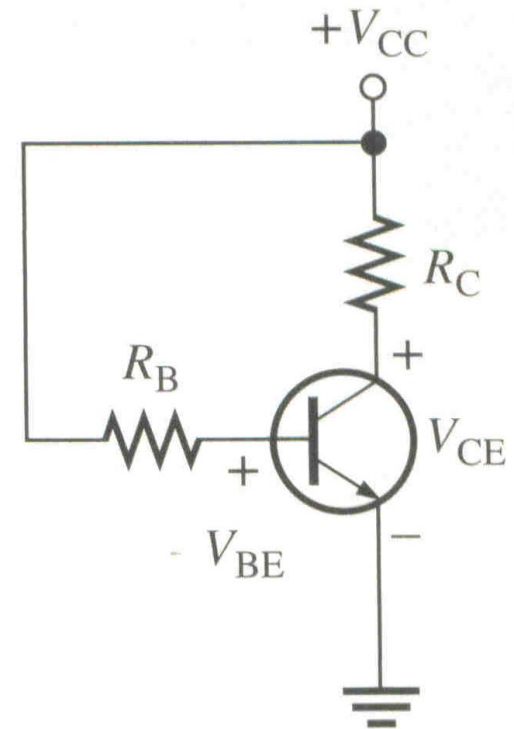

Emitter Feedback


if an emitter resistor R_E is added to the base bias circuit, the result is the emitter-feedback bias circuit shown

the Q-point of this circuit can be obtained as follows:

$$\begin{aligned} V_{CC} &= I_E R_E + V_{BE} + I_B R_B \\ &\cong I_C R_E + V_{BE} + \frac{I_C}{\beta_{DC}} R_B \end{aligned}$$

$$\therefore I_C = \frac{V_{CC} - V_{BE}}{R_E + R_B / \beta_{DC}},$$

$$V_{CE} = V_{CC} - I_C (R_E + R_C)$$

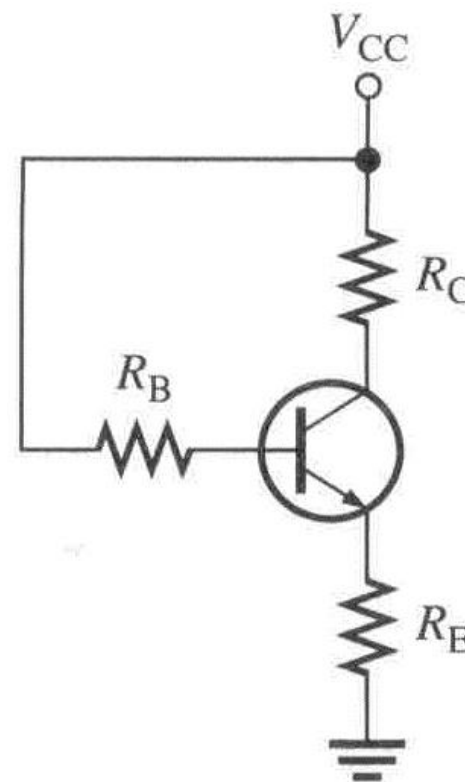

Collector Feedback

this bias method is also similar to the base bias, except for connecting R_B directly to the collector rather than to V_{CC} .


the Q-point can be obtained as follows:

$$V_{CC} = V_{BE} + I_B R_B + (I_C + I_B) R_C$$


$$\cong V_{BE} + \frac{I_C}{\beta_{DC}} R_B + I_C R_C$$

$$\therefore I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}}$$

$$V_{CE} = V_{CC} - I_C R_C$$

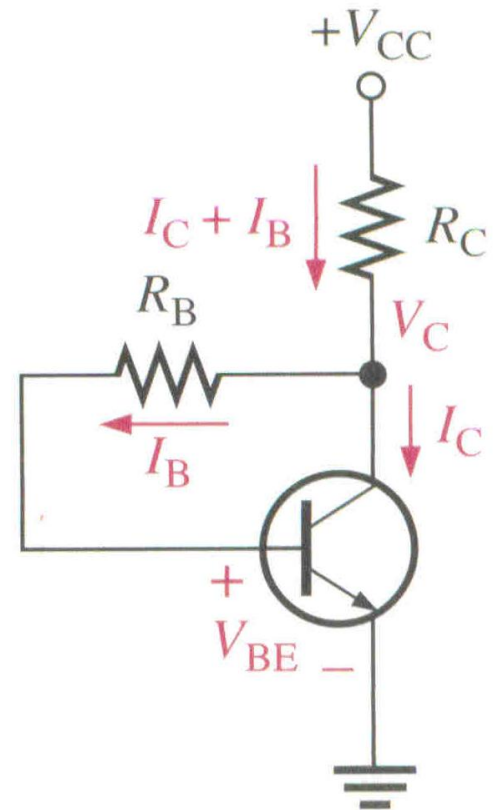

BJT Circuits with AC and DC Sources

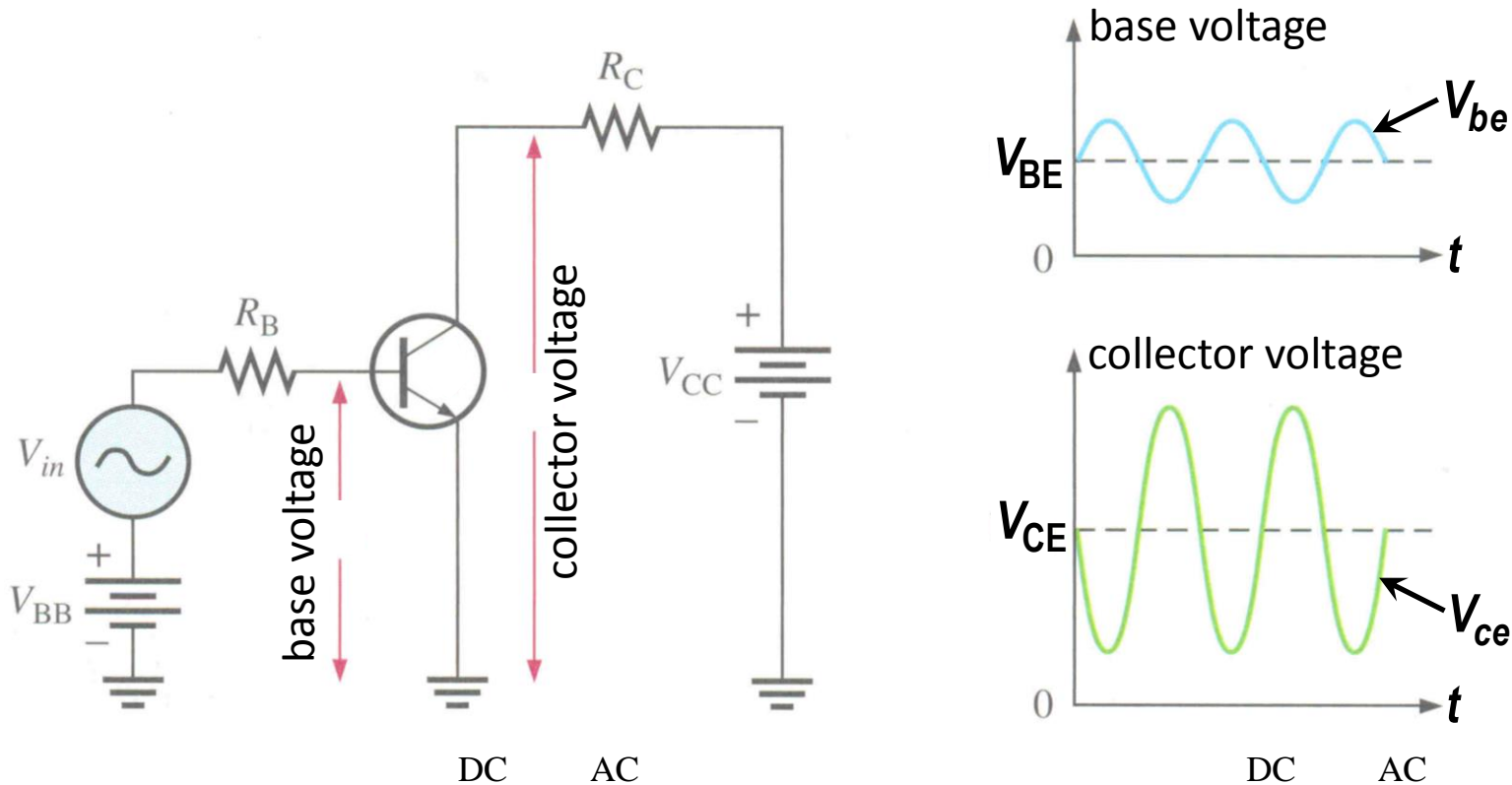


$$\text{base voltage} = \underset{\text{DC}}{V_{BE}} + \underset{\text{AC}}{V_{be}}, \quad \text{collector voltage} = \underset{\text{DC}}{V_{CE}} + \underset{\text{AC}}{V_{ce}}$$

$$\text{base current} = I_B + I_b, \quad \text{collector current} = I_C + I_c$$

Graphical AC Analysis

we solve graphically for I_c and V_{ce} , knowing the applied input signal I_b .

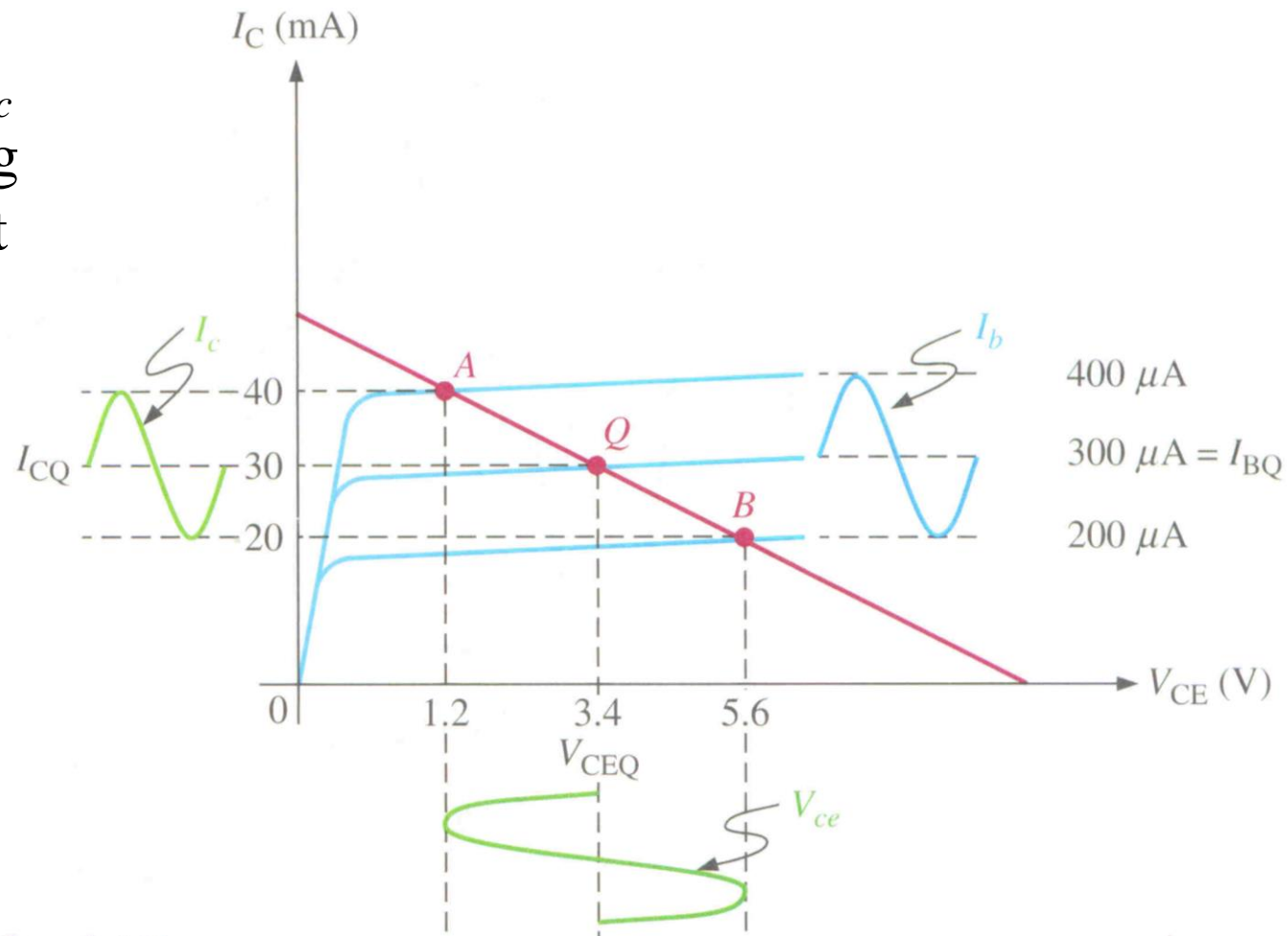the Q-point can be considered as the center of the domain of variation of the transistor's currents and voltages.




Waveform Distortion

Q-point is close to saturation

the projection of the +ve peak of I_b on the DC load line lies outside the active region

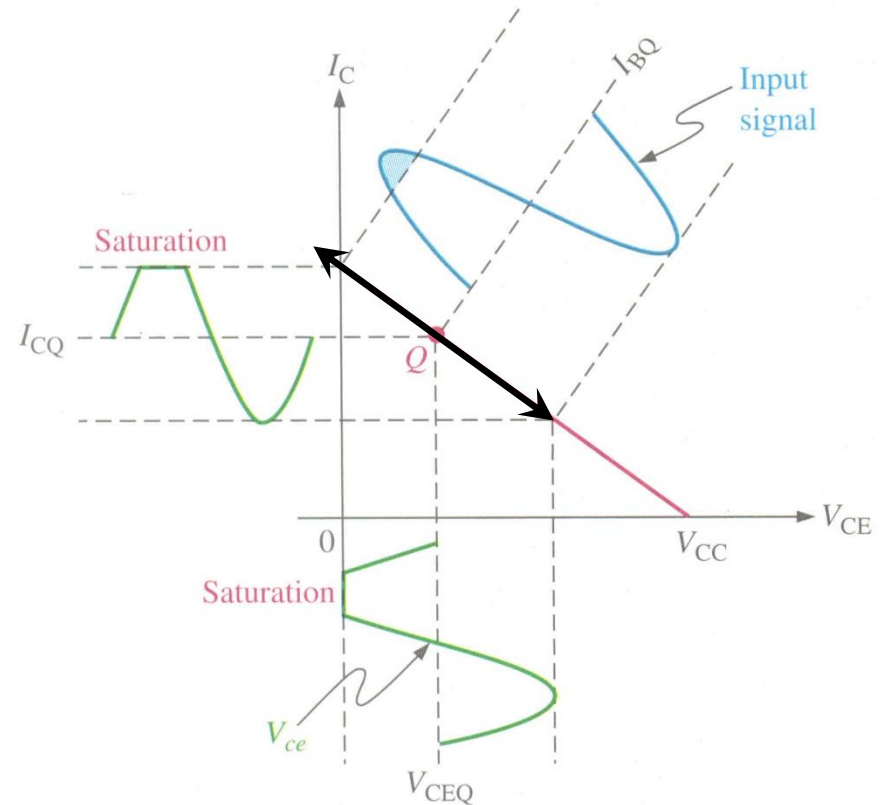I_c and V_{ce} waveforms are one-side distorted.




Waveform Distortion (Cont'd)

Q-point is close to cutoff

the projection of the -ve peak of I_b on the DC load line lies outside the active region

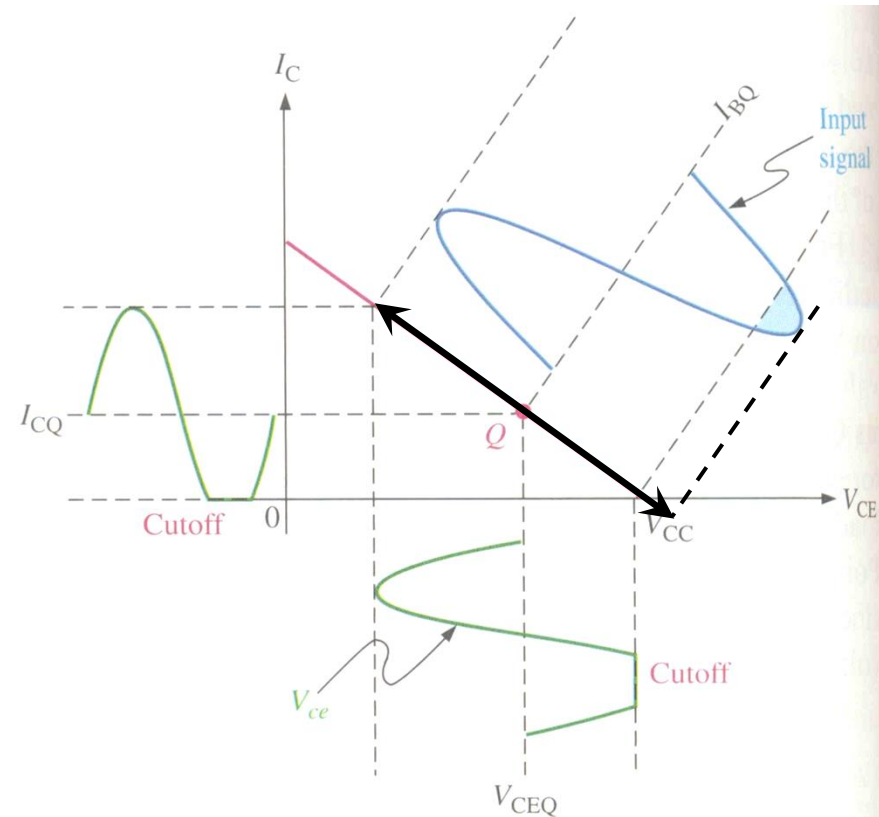I_c and V_{ce} waveforms are one-side distorted



Waveform Distortion

amplitude of I_b is relatively large

the projections of both the +ve and -ve peaks of I_b on the DC load line lie outside the active region

I_c and V_{ce} waveforms are distorted in both sides

waveform distortion is undesired for amplifiers

