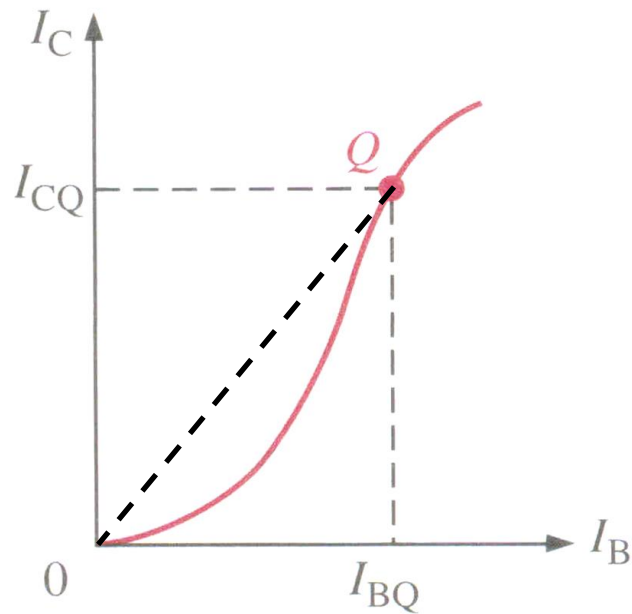


Lecture 27: Bipolar Amplifiers (1)


DC gain vs. AC gain, Common Emitter
Amplifier, Examples

DC vs. AC Current Gain



$$\beta_{DC} = \frac{I_C}{I_B} \Bigg|_{\text{at the Q-point}} = \frac{I_{CQ}}{I_{BQ}}$$

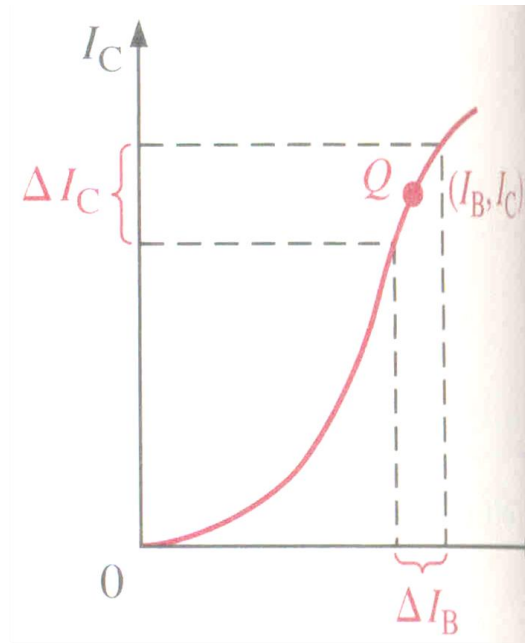= slope of the line from the origin to the Q-point.





$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Bigg|_{\text{around the Q-point}} = \frac{I_{c(pp)}}{I_{b(pp)}}$$

= slope of the tangential line to the curve at the Q-point.


AC Equivalent of a BJT

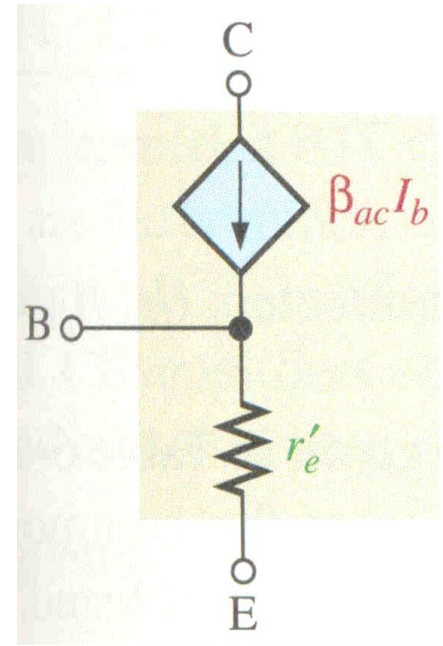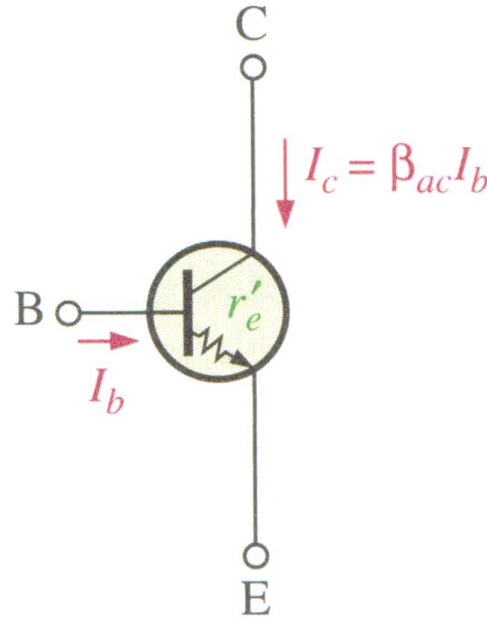since the total (DC + AC) voltage difference across the forward-biased BE junction should be around 0.7 V, the AC part (V_{be}) alone should be very small and is represented by an extremely small resistance.



$$r'_e \cong \frac{25 \text{ mV}}{I_E}, \text{ where } I_E \text{ is the DC emitter current.}$$

Common Emitter Amplifier

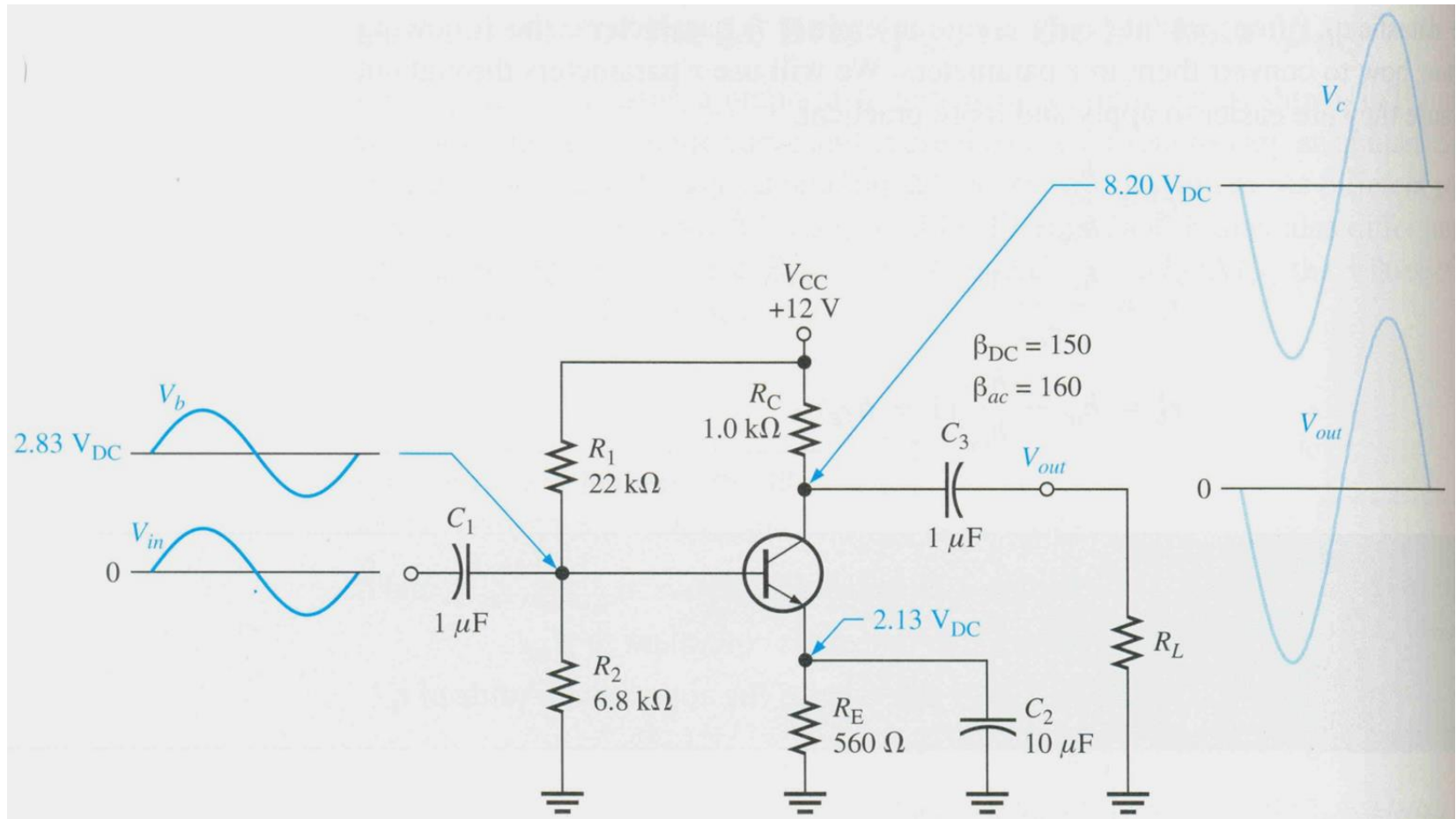


Original Circuit



two sources (DC and AC) are present in the original circuit.

it is equivalent to the superposition of two sub-circuits.

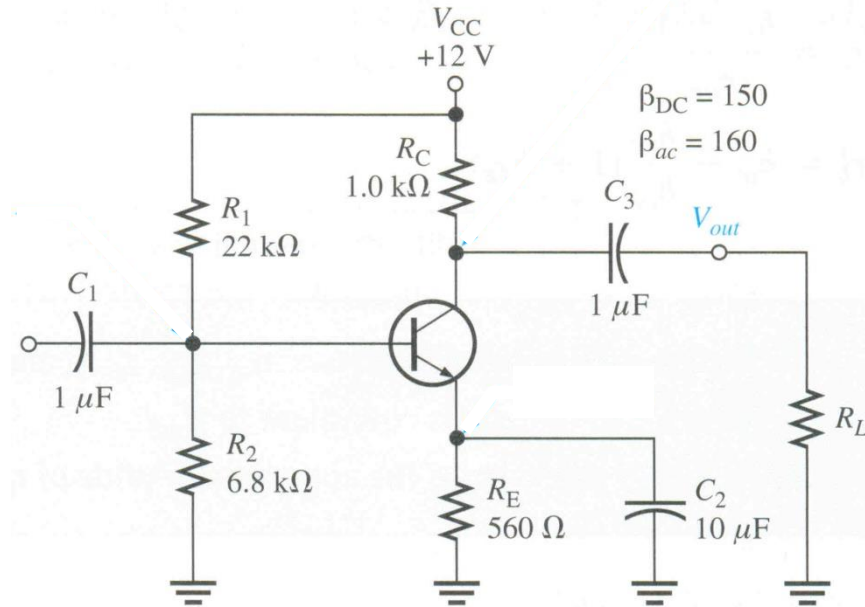only one source is kept in each sub-circuit, the other one is replaced by a s.c.






DC/AC Circuit

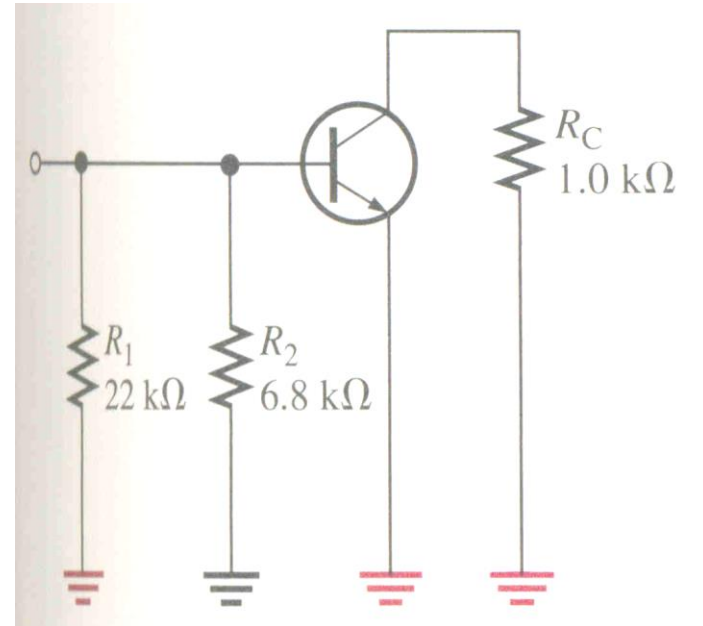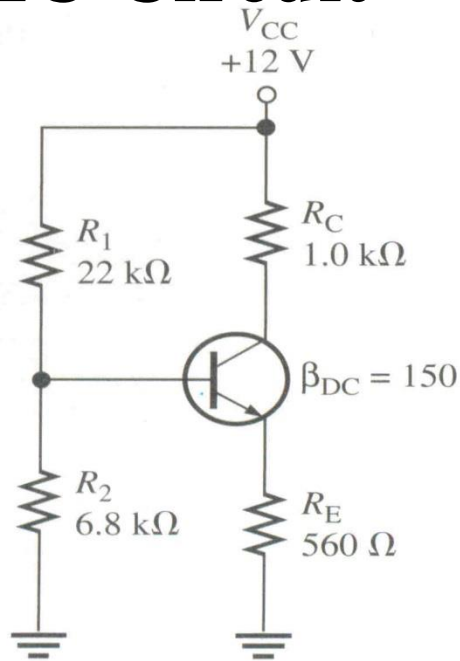

solve the DC circuit for the bias (operating) point. All capacitors are open circuit.

solve the AC circuit for the gain, input resistance, and output resistance. All capacitors are short circuit.

Input Resistance

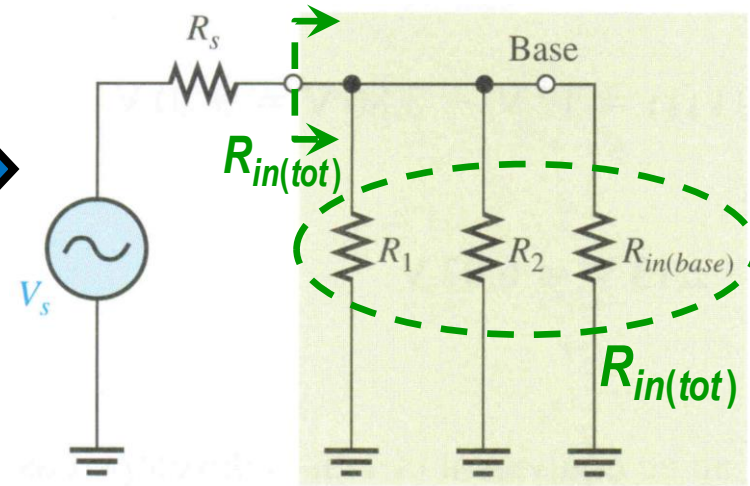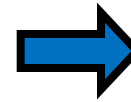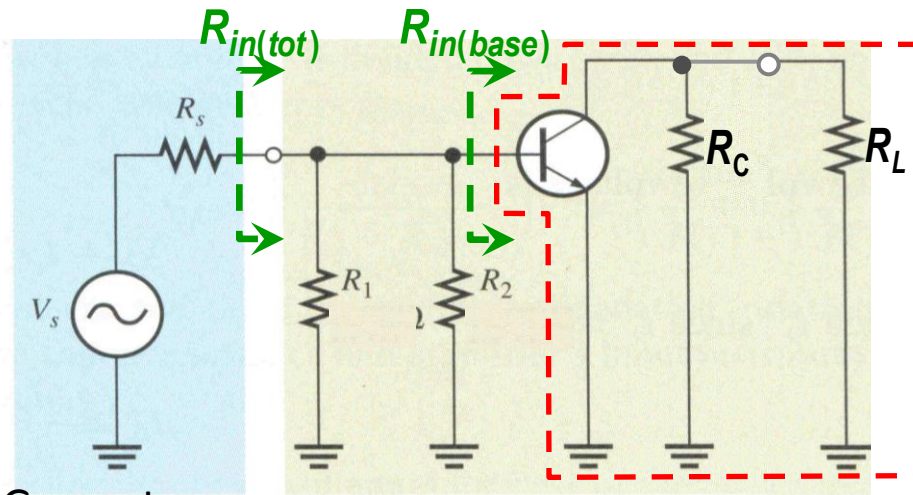


$$R_{in(base)} = \frac{V_b}{I_b}$$

$$= \frac{I_e r'_e}{I_c / \beta_{ac}}$$

$$\approx \frac{I_e r'_e}{I_e / \beta_{ac}}$$

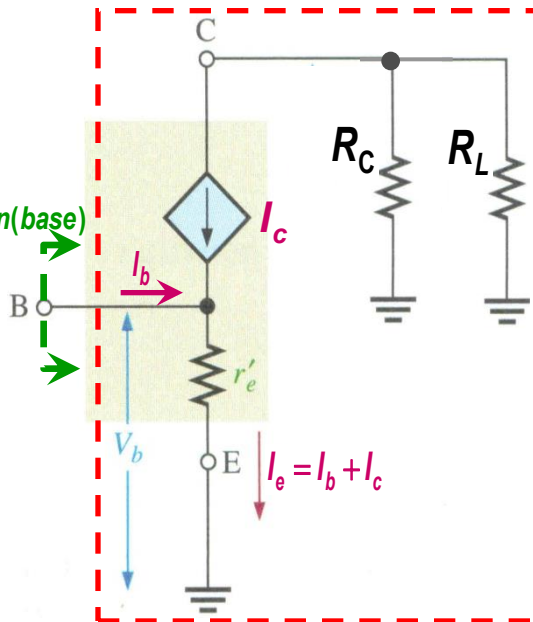
$$\therefore R_{in(base)} = \beta_{ac} r'_e$$



$$R_{in(tot)} = R_1 \parallel R_2 \parallel R_{in(base)}$$

$$V_b = \left(\frac{R_{in(tot)}}{R_s + R_{in(tot)}} \right) V_s$$


Output Resistance

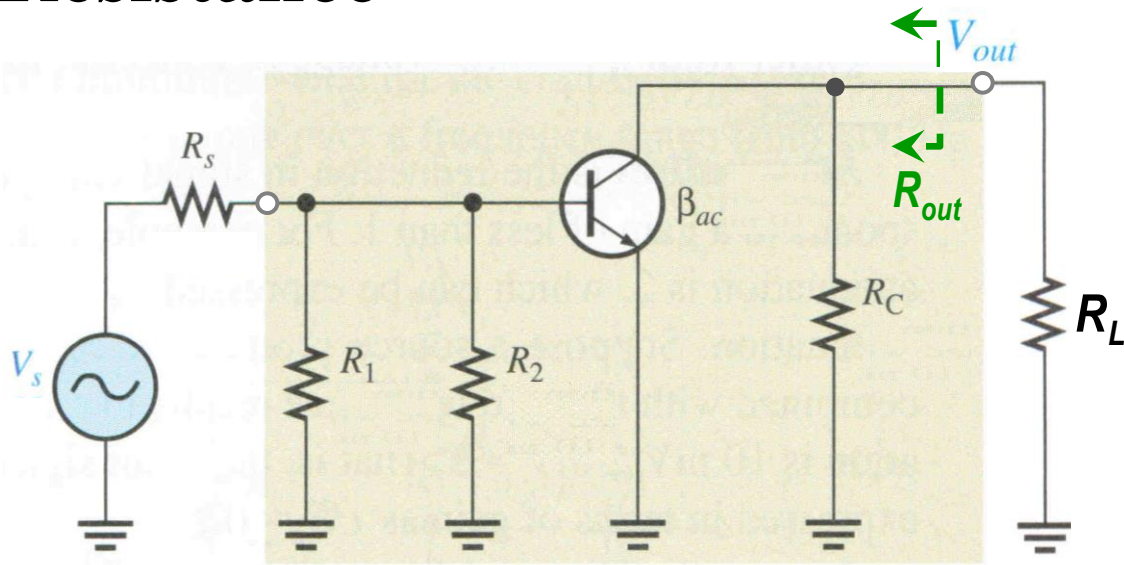



$$R_{out} = \left. \frac{V_{out}}{I_{out}} \right|_{V_s \rightarrow \text{s.c.}}$$

$$= \frac{I_{out} R_C}{I_{out}}$$

$$\therefore R_{out} = R_C$$

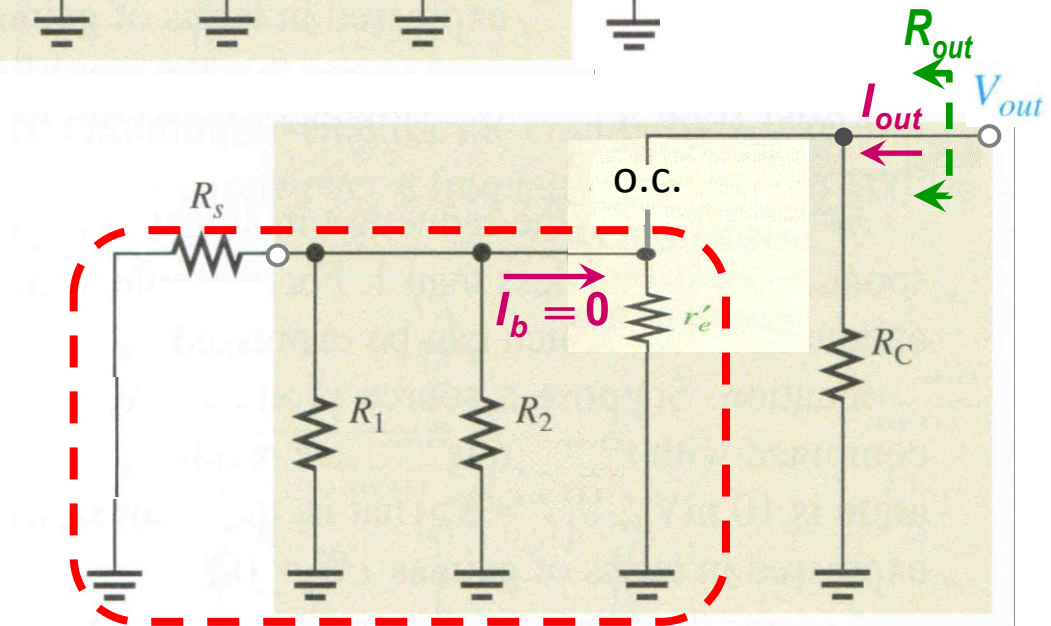

Voltage Gain

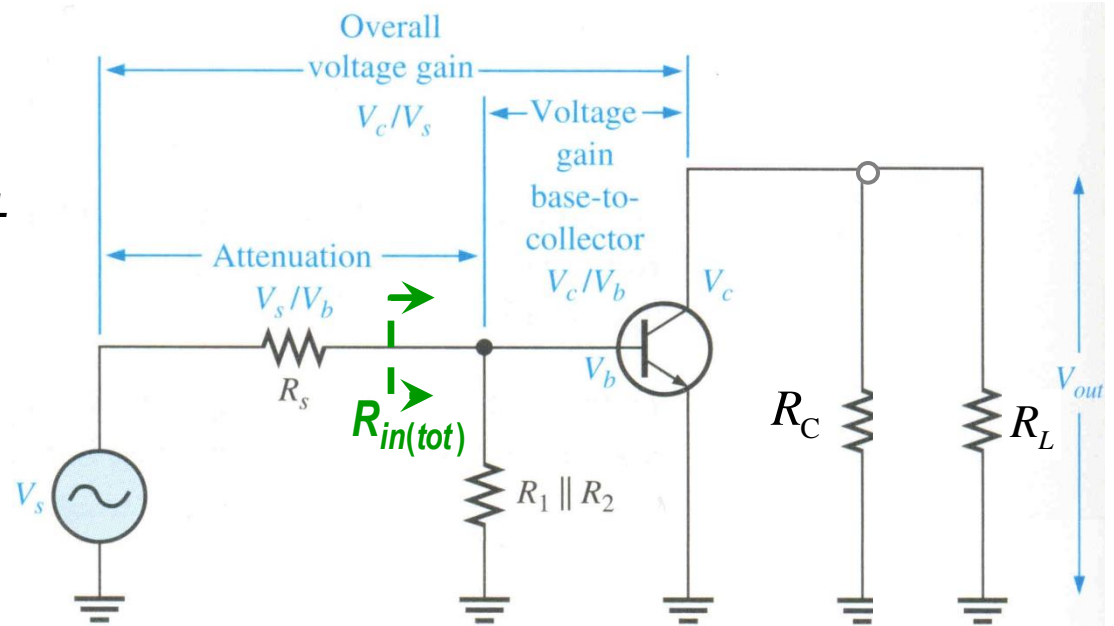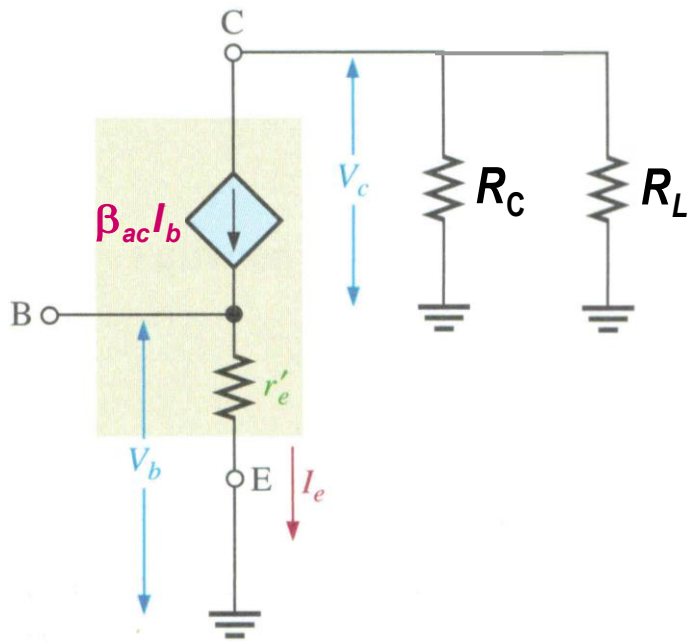


$$A_v \equiv \text{ideal voltage gain} = \frac{V_c}{V_b}$$

$$= \frac{I_c (R_C \parallel R_L)}{I_e r'_e} \cong \frac{R_C \parallel R_L}{r'_e}$$

$$A'_v \equiv \text{overall voltage gain} = \frac{V_c}{V_s} = \left(\frac{V_c}{V_b} \right) \left(\frac{V_b}{V_s} \right) = \frac{A_v}{\text{Attenuation}},$$


$$\text{where: Attenuation} = \frac{V_s}{V_b} = \frac{R_s + R_{in(tot)}}{R_{in(tot)}} \geq 1 \Rightarrow A'_v \leq A_v$$

Effect of Bypass Capacitor

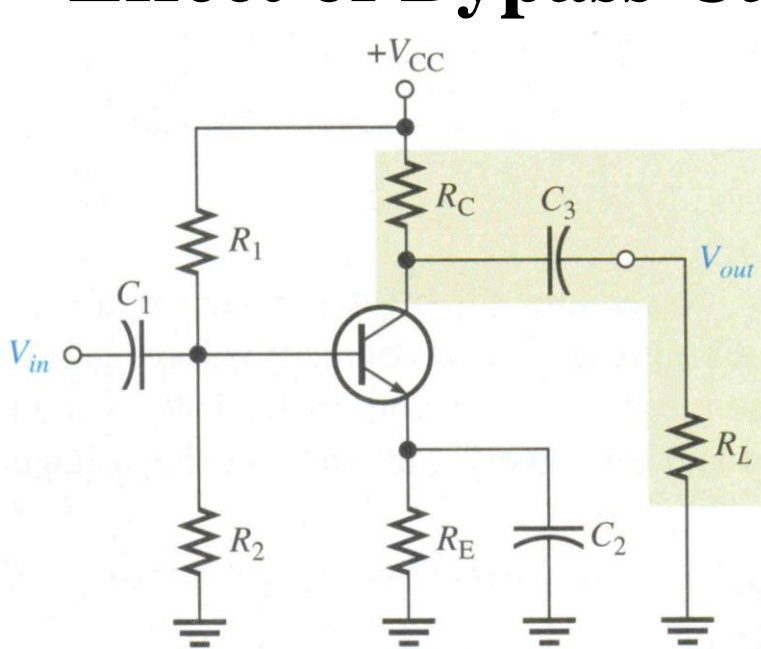

$$A_v = (R_C \parallel R_L) / r'_e, \quad R_{in(base)} = \beta_{ac} r'_e$$

$$r'_e \Rightarrow r'_e + R_E$$

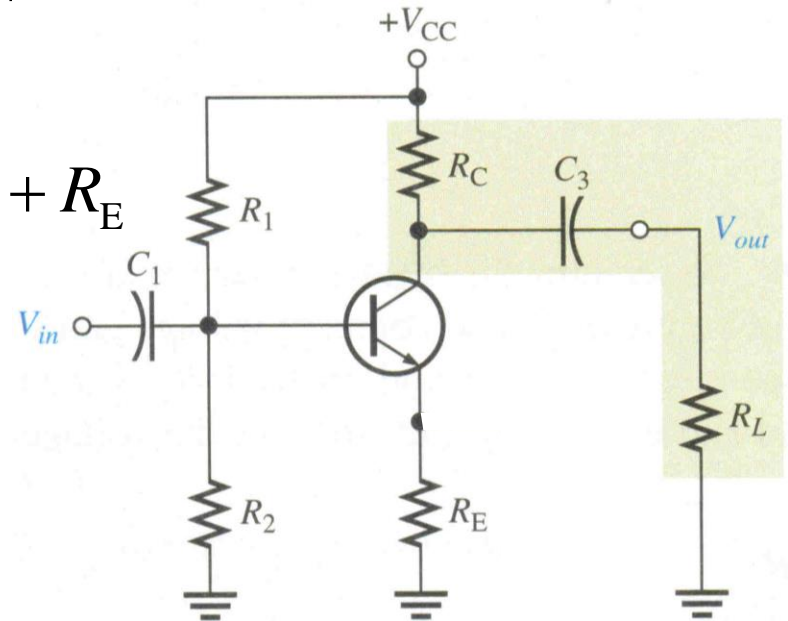

$$A_v = (R_C \parallel R_L) / (r'_e + R_E), \quad R_{in(base)} = \beta_{ac} (r'_e + R_E)$$


the effect of the emitter bypass capacitor is to increase A_v and to decrease $R_{in(base)}$.

$$X_{C(max)} \ll R_E \Rightarrow X_{C(max)} < 0.1R_E \Rightarrow \frac{1}{2\pi f_{min} C_2} < 0.1R_E$$

Voltage Gain Stability


the voltage gain A_v depends on r'_e which depends on temperature. This makes A_v unstable with temperature.

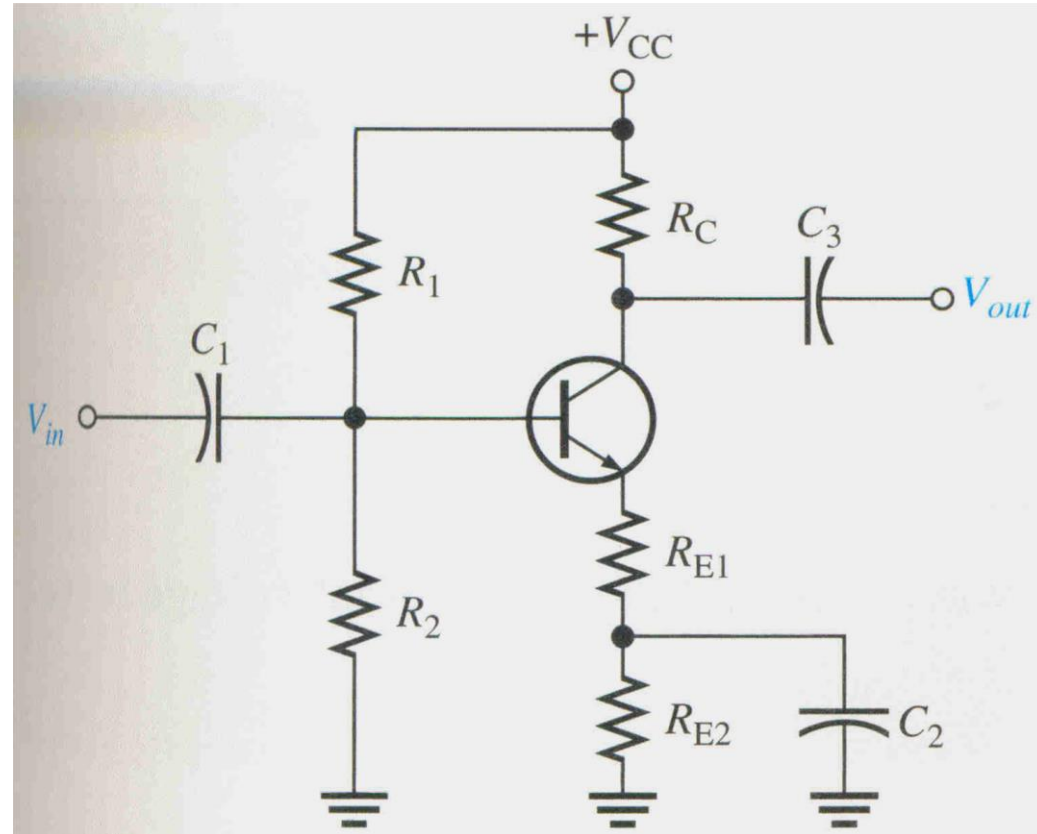one way to overcome this problem without reducing A_v too much is to partially swamp r'_e , which means that R_E is partially bypassed.



$$A_v = \frac{R_C}{r'_e + R_{E1}}, \quad R_{in(base)} = \beta_{ac} (r'_e + R_{E1})$$

Gain Stability (Cont'd)

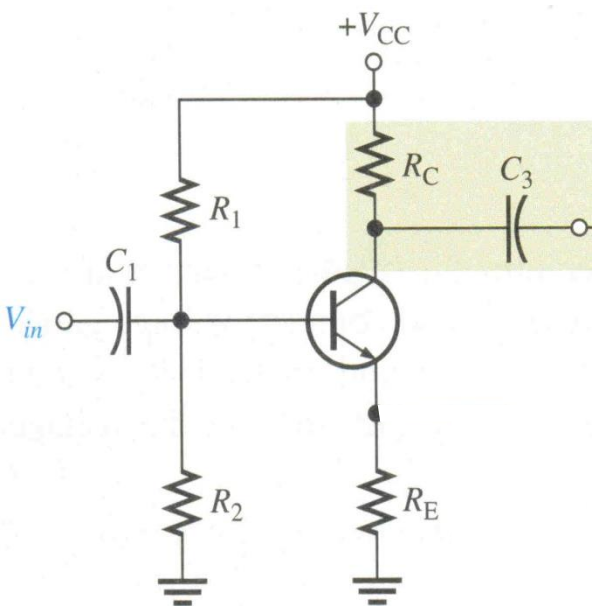


$$R_{in(base)} = \beta_{ac} (r'_e + R_E)$$

$$A_v = \frac{R_C}{r'_e + R_E}$$

Maximum Input Resistance

Minimum Ideal Gain

Maximum Stability

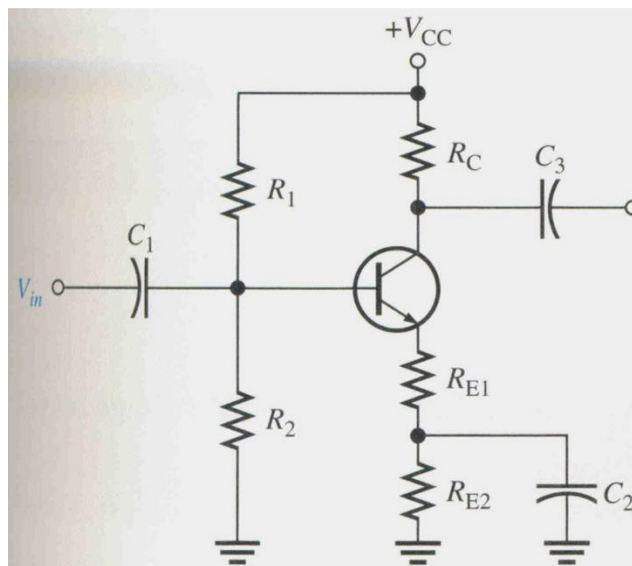


$$R_{in(base)} = \beta_{ac} (r'_e + R_{E1})$$

$$A_v = \frac{R_C}{r'_e + R_{E1}}$$

Moderate Input Resistance

Moderate Ideal Gain

Moderate Stability

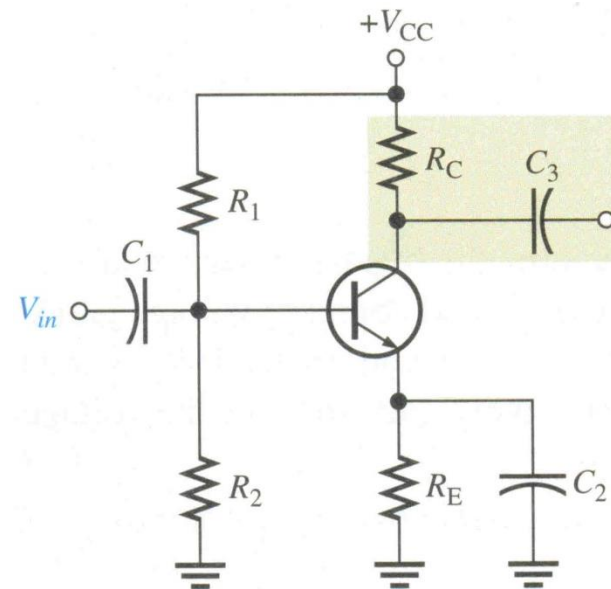

$$R_{in(base)} = \beta_{ac} r'_e$$

$$A_v = \frac{R_C}{r'_e}$$

Minimum Input Resistance

Maximum Ideal Gain


Minimum Stability

Current and Power Gains

$$A_i \equiv \text{ideal current gain} = \frac{I_c}{I_b} = \beta_{ac}$$

$$A'_i \equiv \text{overall current gain} = \frac{I_{out}}{I_s}$$

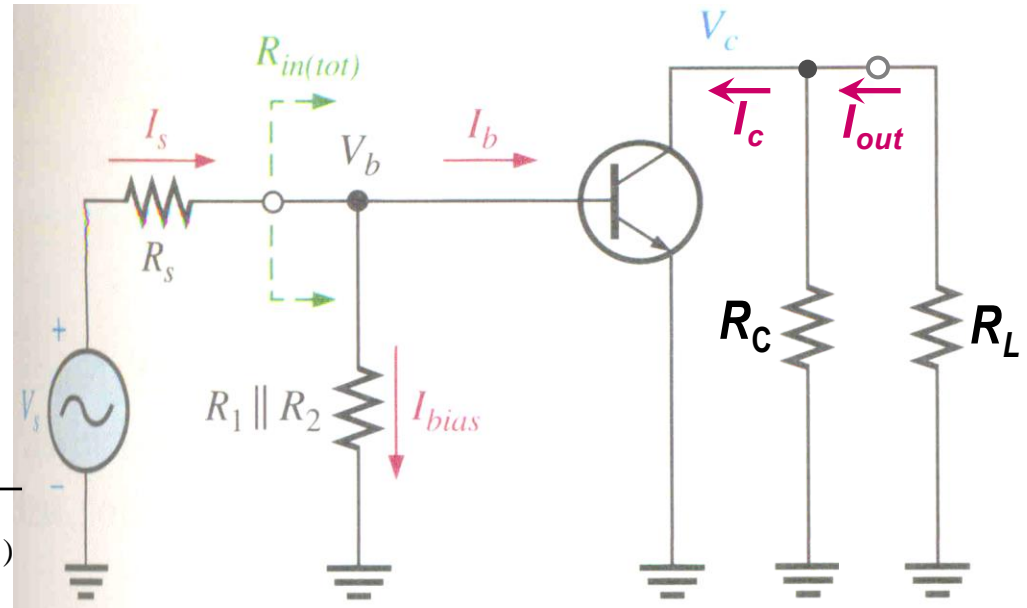where: $I_{out} = \frac{V_c}{R_L}$, $I_s = \frac{V_s}{R_s + R_{in(tot)}}$



$$A'_p \equiv \text{overall power gain} = \frac{\text{amplifier output power}}{\text{amplifier input power}} = \frac{V_c I_{out}}{V_s I_s} = \left(\frac{V_c}{V_s} \right) \left(\frac{I_{out}}{I_s} \right) = A'_v A'_i$$

CE Amplifier Summary

$$R_{in(base)} \equiv \text{input base resistance} = \frac{V_b}{I_b}$$

$$R_{in(tot)} \equiv \text{total input resistance} = \frac{V_{in}}{I_{in}} = \frac{V_b}{I_s}$$

$$R_{out} \equiv \text{output resistance} = \left. \frac{V_{out}}{I_{out}} \right|_{V_s \rightarrow \text{s.c.}}$$

$$A_v \equiv \text{ideal voltage gain} = \frac{V_c}{V_b}$$

$$A'_v \equiv \text{overall voltage gain} = \frac{V_{out}}{V_s} = \frac{V_c}{V_s}$$

$$\text{Attenuation} \equiv \frac{A_v}{A'_v} = \frac{V_s}{V_b} = \frac{R_s + R_{in(tot)}}{R_{in(tot)}} \geq 1$$

$$A_i \equiv \text{ideal current gain} = \frac{I_c}{I_b} \cong \beta_{ac}$$

$$A'_i \equiv \text{overall current gain} = \frac{I_{out}}{I_s}$$

