

Lecture 1

From Sections 1.1, 1.2, 2.1

Solve E1.1, E1.2, E1.3, E1.4, 1.11,
1.15, 1.26, 1.29

E2.1, E2.2, 2.1, 2.4, 2.5, 2.6, 2.8

Some Basic Concepts

* System of Units:

milli (m) = 10^{-3} , micro (μ) = 10^{-6} ,

nano (n) = 10^{-9} , Pico (p) = 10^{-12}

Kilo (K) = 10^3 , Mega (M) = 10^6

Giga (G) = 10^9

example: R = 5.0 M Ω = $5.0 \times 10^6 \Omega$

F = 10 GHz = 10×10^9 Hz

Basic Concepts (Cont'd)


* movement of charges create electric current $i = \frac{dq}{dt}$

* Example: a charge of 0.02 C passes through a cross section in 1.0 msec . The current is


$$i = \frac{dq}{dt} \approx \frac{\Delta q}{\Delta t} = \frac{0.02}{1.0 \times 10^{-3}} = 20\text{ A}$$

Direct and Alternating Signals

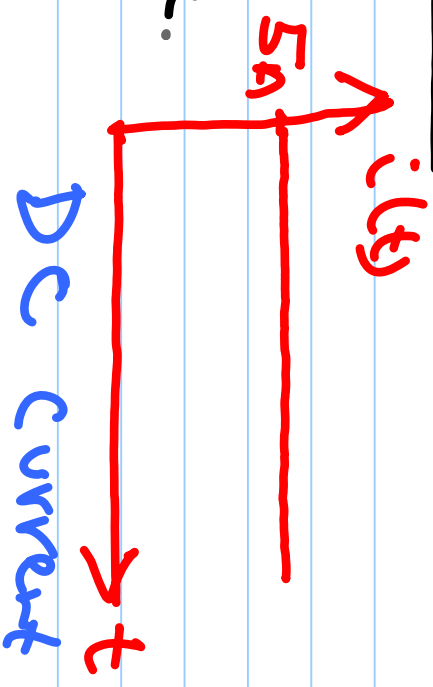
* Direct Current Signals
Do not change with time.



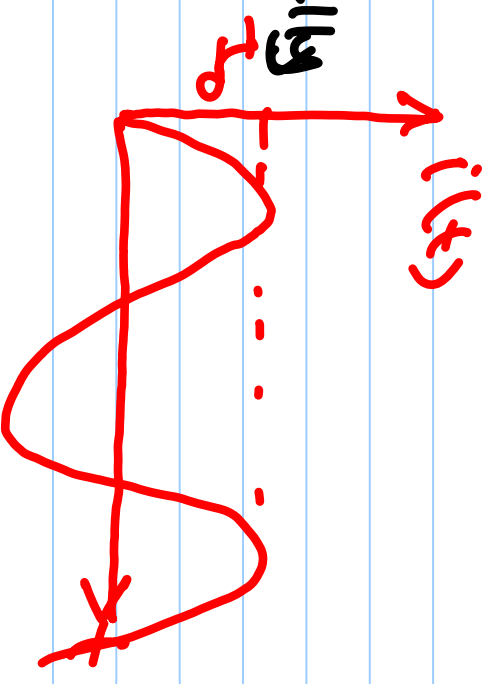* Alternating Current (AC)
Signals change sinusoidally
with time




Example:

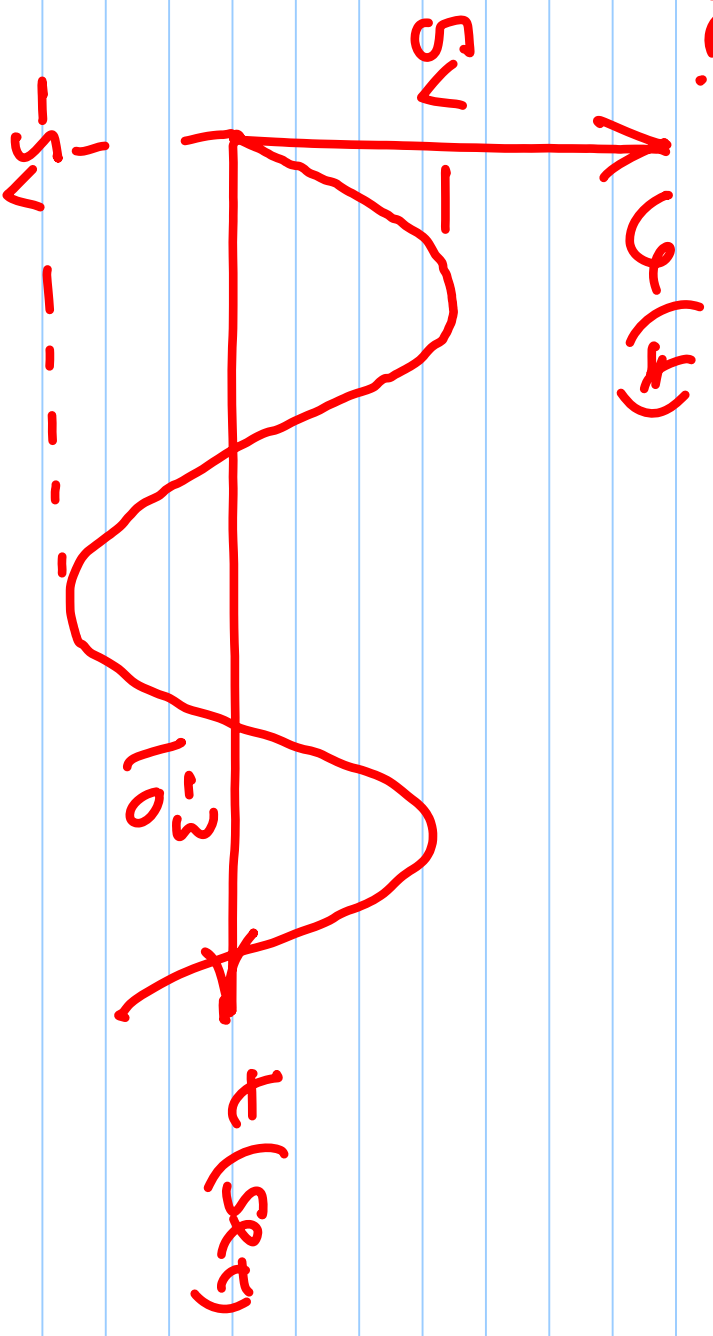

Write the mathematical expression for the shown AC Voltage.


Voltage

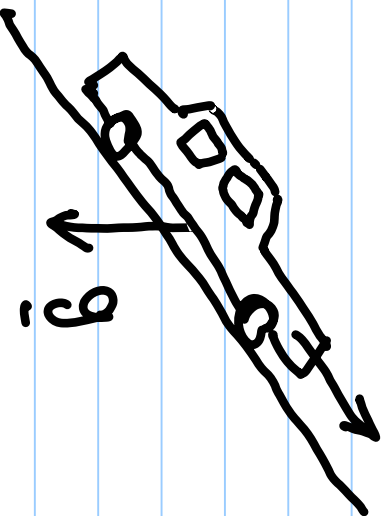

moving **against**

gravity field \rightarrow

energy increases

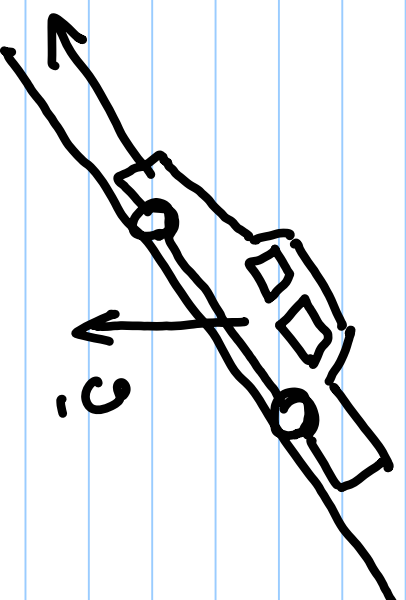


moving **with** gravity

field \rightarrow energy

Decreases

Voltage (Cont'd)

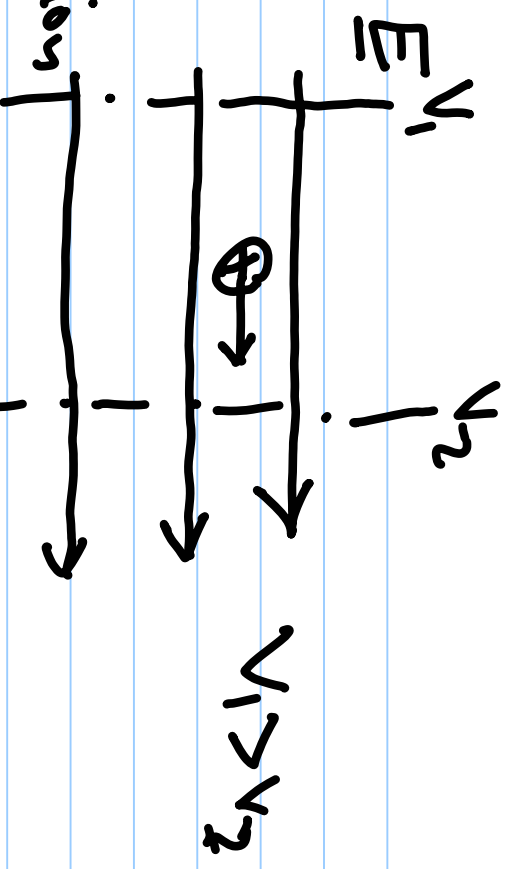


* Electric field moves the charges in its direction


* Moving **against** the electric field **increases** the energy of the charge

* The voltage difference between two points is the work done in moving a unit charge between the two points.

Power Concepts

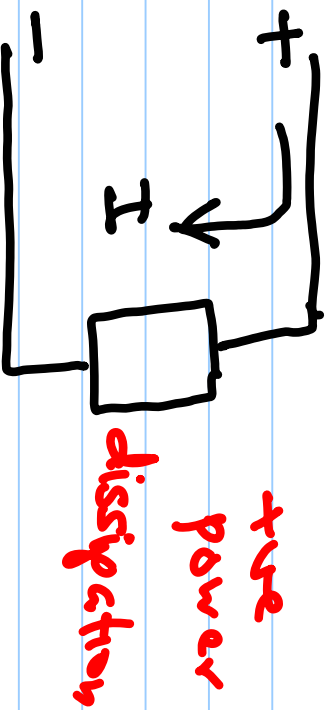


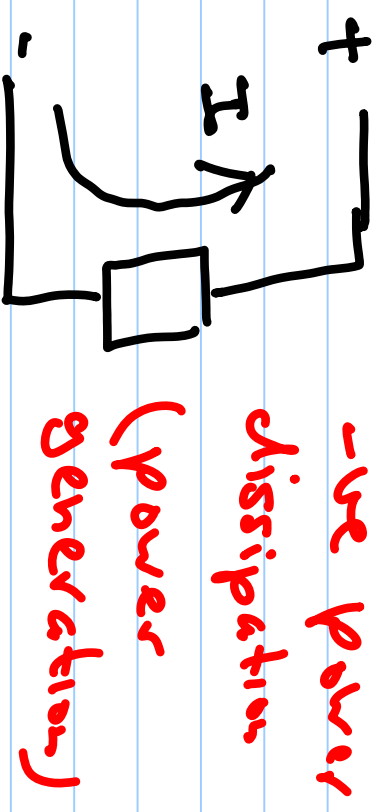
* Positive charges move from high potential to low potential \rightarrow They lose energy




* Positive charges move from low potential to high potential \rightarrow They gain energy

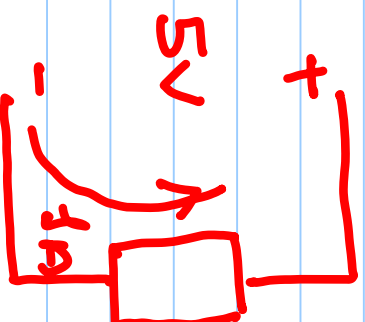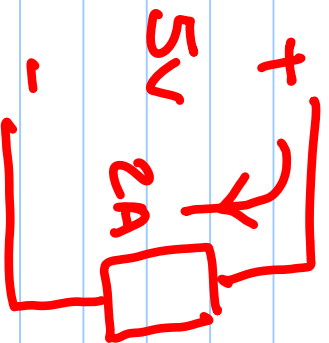Example

Find the dissipated power in the shown two cases



Some Power Concepts

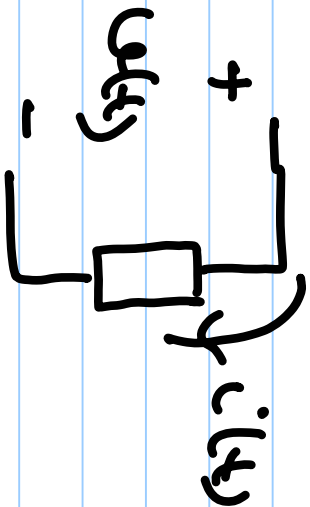* Instantaneous dissipated power + 


$$p(t) = u(t)i(t)$$

* Average Power

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt$$

Where T is a chosen period of time

Example

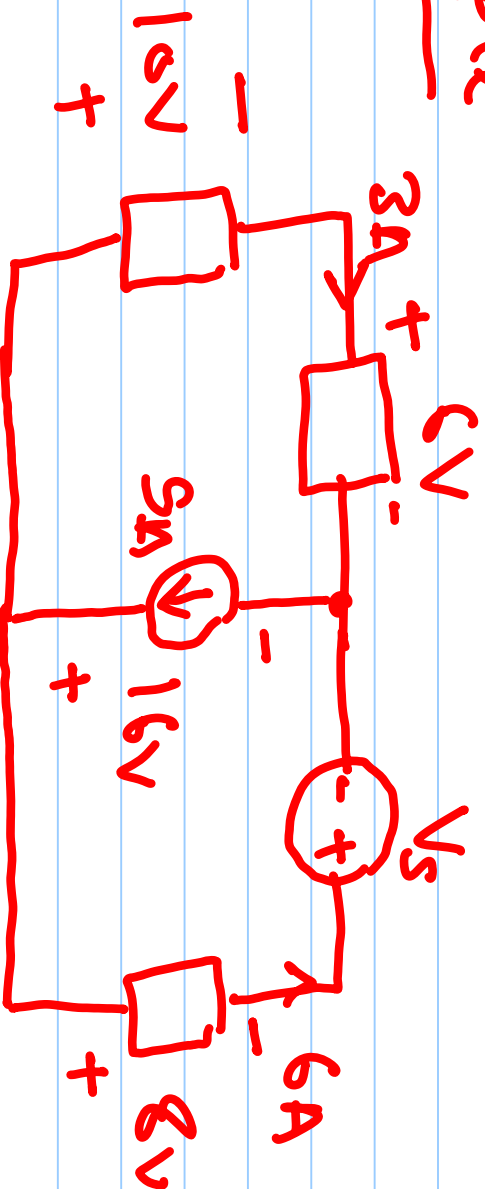

Is the source V_s absorbing or supplying energy and how much?

Ohm's Law

* For a linear resistor



$$V = iR$$

$$\Rightarrow i = \frac{V}{R} = GV$$

where G is conductance


in Siemens
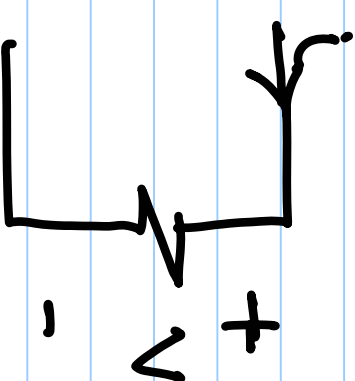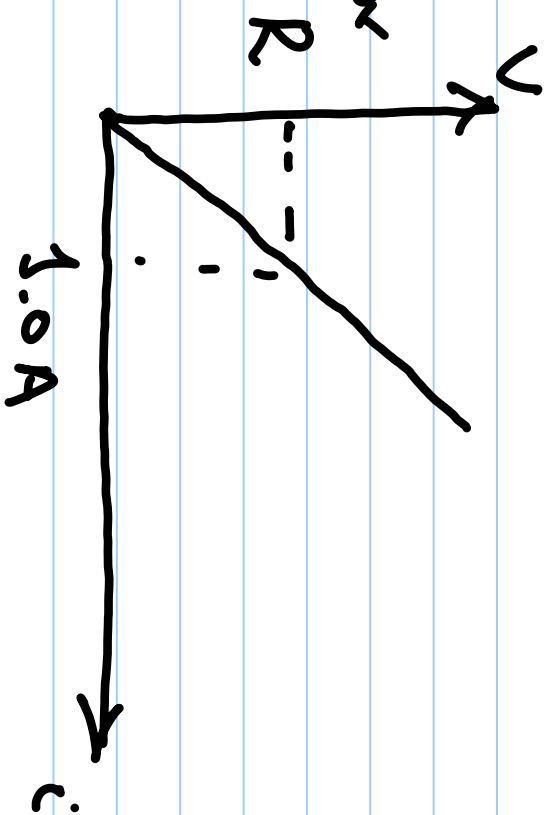
$$* \text{ Power } P = Vi = \frac{V^2}{R} = i^2 R$$




Special Cases

* Open Circuit is an infinite resistance

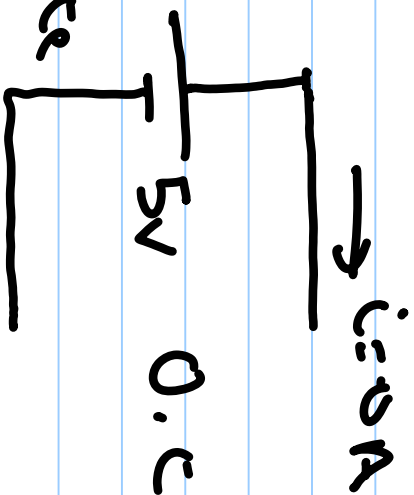


$\Rightarrow i=0$ Regardless of V

* Short Circuit is zero resistance

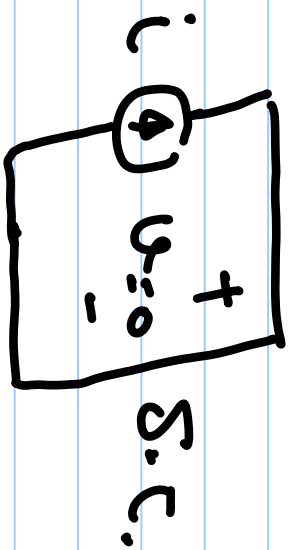


$\Rightarrow V=0$ Regardless of i

Example

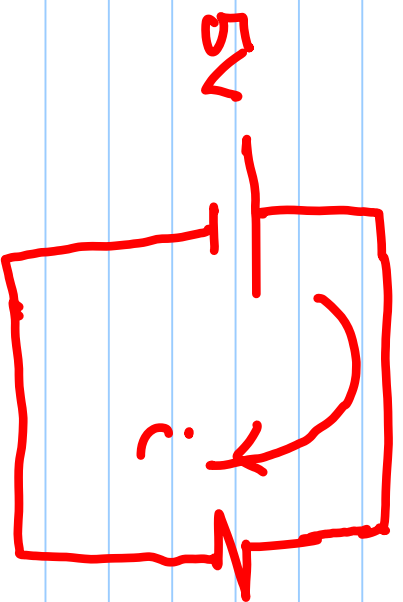

$$10 \sin(120\pi t)$$

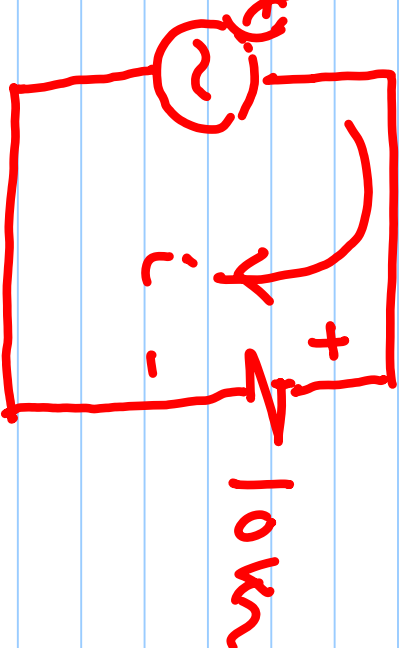

Find the current $i(t)$, the instantaneous power $p(t)$ and the average power P_{av}