

Lecture 3

From Section 2.3 of Textbook

Solve E2.8 and E2.9

Solve 2.24, 2.29, 2.30, 2.32,

2.37

Voltage Divider

* Using Ohm's Law

we want E_0

find V_{R_1} and V_{R_2}

* apply KCL at


node 1 we get

$$i = i_1$$

* Similarly, apply KCL at

node 2 $\Rightarrow i_1 = i_2$

$$i(t) = i_1(t) = i_2(t)$$

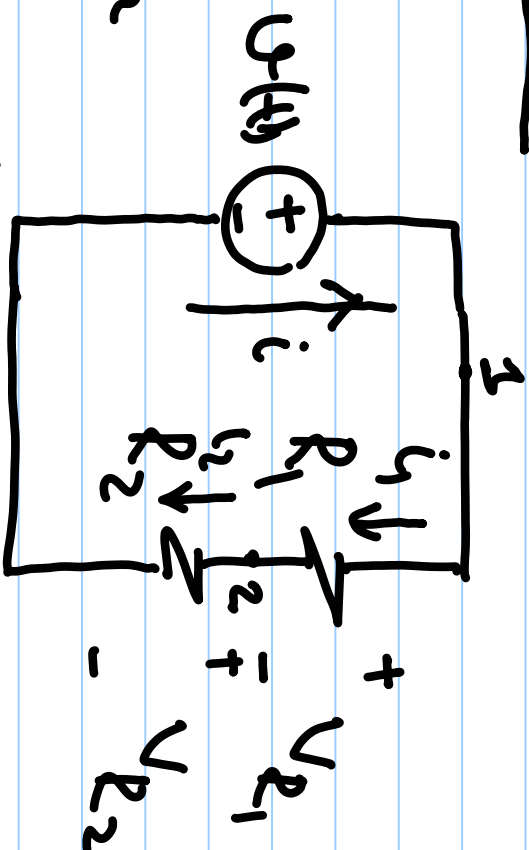

Voltage Divider (Cont'd)

Applying KVL, we get


$$V(t) = V_{R_1} + V_{R_2}$$

$$\Rightarrow V(t) = iR_1 + iR_2$$


$$\Rightarrow i(t) = \frac{V(t)}{R_1 + R_2}$$

$$V_{R_1} = iR_1 = \left(\frac{R_1}{R_1 + R_2} \right) V(t)$$
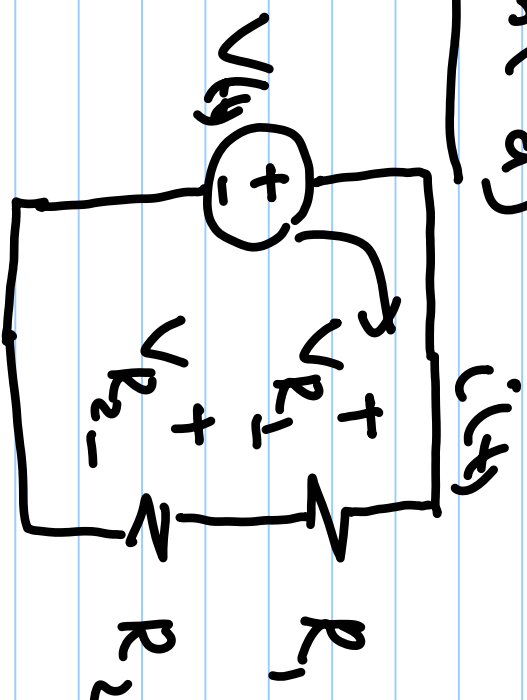
$$\text{Also, } V_{R_2} = iR_2 = \left(\frac{R_2}{R_1 + R_2} \right) V(t)$$




Example

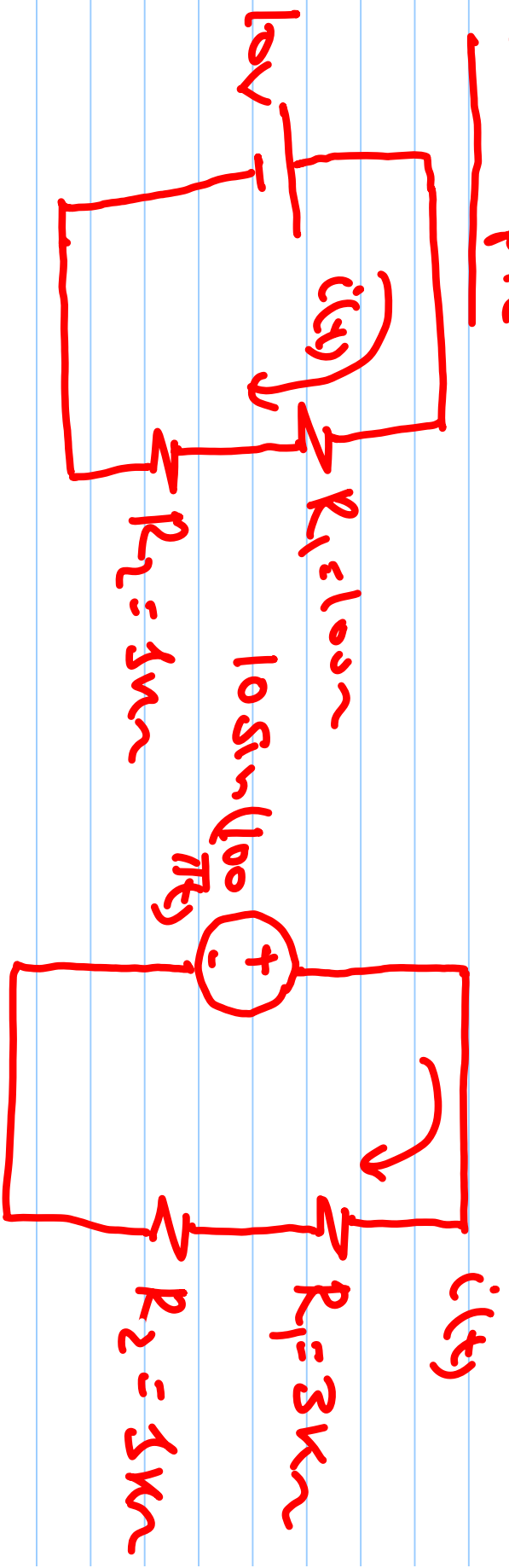

For the shown circuits find $i(t)$, v_{R_1} , v_{R_2} and the power dissipated in R_1

Example

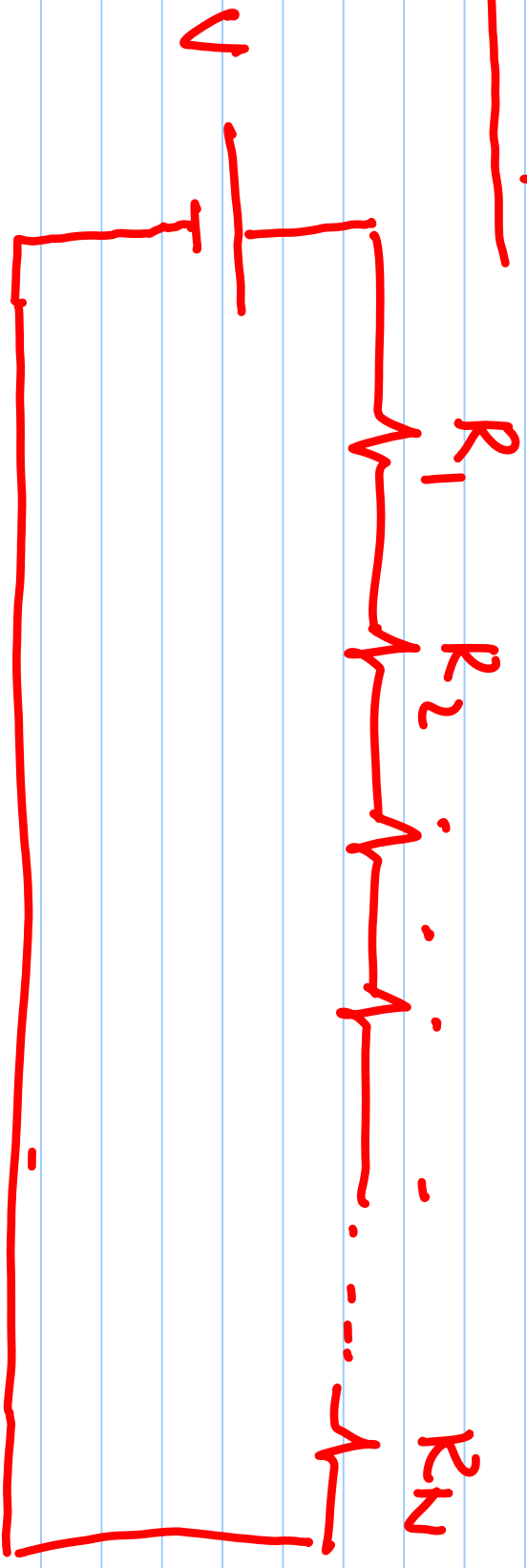

Use Ohm's Law, KCL and KVL

to find the equivalent resistance of the shown series resistances.

Multiple Source Loops

* Assume a current polarization

* Apply KVL

$$V_1(t) + V_3(t)$$

$$= V_{R_1} + V_2(t) + V_{R_2} + V_{R_3}$$


$$\Rightarrow V_1(t) - V_2(t) + V_3(t)$$

$$= i(t) (R_1 + R_2 + R_3)$$

$$V_{eq}$$


$$R_{eq}$$

$$\Rightarrow i(t) = V_{eq} / R_{eq}$$

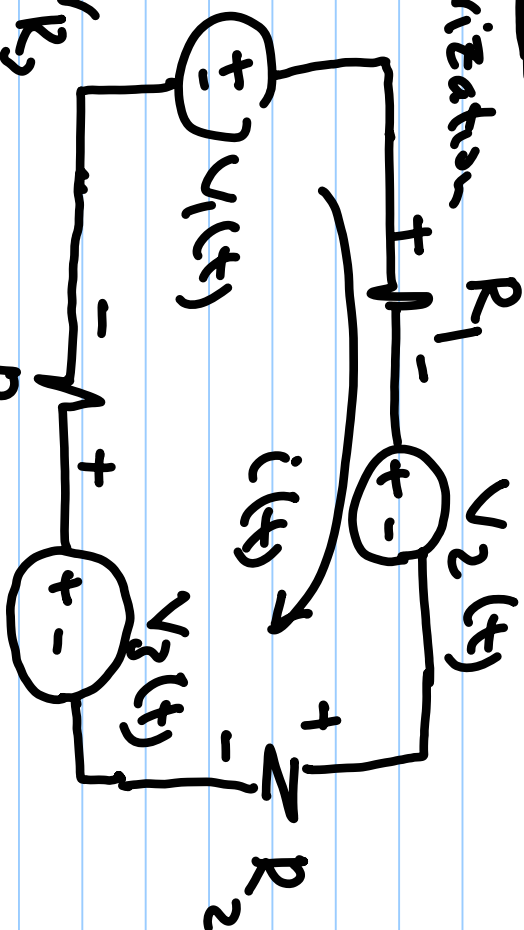


Multiple Source Loops (Cont'd)

* equivalent circuit

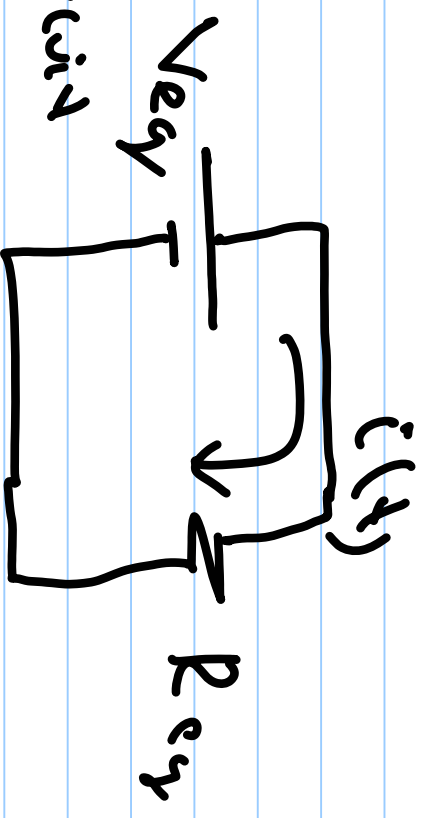

* This equivalent circuit is useful for current calculation

Example

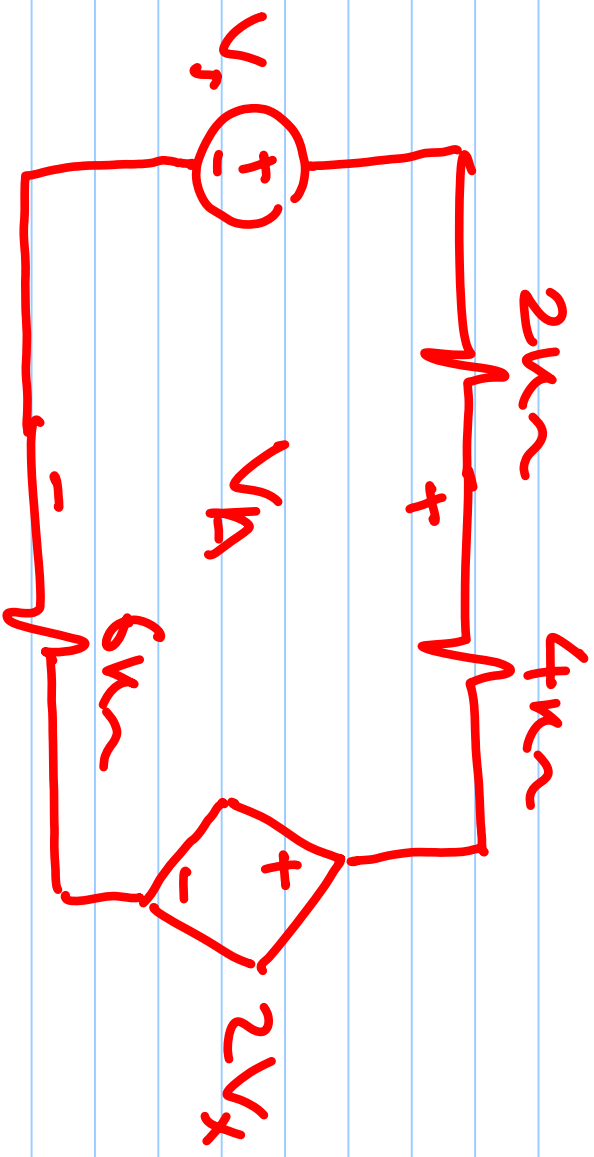

If $V_A = 12V$, find V_s

Example

A Commercial power

Supply is guaranteed

by manufacturer to

deliver $5V \pm 1\%$ across a load

range of $0A$ to $10A$. Find appropriate

values of R and V_0 .

