



Lecture 5

From Section 2.7 and 2.8 of
Textbook. Solve E2.17-E2.18,
2.102, 2.107, 2.108

Wye \leftrightarrow Delta Transformations

- * In some circuits, resistors are not connected in series nor in parallel
- * In this case, the Δ - Y transformation is useful

Δ-Υ Transformation (Cont'd)

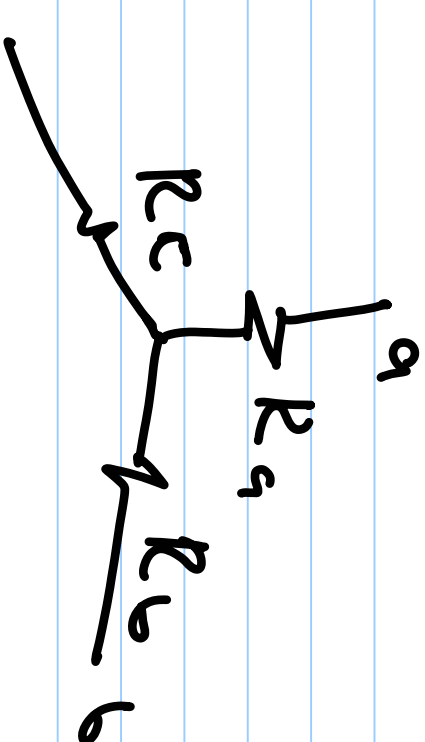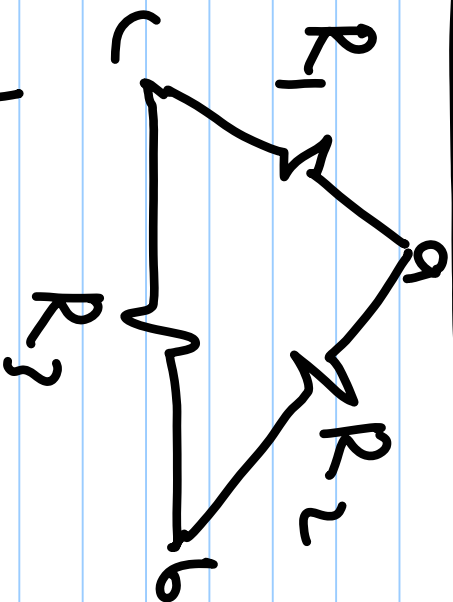

* These two connections are identical if you see the same resistance between

any two terminals (3rd is open)

$$R_a + R_b = R_c \parallel (R_1 + R_3)$$

$$R_a + R_c = R_b \parallel (R_2 + R_3)$$

$$R_b + R_c = R_a \parallel (R_1 + R_2)$$

Δ₂Y Transformation (Cont'd)

* Solving for R_a, R_b ,
and R_c we get

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$


Solving for R_1, R_2 , and
 R_3 , we get

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$


Example

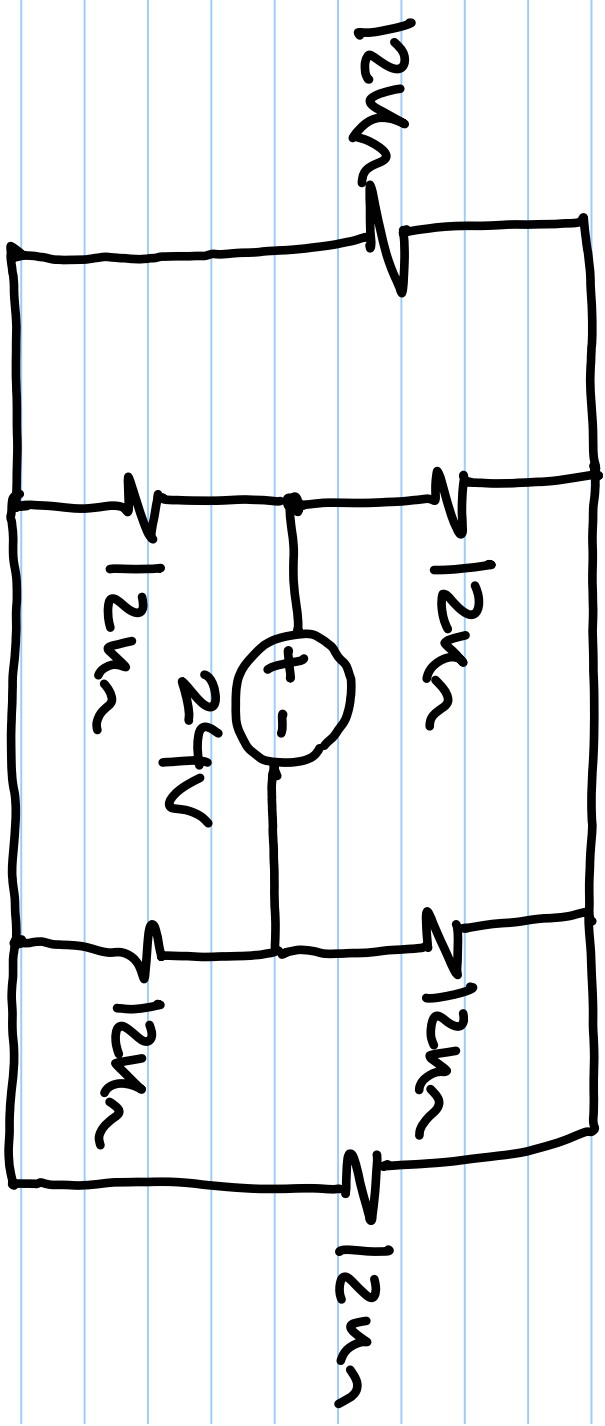


Find the Power Supplied by the 24V source in the shown circuit

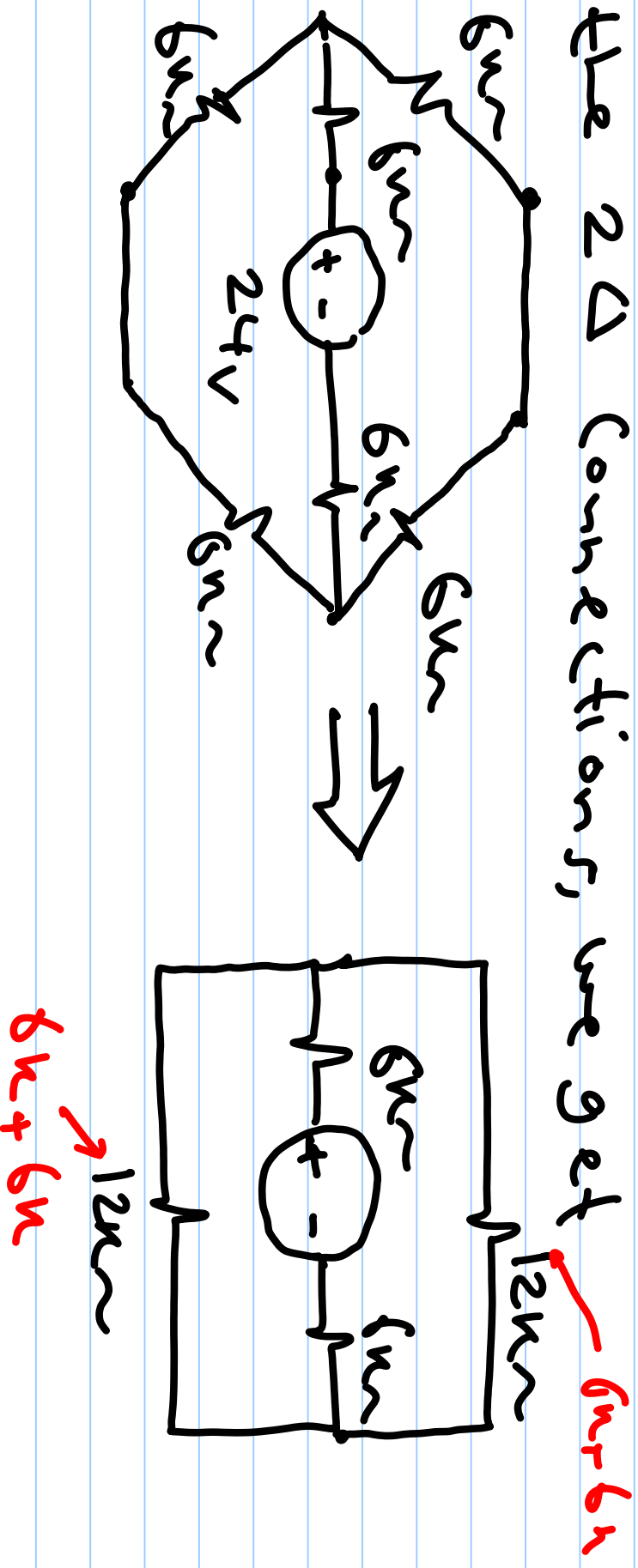Example (Cont'd)

* Using the $\Delta \rightarrow Y$ transformation for the 2Δ connections, we get




Example (Cont'd)

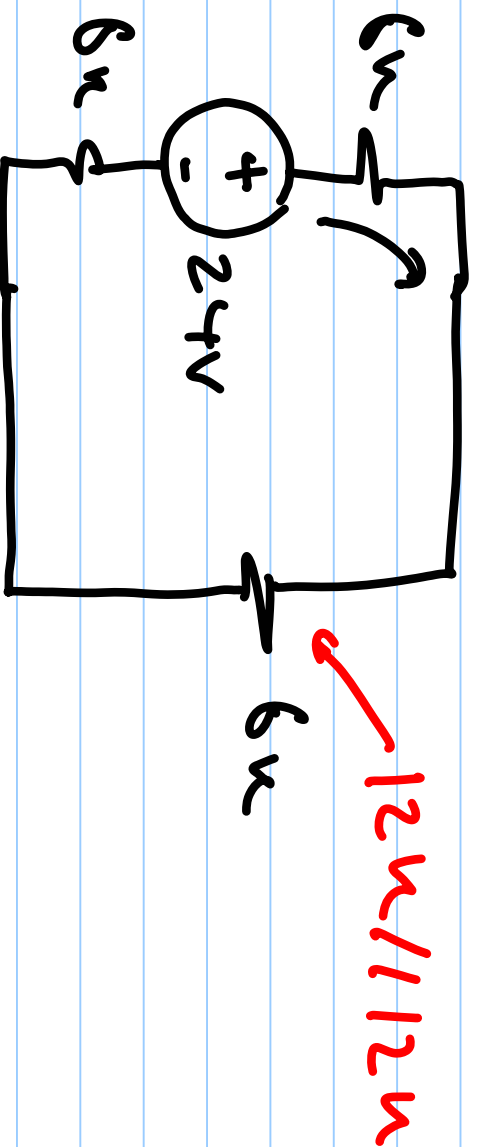

$$i = \frac{24}{18\Omega} = 1.333 \text{ mA}$$

$$P = Vi = 24 * 1.333 = 32 \text{ mW}$$

Example

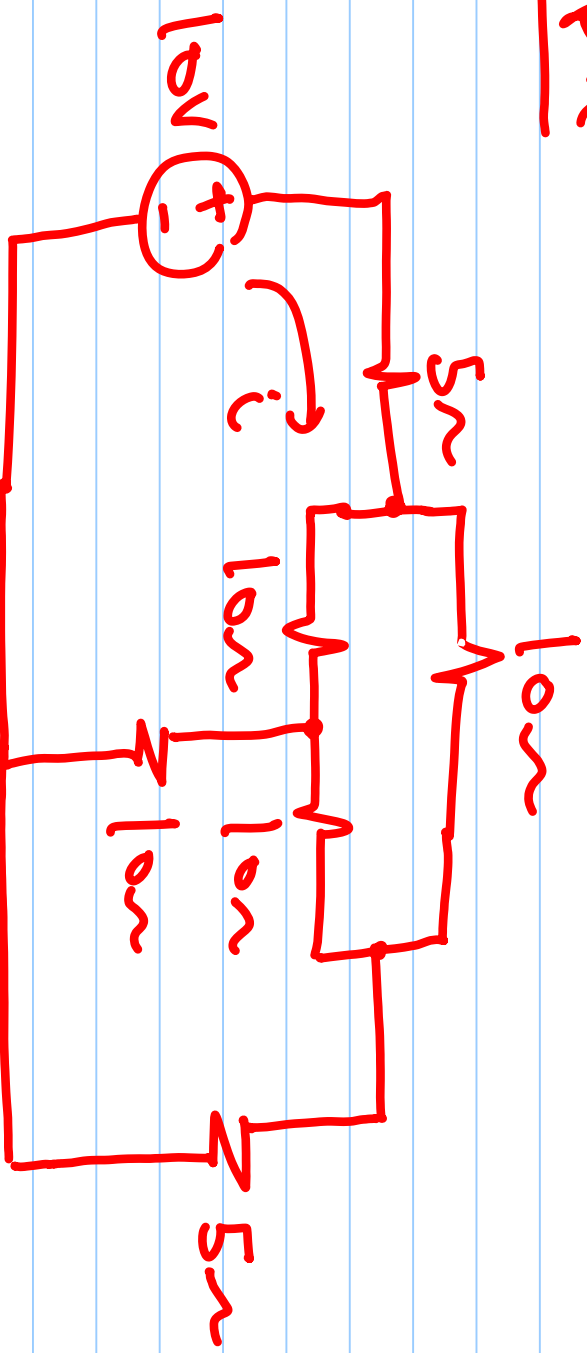

In the shown circuit, find the value of the current i


Dependent Sources

* There are 4 types of dependent


Sources




VCVS

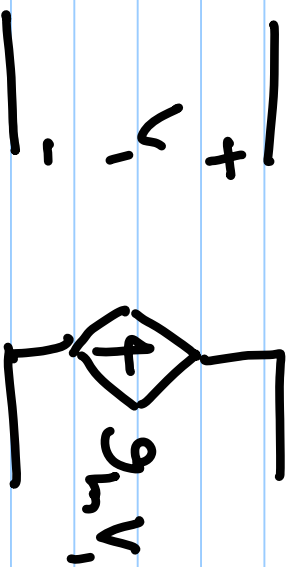

VCCS

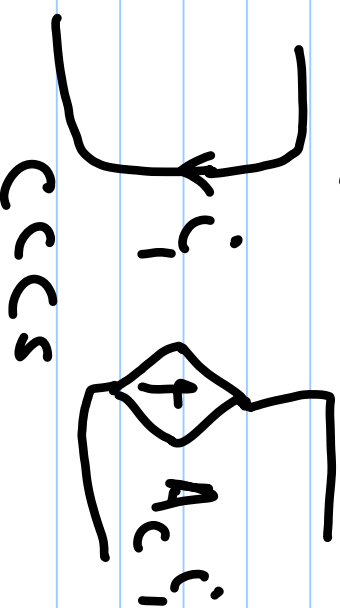

Example

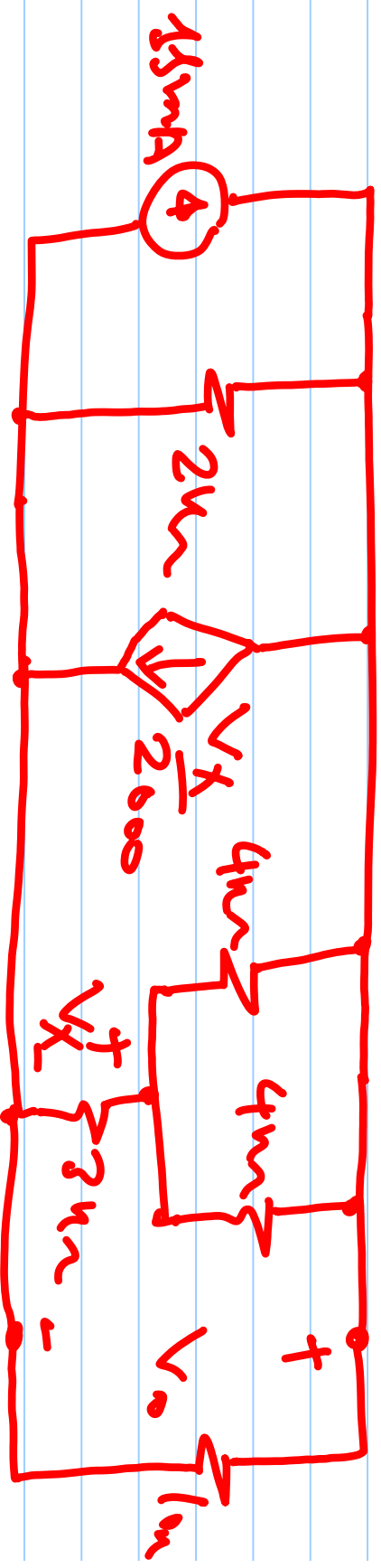

Find the power absorbed by the $3\text{k}\Omega$ resistor in the shown circuit.

