

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

10/8/2007

Lecture 15

From Section 6.1 of Textbook



Solve 6.1, 6.4, 6.6, 6.9,

6.10, 6.14, 6.18

Capacitors


* A Capacitor consists of two conducting electrodes separated by a dielectric

(Insulator)

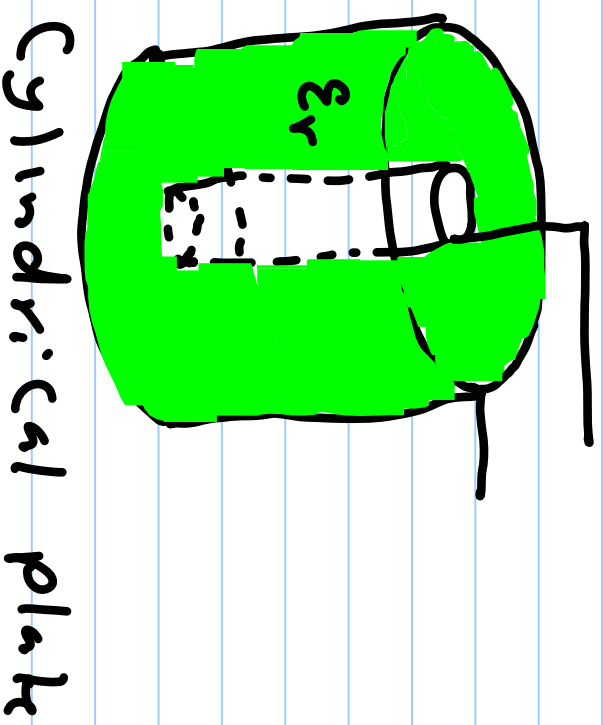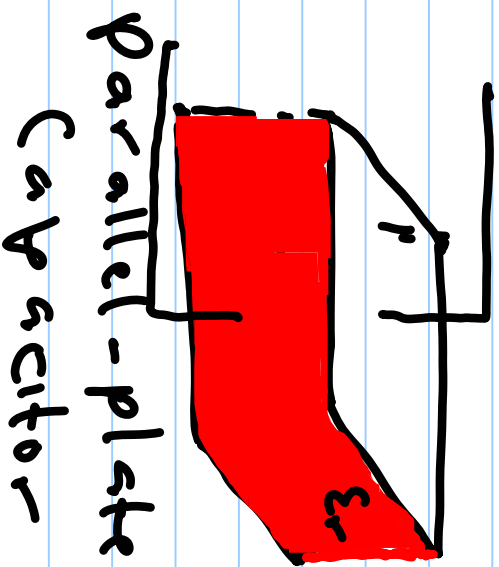

Capacitor (Cont'd)

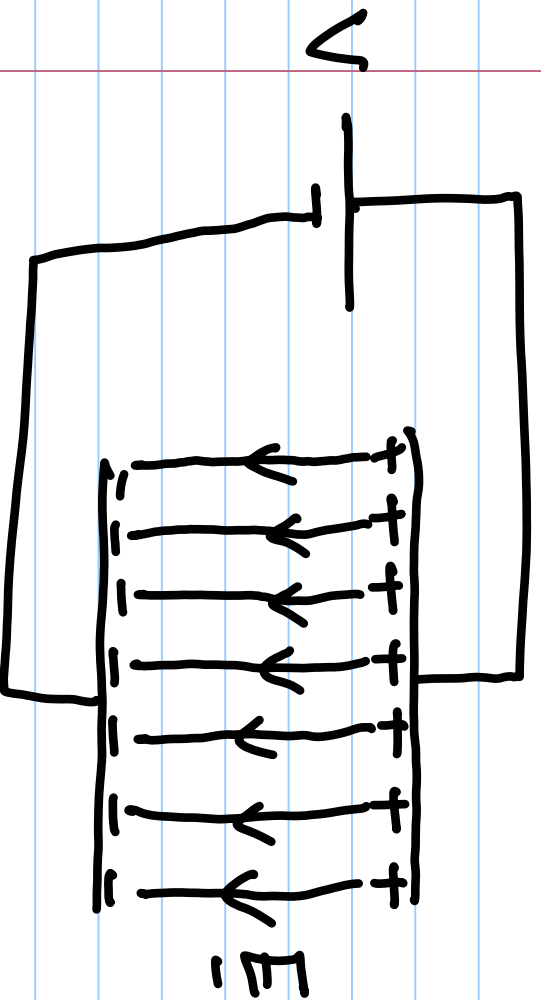* The Capacitor stores energy in the electric field inside the dielectric



The higher the
Voltage of the
Capacitor, the
higher the stored
Charges

Charge and Voltage

- * For a Capacitor we have

$$Q = CV$$

- * The Constant C is the Capacitance of the Capacitor in Farad (C/V)

- * Practical Capacitance Values Range between Pico Farads to thousands of micro Farads.

Example

A Capacitor has an accumulated charge of $600 \mu\text{C}$ with 5 V across it. What is the value of its capacitance?

Voltage and Current

* Current by definition is the time derivative of the charge

$$\Rightarrow i_C = \frac{dQ}{dt} = \frac{d}{dt}(CV) = C \frac{dV}{dt}$$

* The Capacitor Current is proportional to the rate of change of the voltage

Voltage and Current (Cont'd)

$$* i = C \frac{dV}{dt} \Rightarrow i(t) = C \frac{dV(t)}{dt}$$

$$\Rightarrow dV(t) = \frac{1}{C} i(t) dt$$

$$\int_{-\infty}^t dV(\tau) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau \rightarrow Q(t)$$

$$V(-\infty) = 0V$$

$$V(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

Voltage and Current (Cont'd)

$$V(t) = \frac{1}{C} \left[\int_{-\infty}^{t_0} i(\tau) d\tau + \int_{t_0}^t i(\tau) d\tau \right]$$

$Q(t_0)$

$$V(t) = V(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$V(t) = V(t_0) + \frac{Q(t_0 \rightarrow t)}{C}$$

Charge accumulated from t_0 to t

Example

If the voltage

across the

shown source



shown source

capacitor is

$v(t) = 50 \sin(200t)$, find $i(t)$


Example

A voltage pulse given by

$$v(t) = \begin{cases} 0V & t < 0 \\ 2t & 0 \leq t \leq 2 \\ 4e^{-(t-2)} & t \geq 2 \end{cases}$$

is applied to a 10 μ F capacitor, find the current in the capacitor

Example

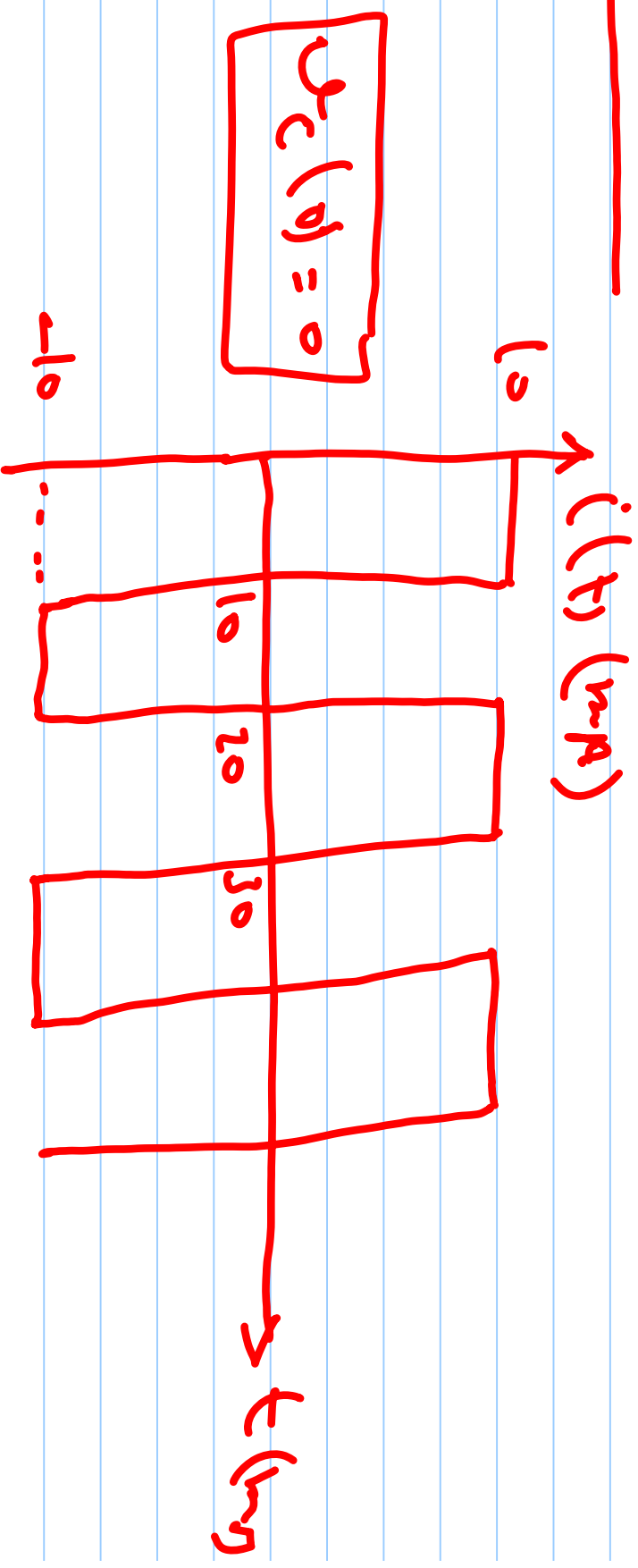

Determine the voltage waveform across a
50mF Capacitor for the shown Current.

Power and Energy

$$* p(t) = v(t) i(t) = v(t) * C \frac{dv(t)}{dt}$$

$$W = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v(\tau) \frac{dv(\tau)}{d\tau} d\tau$$

$$W = C \int_{-\infty}^t v(\tau) dv(\tau) = \frac{C}{2} v^2(\tau) \Big|_{-\infty}^t$$

$$W(t) = \frac{1}{2} C v_c^2(t)$$

Energy stored
in capacitor

Example

* If $C = 50\mu\text{f}$ and $V_C(t) = 100 \sin 200t$,
Determine the energy stored in
the capacitor as a function of
time