

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

10/14/2007


# Lecture 16

From Section 6.2 of Textbook

Solve E6.4, 6.21, 6.23, 6.24, 6.28,  
6.32, 6.35, 6.42
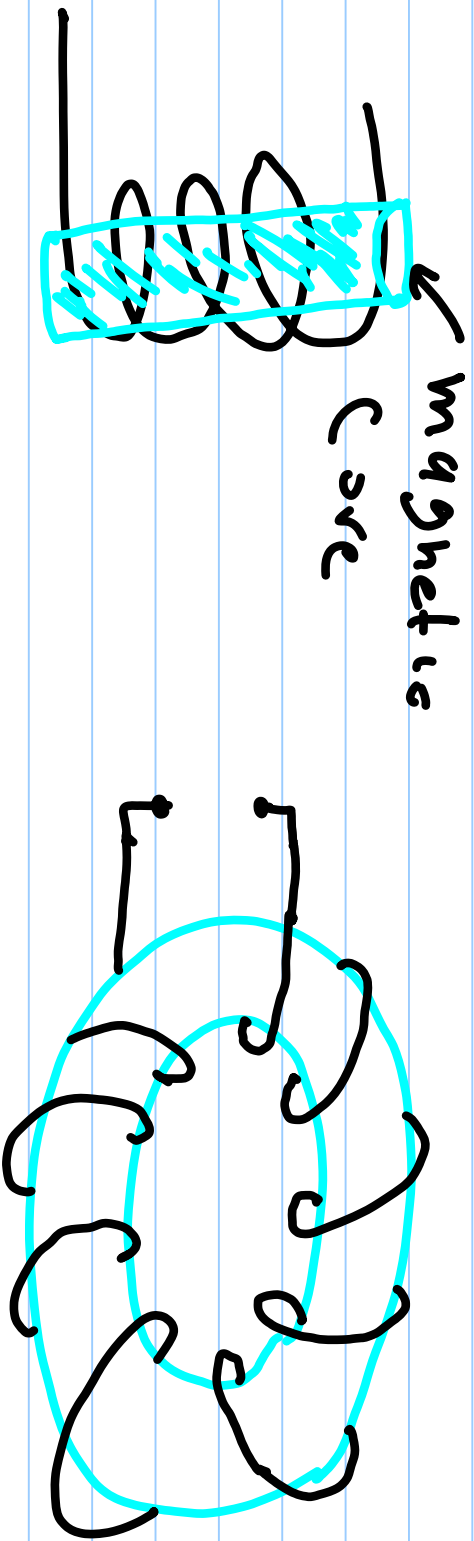
# Inductors

\* An Inductor is a two terminal device that stores energy in its magnetic field.



## Inductors (Cont'd)

\* Current in inductor creates a magnetic flux  $\Phi$ .

\* For a LINEAR inductor  $\Phi = Li$ ,

where  $L$  is the inductance (Henriery)

\* From Faraday's Law, Voltage is equal to rate of change of flux

$$v(t) = \frac{d\Phi}{dt} = L \frac{di}{dt} \quad (\text{Short Circuit is DC})$$

## Voltage and Current


$$v(t) = L \frac{di}{dt}$$

$$\Rightarrow di = \frac{1}{L} v(t) dt$$

$$\int_{-\infty}^t di(\tau) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$i(-\infty) = 0$$
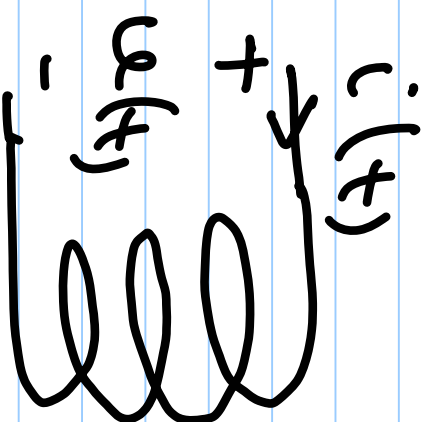
$$\Rightarrow i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$



## Voltage and Current (Cont'd)


\* Assume we have  $i(t_0) = i_0$

$$i(t) = \frac{1}{L} \left( \int_{-\infty}^{t_0} v(\tau) d\tau + \int_{t_0}^t v(\tau) d\tau \right)$$

$$\Rightarrow i(t) = i(t_0) + \underbrace{\int_{t_0}^t v(\tau) d\tau}_{i(t_0 \rightarrow t)}$$

$$i(t_0 \rightarrow t)$$

## Example

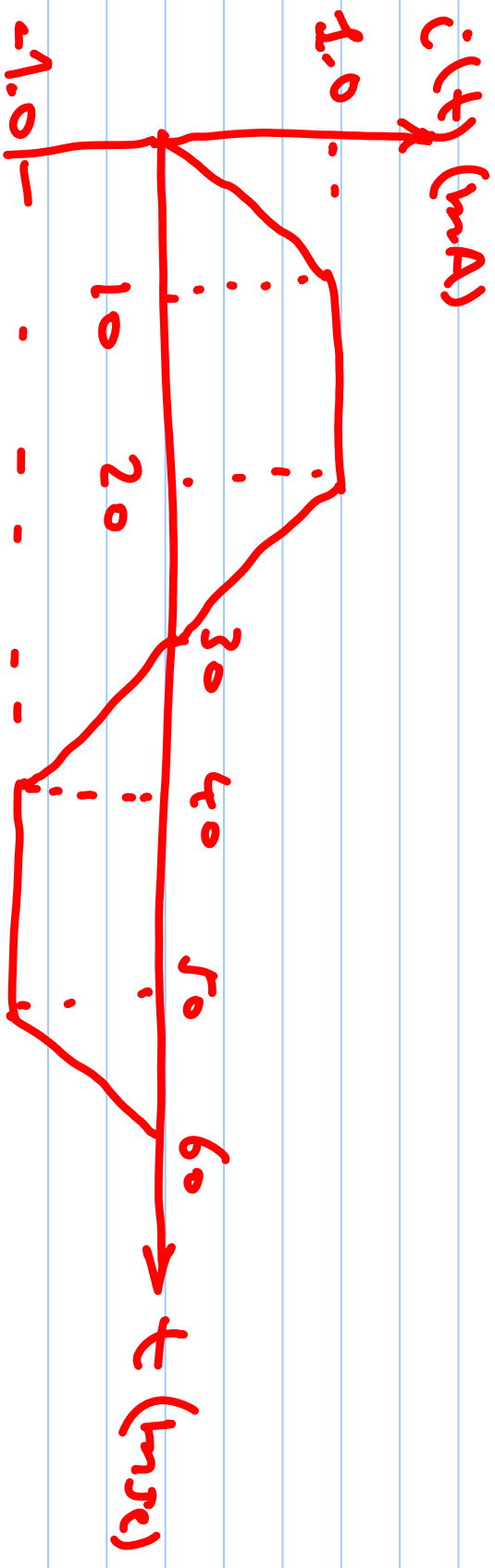

Find the voltage across an Inductor

$L = 0.5 \text{ H}$  for the shown current waveform


## Example

If the current through an inductor

$$i = 0.1 \sin(200\pi t) \text{ A}$$

find the inductor voltage as a function of time


## Example

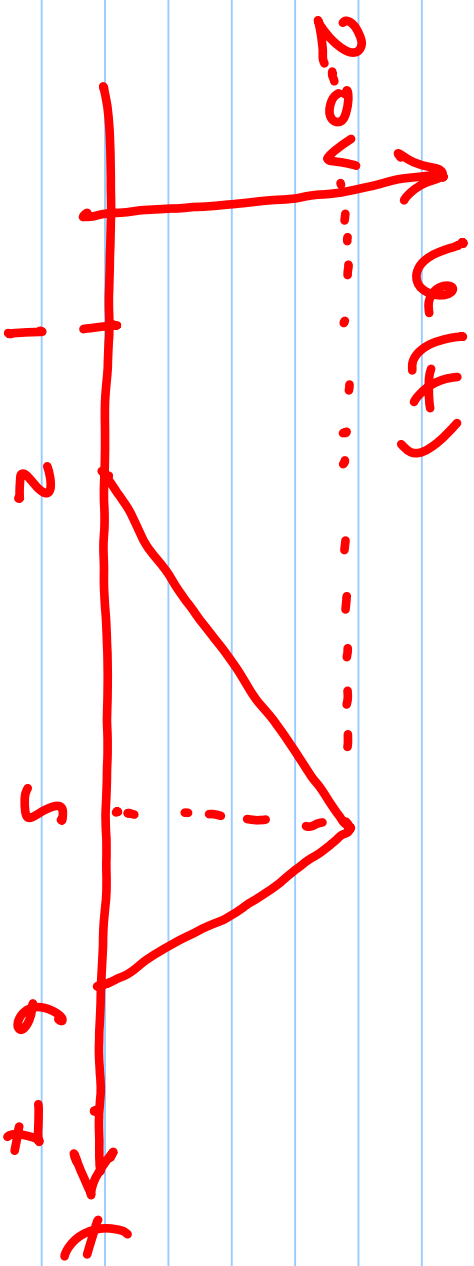

Find the current waveform of an inductor  $L = 2\text{H}$ . Take  $i(0) = 0\text{A}$ .



## Example

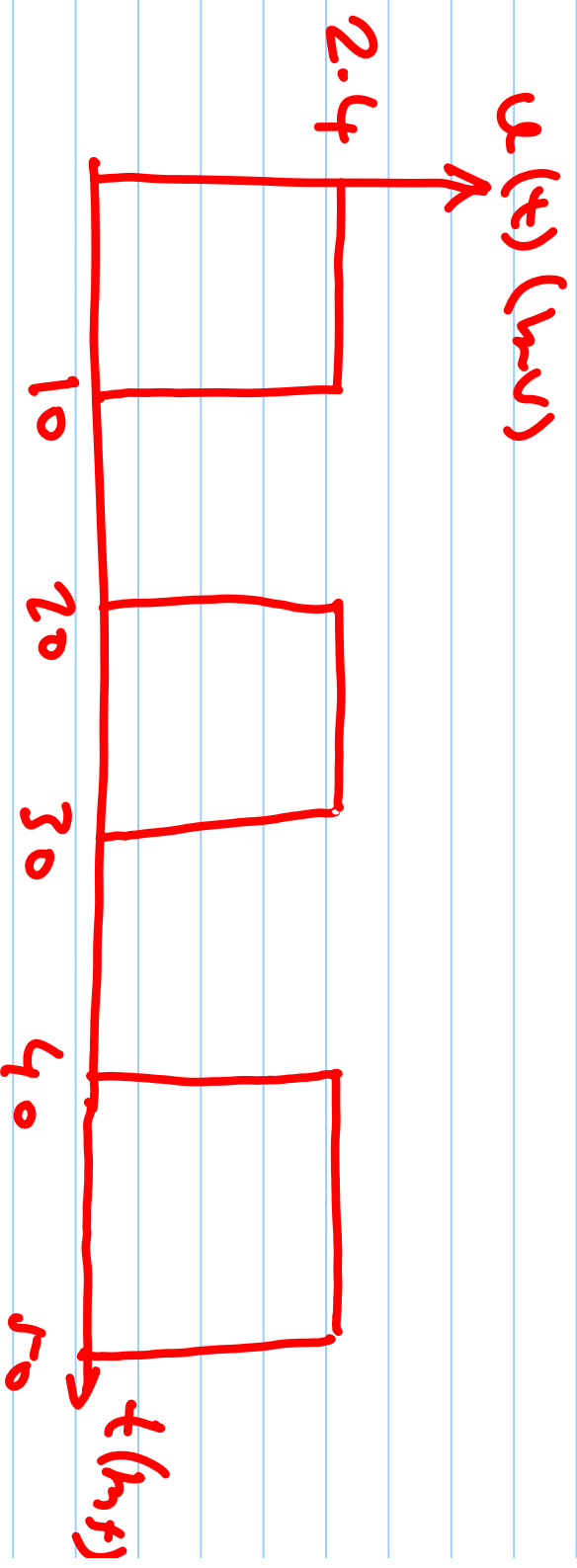

Find the current waveform in an inductor  
 $L = 4\text{H}$  for the shown voltage. Take  $i(t) = 0$   
for  $t < 0$

## Power and Energy

\* Power supplied to the inductor is given by  $p(t) = v(t)i(t)$

$$p(t) = i(t) * L \frac{di(t)}{dt}$$

\* Notice that current must change in a continuous way in an inductor.


## Power and Energy (cont'd)

$$W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t i(\tau) \times L \frac{di(\tau)}{d\tau} d\tau$$

$$W(t) = L \int_{-\infty}^t i(\tau) d\tau$$

$$W(t) = \frac{1}{2} L i^2(t) \quad \text{J}$$

## Example

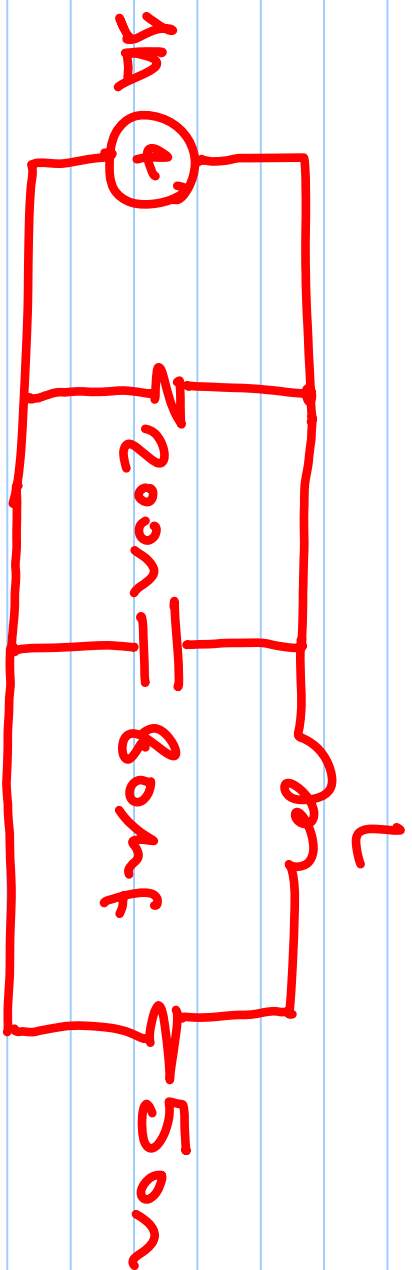

If the total energy stored in this circuit is  $80nJ$ , what is the value of  $L$ ?