

Dr. Mohamed Bakr. EE2C15. 2007

Note Title

10/14/2007

Lecture 17

From Section 6.3 of Textbook

Solve E6.6-E6.8, 6.46, 6.47,

6.50, 6.56, 6.60, 6.64, 6.66, 6.71

Capacitors vs. Inductors



$$i_C = C \frac{dV_C}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

Voltage is continuous

O.C. at DC

$$W_C(t) = \frac{1}{2} C V_C^2(t)$$



$$i_L = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$


$$v_L(t) = L \frac{di_L}{dt}$$

Current is continuous

S.C. at DC

$$W_L(t) = \frac{1}{2} L i_L^2(t)$$

Connections of Inductors

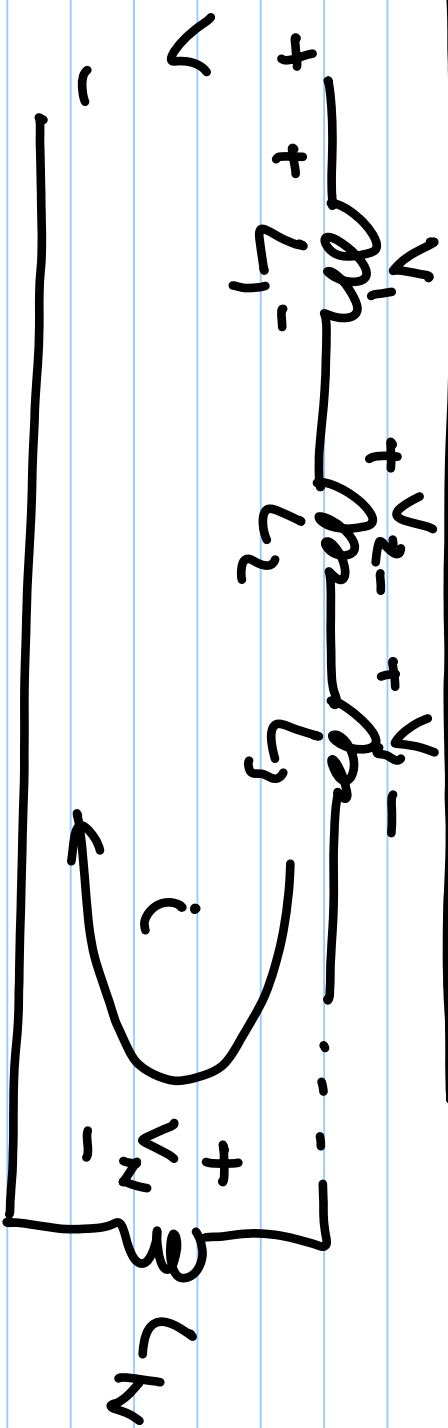


$$V = V_1 + V_2 + \dots + V_N$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$V = (L_1 + L_2 + \dots + L_N) \frac{di}{dt}$$

$$V = L_{eq} \frac{di}{dt} \Rightarrow \text{One equivalent Inductor}$$

Parallel Inductors

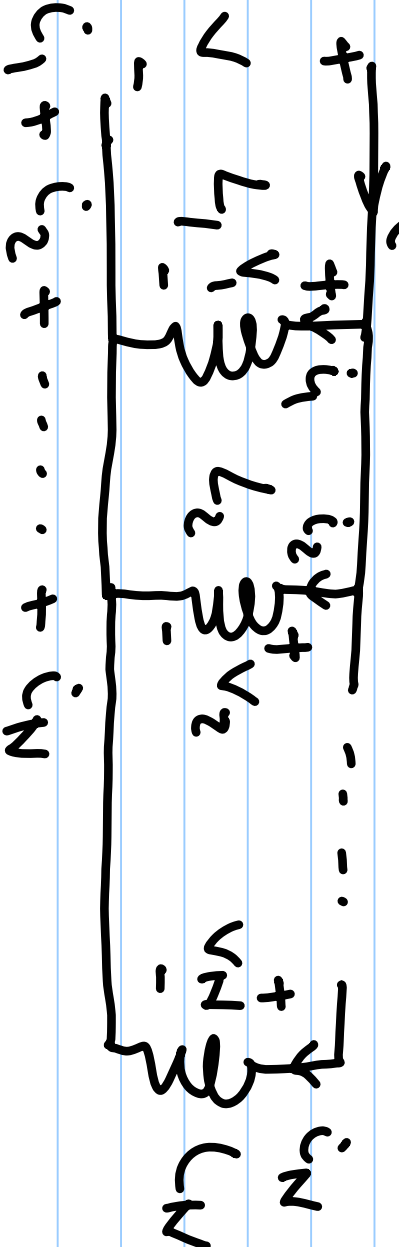


$$i = i_1 + i_2 + \dots + i_N$$

$$i = \frac{1}{L_1} \int_{-\infty}^t v_1(\tau) d\tau + \frac{1}{L_2} \int_{-\infty}^t v_2(\tau) d\tau + \dots + \frac{1}{L_N} \int_{-\infty}^t v_N(\tau) d\tau$$

$$i = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{-\infty}^t v(\tau) d\tau$$

$$i = \frac{1}{L_{eq}} \int_{-\infty}^t v(\tau) d\tau \Rightarrow \text{one equivalent Inductor}$$


Example

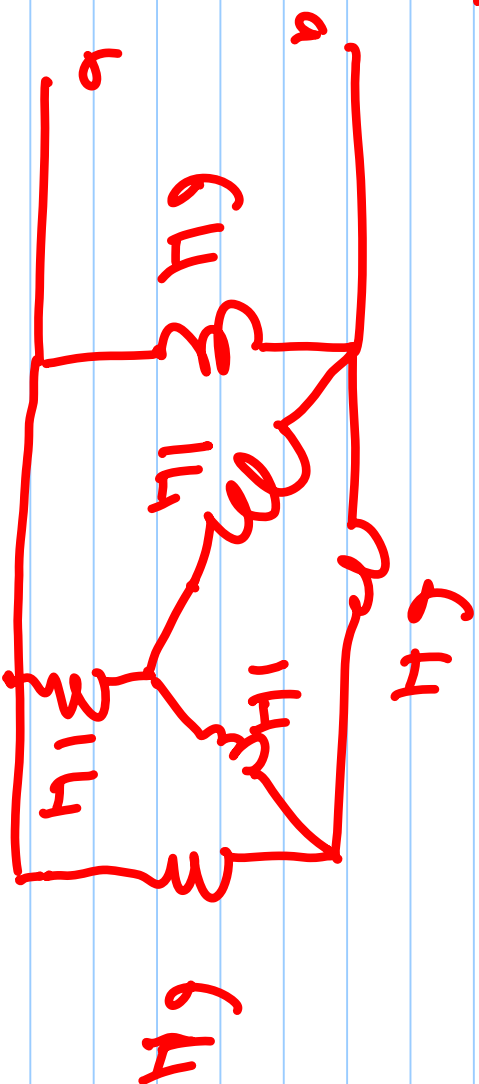


Find the equivalent inductance at the terminals a, b .

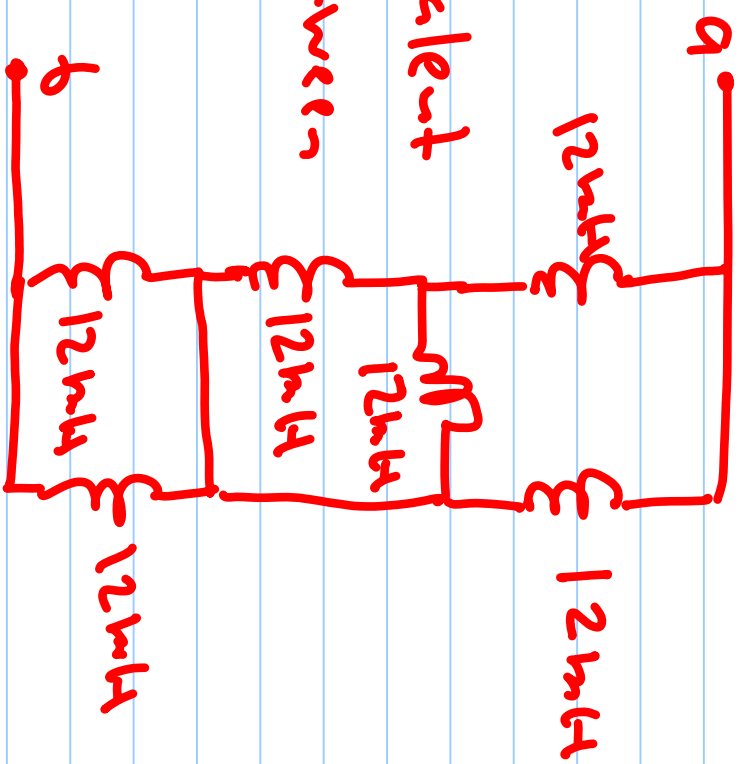Example

Find the equivalent
Inductance between
terminals a and b



Capacitors in Series

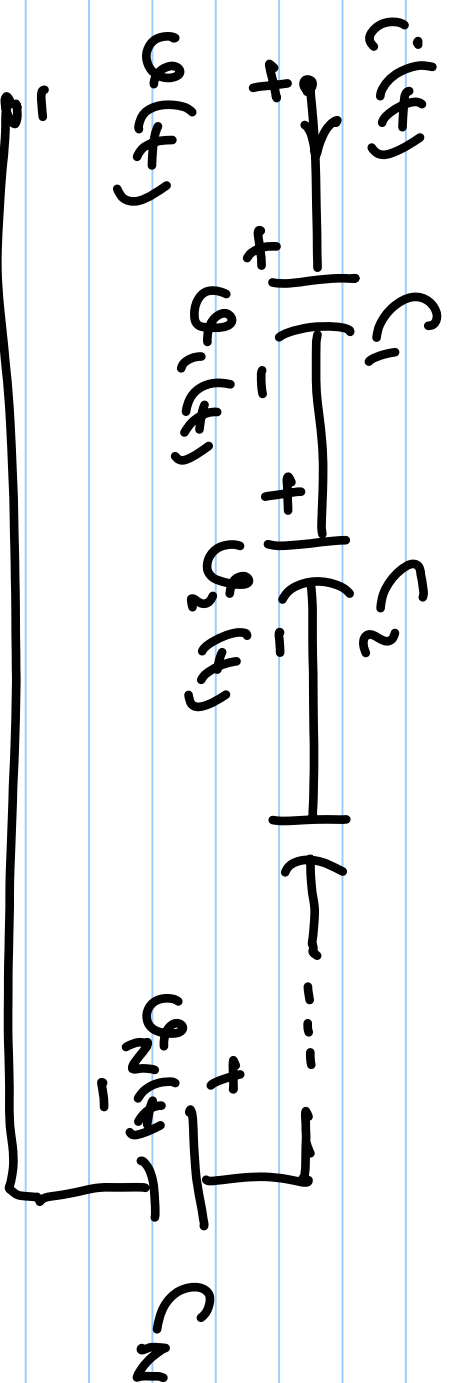


$$U(t) = U_1(t) + U_2(t) + \dots + U_N(t)$$

$$U(t) = \frac{1}{C_1} \int_{-\infty}^t i_1(\tau) d\tau + \dots + \frac{1}{C_N} \int_{-\infty}^t i_N(\tau) d\tau$$

$$U(t) = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{-\infty}^t i(\tau) d\tau$$

$$U(t) = \frac{1}{C_{eq}} \int_{-\infty}^t i(\tau) d\tau \Rightarrow \text{one equivalent capacitor}$$

Capacitors in Parallel

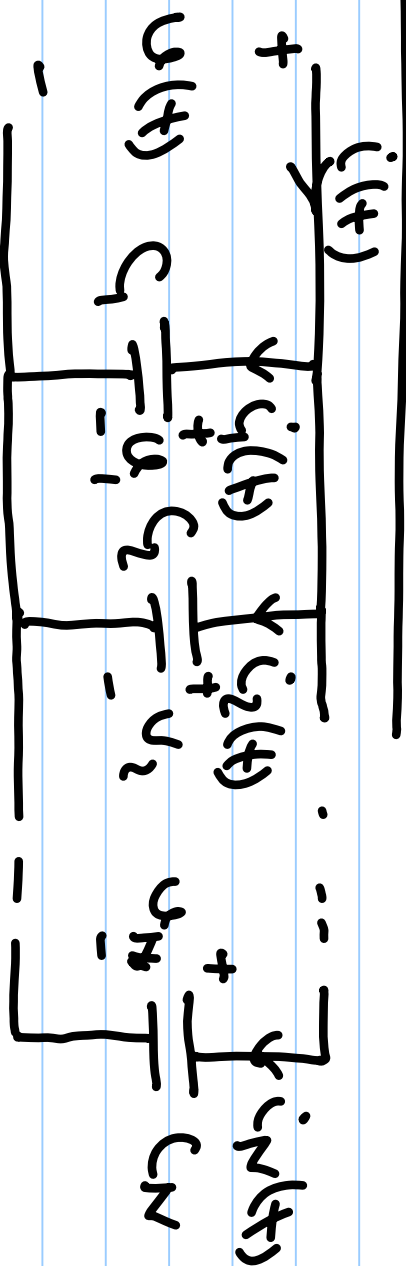

$$i(t) = i_1(t) + i_2(t) + \dots + i_N(t)$$

$$i(t) = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt} + \dots + C_N \frac{dV_N}{dt}$$

$$i(t) = (C_1 + C_2 + \dots + C_N) \frac{dV_N(t)}{dt}$$

$$i(t) = C_{eq} \frac{dV_N(t)}{dt} \rightarrow \text{one equivalent capacitor}$$


Example

Select the

Value of C

Such that

$$C_T = 1\mu\text{f}$$

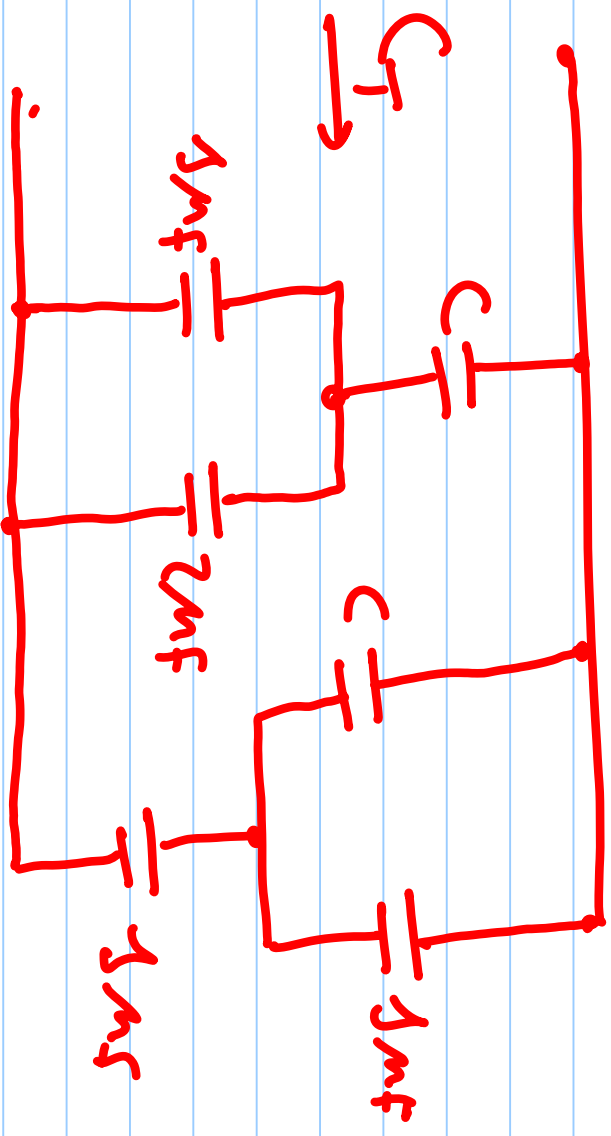

Example

For the circuit

shown determine

$v_1(t)$ and $v_2(t)$

with s open.

If s is closed find C such that the

current $i(t)$ has a peak of $0.25A$.

