

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

10/21/2007

# Lecture 13

From Section 7.2 of Text

Repeat all Examples of Lecture  
18 Using Circuit Approach

## Circuit Approach

\* We know that for a first order circuit, all responses have the

$$\text{form } x(t) = K_1 + K_2 e^{-t/\tau}$$

\* All three unknowns  $K_1$ ,  $K_2$  and

$\tau$  can be found through circuit analysis.

\*  $K_1$  is the steady state response

( $t \rightarrow \infty$ ). Capacitor  $\rightarrow$  D.C.,

Inductor  $\rightarrow$  S.C.

## Circuit Approach

\* Initial value of response  $x(0^+)$

$$\text{is } x(0^+) = K_1 + K_2 \Rightarrow K_2 = x(0) - x(0)$$


\* Building a Thevenin Looking

into the energy storage element

We get  $R_{Th}$ .  $\tau$ , the time constant,


is given by  $\tau = R_{Th}C$  or  $\frac{R_{Th}}{L}$

## Example

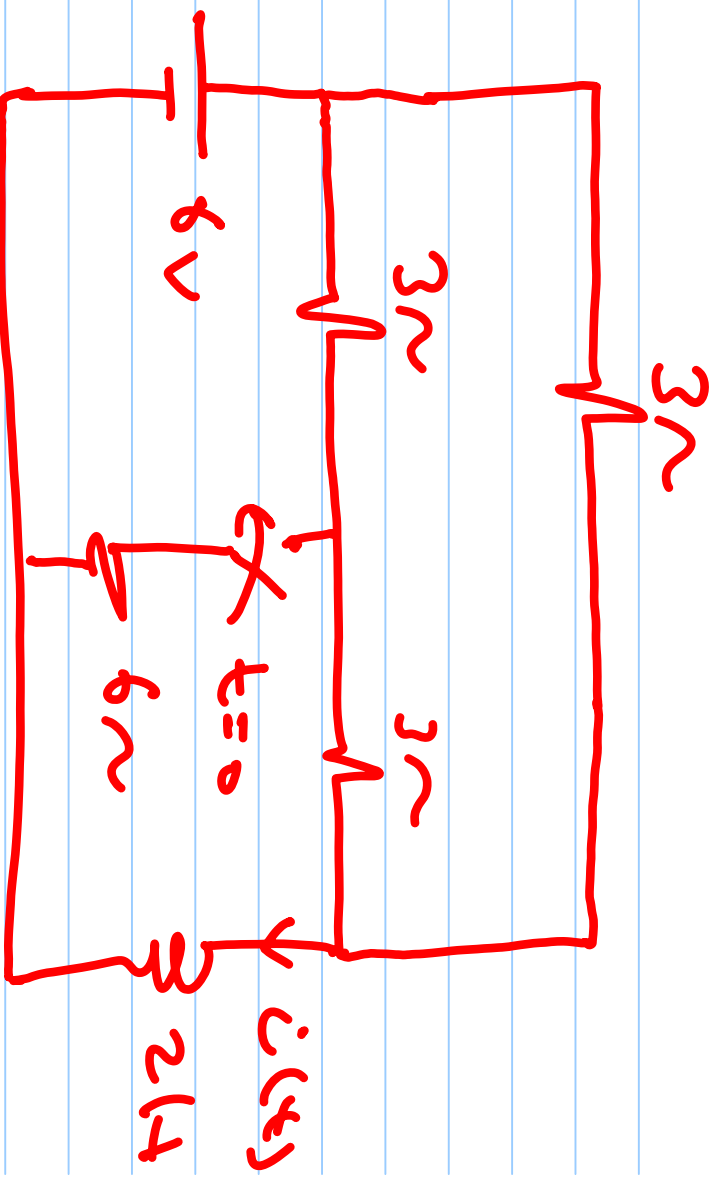


Using Steer to step approach, find  $i(t)$ . Switch is closed at  $t=0$ .

# Example

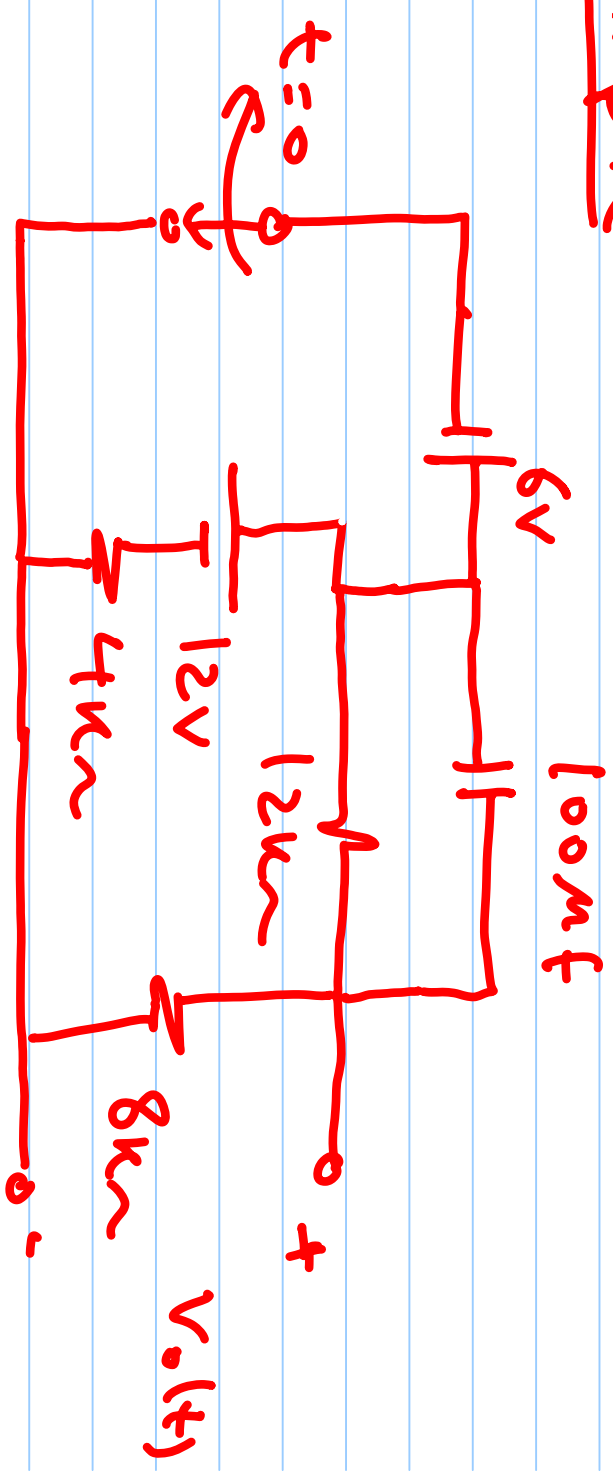

Use circuit approach to find  $V_o(t)$  for  $t > 0$

## Example

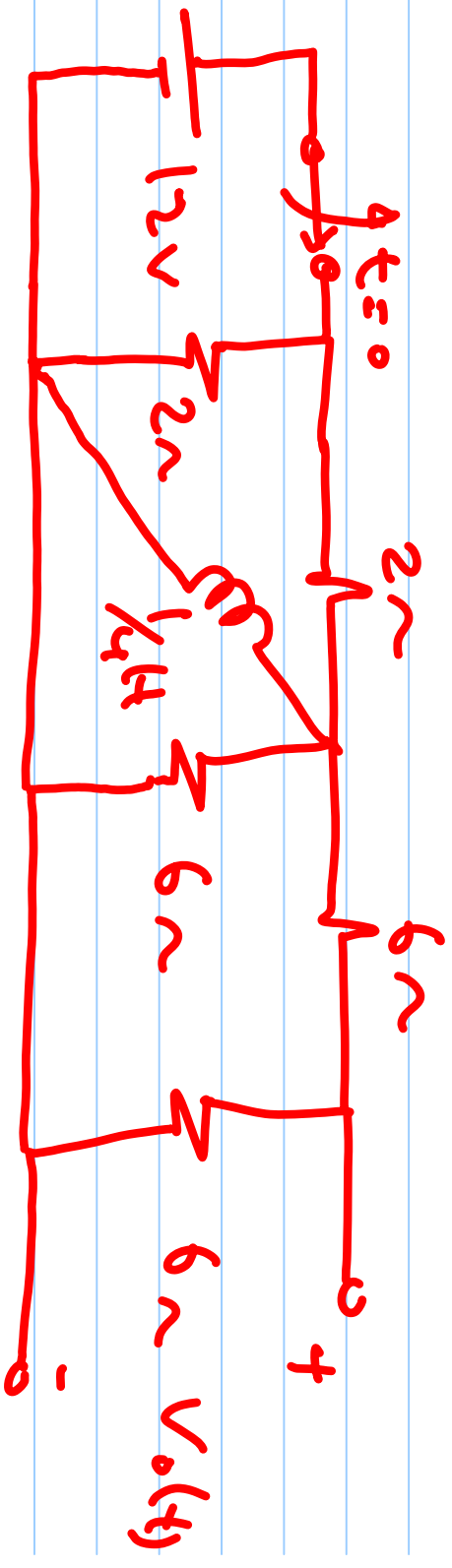

Use the step by step approach.

Find  $V_o(t)$

## Pulse Excitation

\* A pulse can be

considered as the

sum of two

sources



\* The circuit can be

analysed for each -  $-A$  - - - - -

Segment using the response in the


previous segment as the initial

response.

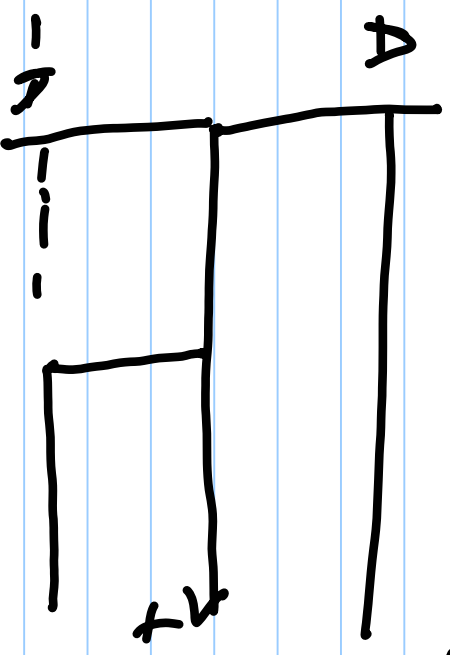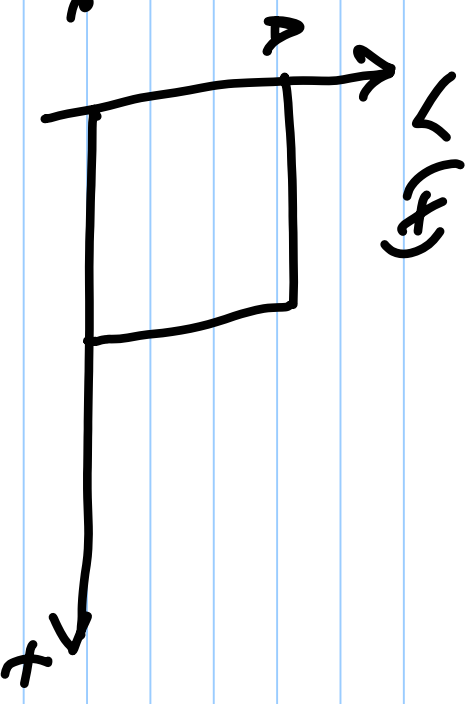
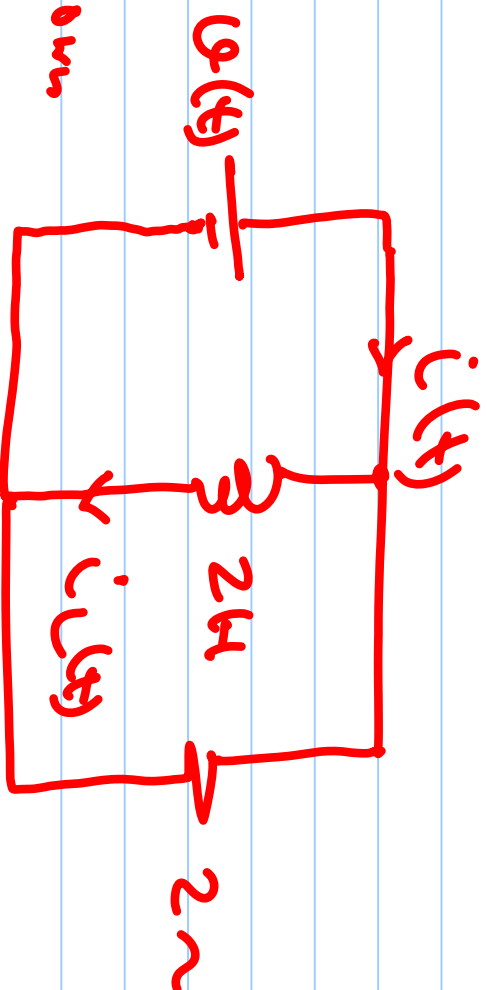
# Example


\* Find  $i(t)$  &  $q(t)$  for the shown



excitation.

How much energy

is stored at  $t = 3\pi$ .

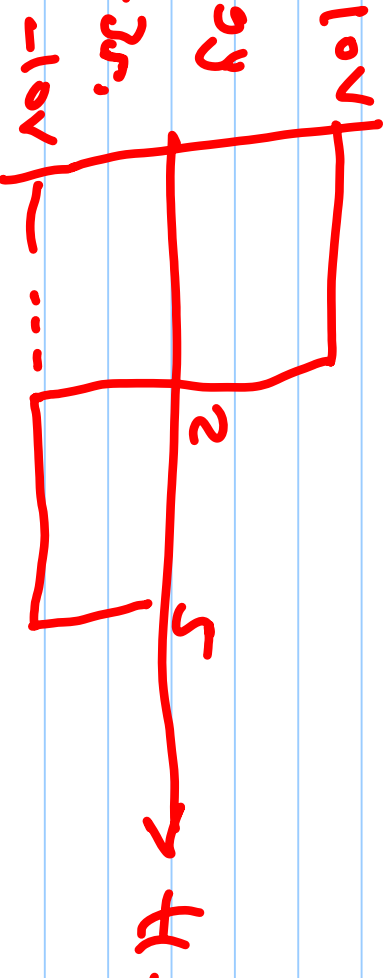

How much power is supplied by the source at  $t = 4\pi$ ?