

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

10/23/2007

## Lecture 20

Form Section 7.3 of Textbook

Solve E7.7 - E7.11, 7.75, 7.80,

7.83, 7.87, 7.90, 7.92

## Second order Circuit

\* A Second order Circuit has 2 energy storage elements

\* IEs (responsible current or voltage) are represented by a 2nd order differential equation

\* This circuits include LC series resonance circuits and parallel resonance circuits.

## Mathematical Background

The D.E. 
$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2 x(t) = f(t)$$

For two solutions, the homogeneous solution and the particular integral solution

$$x(t) = x_h(t) + x_{p.i.}(t)$$

## Mathematical Background (Cont'd)

\* The homogeneous solution  $x_h(t)$  is a solution of the system

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx}{dt} + a_2 x(t) = 0$$

\* Rewriting the D.E.

$$\frac{d^2x(t)}{dt^2} + 2\zeta\omega_0 \frac{dx(t)}{dt} + \omega_0^2 x(t) = 0$$

\* This D.E. has a solution of the form

## Homogeneous Solution

$$* x(t) = K e^{st}$$

Substituting into the D.E, we get

$$K s^2 e^{st} + 2K(\omega_0 s e^{st} + \omega_0^2 K e^{st}) = 0$$

$$\rightarrow s^2 + 2\beta \omega_0 s + \omega_0^2 = 0$$

↳ The characteristic equation

\* The natural frequencies are

$$s_1 = -\beta \omega_0 + \omega_0 \sqrt{\beta^2 - 1} \quad \text{and} \quad s_2 = -\beta \omega_0 - \omega_0 \sqrt{\beta^2 - 1}$$

## Homogenous Solution (Cont'd)

\* Overdamped Case (IFT1)

$x_n(t) = K_1 e^{s_{1t}} + K_2 e^{s_{2t}}$ ,  $s_1 \neq s_2$  and  
both are real

\* Critically damped Case FE1

$x_n(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$  ( $s_1 = s_2$ ) and  
both are real

## Homogeneous Solution

\* Underdamped Case  $\zeta < 1$

⇒ Roots are Complex

$$S_1 = -\zeta\omega_0 + j\omega_0\sqrt{1-\zeta^2} = -\sigma + j\omega_d$$

$$S_2 = -\zeta\omega_0 - j\omega_0\sqrt{1-\zeta^2} = -\sigma - j\omega_d$$

$$\Rightarrow x_h(t) = e^{-\sigma t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

## The P.I Case

- \* The Particular Integral Solution is a solution to  $\frac{d^2x}{dt^2} + a_1 \frac{dx}{dt} + a_2 x(t) = f(t)$
- \* For the case  $f(t) = A$ , we have


$$x_{p.i}(t) = \frac{A}{a_2}$$

- \* It follows that

$$x(t) = x_h(t) + x_{p.i}(t)$$




## Example

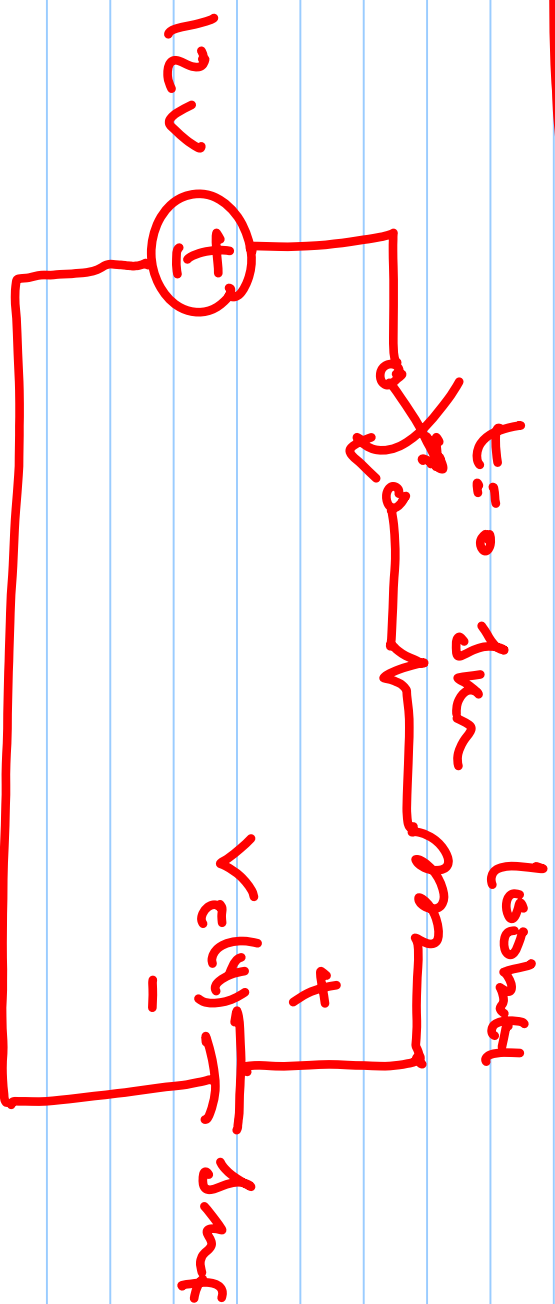


Find  $V_c(s)$  for  $t > 0$ , if  $V_c(0) = 0$ .

## Example

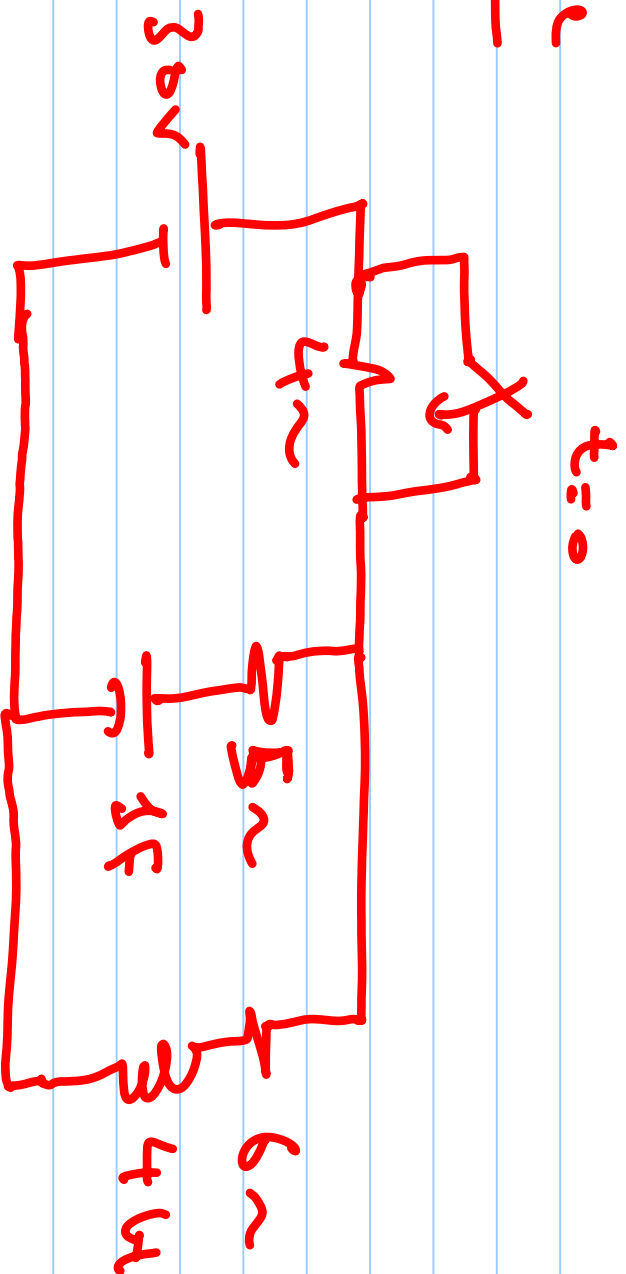

\* obtain the initial conditions for  $i_C$  and  $i_L$ . Find  $i_C(t)$  for  $t > 0$

## Example

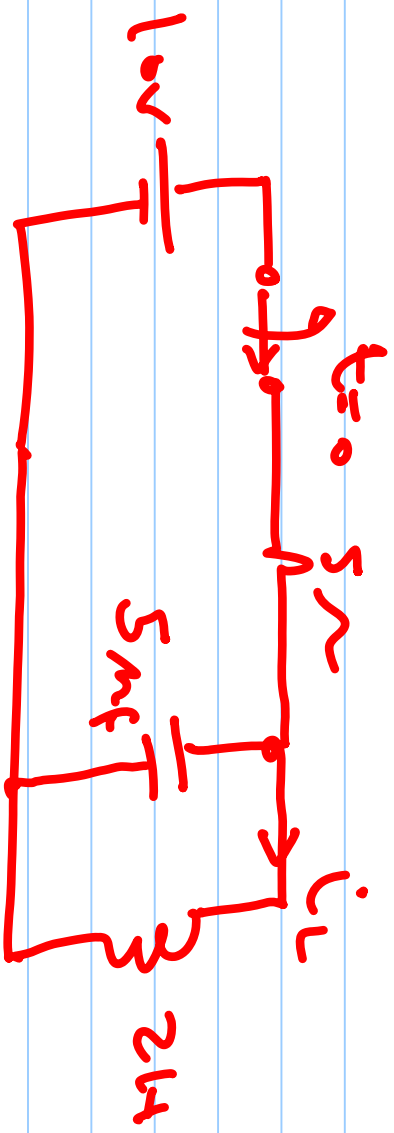

find the natural frequency of  
the current  $i_L$