

Dr. Mohamed Bakr, EE2CI5, 2007

Note Title

1/18/2007


Lecture 23

From Section 8.4 and 8.5

Solve E8.5-E8.10, 8.8, 8.11,
8.13, 8.15, 8.18

Phase Relation For Resistor

$$v(t) = A_v \cos(\omega t + \theta_v)$$
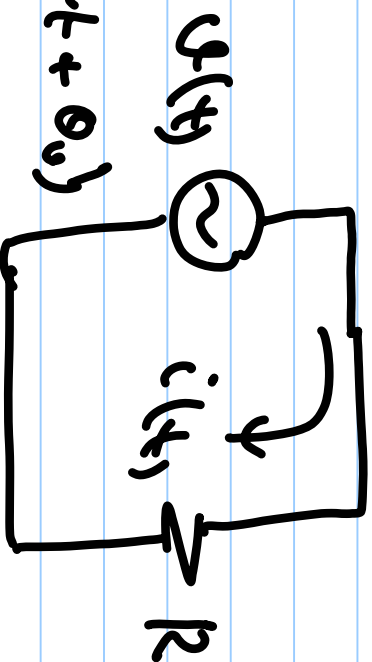
$$i(t) = \frac{v(t)}{R} = \frac{A_v}{R} \cos(\omega t + \theta_v)$$


$$i(t) = A_i \cos(\omega t + \theta_i)$$

$$\vec{V} = A_v e^{j\theta_v}, \quad \vec{I} = A_i e^{j\theta_i}$$


$$\theta_i = \theta_v, \quad A_i = \frac{A_v}{R}$$

$$\boxed{V^2 = R I^2}$$

In Phase

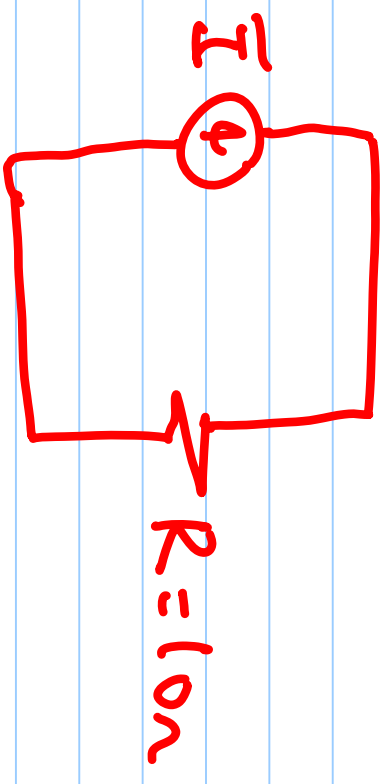Example


If $I = 3 \angle 30^\circ$,
 $f = 60\text{Hz}$, find,
 v , $i(t)$, and $s(t)$



Phasor Relation for Inductors

$$i(t) = i_0 \cos(\omega t + \theta_0)$$
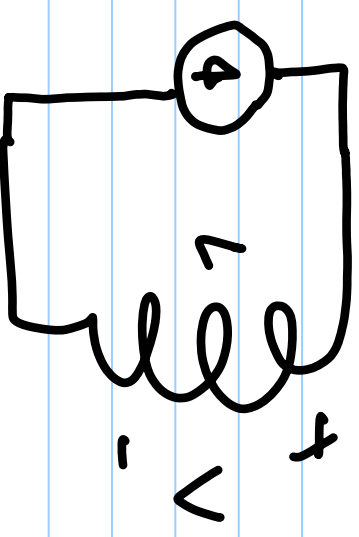
$$I = i_0 \angle \theta_0 = i_0 e^{j\theta_0} \quad i$$



$$v(t) = L \frac{di}{dt}$$

$$= L i_0 \omega \sin(\omega t + \theta_0)$$

$$v(t) = \omega L i_0 \cos(\omega t + \theta_0 + \pi/2)$$

$$V = \omega L i_0 e^{j(\theta_0 + \pi/2)} = j\omega L i_0 e^{j\theta_0}$$

$$V = j\omega L I \rightarrow \text{Voltage Leads}$$


Example

If $V = 10 \angle 60^\circ$,

$$f = 50 \text{ Hz}$$

find I , $v(t)$,

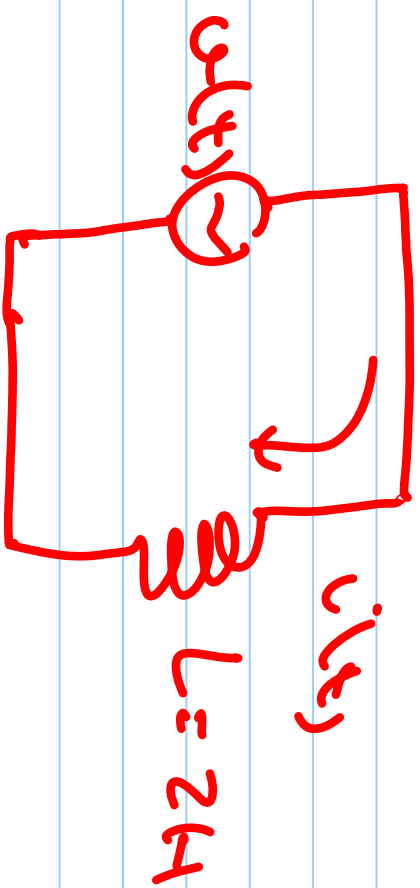and $i(t)$. Plot $v(t)$, $i(t)$, V and I .




Phasor Relation for Capacitors

$$v(t) = A \cos(\omega t + \theta_v)$$

$$\vec{V} = A \angle \theta_v = A \angle \theta_v$$

$$i(t) = C \frac{dv(t)}{dt}$$

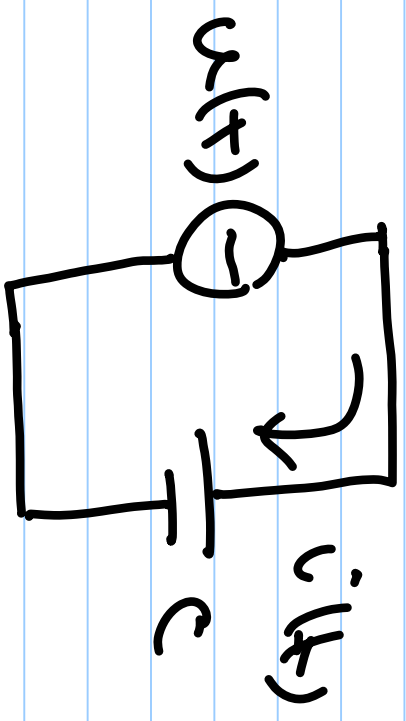

$$i(t) = A \omega C \cos(\omega t + \theta_v)$$

$$i(t) = A \omega C \cos(\omega t + \theta_v + \pi/2)$$

$$\vec{I} = \omega C A \angle (\theta_v + \pi/2) = j \omega C A \angle \theta_v$$

$$\vec{I} = j \omega C \vec{V} \rightarrow \vec{V} = \frac{1}{j \omega C} \vec{I} \rightarrow \text{Current Leads}$$


Example

If $\tilde{I} = 0.1 \angle 120^\circ$,

and $\omega = 10\text{kHz}$, $i(t)$

find \tilde{V} , $i(t)$, and

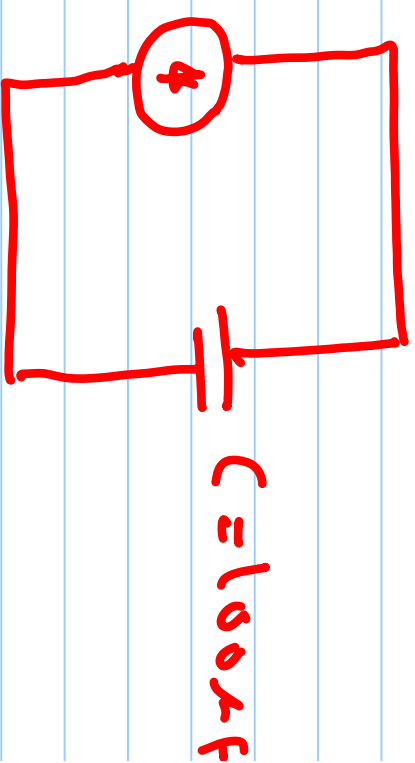$q(t)$. Plot $i(t)$, $q(t)$, \tilde{I} , and \tilde{V} .



Impedance

* Resistor $\Rightarrow \vec{V} = R\vec{I}$, $Z_R = R \angle 0^\circ$

* Inductor $\Rightarrow \vec{V} = j\omega L\vec{I}$, $Z_L = j\omega L$


$$Z_L = \omega L \angle 90^\circ$$

* Capacitor $\Rightarrow \vec{V} = \frac{1}{j\omega C}\vec{I}$, $Z_C = \frac{1}{j\omega C}$

$$Z_C = \frac{1}{\omega C} \angle -90^\circ$$

* Impedances are added in the same way we add resistors

Impedance (Cont'd)

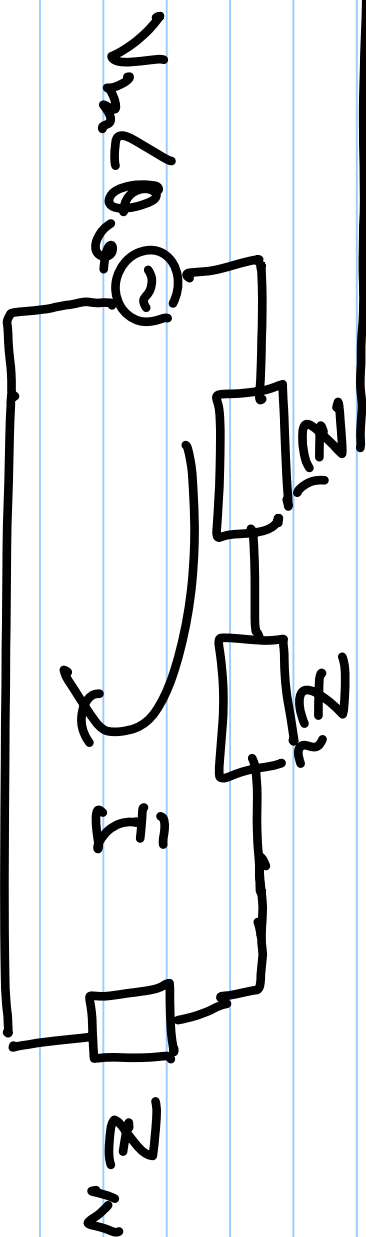

$$Z = Z_1 + Z_2 + \dots + Z_N$$

$$Z = R(\omega) + jX(\omega) \sim$$

$R(\omega)$: Resistive part of Impedance

$X(\omega)$: Reactive part of Impedance


Impedance (cont'd)

$$Z = |Z| \angle \theta_z$$

$$I = \frac{V}{Z} = \frac{V_m \angle \theta_v}{|Z| \angle \theta_z} = \frac{V_m}{|Z|} \angle \theta_v - \theta_z$$

* Impedance changes magnitude and phase of voltage to give the current phase

Example

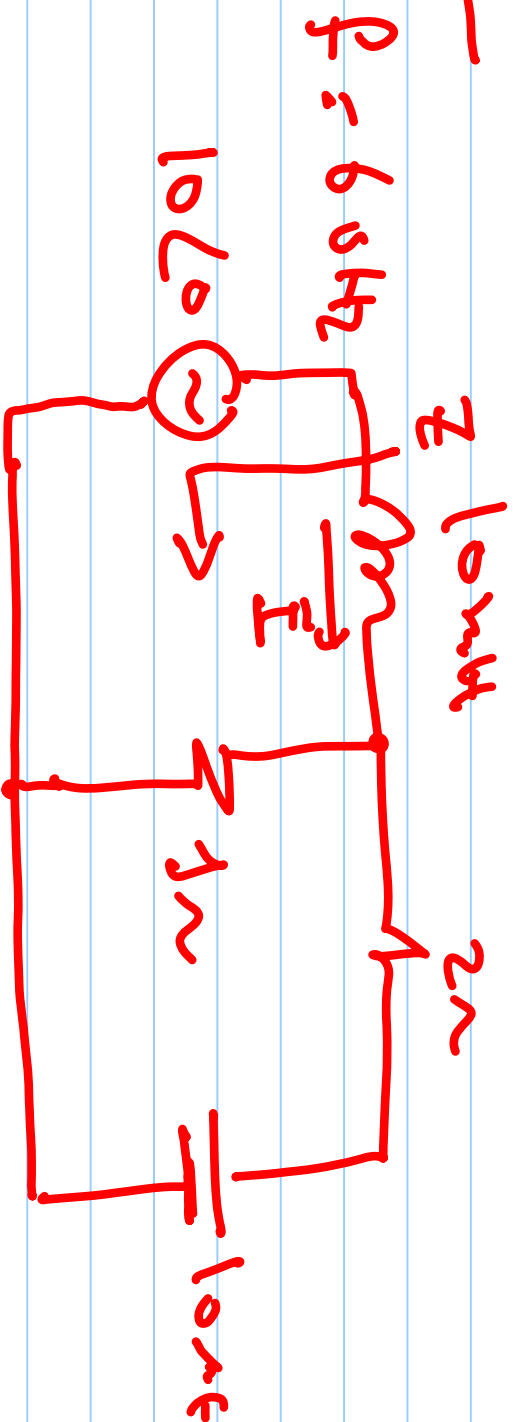

Find the impedance Z seen by the source. Find also I and $i(t)$

Example

Find Z , V , $i(t)$,
and $v(t)$

