

Dr. Mohamed Bakr, EE2C15, 2007

Note Title

11/13/2007

Lecture 24

from Sections 8.5-8.8 of Text

Solve E8.9-E8.12, 8.20, 8.24,
8.28, 8.32, 8.34, 8.37, 8.40,
8.44

Admittance

* Admittance is the inverse of impedance

$$Y = \frac{1}{Z} = \frac{I}{V} = Y_H \angle \theta_Y$$



$$Y = G + jB \leftarrow \frac{1}{Z}$$

Conductance Susceptance

* Notice that $G + jB = \frac{1}{Z} = \frac{1}{R + jX}$


Admittances (Cont'd)

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

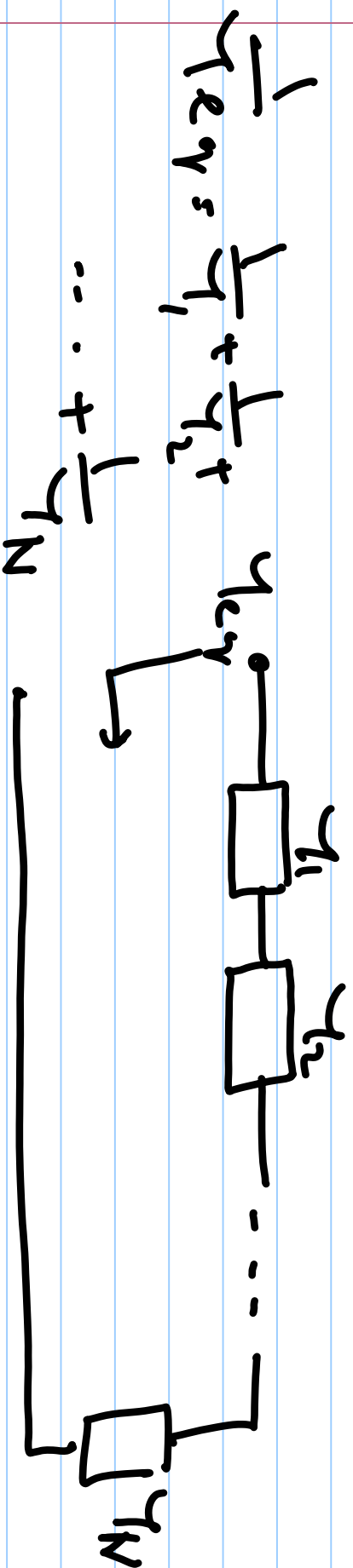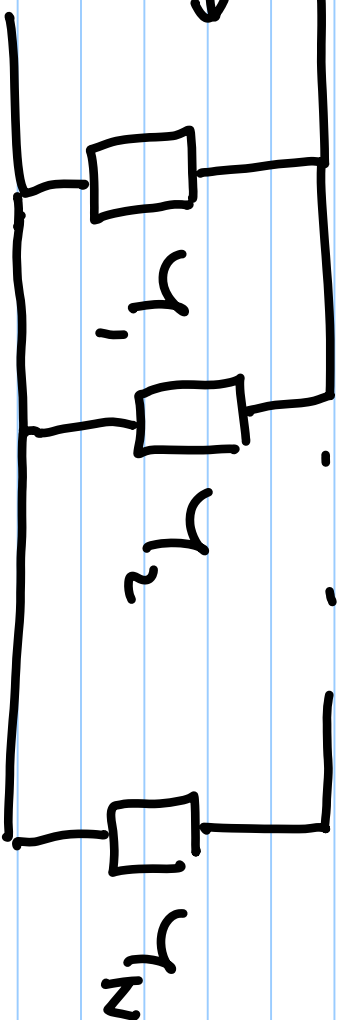


$$\frac{1}{Y_{eq}} = \frac{1}{Y_1} + \frac{1}{Y_2} + \dots + \frac{1}{Y_N}$$

Example

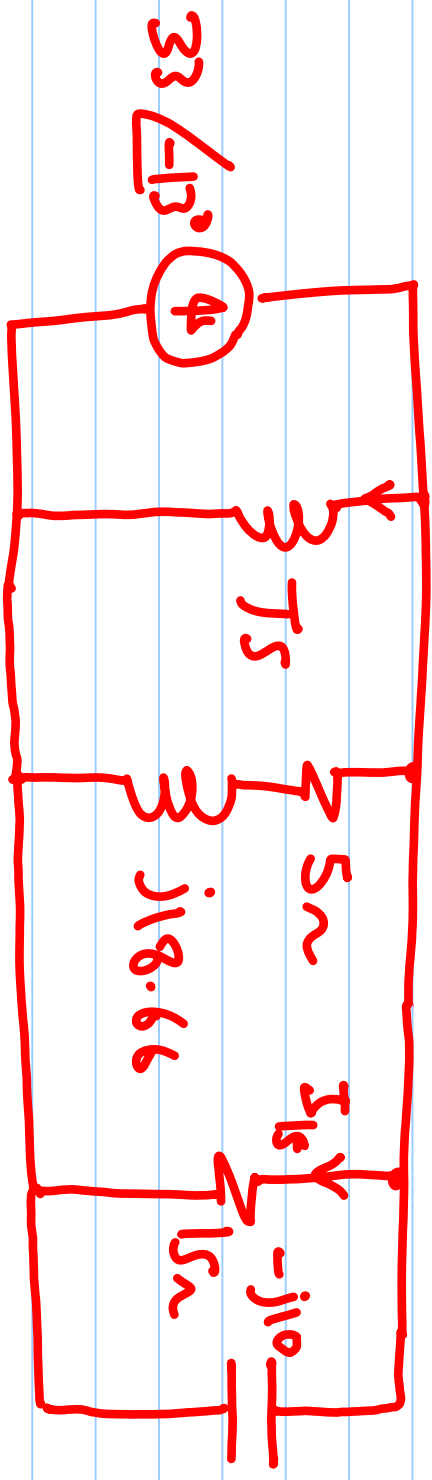

Calculate the current in the
 15Ω resistor

Example

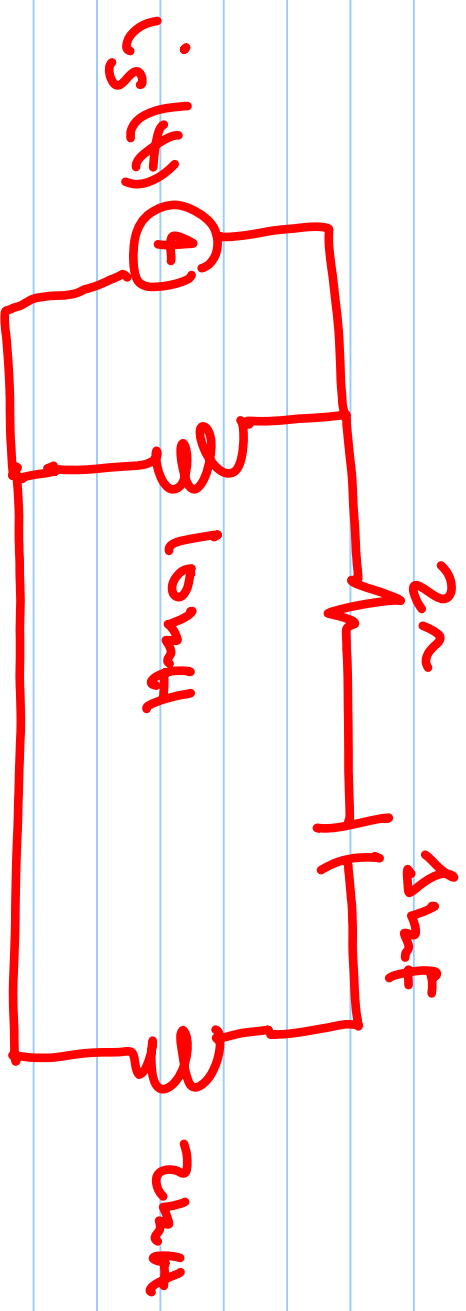

Draw the frequency domain circuit
and calculate $v(t)$ if

$$i_s(t) = 2 \cos(1000t + 120^\circ) \text{ A}$$


Phasor Diagrams

* Frequency domain currents and voltages are phasors

* KCL gives the phasor sum of currents at a node

* KVL gives the phasor sum of voltages in a loop

Example

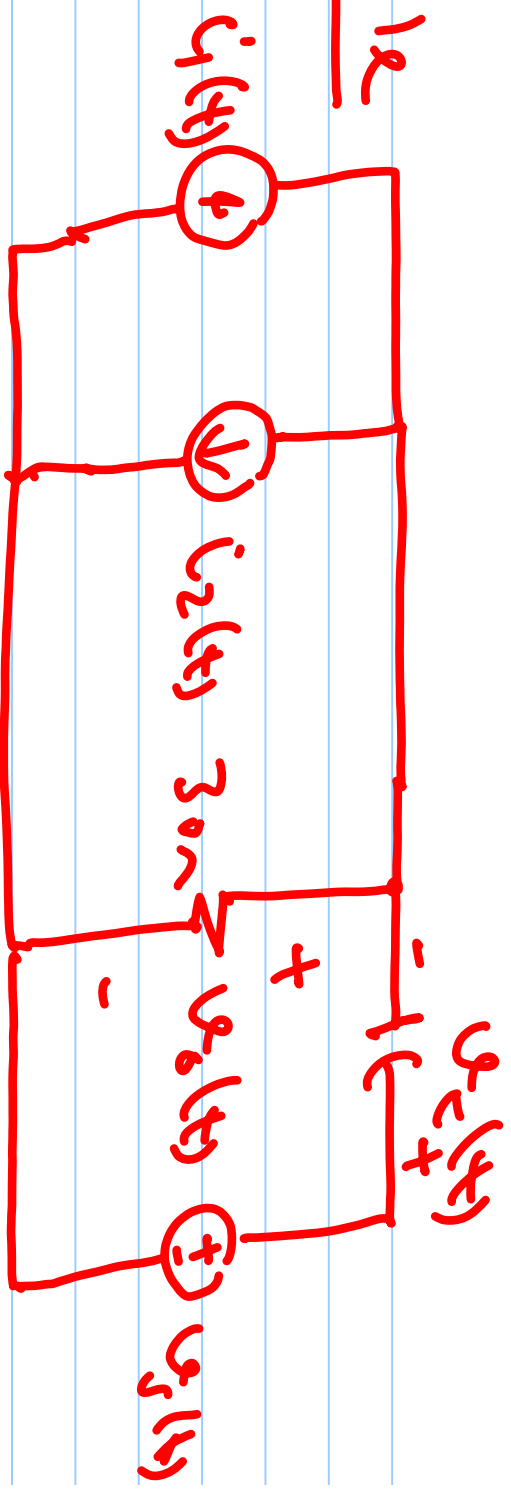

* Calculate $v_o(t)$ if


$$i_1(t) = 200 \cos(10^3 t + 60^\circ),$$

$$i_2(t) = 150 \sin(10^3 t + 30^\circ), \text{ and}$$

$$v_s(t) = 10 \sin(10^3 t) \text{ V. Use a phasor}$$

diagram to find $v_o(t)$

Example

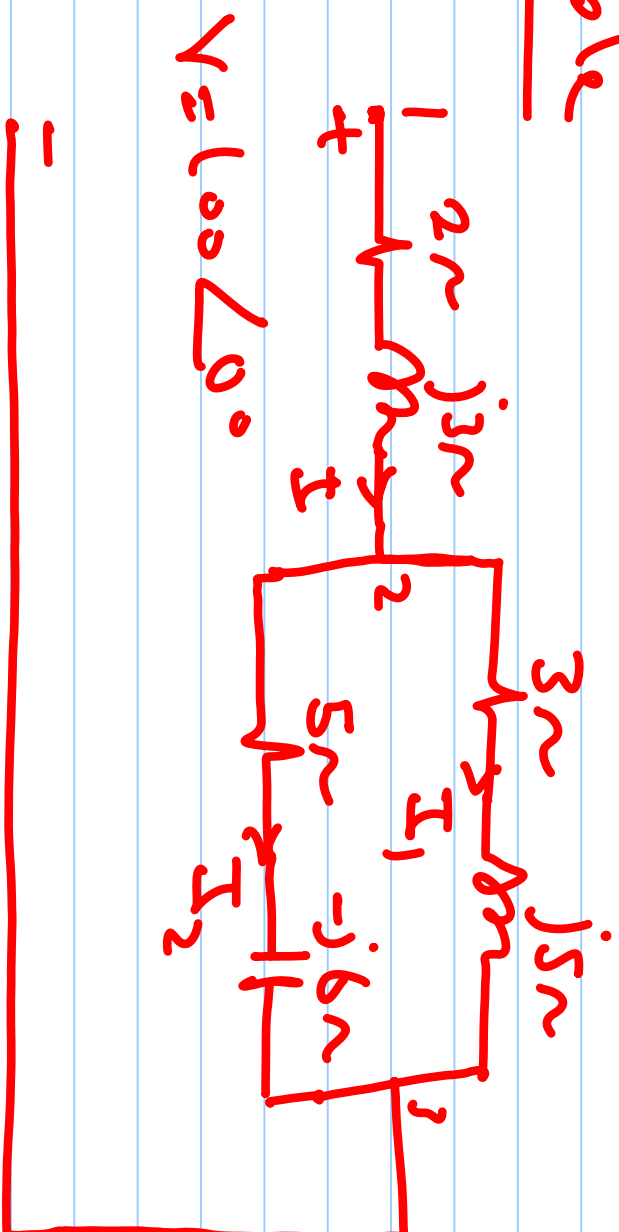

- * Find the currents I , I_1 , and I_2
- * Draw a phasor diagram showing V_1 , V_{12} , and V_{23} .