

Dr. Mohamed Bakr, EE2CI5, 2007

Note Title

11/26/2007



Lecture 27

From Sections 9.4-9.6

Solve E9.7 - E9.12, 9.44, 9.47,

9.50, 9.53, 9.56, 9.61, 9.66, 9.69

Root Mean Square (RMS) value

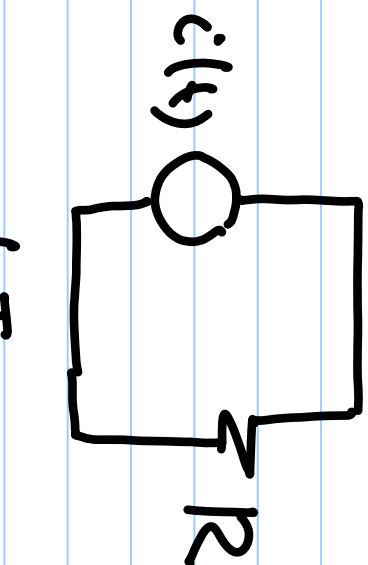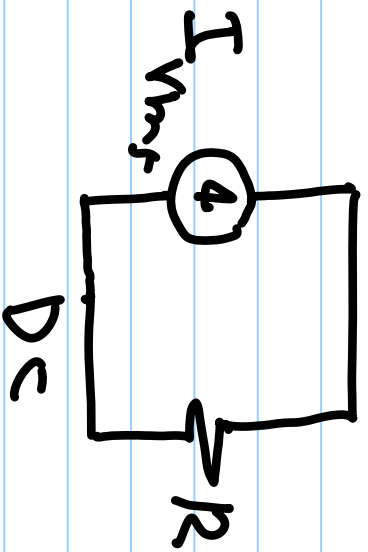

$$P = I_{rms}^2 R$$

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt$$


To have the same power, we must

$$\text{have } I_{rms}^2 R = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt$$

$$\text{or } I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt}$$

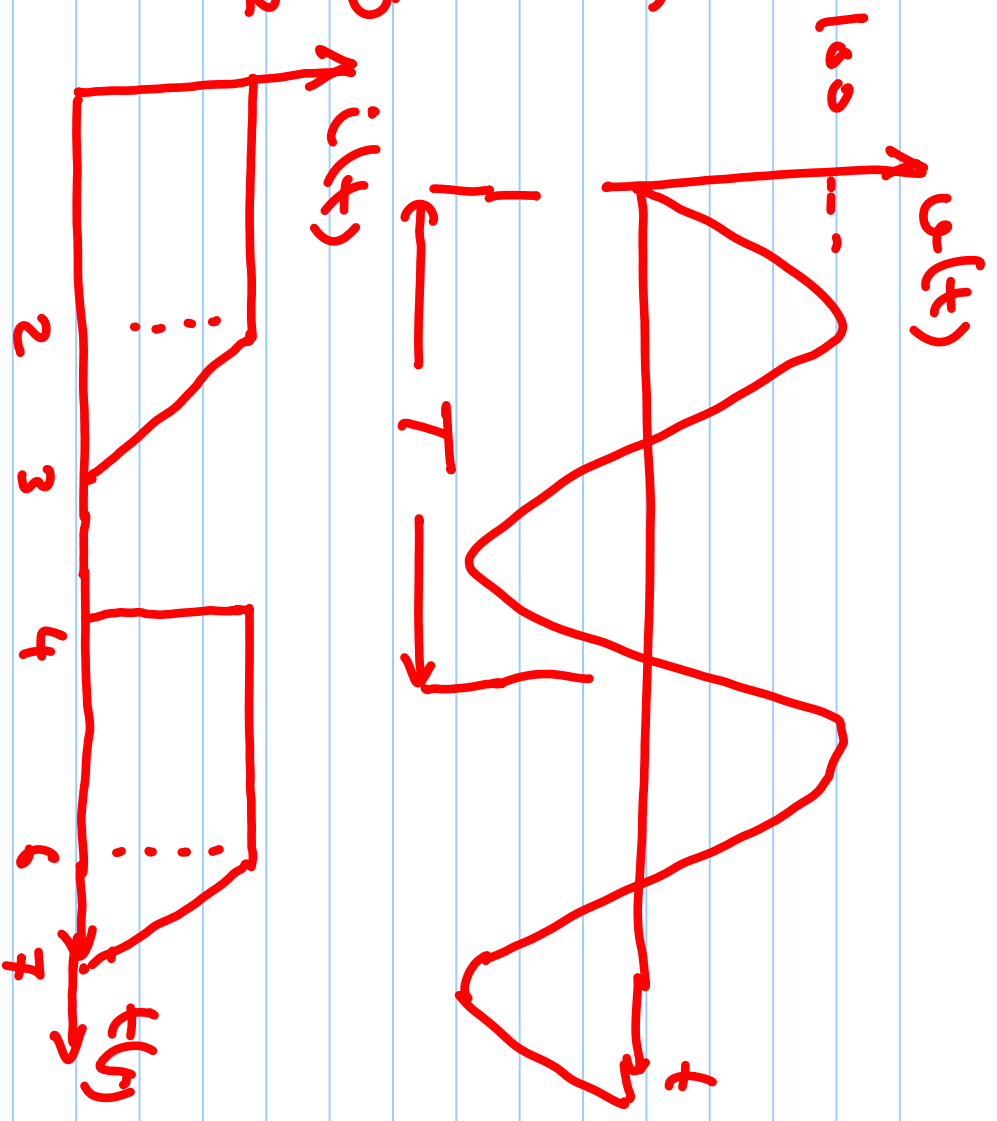Example

find the RMS values for the following waveforms



Complex Power

$$* v(t) = A_v \cos(\omega t + \theta_v)$$

$$\bar{V} = A_v \angle \theta_v$$


$$V_{rms} = \frac{A_v}{\sqrt{2}} \angle \theta_v$$

$$V_{rms} = V_{rms} \angle \theta_v$$

$$* i(t) = A_i \cos(\omega t + \theta_i)$$

$$\bar{I} = A_i \angle \theta_i$$
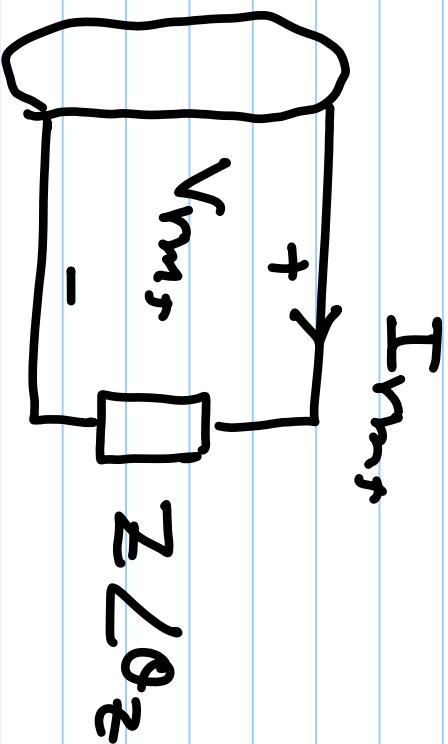
$$I_{rms} = \frac{A_i}{\sqrt{2}} \angle \theta_i = I_{rms} \angle \theta_i$$



Complex Power

* Complex Power is defined as

$$S^T = \bar{V}_{rms} \bar{I}_{rms}^* = V_{rms} \angle \theta_v I_{rms} \angle -\theta_i$$

$$S^T = V_{rms} I_{rms} \angle \theta_v - \theta_i = V_{rms} I_{rms} e^{j(\theta_v - \theta_i)}$$

$$S^T = V_{rms} I_{rms} (\cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i))$$

$$+ j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$S = P + jQ$$

Real power

Reactive Power

Complex Power (Cont'd)

$$\theta_s = \theta_i \rightarrow R$$

$$P = V_{rms} I_{rms}$$

$$Q = 0$$

$$P = I_{rms}^2 R$$

$$S = P$$

$$\theta_s = \theta_i = \frac{\pi}{2}$$

$$P = 0$$

$$Q = V_{rms} I_{rms}$$

$$Q = I_{rms}^2 \omega L$$

$$S = jQ$$

$$\theta_s = \theta_i = -\frac{\pi}{2}$$


$$P = 0$$

$$Q = -V_{rms} I_{rms}$$

$$Q = -I_{rms}^2 \omega C$$

$$S = -jQ$$

Example

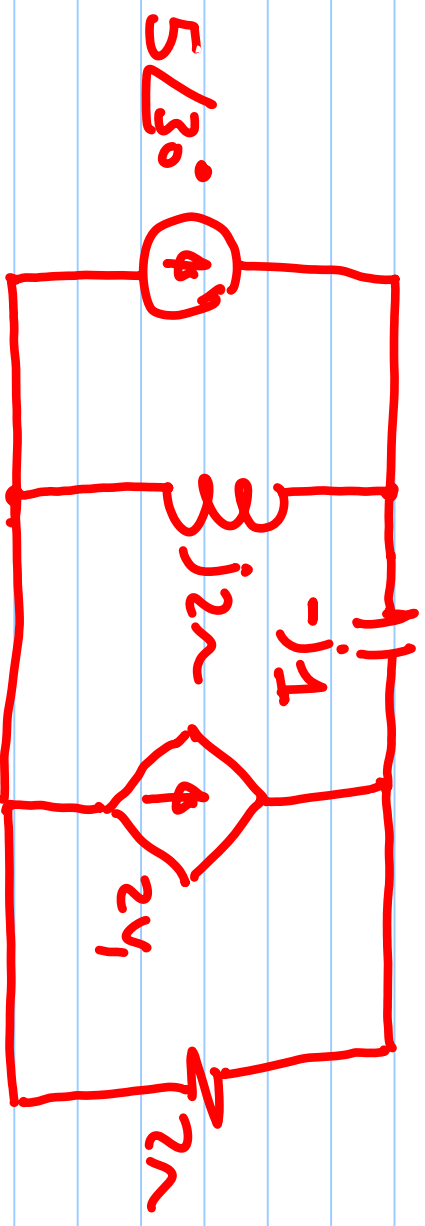


* Find the complex power supplied by the two current sources

* Verify Conservation of complex power

Example

$$0.5\Omega \quad j0.2\Omega$$

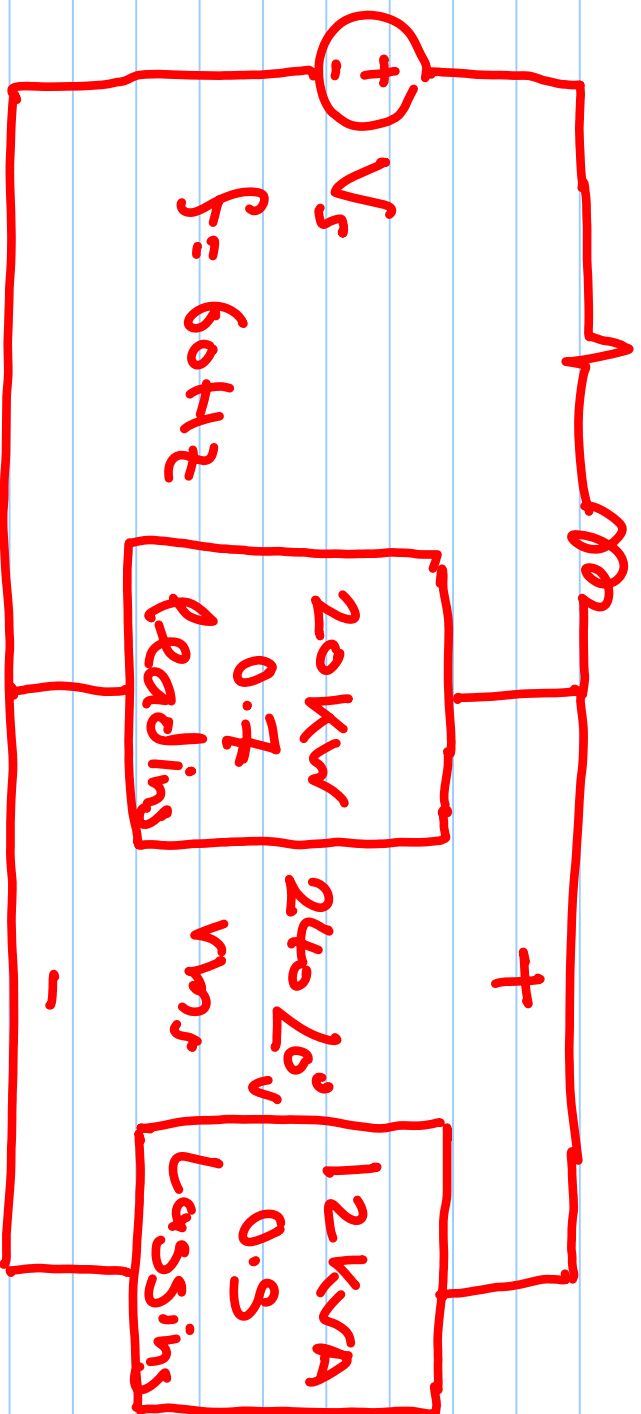

Find the Complex power supplied by the source, the power factor of the source, and $V_r(t)$