

Solution to Chapter 10 Problems

Problem 10

In steady state, the internal circuit voltages can't exceed the power supply limits.

$$a. V_o)_{\max} = +15V$$

$$b. V_o)_{\min} = -9V$$

Problem 11

- From the given gain plot & using a value for $V_i = V_B = 0.6V$, we can calculate the small signal gain as the slope of the curve.

$$\therefore A_v = \frac{4-12}{0.7-0.5} = -40$$

$$\Rightarrow |A_v| = 20 \log |A_v| = 32 \text{ dB}, \angle A_v = 180^\circ$$

- To have an undistorted output signal, the amplifier should be operating in the linear region.
 $\therefore V_{Th} \ll 0.1V$ for the linear operation


Problem 20

First we open circuit the op-amp for $i_2 = 0$, so the circuit will be as shown:

$$\therefore g_{11} = i_1 / V_1 \rightarrow g_{21} = V_2 / V_1$$

$$V_1 = 10k \cdot i_1 + 240k \cdot 10i_1 = 24.25 \times 10^6 i_1$$
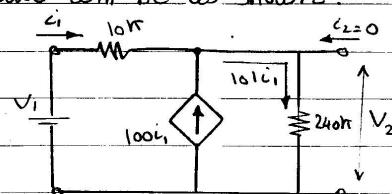
$$\Rightarrow g_{11} = 4.12 \times 10^{-8} \text{ S}$$




$$V_2 = 240k \cdot 10i_1 \Rightarrow g_{21} = \frac{24.24 \times 10^6 i_1}{24.25 \times 10^6 i_1}$$

$$\therefore g_{21} \approx 1$$

Now, we short circuit the i/p for $V_1 = 0$
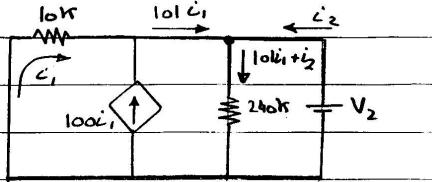
$$\therefore g_{12} = i_1 / i_2 \quad , \quad g_{22} = V_2 / i_2$$



$$\text{We have } V_2 = 240k (10i_1 + i_2)$$

$$= -10k (i_1)$$

$$\therefore 240k (10i_1 + i_2) = -10k \cdot i_1$$

$$2400i_1 + 24i_2 = -10i_1 \Rightarrow 2434i_1 = -24i_2$$

$$\Rightarrow g_{12} = i_1 / i_2 = -9.86 \times 10^{-3}$$


$$\& V_2 = -10k \cdot i_1 = -10k \cdot \frac{-24}{2434} i_2 = 98.6 i_2$$

$$\Rightarrow g_{22} = V_2 / i_2 = 98.6 \text{ S2}$$

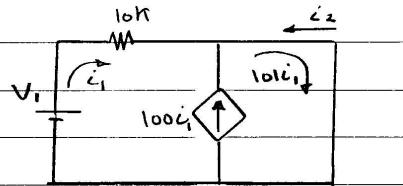Problem 21

First, we short circuit the o/p for $V_2 = 0$

$$\therefore h_{11} = V_1 / i_1 \quad , \quad h_{21} = i_2 / i_1$$




From the circuit, we directly find $i_2 = -10i_1$

$$\Rightarrow h_{21} = -10$$

$$\text{Also } V_1 = 10k \cdot i_1 \Rightarrow h_{11} = 10k$$

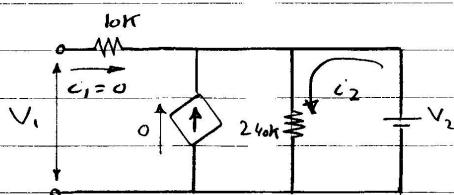Now, we open circuit the i/p for $i_1 = 0$




$$\therefore h_{12} = V_1 / V_2 \quad , \quad h_{22} = i_2 / V_2$$

$$V_1 = V_2 \Rightarrow h_{12} = 1 \quad \& \quad V_2 = 240k (i_2) \Rightarrow h_{22} = 24.00 \mu\text{s}$$

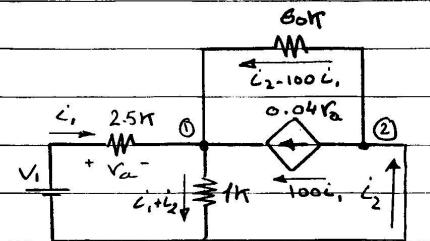Problem 27

First, we ^{short} circuit the opamp for $V_2 = 0$

$$\therefore Y_{11} = i_1 / V_1 \quad \Rightarrow \quad y_{21} = i_2 / V_1$$



$$V_a = 2.5k \cdot i_1 \quad \therefore 0.04 V_a = 100 i_1$$

$$\text{We've } V_{21} = 60k \cdot (i_2 - 100 i_1) = -1k \cdot (i_1 + i_2)$$

$$\therefore 60i_2 - 6000i_1 = -i_1 - i_2 \quad \Rightarrow \quad \frac{i_1}{i_2} = \frac{61}{5999}$$


$$V_1 = 2.5k \cdot i_1 + 1k \cdot (i_1 + i_2) = (2.5k + 1k + \left(\frac{61}{5999}\right)^{-1} \cdot 1k) i_1 = 101844.26 i_1$$

$$\Rightarrow Y_{11} = i_1 / V_1 = 9.82 \mu S$$

$$\& \quad y_{21} = i_2 / V_1 = Y_{11} \cdot (i_2 / i_1) = 0.9656 mS$$

Now, we short circuit the IIP for $V_1 = 0$
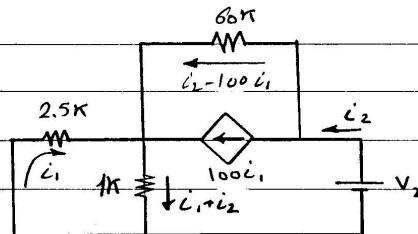
$$\therefore Y_{12} = i_1 / V_2 \quad \Rightarrow \quad y_{22} = i_2 / V_2$$



For the parallel resistors 2.5k & 1k:

$$-2.5k \cdot i_1 = 1k \cdot (i_1 + i_2) \quad \Rightarrow \quad i_2 = -3.5 i_1$$

Now using KVL for the outer loop: $V_2 = 60k \cdot (i_2 - 100 i_1) - 2.5k \cdot i_1$

$$\therefore V_2 = 60k (-3.5 i_1) - 60k (100 i_1) - 2.5k i_1 = -6212500 i_1$$

$$\Rightarrow Y_{12} = -0.161 \mu S$$


$$\& \quad y_{22} = Y_{12} \cdot (i_2 / i_1) = 0.5634 \mu S$$

Problem 28

First, we open circuit the o/p for $i_2 = 0$

$$\therefore Z_{11} = V_1 / i_1 \rightarrow Z_{21} = V_2 / i_1$$
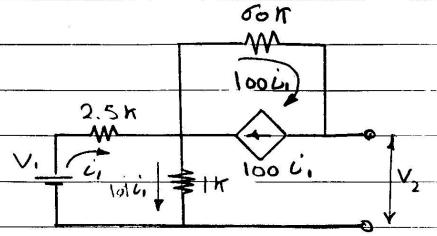
$$V_1 = 2.5k \cdot i_1 + 1k \cdot i_1 = 3.5k \cdot i_1$$




$$\Rightarrow Z_{11} = 3.5k \Omega$$

$$\text{Using KVL: } V_2 = -100i_1 \cdot 60k + i_1 \cdot 1k = (-6000k + 1k) i_1 = -5999k i_1$$

$$\Rightarrow Z_{21} = -5.999 M\Omega$$

Now, we open circuit the i/p for $i_1 = 0$
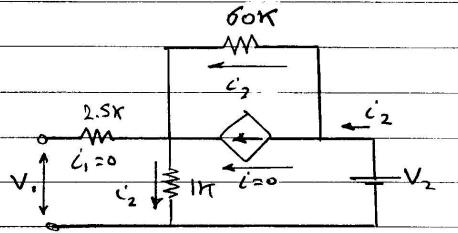
$$V_2 = 60k \cdot i_2 + 1k \cdot i_2 = 61k \cdot i_2$$




$$\Rightarrow Z_{22} = V_2 / i_2 = 61 k \Omega$$

$$V_1 = 1k \cdot i_2 \Rightarrow Z_{12} = 1k \Omega$$

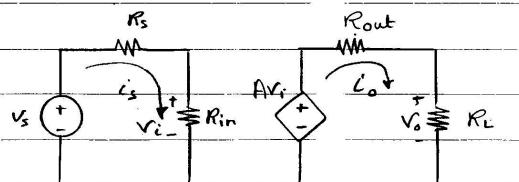Problem 40

We can redraw the circuit as follows:

$$A = 54 \text{ dB} \Rightarrow A = 10^{\frac{54}{20}} = 501.2$$



$$\text{a. } A_V = \frac{V_o}{V_s} \quad \text{but } V_o = R_L i_o = \frac{A V_i}{R_L + R_{out}} \cdot R_L$$

$$\& V_i = R_{in} i_s = \frac{V_s}{R_s + R_{in}} \cdot R_{in}$$

$$A_i = \frac{i_o}{i_s} \text{ but } i_o = \frac{A_v i_s}{R_{out} + R_L} \& i_s = \frac{V_s}{R_s + R_{in}}$$

$$\therefore A_i = \frac{A_v R_{in} i_s}{R_{out} + R_L} / \frac{V_s}{R_s + R_{in}} \text{ but } i_s = \frac{V_s}{R_s + R_{in}}$$

$$\therefore A_i = \frac{A_v R_{in}}{R_{out} + R_L} = \frac{3.04 \times 10^7}{1} = 149.65 \text{ dB} \approx 150 \text{ dB}$$

$$A_p = \frac{V_o i_o}{V_s i_s} = A_v \cdot A_i = 1.47 \times 10^{10} = 101.7 \text{ dB} \approx 102 \text{ dB}$$

Remember $A_p)_{dB} = 10 \log A_p$

$$b. P_{R_L} = \frac{V_o^2}{2 R_L} = 1 \text{ W} \Rightarrow V_o = \sqrt{2 R_L} = 5.657 \text{ V}$$

$$\therefore V_s = \frac{V_o}{A_v} = 11.65 \text{ mV}$$

c. The power dissipated in the amplifier is that dissipated in R_{in} & R_{out}

$$\therefore P = P_{R_{in}} + P_{R_{out}} = \frac{i_s^2 R_{in}}{2} + \frac{i_o^2 R_{out}}{2}$$

$$\text{but } i_s = \frac{V_s}{R_s + R_{in}} = 1.164 \times 10^{-8} \text{ A} \& i_o = \frac{V_o}{R_L} = 0.3536 \text{ A}$$

$$\therefore P = 87.7 \text{ pW} + 31.26 \text{ mW} = 31.26 \text{ mW}$$

Problem 57

$$A_r(s) = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000 s}{(s + 20\pi)(1 + \frac{s}{2\pi \times 10^4})} = A_0 \frac{s}{(s + \omega_L)} \cdot \frac{1}{(1 + \frac{s}{\omega_H})}$$

The midband gain $A_0 = 1000 = 60 \text{ dB}$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \rightarrow f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz}$$

$$\Delta \omega = f_H - f_L = 9.99 \text{ kHz}$$

11

11

Problem 58

$$A_v(s) = \frac{2\pi \times 10^6}{s + 20\pi} = \frac{10^5}{1 + \frac{s}{20\pi}} = \frac{A_0}{1 + \frac{s}{\omega_H}} \Rightarrow \text{Low pass amplifier}$$

$$A_{mid} = 10^5 = 100 \text{ dB}$$

$$f_H = \frac{20\pi}{2\pi} = 10 \text{ Hz}, f_L = 0 \text{ Hz}, BW = 10 \text{ Hz}$$

Problem 59

$$A_v(s) = \frac{10^4 s}{s + 100\pi} = \frac{A_0 s}{s + \omega_L} \Rightarrow \text{High-pass amplifier}$$

$$A_{mid} = 10^4 = 80 \text{ dB}$$

$$f_H = \infty, f_L = \frac{100\pi}{2\pi} = 50 \text{ Hz}, BW = \infty$$

Problem 12

For $V_B = 0.8V$ the voltage gain is calculated as follows

$$A_V = \frac{2-4}{0.9-0.7} = -10 \Rightarrow |A_V| = 20 \text{ dB} \quad \angle A_V = 180^\circ$$

For linear operation $V_I \leq 0.1V$

Problem 48

$$V_1 = \frac{V_s R_{in}}{R_s + R_{in}} \rightarrow V_2 = \frac{A V_1 R_{in}}{R_{in} + R_{out}} \rightarrow V_o = \frac{A V_2 R_L}{R_L + R_{out}}$$

$$A_V = \frac{V_o}{V_s} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_1} \cdot \frac{V_1}{V_s} = \frac{A R_L}{R_L + R_{out}} \cdot \frac{A R_{in}}{R_{in} + R_{out}} \cdot \frac{R_{in}}{R_s + R_{in}} = 2.27 \times 10^5$$

$$\Rightarrow |A_V| = 107.12 \text{ dB}$$

$$A_i = \frac{I_o}{I_s} = \frac{V_o / R_L}{V_s / (R_s + R_{in})} = \frac{V_o}{V_s} \cdot \frac{R_s + R_{in}}{R_L} = A_V \cdot \frac{R_s + R_{in}}{R_L} = 1.36 \times 10^7$$

$$\Rightarrow |A_i| = 142.68 \text{ dB}$$

$$A_p = \frac{V_o I_o}{V_s I_s} = A_V \cdot A_i = 3.087 \times 10^{12}$$

$$\Rightarrow |A_p| = 124.9 \text{ dB}$$