
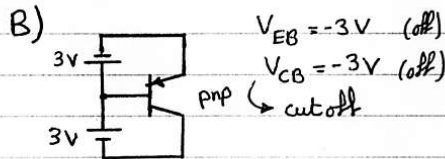
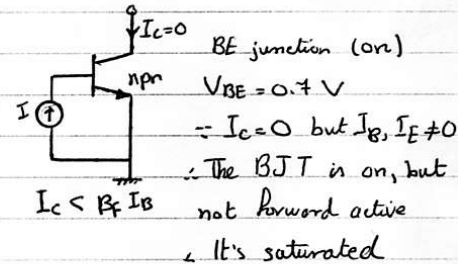
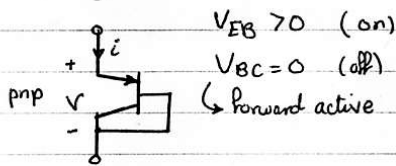
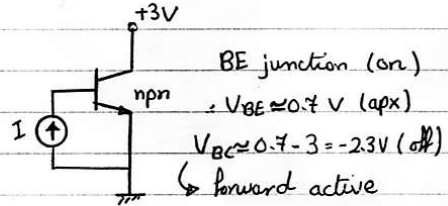
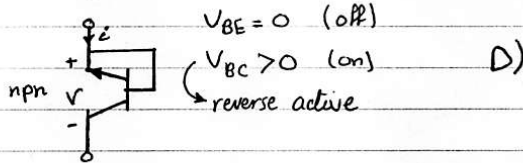
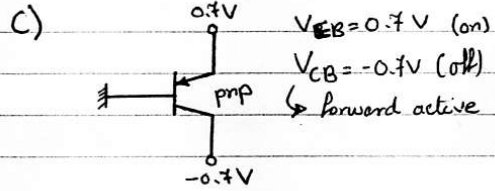


Answers to Chapter 5

5.32

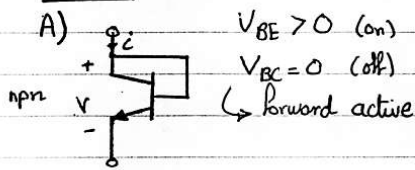

5.61

PNP $V_{EB} = 0.7V$ $V_{CB} = -0.7V \Rightarrow$ Forward active
 $I_C = \beta_F I_B \Rightarrow \beta_F = \frac{2.5mA}{50\mu A} = 50$

Also $I_C = I_S e^{(V_{EB}/V_T)} \Rightarrow I_S = \frac{2.5mA}{e^{(0.7/0.025)}} = 1.73 \text{ fA}$

5.65

NPN $V_{BE} = -0.7V$, $V_{BC} = 0.7V \Rightarrow$ reverse active
 $I_C = -(\beta_R + 1) I_B \Rightarrow \beta_R = -\frac{I_C}{I_B} - 1 = -\frac{-75\mu A}{50\mu A} - 1 = 0.5$

$I_E = -I_S e^{(V_{BC}/V_T)} = I_B + I_C = -25\mu A$

$I_S = -\frac{-25\mu A}{e^{(0.7/0.025)}} = 17.3 \times 10^{-18} \text{ A}$

Alroy

5.73

A) NPN Forward active

$$I_C = \beta_F I_B = I_S e^{(V_{BE}/V_T)} \Rightarrow V_{BE} = V_T \ln\left(\frac{50 \times 250 \mu A}{10 \text{ pA}}\right) = 0.812 \text{ V}$$

B) NPN Saturation ($\because I_C < \beta_F I_B$)

$$\text{Use eq. 5.53 } V_{BE} = V_T \ln \frac{I_B + (1 - \alpha_R) I_C}{I_S \left[\frac{1}{\beta_F} + (1 - \alpha_R) \right]} = 0.025 \ln \frac{250 \times 10^{-6} + 0}{10^{-16} \left[\frac{1}{50} + \left(1 - \frac{0.5}{1.5}\right) \right]} = 0.723$$

$$\text{eq. 5.54 } V_{CEsat} = V_T \ln \left[\left(\frac{1}{\alpha_R} \right) \frac{1 + \frac{I_C}{(\beta_{RH}) I_B}}{1 - \frac{I_C}{\beta_F I_B}} \right] \Rightarrow V_{CEsat} = V_T \ln \left(\frac{1}{\alpha_R} \right) = 27.5 \text{ mV}$$

5.74

$$\text{A) } I_C = I_S \left[e^{(V_{BE}/V_T)} - 1 \right] \left(1 + \frac{V_{CE}}{V_A} \right) = 10^{-16} \left[e^{(0.72/0.025)} - 1 \right] \left(1 + \frac{10}{85} \right) = 371 \mu A$$

$$\text{B) } I_C = 10^{-16} \left[e^{(0.72/0.025)} - 1 \right] = 322 \mu A$$

$$\text{C) } \frac{I_{C1}}{I_{C2}} = \frac{371 \mu A}{322 \mu A} = 1.15$$

5.82

A) The circuit can be reduced as follows:


KVL $3.462 - (23.54k)I_B - 0.7 - (33k)(51I_B) = 0$

$\Rightarrow I_B = 1.618 \mu A \quad \therefore I_C = 50I_B = 80.9 \mu A$

KVL $10 - (43k)(80.9 \mu A) - V_{CE} - (33k)(82.5 \mu A) = 0$

$\Rightarrow V_{CE} = 3.797V$

$\therefore Q = (80.9 \mu A, 3.797V)$

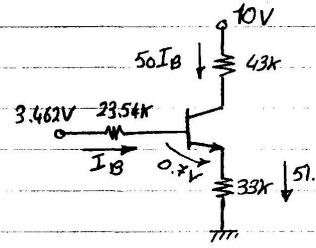

B) After simplifying the circuit the same way

KVL $3.462 - (4.708k)I_B - 0.7 - (6.6k)(51I_B) = 0 \Rightarrow I_B = 8.09 \mu A$

KVL $10 - (8.6k)I_C - V_{CE} - (6.6k)I_E = 0 \Rightarrow V_{CE} = 3.797V$

$\therefore Q = (405 \mu A, 3.797V)$


C) KVL $10 - (33k)(51I_B) - 0.7 - (23.54k)(I_B) - 6.538 = 0$

$\Rightarrow I_B = 1.618 \mu A \quad \therefore I_C = 80.9 \mu A$

KVL $10 - (33k)(51I_B) - V_{CE} - (43k)(50I_B) = 0$

$\Rightarrow V_{CE} = 3.797V$

$\therefore Q = (80.9 \mu A, 3.797V)$

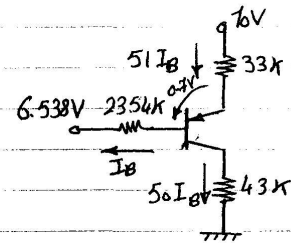

D) Using same procedure

$\Rightarrow I_B = 8.092 \mu A \quad \therefore I_C = 404.6 \mu A$

& $V_{CE} = 3.797V$

$\therefore Q = (404.6 \mu A, 3.797V)$


5.91

First we need to simplify the ct. using Thevenin eq.

From the ckt's we need to calculate β_F

so if we choose $V_{CE} = 5V \Rightarrow \beta_F \approx \frac{5mA}{60 \mu A} = 83$

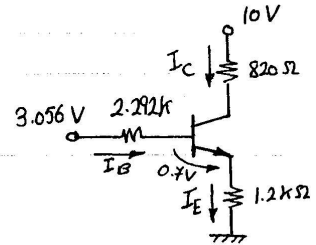KVL $V_{CE} = 10 - 820 I_C - 1200 I_E = 10 - 2034 I_C$




Draw this loadline on the ckt's & then calculate I_B

KVL $3.056 - (2.292k)I_B - 0.7 - (1.2k)(83+1)I_B = 0 \Rightarrow I_B = 23 \mu A$

So using the given ckt's:

$Q = (1.9mA, 6V)$

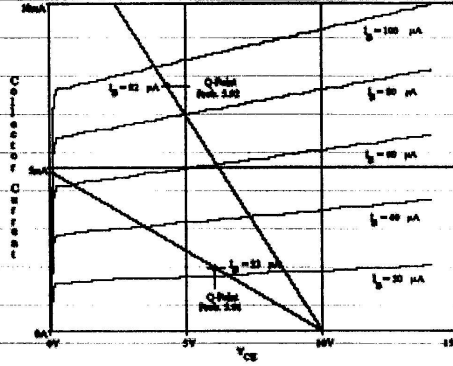

5.95

$$A) 5 - V_{EC} - (I_C + I_B)R_C - (-5) = 0 \Rightarrow R_C = \frac{10 - V_{EC}}{I_E} = \frac{7V}{I_E}$$

$$\text{but } I_E = \frac{\beta + 1}{\beta} I_C = 10.13 \text{ mA} \Rightarrow R_C = 691 \Omega \rightarrow 680 \Omega \text{ (practical value)}$$

$$\text{KVL } V_{EC} = V_{EB} + I_B R_B \Rightarrow R_B = \frac{V_{EC} - V_{EB}}{I_B} = \frac{3 - 0.7}{0.133 \text{ mA}} = 17.3 \text{ k}\Omega \rightarrow 18 \text{ k}\Omega$$

$$B) \text{ KVL } 5 - 0.7 - (18 \text{ k}) I_B - (0.68 \text{ k})(4 I_B) - (-5) = 0 \Rightarrow I_B = 202.7 \mu\text{A}$$

$$\therefore I_C = 8.108 \text{ mA}$$

$$\text{KVL } 5 - V_{EC} - (0.68 \text{ k})(4 I_B) = 0 \Rightarrow V_{EC} = 4.35 \text{ V}$$

$$\Rightarrow Q = (8.11 \text{ mA}, 4.35 \text{ V})$$

5.98

Read section 5.13

$$A) I = I_{REF} \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE}}{V_A} + \frac{2}{\beta_0}} = \frac{18V - 0.7V}{470 \text{ k}} \frac{(1+0)}{(1+0 + 2/40)} = 35.1 \mu\text{A}$$

$$B) I = \frac{18V - 0.7V}{470 \text{ k}} \frac{1 + \frac{18}{35}}{1 + \frac{0.7}{35} + \frac{2}{40}} = 52.1 \mu\text{A}$$

$$C) \text{ ④ } I = I_{REF} \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{BE}}{V_A} + \frac{2}{\beta_0}} = \frac{18V - 0.7V}{470 \text{ k}} \frac{1}{1 + 2/40} = 33.5 \mu\text{A}$$

$$\text{⑥ } I = \frac{18V - 0.7V}{470 \text{ k}} \frac{1 + \frac{18}{35}}{1 + \frac{0.7}{35} + \frac{2}{40}} = 49.8 \mu\text{A}$$