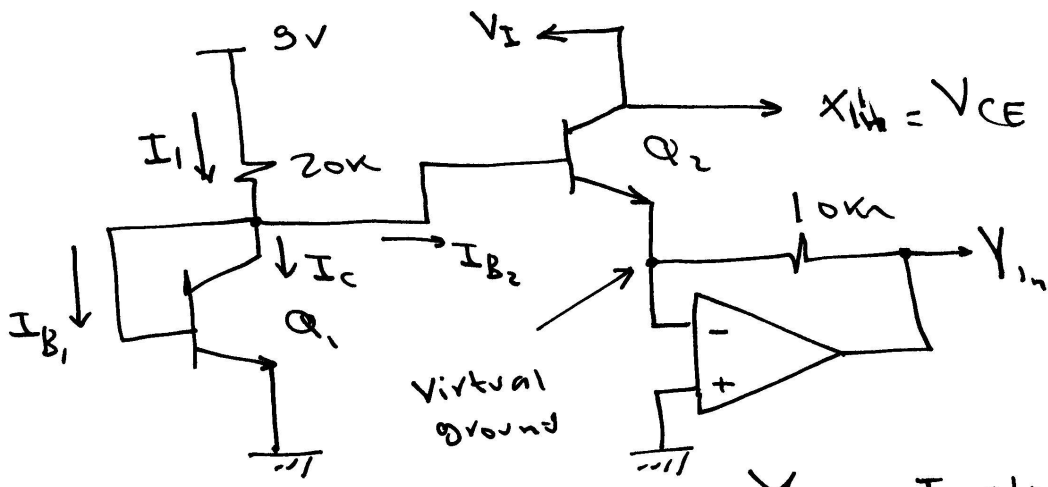


(1)



$$V_{BE1} = V_{BE2}$$

$$Y_{in} = -I_E \times 10k$$

$$Y_{in} \approx -I_C \times 10k$$

$V_{CB1} = 0 \Rightarrow Q_1$  in forward active region

Region

$$\frac{9 - V_{BE}}{20k} = (I_C + 2I_B)$$


$$\frac{9 - V_{BE}}{20k} = I_B (\beta + 2) = I_B (V_{BE}) (\beta + 2)$$

$$\text{or } V_{BE} \approx 0.7V$$

$$\therefore I_1 = \frac{9 - 0.7}{20k}$$

$$I_{B1} = I_{B2} = \frac{I_1}{(\beta + 2)}$$

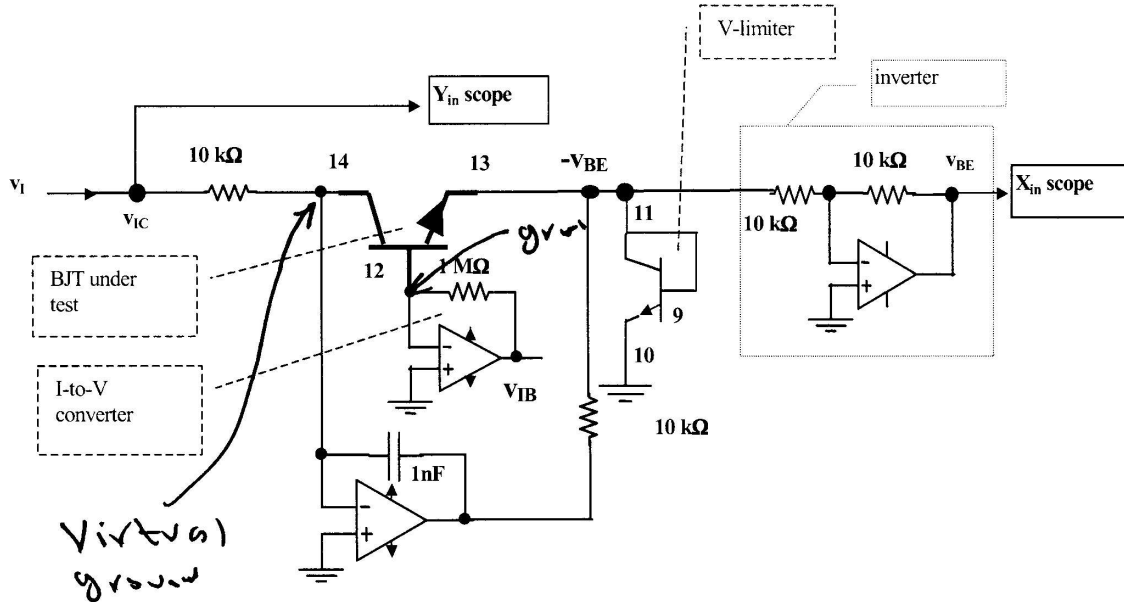
- L3. (a) Connect the circuit shown. Set the FG controls so that  $v_I$  is a triangle-wave of 100 Hz varying between 0 V and +5 V, i.e. +2.5 V dc offset. Hence display, *first* the  $i_C$  versus  $v_{BE}$  characteristic, and *then* the  $i_B$  versus  $v_{BE}$  characteristic, on the scope.



- L3. (b) Using the FG as a variable dc voltage source, adjust the dc offset control so that  $V_{IC}$  has the dc values in the following table:

$\beta_F = \beta_F$	$I_C$ [ $\mu A$ ]	$V_{IC}$ [Volts dc]	$V_{IB}$ [Volts dc]	$V_{BE}$ [Volts dc]	$\Delta V_{BE}$ [Volts dc]
		0.100			
		0.200			
		0.500			
		1.00			
		2.00			
		5.00			

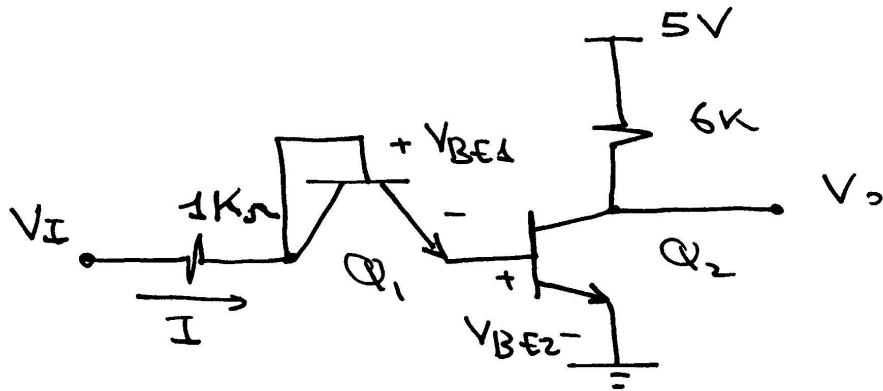Complete the table by measuring  $V_{IB}$  and  $V_{BE}$  with the digital scope (*mean* or dc value) or DMM.



if  $V_I = 0 \Rightarrow$  both  $Q_1$  and  $Q_2$  are off  $\Rightarrow V_0 = 5V$


if  $V_I = 5V$

$$I = \frac{5 - 1.4}{1k} = 3.6 \text{ mA}$$


$$I_{BE} = I_{E1} \approx I = 3.6 \text{ mA}$$

This very large current causes  $Q_2$  to saturate  $\Rightarrow V_0 \approx 0.2V$

INVERTER CIRCUIT

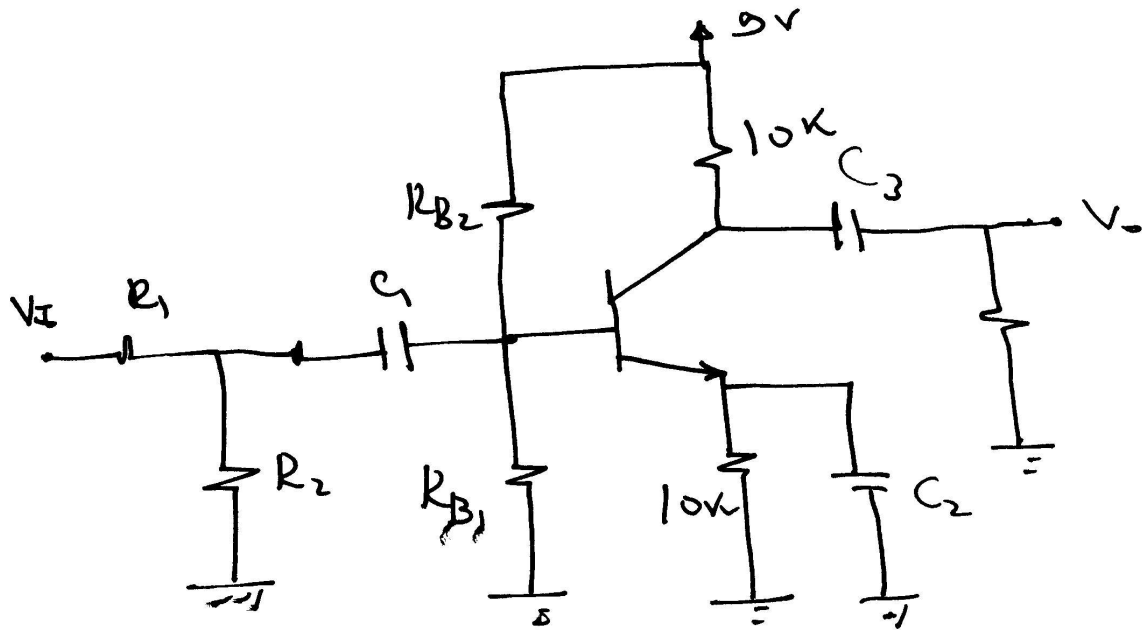

Dc Analysis

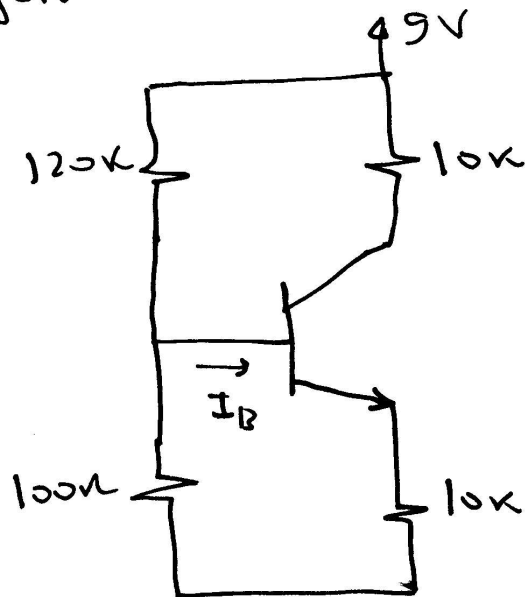

neglecting  $I_B$ , we get

$$V_B = 9 \times \frac{100k}{220k}$$

$$V_E = V_B - 0.7V$$

$$I_E = \frac{V_E}{10k}$$

$$I_C = I_E \times \alpha$$

operating point ( $V_{CE}$ ,  $I_C$ )

~~$V_{CE}$~~