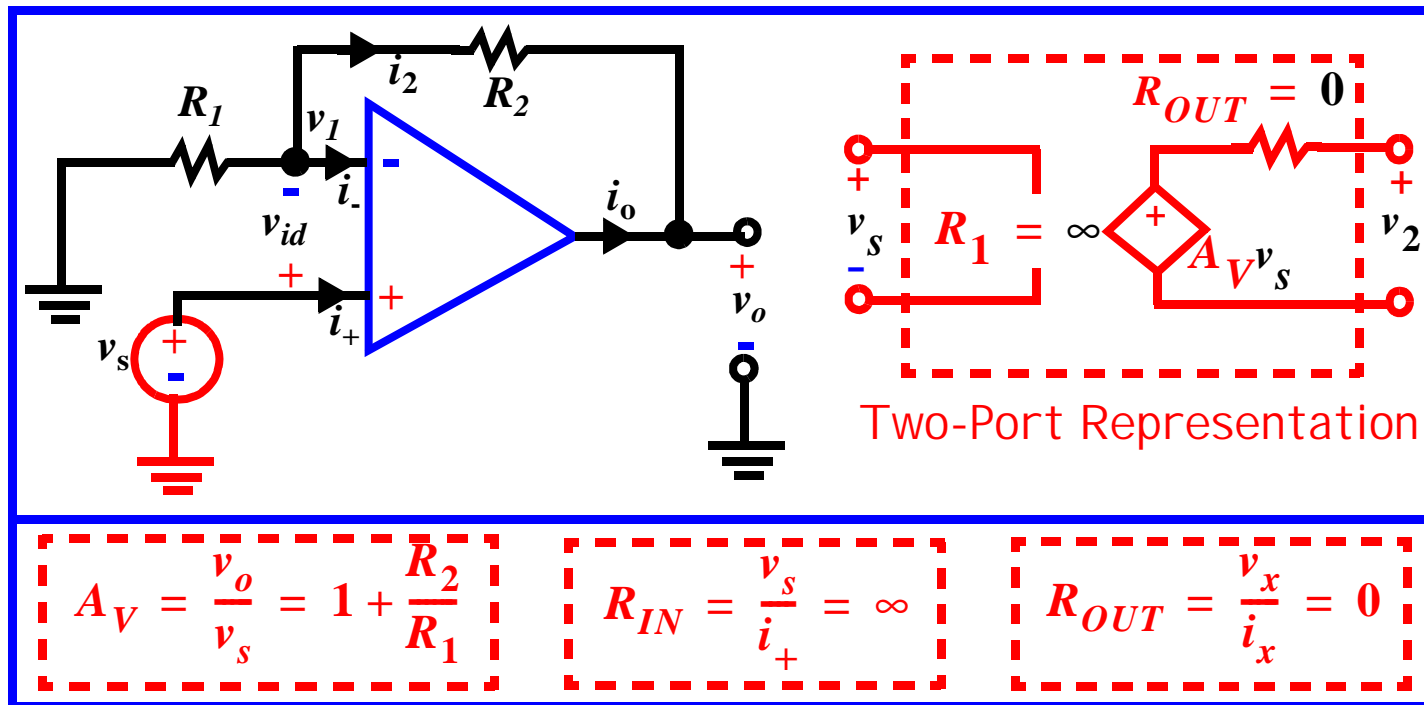


ECE 2E1 4 - Lecture 7

We will discuss the following topics

- Non-inverting amplifier
- Voltage follower
- Low Pass filter
- Integrator
- Two-port representation of amplifier
- Non-ideal non-inverting amplifier
- Gain error

The Non-Inverting Amplifier




Non-inv amp $v_- = \frac{R_1}{R_1 + R_2} v_o = \beta v_o$ & $v_o = A(v_+ - v_-) = A(v_s - \beta v_o)$.

Non-inv. amp., $A_V = \frac{v_o}{v_s} = \frac{A}{1 + A\beta} = \frac{1}{\beta} \cdot \frac{1}{1 + (A\beta)^{-1}}$.

$$A_{V, ideal} = \lim_{A\beta \rightarrow \infty} (A_V) = \frac{1}{\beta} = 1 + \frac{R_2}{R_1}$$

β is the **feedback factor**. It is the portion of the OP feedback to the IP.

The Non-Inverting Amplifier

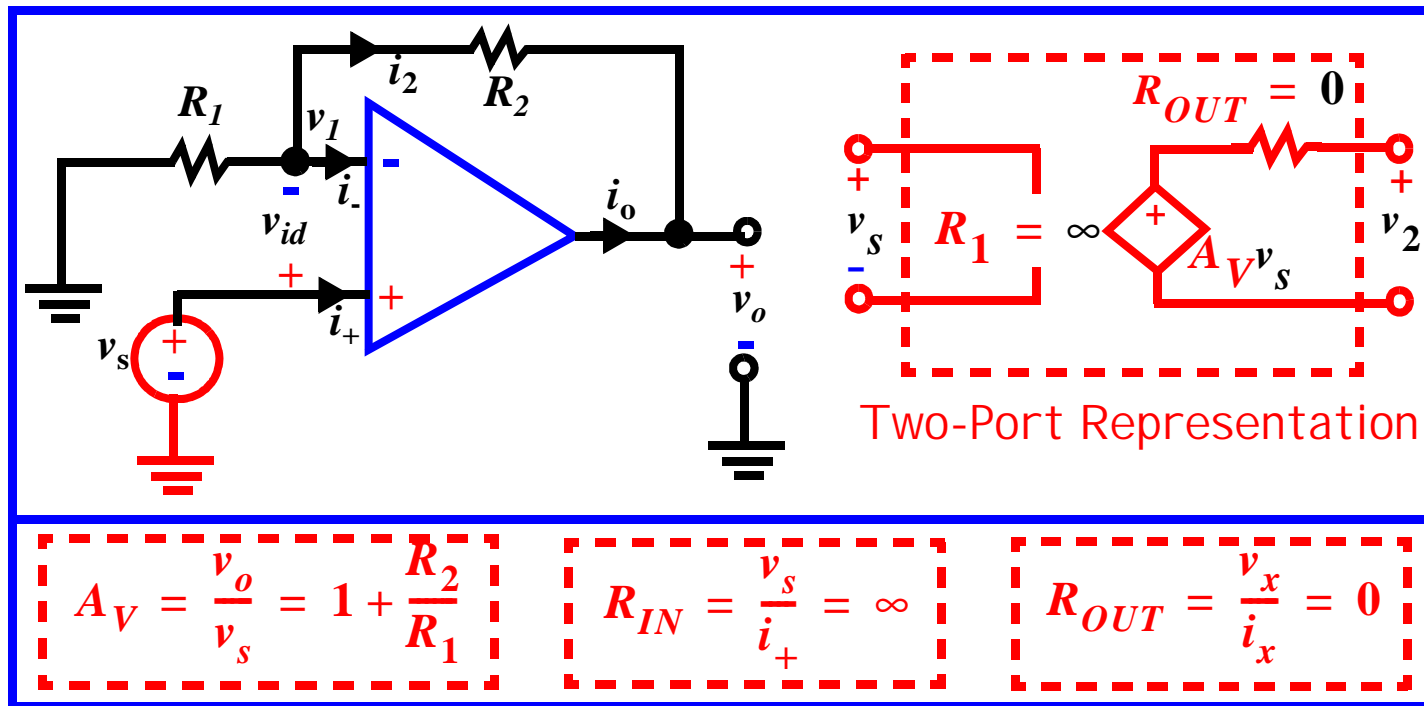

Now A_V depends only on the ratio of R's. This is important, e.g., R's can vary with temperature, but their ratio remains the same. That is, we **can make a stable circuit using unstable components**.


Also, OP and IP are in phase with each other (no phase shift).

Explain the **unity-gain buffer** or **voltage follower** used for **impedance transformation** with **unity voltage gain**.

The Voltage-Follower or Unity-Gain Amplifier

It is an ideal circuit that does not require any input current and can drive any R_L without loss of signal.

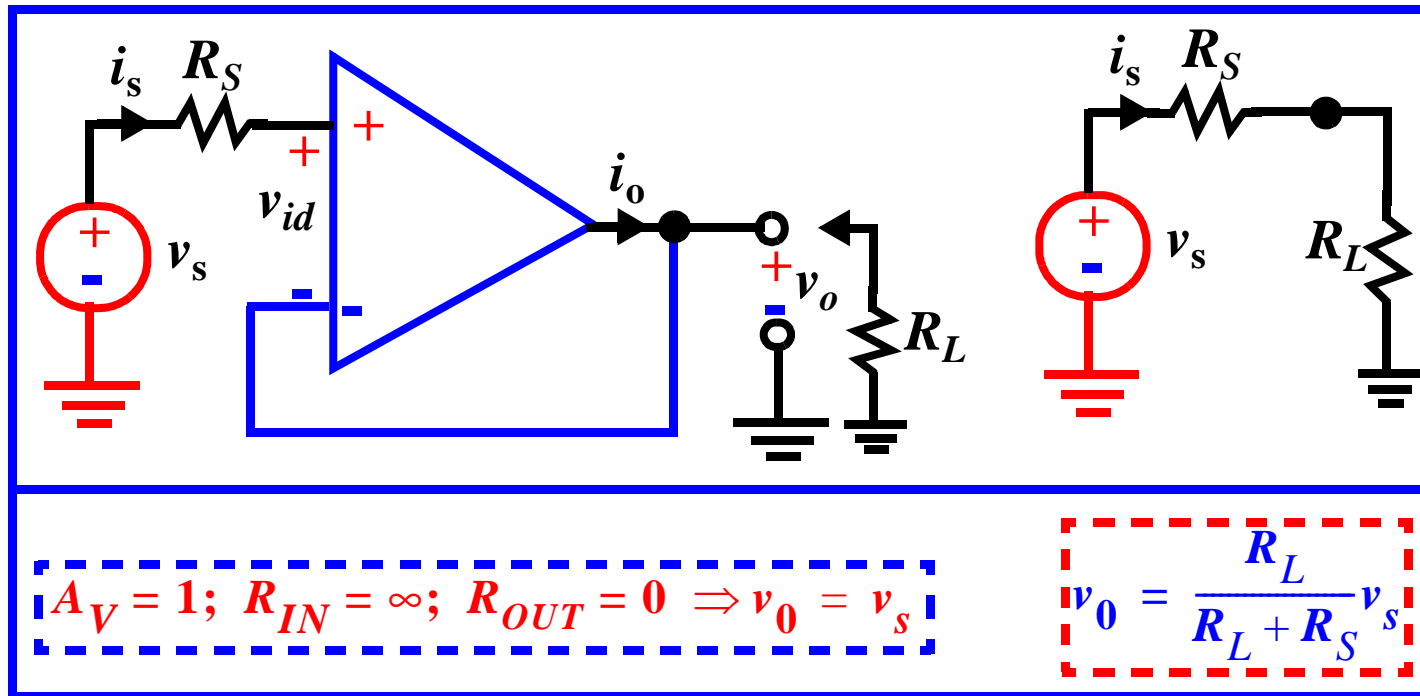Found in many sensor and data acquisition applications.



This is a resistance translator. The source delivers no current; dissipates no energy; current and energy absorbed by R_L is supplied by OA.


Table 1: Summary of Ideal Amplifier Characteristics

| Characteristic | Inverting | Non-Inverting | Buffer |
|-----------------------------|--------------|-----------------|----------|
| Voltage Gain A_V | $-(R_2/R_1)$ | $1 + (R_2/R_1)$ | 1 |
| Input Resistance R_{IN} | R_1 | ∞ | ∞ |
| Output Resistance R_{OUT} | 0 | 0 | 0 |

Please read - summing, difference & instrumentation amplifiers
(p. 497 - 500)

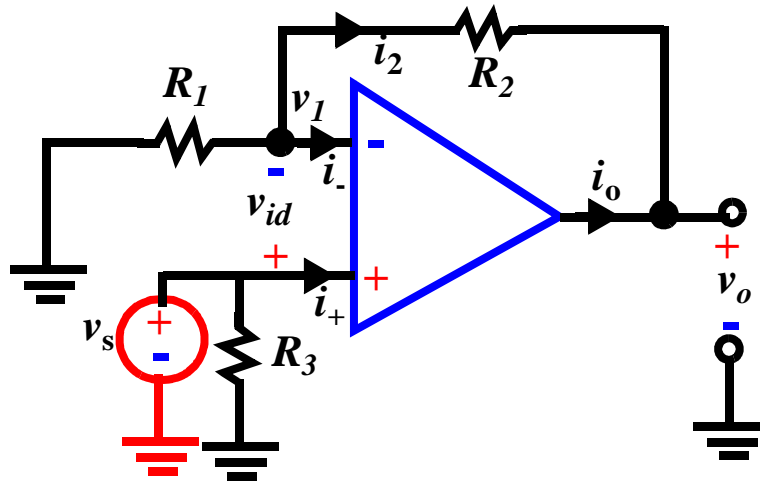Example:

What are the voltage gain, input resistance, and output resistance of the following circuit if $R_1 = 10k\Omega$, $R_2 = 100k\Omega$, and $R_3 = 200k\Omega$?




$$A_V = 1 + \frac{R_2}{R_1} = 1 + \frac{100k}{10k} = 11$$

$$R_{IN} = R_3 \parallel \infty = R_3 = 200k\Omega$$

$$R_{OUT} = 0\Omega$$

Low Pass Filter

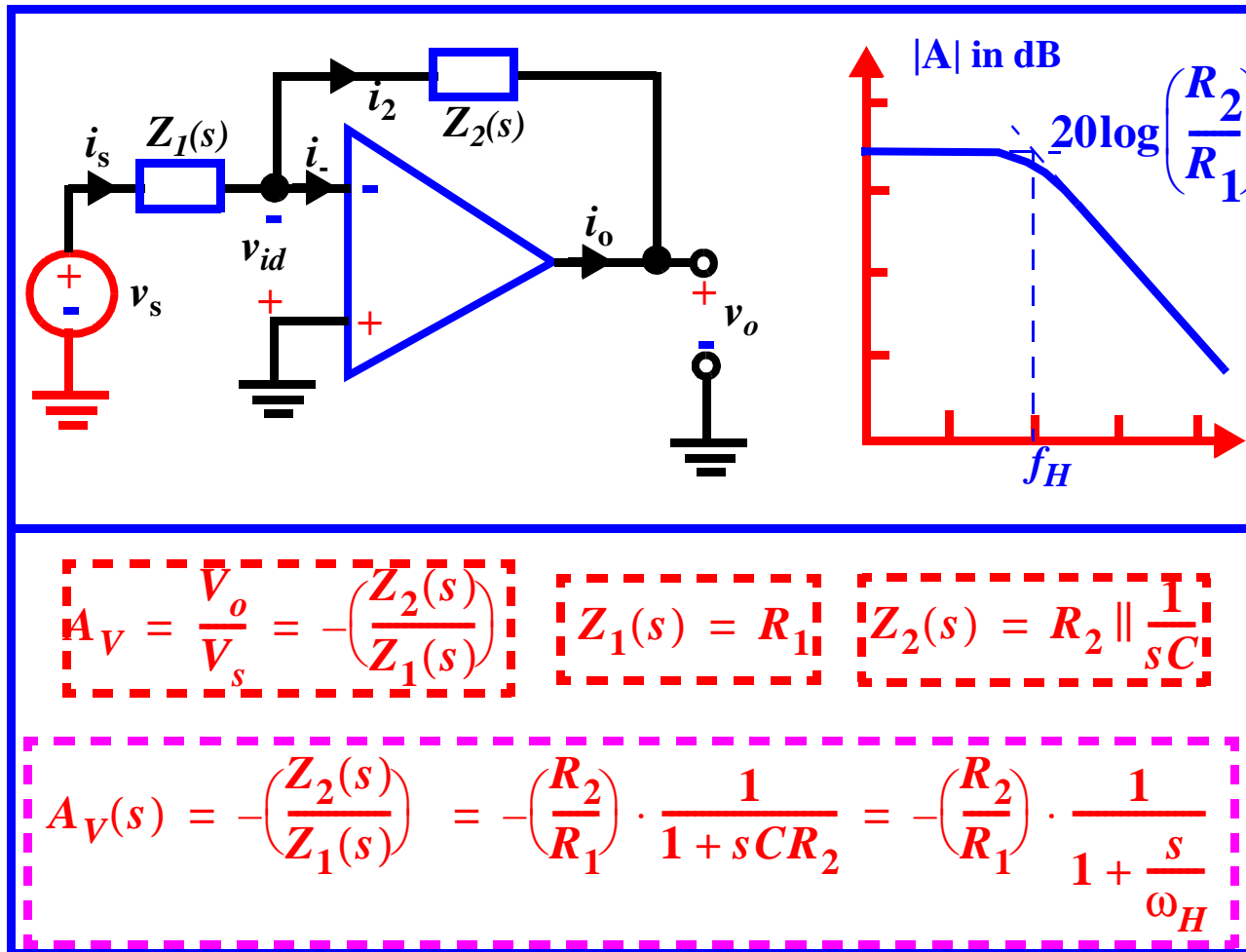


Two design parameters - low frequency gain and 3dB frequency can be set independently since we have 3 parameters - R_1 , R_2 and C .

Input resistance $R_{IN} = R_1$ can be third design parameter.

The 3-dB frequency is $f_H = 1/2\pi R_2 C$. Question: What happens if $R_2 \gg R_1$?

Integrator (Please read carefully)

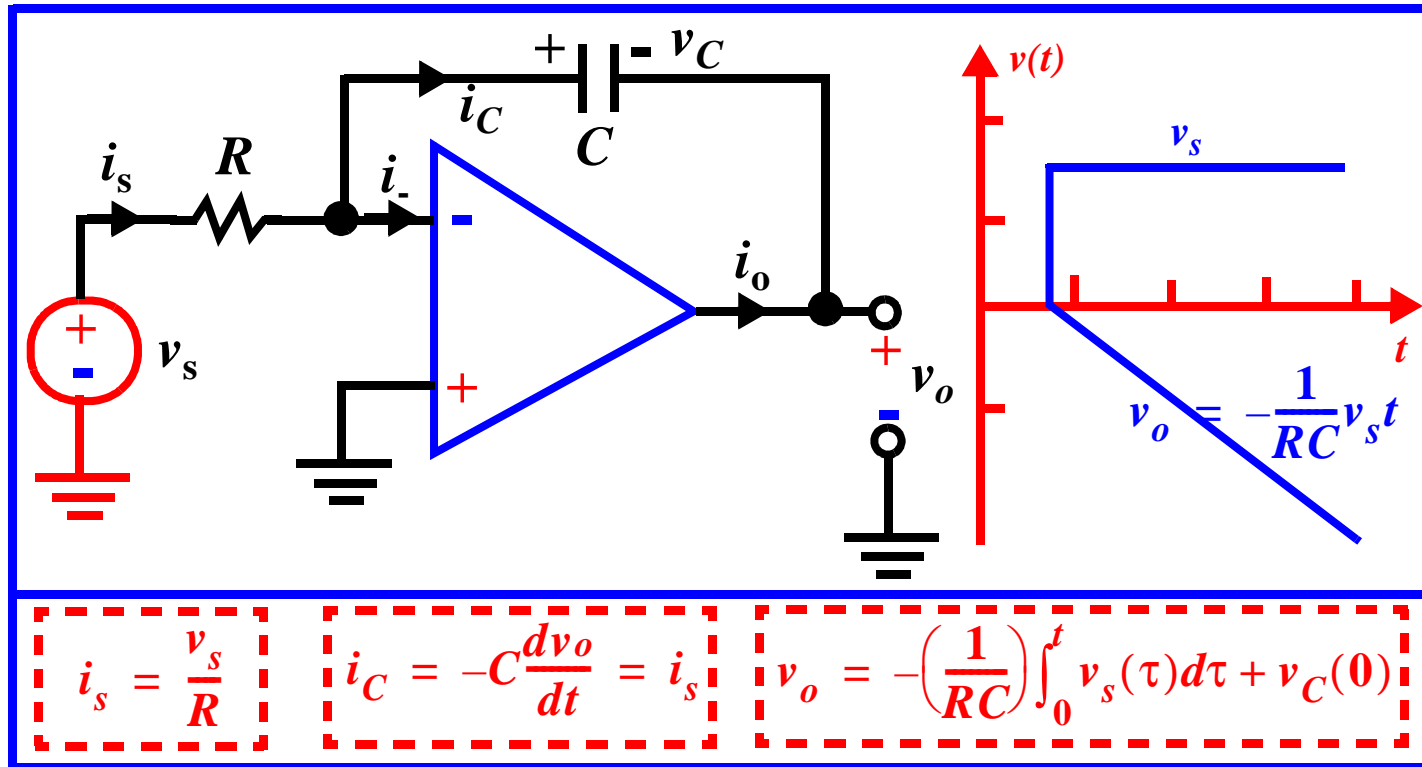


Used in function generators (triangular and sawtooth wave generators), active filters, ADC and analog control.

Two design parameters - R and C.


Input resistance $R_{IN} = R_1$ can be third design parameter.

Two Port Representations - The Inverting Amplifier

(Please read carefully)

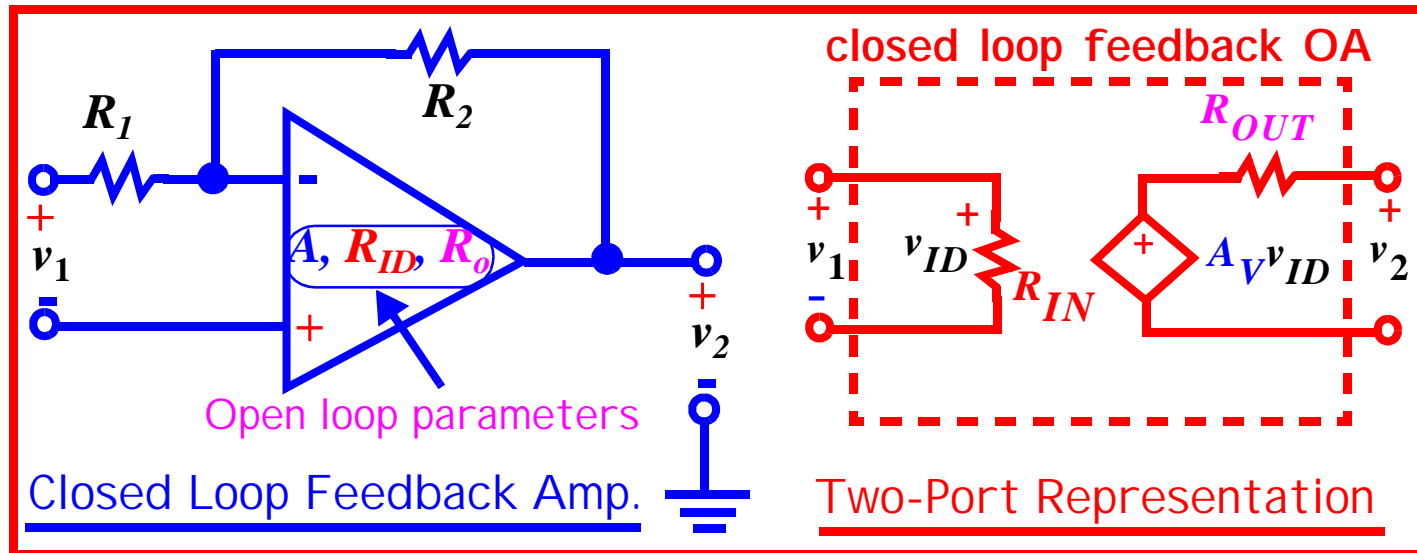

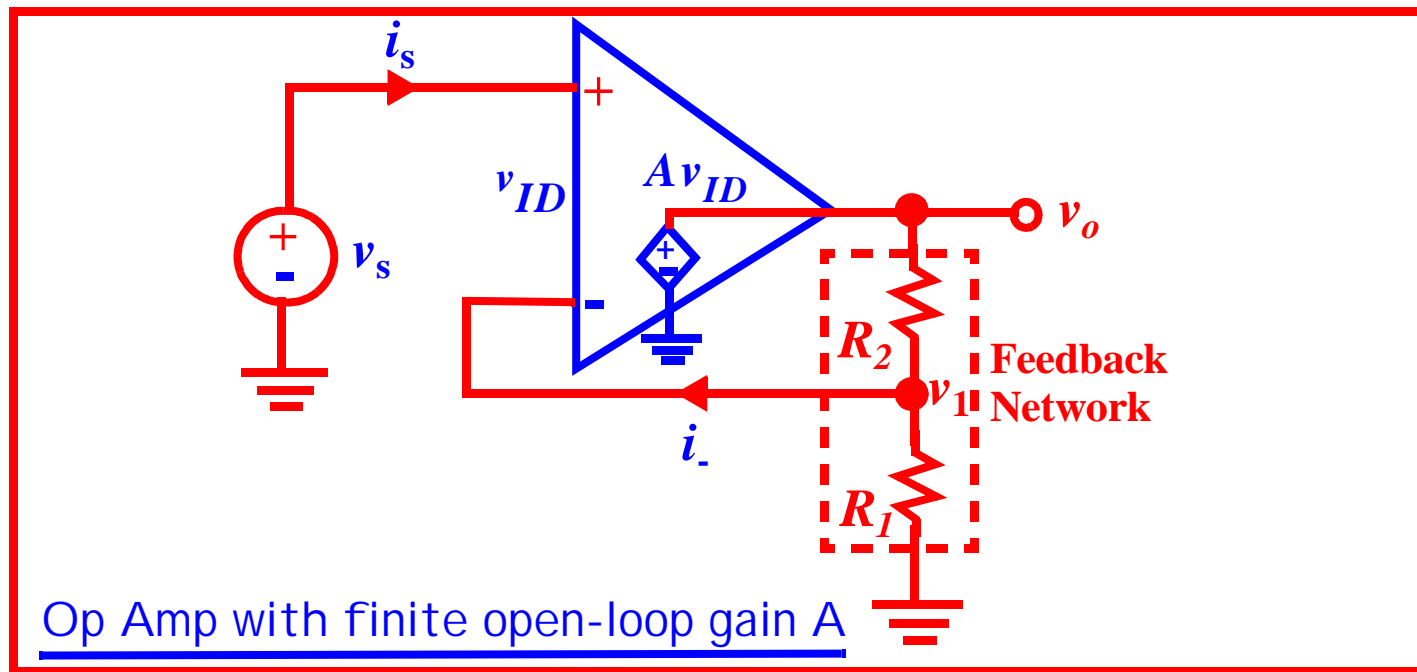Non-Ideal Non-Inverting Amplifier (Please read carefully)



$$v_o = A \cdot v_{id} = A \cdot (v_s - v_1); \quad v_1 = \frac{R_1}{R_1 + R_2} \cdot v_o = \beta \cdot v_o.$$

$$v_o = A \cdot (v_s - \beta \cdot v_o); \quad A_V = \frac{v_o}{v_s} = \frac{A}{1 + A\beta}; \quad A_{ideal} = \frac{1}{\beta} = 1 + \frac{R_2}{R_1}.$$

$$v_{id} = v_s - v_1 = v_s - \beta \cdot v_o = v_s - \frac{A\beta}{1 + A\beta} v_s = \frac{v_s}{1 + A\beta}.$$

Gain Error

Gain Error= Ideal Gain-Actual Gain

Relative Gain Error=(Ideal Gain-Actual Gain)/(Ideal Gain)

$$GE = \frac{1}{\beta} - \frac{A}{1+A\beta} = \frac{1}{\beta(1+A\beta)}$$

$$FGE = \frac{\frac{1}{\beta} - \frac{A}{1+A\beta}}{\beta^{-1}} = \frac{1}{(1+A\beta)} \approx \frac{1}{A\beta} \text{ for } A\beta \gg 1$$



Example: For a non-inverting amplifier, find v_{id} , v_o and FGE if $A = 10^5$, $\beta = 10^{-2}$, $v_s = 100\text{mV}$.

$$v_{id} = \frac{v_s}{1+A\beta} \approx 100\mu\text{V} \text{ Recall } v_{id} = v_s - v_1 = v_s - \beta \cdot v_o = v_s - \frac{A\beta}{1+A\beta} v_s = \frac{v_s}{1+A\beta}$$

$$v_o = A_v \times v_s \approx 10\text{V} \text{ Recall } A_v = \frac{v_o}{v_s} = \frac{A}{1+A\beta}$$

$$FGE = \frac{1}{(1+A\beta)} \approx 10^{-3}$$

PSpice Example

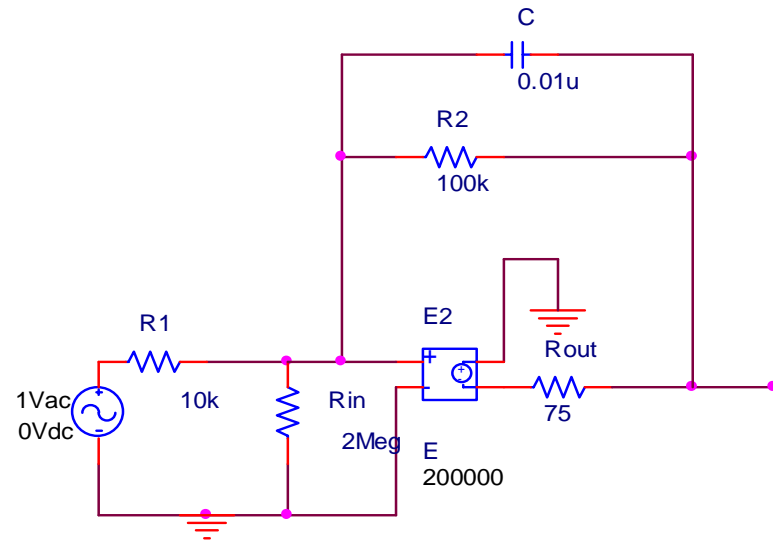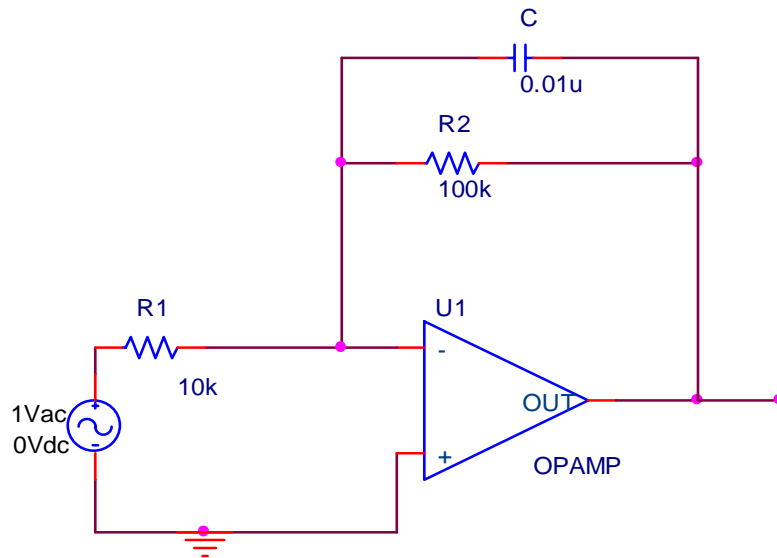

*Libraries:

* Local Libraries :

* From [PSPICE NETLIST] section of C:\Program Files\OrCAD\PSpice\PSpice.ini file:

```
.lib "nom.lib"
```

*Analysis directives:

```
.AC LIN 50 1 1k
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.INC ".\example3-SCHEMATIC1.net"
```

```
**** INCLUDING example3-SCHEMATIC1.net ****
```

* source EXAMPLE3

```
E_E2      0 N004843 N00983 0 200000
```

```
V_V7      N042211 0 DC 0Vdc AC 1Vac
```

PSpice Example (Cont'd)

R_Rout N004843 N04056 75

R_R1 N042211 N00983 10k

R_Rin 0 N00983 2Meg

C_C N00983 N04056 0.01u

R_R2 N00983 N04056 100k

**** RESUMING example3-SCHEMATIC1-Examp13Profile.sim.cir ****

.END

