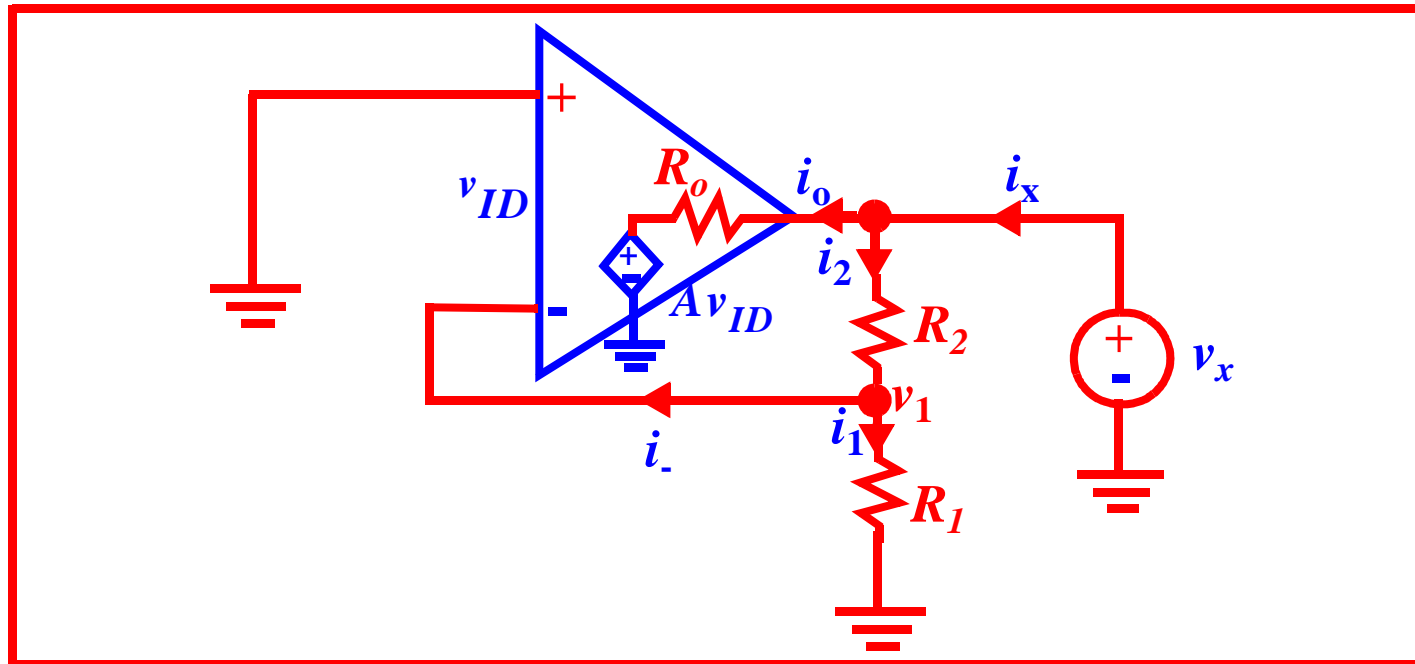


ECE 2EI 4 - Lecture 8

Non-Zero Output Resistance - Non-Inv. Amplifier




$$v_1 = \frac{R_1}{R_1 + R_2} \cdot v_x = \beta v_x; \quad i_x = i_o + i_2 = \frac{v_x - Av_{ID}}{R_o} + \frac{v_x}{R_1 + R_2};$$

$$v_1 = -v_{ID} = \beta v_x. \text{ Therefore, } \frac{1}{R_{OUT}} = \frac{i_x}{v_x} = \frac{1 + A\beta}{R_o} + \frac{1}{R_1 + R_2}.$$

$$R_{OUT} = \frac{R_o}{1 + A\beta} \parallel (R_1 + R_2) \approx \frac{R_o}{1 + A\beta} \approx \frac{R_o}{A\beta}.$$

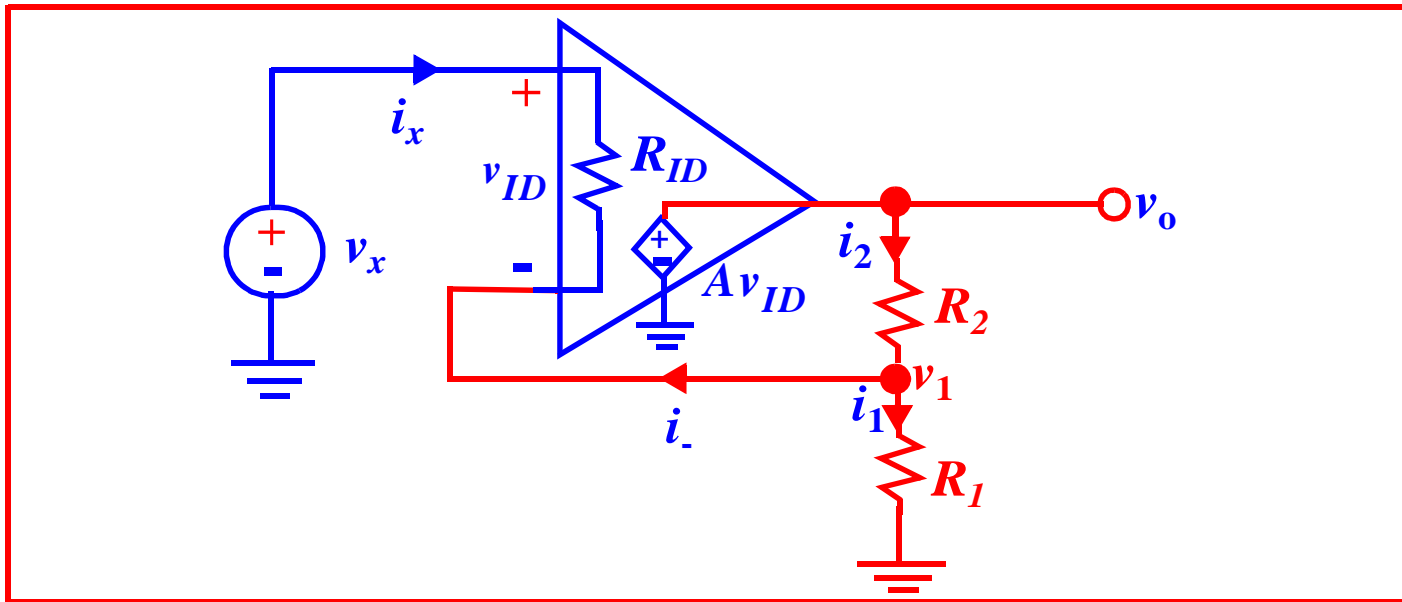Finite Input Resistance- Non-Inv. Amplifier




$$v_1 \approx \frac{R_1}{R_1 + R_2} \cdot v_o = \beta v_o = \beta A v_{ID} = A \beta (v_x - v_1).$$

$$v_1 = \frac{A \beta}{1 + A \beta} v_x \quad \text{and} \quad i_x = \frac{v_x - \frac{A \beta}{1 + A \beta} v_x}{R_{ID}} = \frac{v_x}{(1 + A \beta) R_{ID}}$$

Since $R_{IN} = v_x / i_x$, then $R_{IN} = R_{ID} \cdot (1 + A \beta) \approx A \beta R_{ID}$.

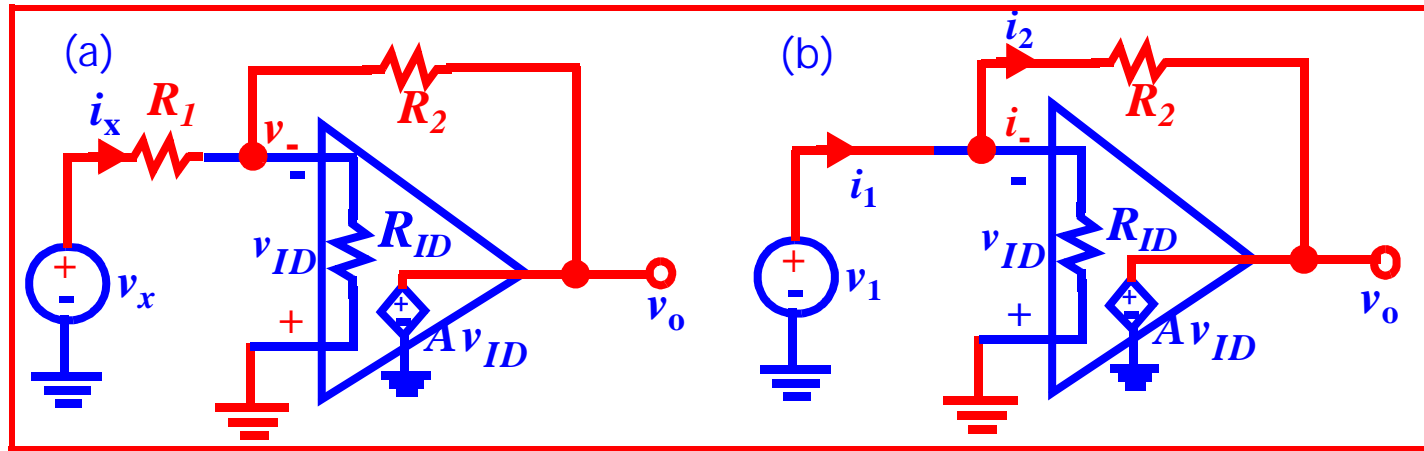Input Resistance for Inverting Amplifier (Read carefully)



$$R_{IN} = \frac{v_x}{i_x}; v_x = i_x R_1 + v_- \text{ so, we get that } R_{IN} = R_1 + \frac{v_-}{i_x}.$$

Total input resistance $R_{IN} = R_1 +$ Resistance looking into the inverting terminal of the amplifier (use second circuit (b) above)

$$i_1 = i_- + i_2 = \frac{v_1}{R_{ID}} + \frac{v_1 - v_0}{R_2} = \frac{v_1}{R_{ID}} + \frac{v_1(1+A)}{R_2} \text{ since } v_0 = -Av_1.$$

$$G_{1,IP} = \frac{i_1}{v_1} = \frac{1}{R_{ID}} + \frac{1+A}{R_2} \text{ or } R_{1,IP} = R_{ID} \parallel \frac{R_2}{1+A}.$$

In ckt (a), overall R_{IN} is $R_{IN} = R_1 + R_{ID} \parallel \frac{R_2}{1+A} \approx R_1 + \frac{R_2}{1+A} \approx R_1.$


Comparison of Inv. and Non-Inv. Amplifier

(Read carefully)

	Inverting Amplifier	Non-Inverting Amplifier
Voltage Gain A_V	$-\frac{R_2}{R_1} \left(\frac{A\beta}{1+A\beta} \right) \approx -\frac{R_2}{R_1}$	$\left(\frac{A}{1+A\beta} \right) \approx \frac{1}{\beta} = 1 + \frac{R_2}{R_1}$
Input Resistance R_{IN}	$R_1 + R_{ID} \parallel \frac{R_2}{1+A} \approx R_1$	$R_{ID} \cdot (1 + A\beta)$
Output Resistance R_{OUT}	$\frac{R_O}{1+A\beta} \approx \frac{R_O}{A\beta}$	$\frac{R_O}{1+A\beta} \approx \frac{R_O}{A\beta}$

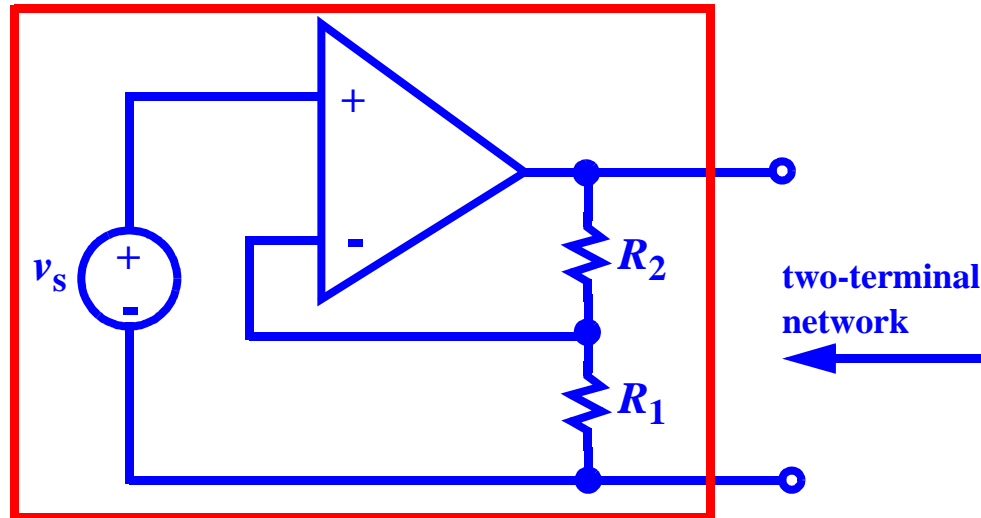Example:

The following circuit is a two-terminal network with $R_1 = 400\Omega$ and $R_2 = 60k\Omega$. What is its Thevenin equivalent circuit if the operational amplifier has $A = 2 \times 10^4$, $R_{ID} = 200k\Omega$, and $R_O = 100\Omega$?




$$A\beta = (2 \times 10^4) \left(\frac{400}{400 + 60k} \right) = 132$$

The open circuit voltage is $v_{th} = \frac{A}{1 + A\beta} v_s = \frac{2 \times 10^4}{1 + 132} v_s = 150 v_s$.

$$R_{th} = R_{OUT} = \frac{R_O}{1 + A\beta} = \frac{100}{1 + 132} = 0.749\Omega$$

Finite Common Mode Rejection Ratio

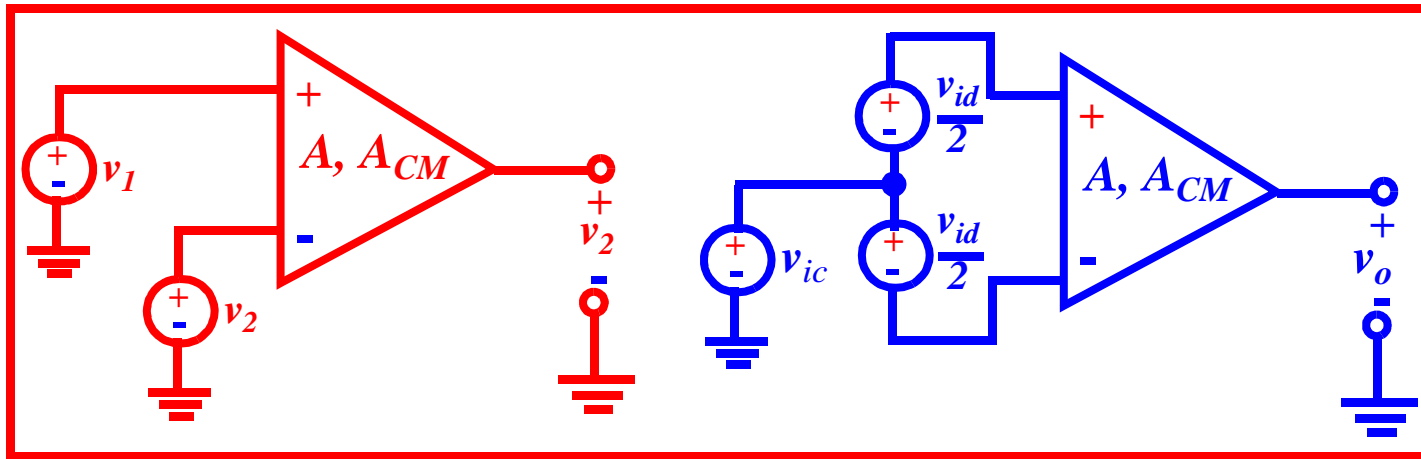


$$v_{ic} = \frac{v_1 + v_2}{2} ; v_o = A(v_1 - v_2) + A_{CM}\left(\frac{v_1 + v_2}{2}\right) = Av_{id} + A_{CM}v_{ic}$$

$$v_1 = v_{ic} + \frac{v_{id}}{2} ; v_2 = v_{ic} - \frac{v_{id}}{2}$$

$$v_o = A\left(v_{id} + \frac{A_{CM}v_{ic}}{A}\right) = A\left(v_{id} + \frac{v_{ic}}{CMRR}\right)$$

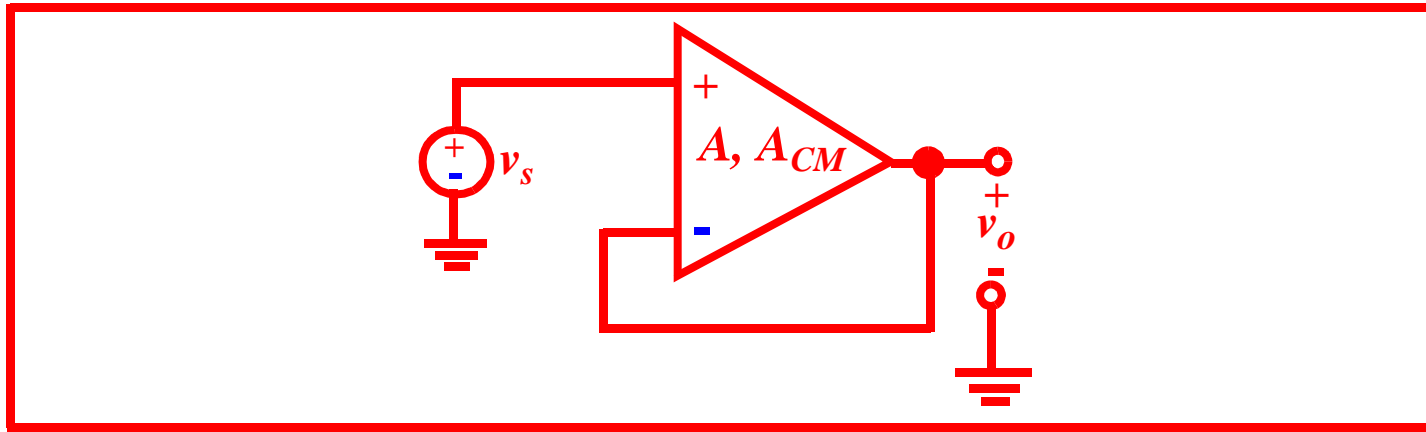Voltage-Follower Gain Error Due to CMRR (Read carefully)



$$v_{id} = v_s - v_o \quad \text{and} \quad v_{ic} = \frac{v_s + v_o}{2}.$$

$$v_o = A \left(v_s - v_o + \frac{v_s + v_o}{2 \cdot CMRR} \right).$$

$$A_V = \frac{v_o}{v_s} = \frac{A(1 + \{2 \cdot CMRR\}^{-1})}{1 + A(1 - \{2 \cdot CMRR\}^{-1})} \quad \text{and the Gain Error is } A_{v,ideal} - A_{v,actual}$$

Gain Error Due to CMRR (Read carefully)

$$GE = 1 - \frac{A(1 + \{2 \cdot CMRR\}^{-1})}{1 + A(1 - \{2 \cdot CMRR\}^{-1})} = \frac{(1 - A \cdot CMRR^{-1})}{1 + A(1 - \{2 \cdot CMRR\}^{-1})}$$

$$GE \approx A^{-1} - CMRR^{-1}$$


A^{-1} => error due to finite gain

$CMRR^{-1}$ => error due to finite CMRR

PSRR

PSRR is a parameter closely related to CMRR and is a measure of the ability of the Op Amp to reject variations in the power supply. It is the change in I P voltage per unit change in power supply voltage. It is $PSRR = \frac{\Delta V_{input}}{\Delta V_{supply}}$ in dB or $\mu V/V$. Its values are similar to CMRR.

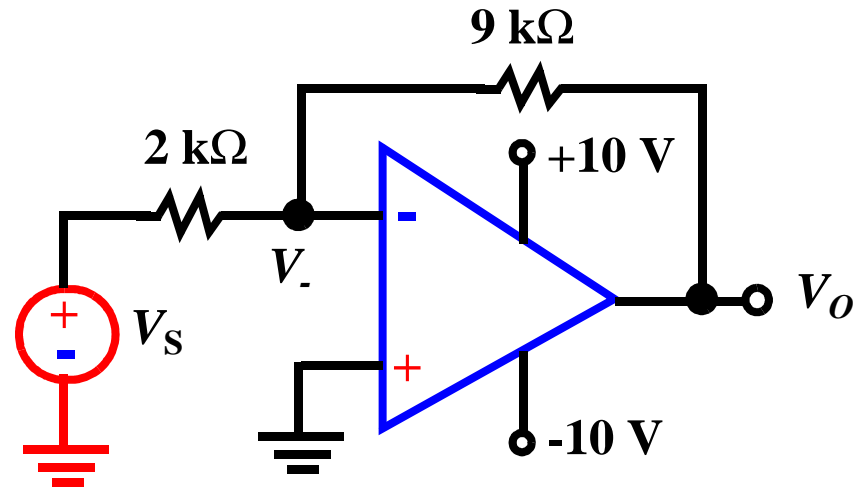Example: The output-voltage range of the op amp in the following figure is equal to the power supply voltages. What are the values of V_o and V_- for the amplifier if the dc input V_S is (a) -2 V and (b) 4 V ?



Inverting Amplifier: $v_o = A_V v_S = -\frac{9k}{2k} v_S = -4.5v_S$ as long as $|v_o| \leq 10V$ as restricted by the op amp power supply voltages.

(a) $V_o = -4.5(-2) = 9V$, feedback loop is working and $V_- = 0V$


(b) $V_o = -4.5(4) = -18V$; V_o saturates at $V_o = -10V$.

The feedback loop is broken since the open-loop gain is now 0.

The output voltage does not change when the input changes so $A = 0$.

By superposition, $V_- = 4\left(\frac{9k}{2k + 9k}\right) - 10\left(\frac{2k}{2k + 9k}\right) = 1.45V$

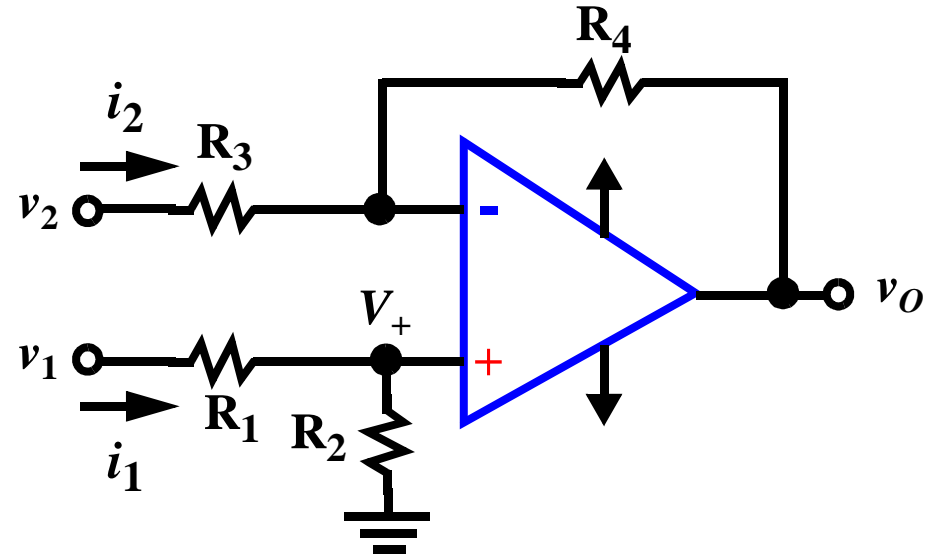Example: (a) Use ideal op amp assumptions to derive an expression for the output voltage of the following circuit. (b) Find the input resistance presented to v_1 and v_2 .



(a) **Inv. Input:** $v_O = \left(-\frac{R_4}{R_3}\right)v_2$

Non-inv. Input: $v_O = \left(1 + \frac{R_4}{R_3}\right)v_+ = \left(1 + \frac{R_4}{R_3}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_1$

Superposition: $v_O = \left(-\frac{R_4}{R_3}\right)v_2 + \left(1 + \frac{R_4}{R_3}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_1$

(b) for v_1 , $R_{IN} = \left.\frac{v_1}{i_1}\right|_{v_2=0} = R_1 + R_2$

for v_2 , $R_{IN} = \left.\frac{v_2}{i_2}\right|_{v_1=0} = R_3$

(Verify Results using PSpice)