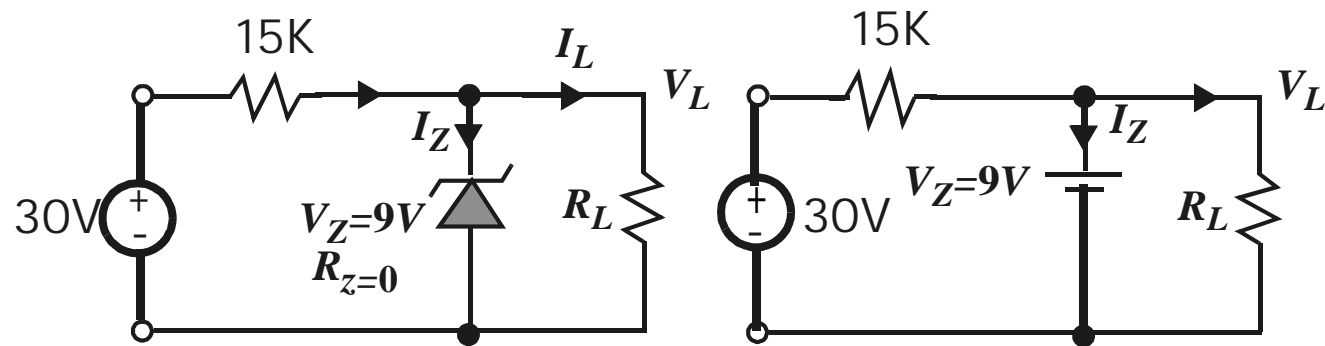


## Lecture 13

- More on Zener regulation
- Limiter/clipper circuits
- Clamping and peak detection circuits
- Half-wave rectifiers

## Zener Example




Find the maximum load current and the corresponding load resistance to maintain a regulated output
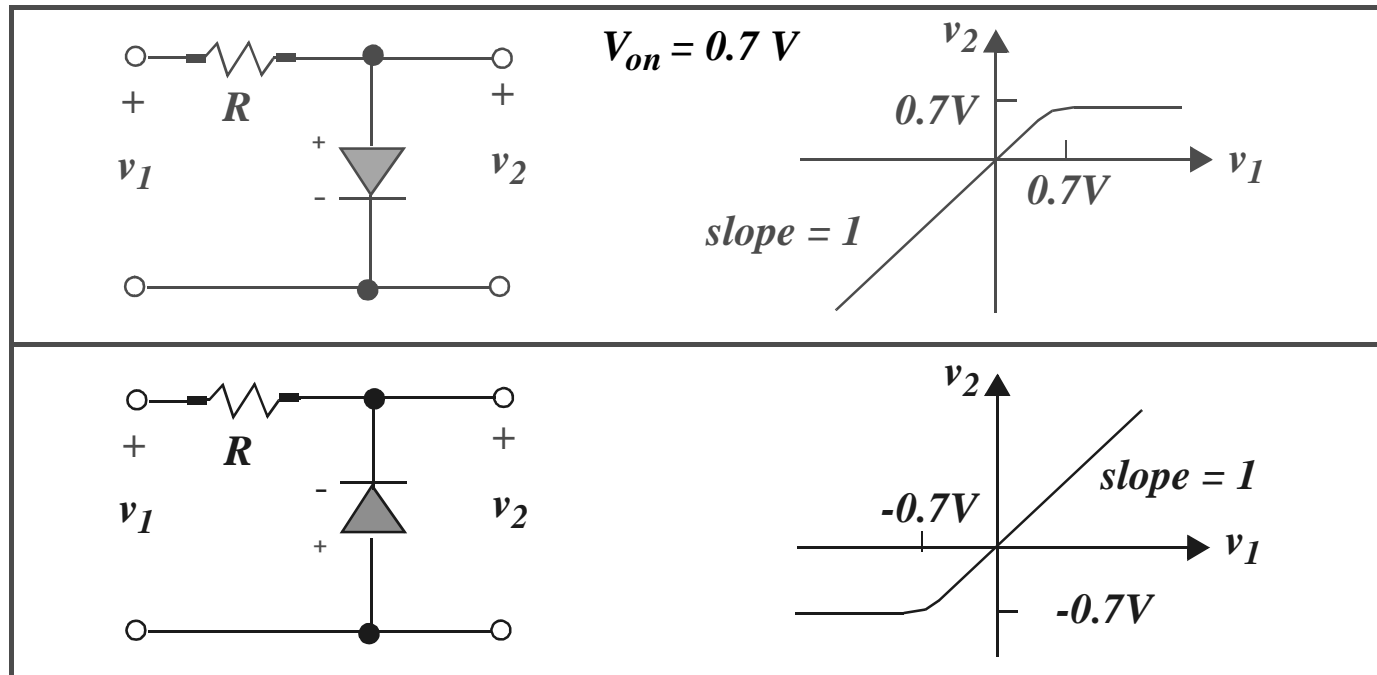
## Limiters or Clipper Circuits

Used in signal processing circuits; Limits voltage between I Ps of Op-Amp.

Provides  $v_{out} \propto v_{in}$  up to a certain value(s), beyond which voltage is clipped off.




## Limiters or Clipper Circuits

Used in signal processing circuits;

Limits voltage between two inputs of Op-Amp.

Provides  $v_{out} \propto v_{in}$  up to a certain value(s), beyond which voltage is clipped

off.

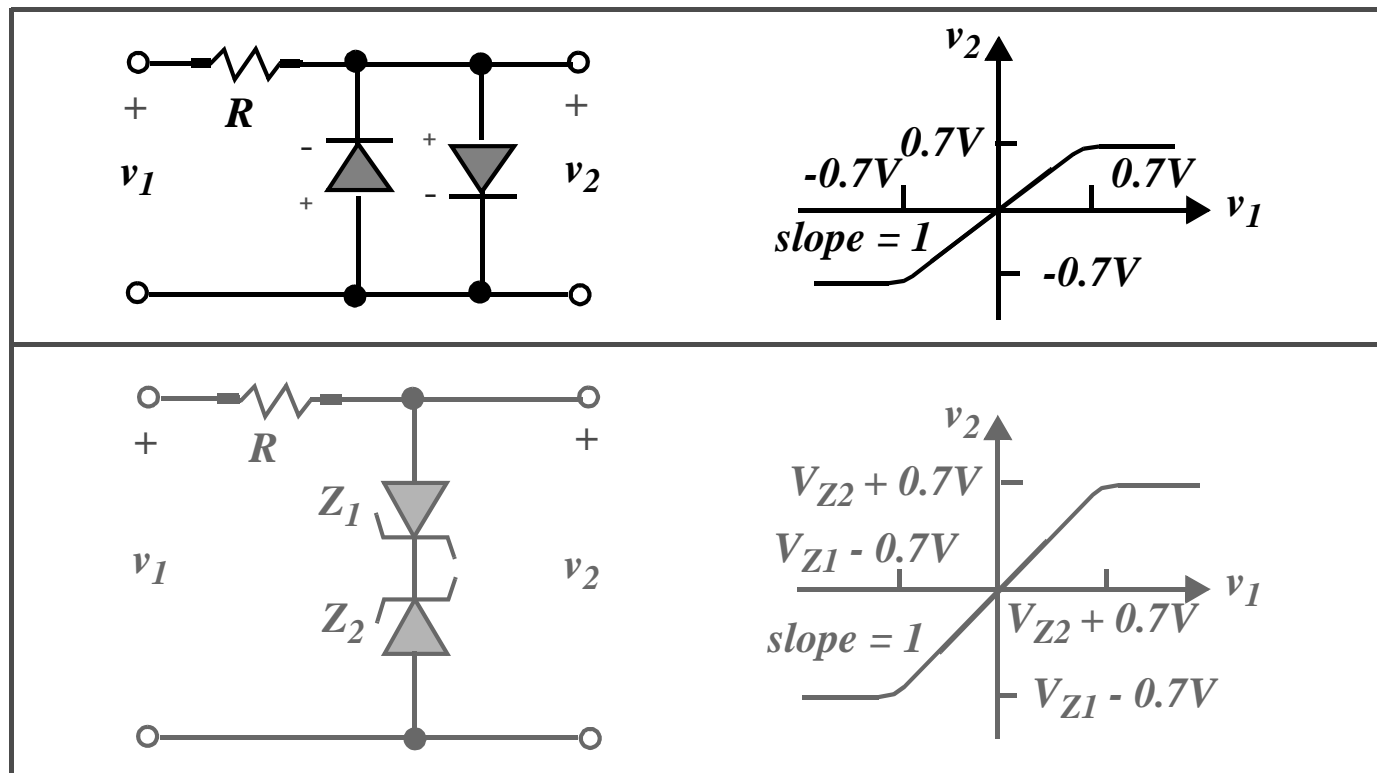


## Clamping Circuits


In TV receivers, peak values of certain signals must be held clamped to pre-determined levels

Provides  $v_{out} \propto v_{in}$  but clamps  $v_{out}$  to a certain value.

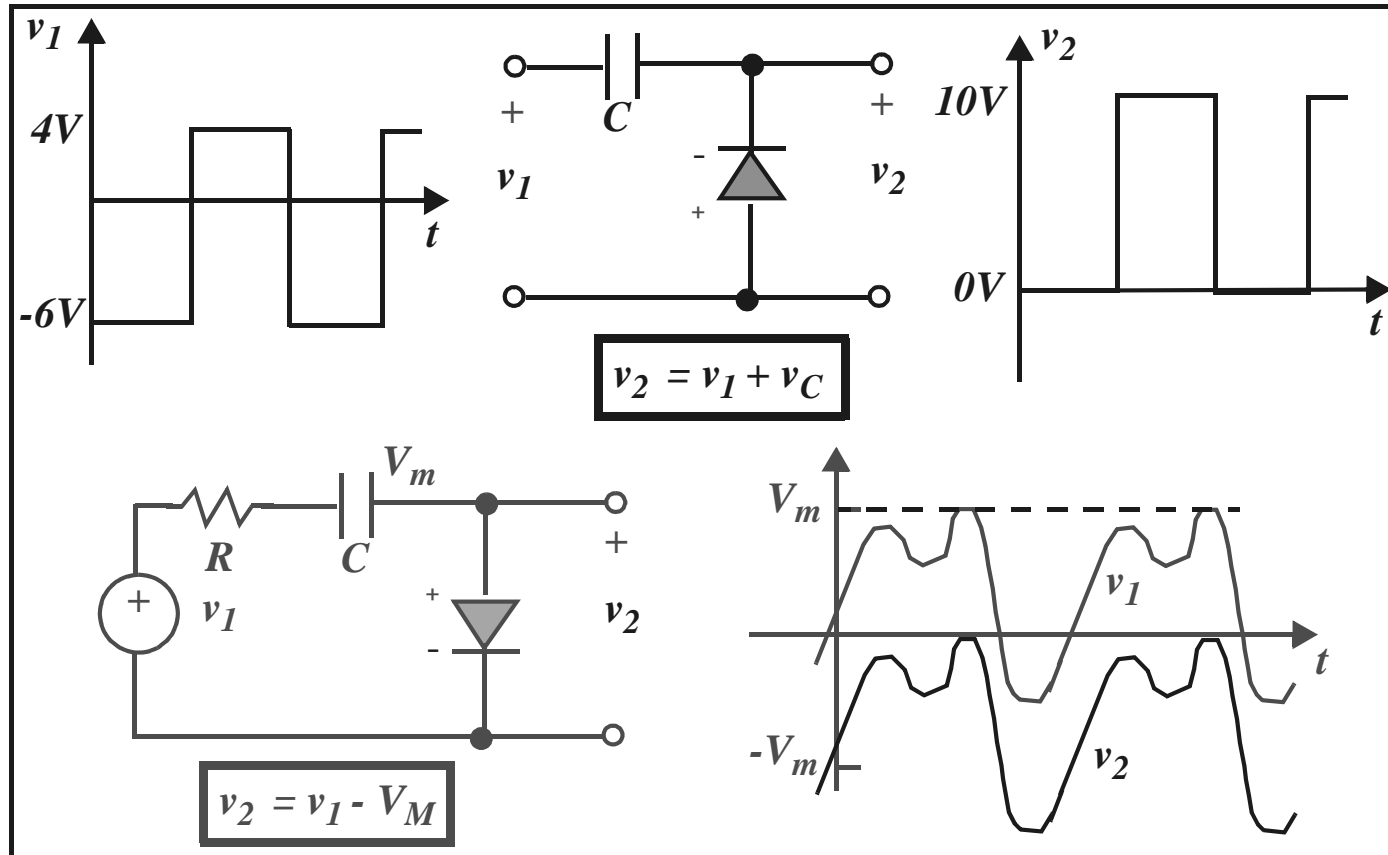In clamping, the variable component of  $v_{in}$  is transmitted and the dc value is restored.



## More Diode Clamping Circuits

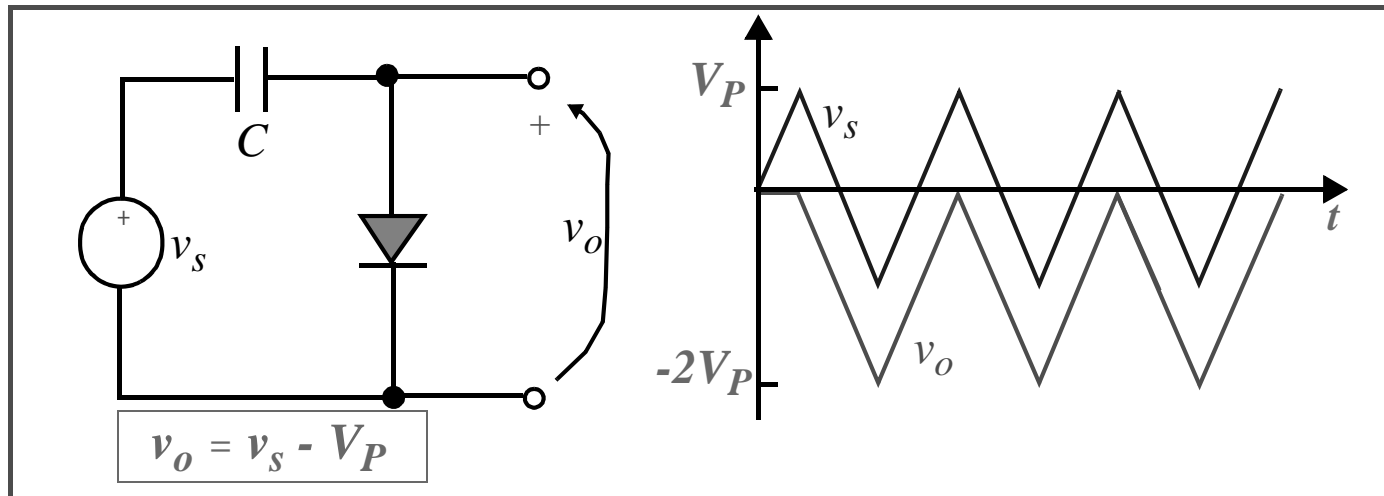

$v_s$  increases ( $> 0$ ), diode turns on,  $v_o = 0$ ,  $C$  charges up,  $v_C = v_s$ .

$v_s$  decreases from peak, diode turns off,  $v_o = v_s - V_P$ .


No discharge path and  $v_C = V_P$ . Waveform peak clamped to 0.

## More Diode Clamping Circuits

Here, initial transient lasts for 3/4 cycle.

When  $v_s > 0$ , diode is reverse biased initially,  $v_o = v_s$ .

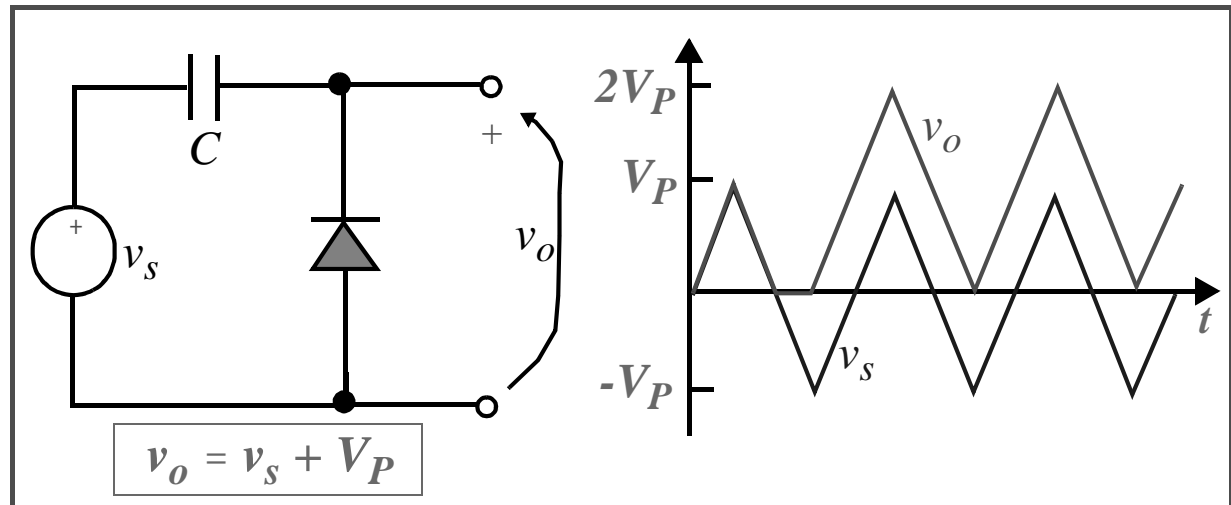
However, when  $v_s < 0$  but increasing, diode turns on,  $v_C = -V_P$ .



After initial transient for 3/4 cycle,  $v_o = V_P + v_s$ .


Waveform minimum value clamped to zero.

## Peak Detector Circuit

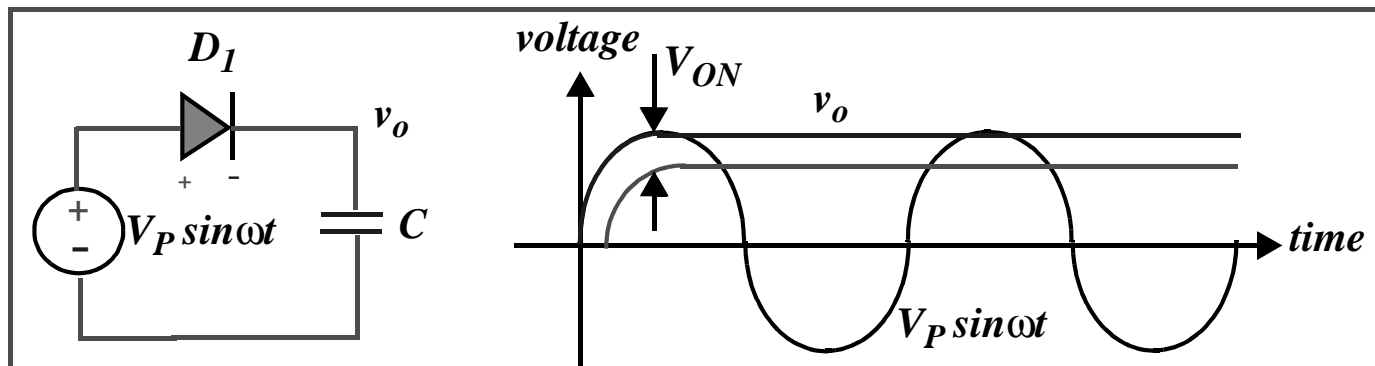
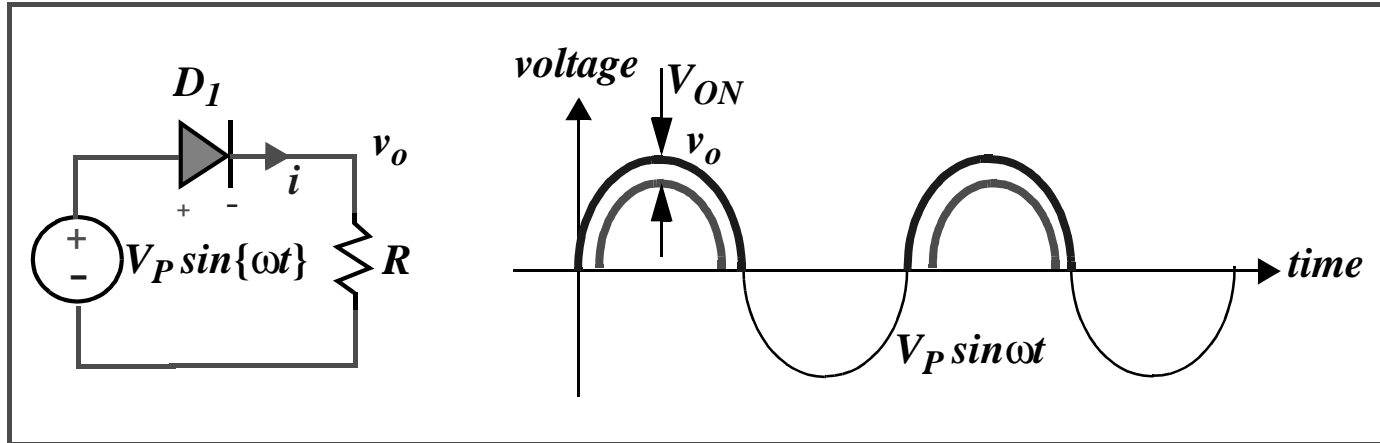
## Half-Wave Rectifier Circuits

In rectifying circuits, the variable component of  $v_s$  is rejected and the dc value is transmitted.




$$i = \frac{V_P \sin(\omega t)}{R} \quad \text{for } 0 \leq \omega t \leq \pi \quad \text{and} \quad i = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi.$$

$$I_{DC} = \frac{1}{2\pi} \int_0^{2\pi} i \cdot d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} \frac{V_P \sin(\omega t)}{R} \cdot d(\omega t) = \frac{V_P}{\pi R} = \frac{I_P}{\pi}.$$

Explain the effect of  $V_{ON}$  on  $v_o$  for the R and C loads.



## Case of RC Load

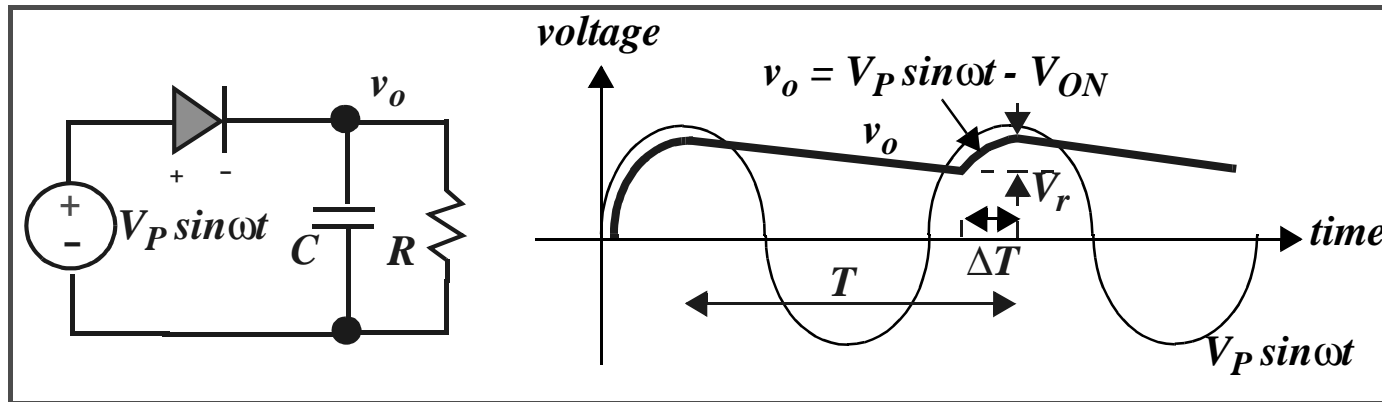

Ripple voltage 
$$V_r = (V_P - V_{ON}) - \left( (V_P - V_{ON}) \cdot \exp\left(-\frac{T - \Delta T}{RC}\right) \right).$$

$$V_r \approx (V_P - V_{ON}) \left( \frac{T}{RC} \right) \cdot \left( 1 - \frac{\Delta T}{T} \right) \approx \left( \frac{V_P - V_{ON}}{R} \right) \frac{T}{C} \quad \text{for } \Delta T \ll T.$$

Need to find the conduction interval  $\Delta T$ . Put  $t' = T - \Delta T$ .

$$(V_P - V_{ON}) \cdot \exp\left(-\frac{T - \Delta T}{RC}\right) = V_P \cos \omega(T - \Delta T) - V_{ON}.$$

$$(V_P - V_{ON}) \cdot \left( 1 - \frac{T}{RC} \right) = V_P \cos \{ \omega \cdot \Delta T \} - V_{ON}.$$

$$\boxed{(V_P - V_{ON}) \cdot \left(1 - \frac{T}{RC}\right) = V_P \left(1 - \frac{(\omega \cdot \Delta T)^2}{2}\right) - V_{ON}} \text{ Solve for } \Delta T.$$

$$\boxed{\Delta T \approx \frac{1}{\omega} \sqrt{\frac{2}{V_P} \cdot T \frac{V_P - V_{ON}}{RC}}} = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}} \cdot \boxed{\theta_c = \omega \cdot \Delta T = \sqrt{\frac{2V_r}{V_P}}} \text{ in radians.}$$

Explain diode current, surge current and peak-inverse-voltage (PIV) rating.