
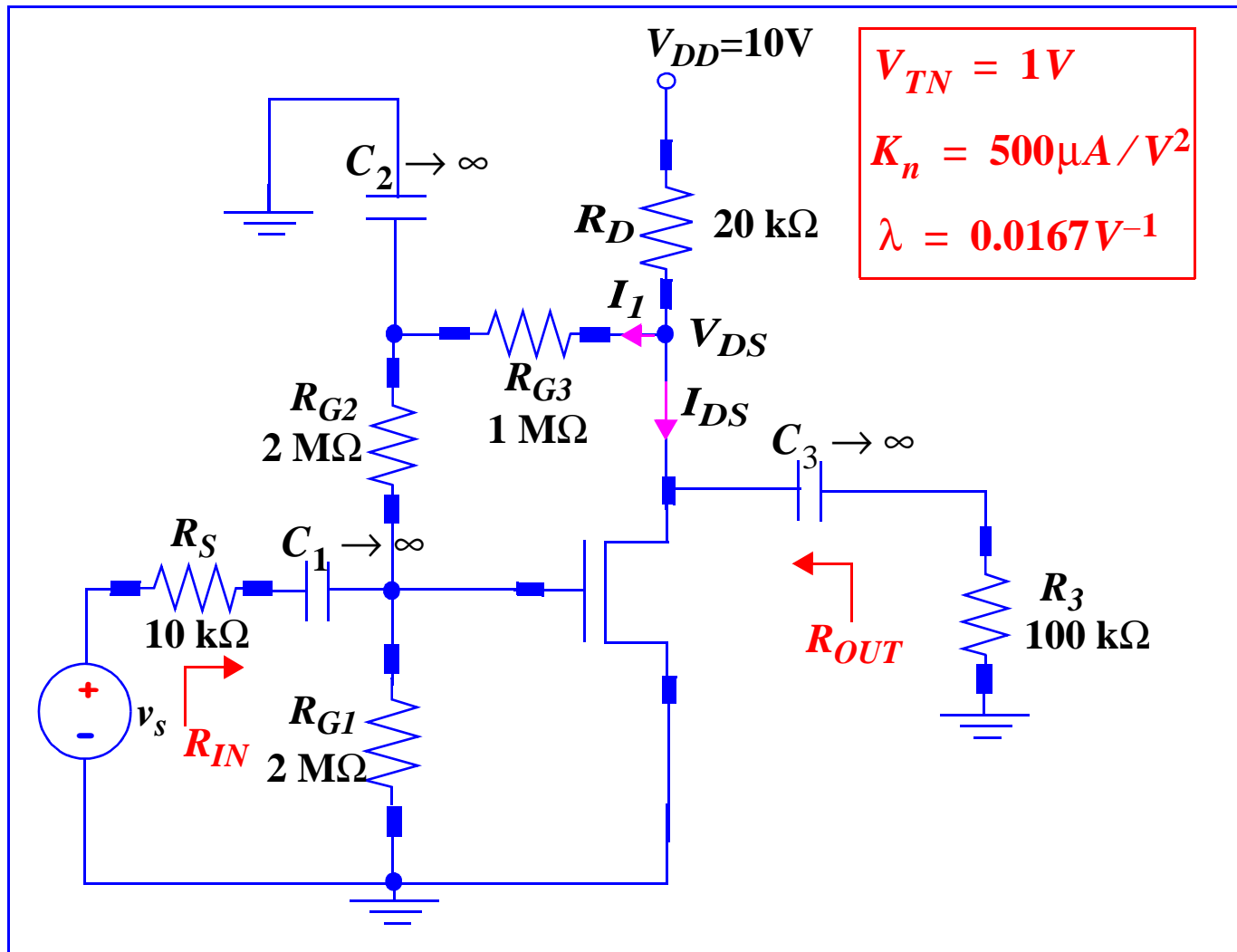


## Example of CS Amplifier

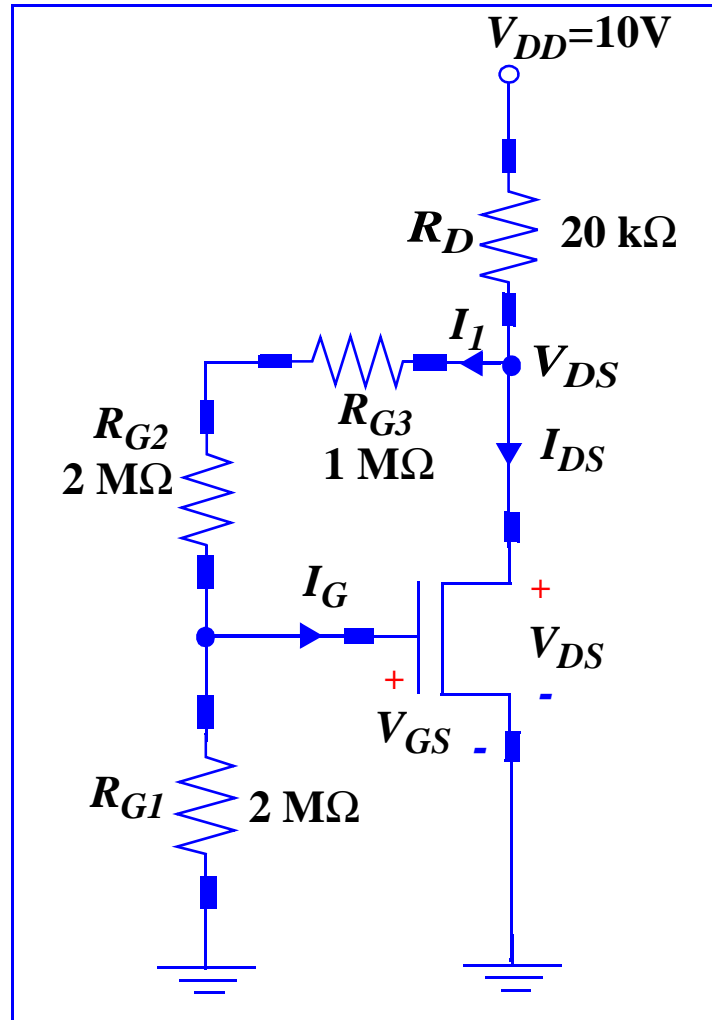

## DC Analysis (p. 631)



$$V_{DS} = 10 - 2 \times 10^4 (I_{DS} + I_1)$$

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \text{ for } V_{DS} \geq (V_{GS} - V_{TN}) \text{ and } \lambda \approx 0.$$

$$\text{Since } I_G = 0, \text{ then, } I_1 = \frac{V_{DS}}{R_{G3} + R_{G2} + R_{G1}} = \frac{V_{DS}}{5 \times 10^6}$$

$$V_{GS} = \frac{R_{G1}}{R_{G3} + R_{G2} + R_{G1}} V_{DS} = \frac{2 \times 10^6}{5 \times 10^6} V_{DS} = 0.4 V_{DS}$$

$$V_{DS} = 10 - 2 \times 10^4 \left( \left\{ \frac{5 \times 10^{-4}}{2} (0.4 V_{DS} - V_{TN})^2 \right\} + \frac{V_{DS}}{5 \times 10^6} \right)$$


$$0.8 V_{DS}^2 - 3 V_{DS} - 5 = 0. \text{ Solving, } V_{DS} = 5V \text{ or } V_{DS} = -1.25V.$$


For  $V_{DS} = 5V$ ,  $V_{GS} = 2V$  and  $I_{DS} = 250\mu A$ .

Since  $V_{DS} \geq V_{GS} - V_{TN}$ , then our assumption is correct.

Quiescent Point is  $(I_{DS}, V_{DS}) = (250\mu A, 5V)$ .

# AC Analysis

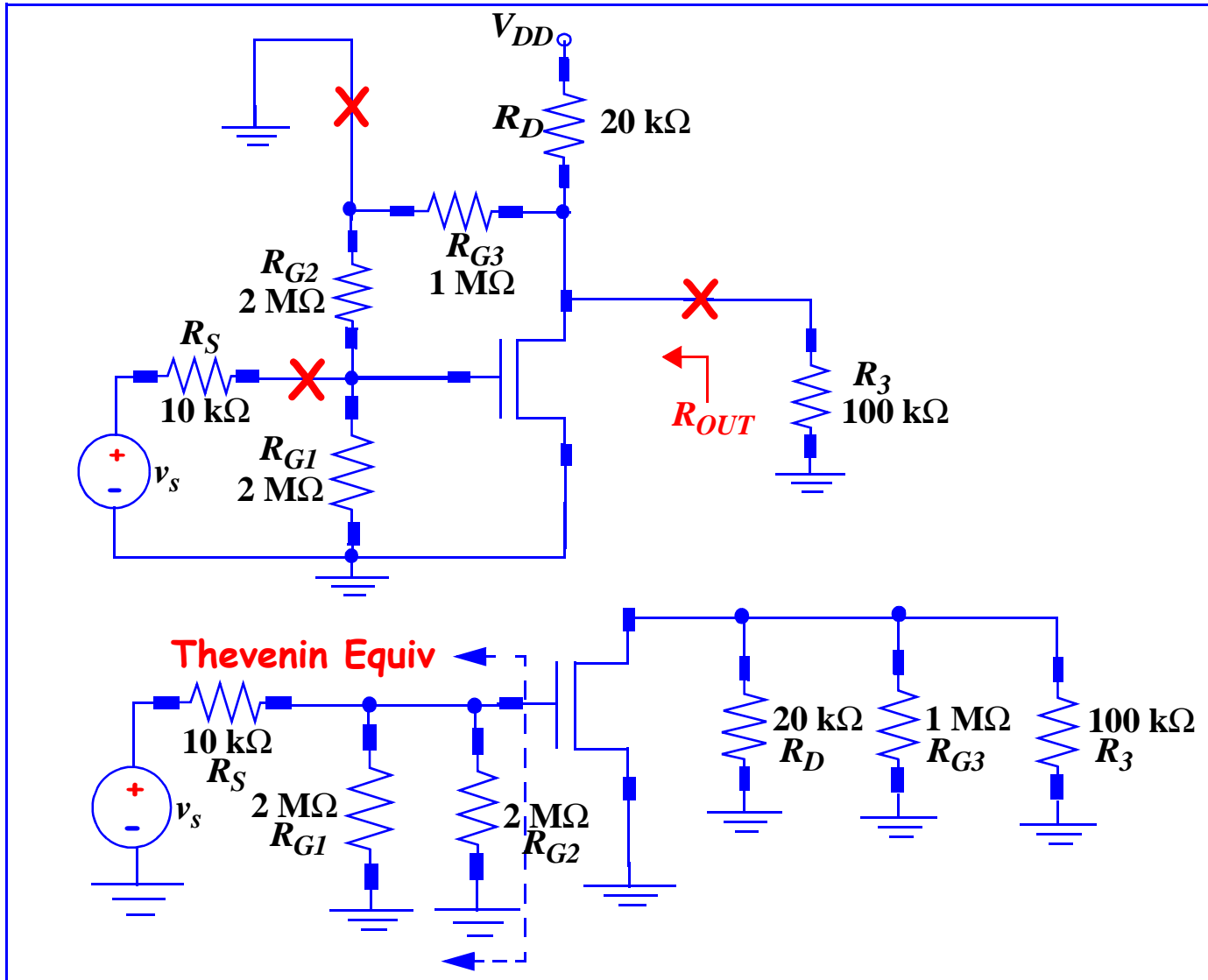

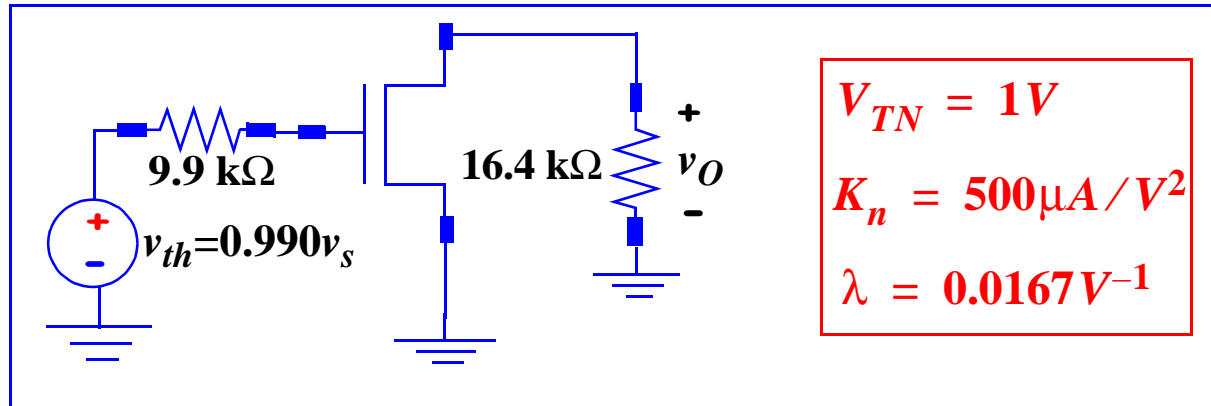


Transconductance -  $g_m = \sqrt{2K_n I_{DS}(1 + \lambda V_{DS})} = 5.20 \times 10^{-4} \text{S}$

Output Resistance of MOSFET -  $r_o = \frac{(1/\lambda) + V_{DS}}{I_{DS}} = 260 \text{k}\Omega$

Output Voltage  $v_o = (-g_m v_{gd})(r_o \parallel 16.4 \text{k}) = -8.02 v_{gs}$  and  $v_{gs} = 0.990 v_s$ ,

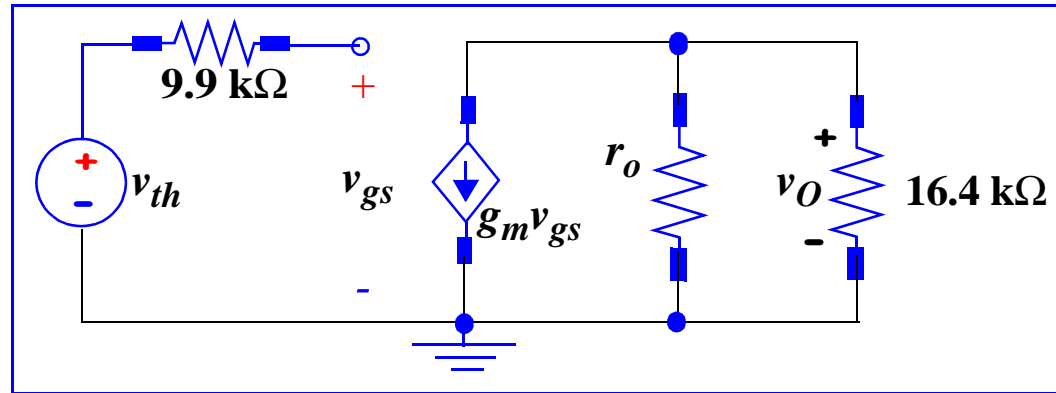so  $A_V = \frac{v_o}{v_s} = -8.02 \times 0.990 = -7.94$



What is the amplification factor  $\mu_f$  of the MOSFET above and how does it compare with  $A_V$ ?  $\mu_f = g_m r_o = 135$  and  $A_V \ll \mu_f$

What is the largest value of  $v_s$  of the circuit that corresponds to a small-signal for the amplifier for the circuit at the top of page 22-1? What is the largest value of  $v_o$  that corresponds to a small-signal for this amplifier?

$$v_s = \frac{v_{gs}}{0.990} = \frac{0.2(V_{GS} - V_{TN})}{0.990} = 202mV \quad \text{and} \quad v_o = A_V v_s = 1.60V$$

### Input Resistance

Is limited by gate bias resistors since input gate impedance is  $\infty$ .

$$R_{IN} = R_{G1} \parallel R_{G2} = 1M\Omega$$

### Output Resistance

$$R_{OUT} = R_D \parallel R_{G3} \parallel r_o = 18.2k\Omega$$