

Lecture #23

from Chapter 7 in Jaeger, Chapter 15 in Spencer

CMOS Logic Design


Outline/Learning Objectives:

- Explain the basic function of the primary digital circuit building block -the inverter.
- Describe (static) CMOS logic inverter technology.
- Analyze the (static) CMOS inverter circuit, including its voltage transfer characteristic and static and dynamic power dissipation.

Selected problems:

- 7.8, 7.23, 7.58, 7.60, 7.63

CMOS Inverter

 

B tied to S in both NMOS and PMOS devices.

$$V_{TH \text{ NMOS}} - V_{TN} = V_{T0N} + \gamma_N (\sqrt{v_{SBN} + 2\phi_{FN}} - \sqrt{2\phi_{FN}}) \quad (1)$$

$$V_{TH \text{ PMOS}} - V_{TP} = V_{T0P} - \gamma_P (\sqrt{v_{BSP} + 2\phi_{FP}} - \sqrt{2\phi_{FP}}) \quad (2)$$


$$\gamma = \frac{\sqrt{2qN_{sub}\epsilon_s}}{C_{ox}} = \text{body effect parameter (V}^{0.5}\text{)} \quad (3)$$


$$2\phi_F = \text{surface potential parameter} \quad \phi_F = \frac{kT}{q} \ln\left(\frac{N_{sub}}{n_i}\right) \quad (4)$$

Sample NMOS and PMOS Parameters

Parameter	NMOS	PMOS
V_{T0}	1 V	-1 V
γ	$0.5 \text{ V}^{1/2}$	$0.75 \text{ V}^{1/2}$
ϕ_F	0.60 V	0.70 V
K'	$25 \mu\text{A}/\text{V}^2$	$10 \mu\text{A}/\text{V}^2$
λ	0.02 V^{-1}	0.02 V^{-1}

Static Characteristics of CMOS Inverter

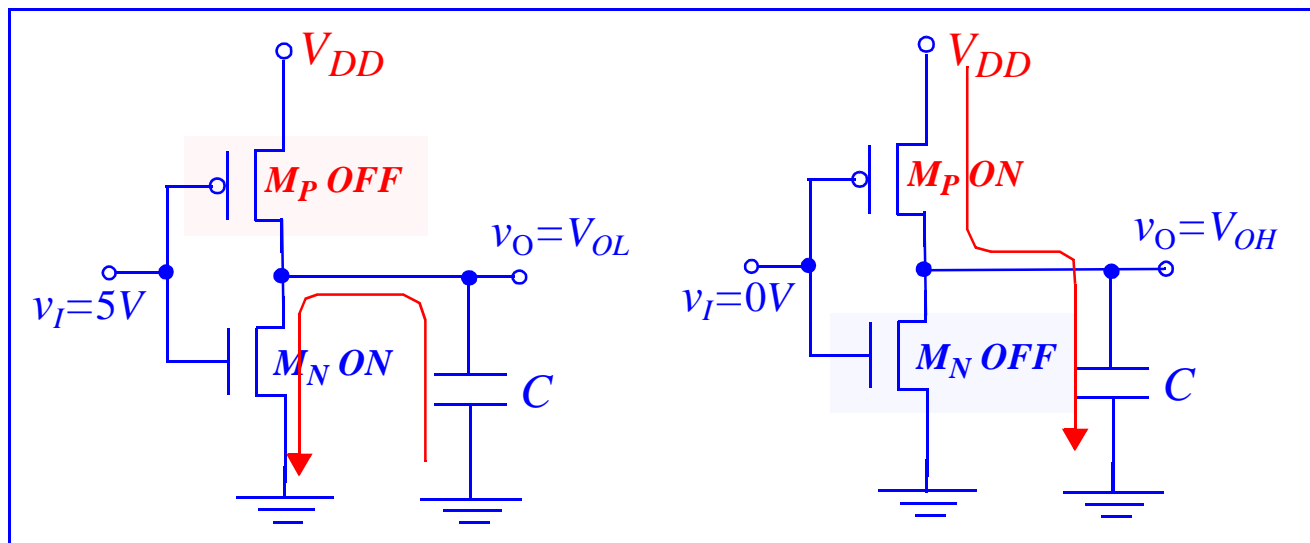

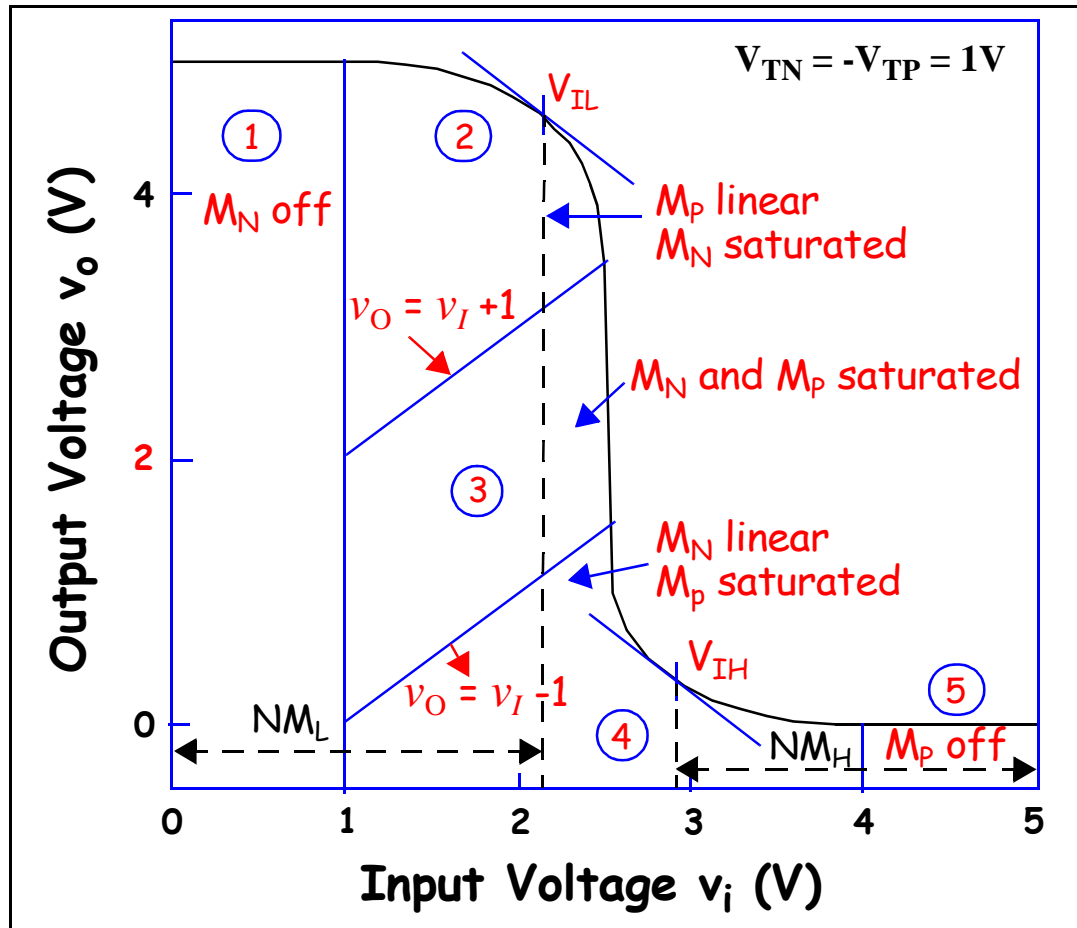

Sat. of PMOS requires $v_{SD} \geq v_{SG} + V_{TP}$ or $(5 - v_o) \geq (5 - v_i) - 1$ or $v_o \leq v_i + 1$ (5)

Sat. of NMOS requires $v_{DS} \geq v_{GS} - V_{TN}$ or $v_o \geq v_i - 1$ (6)

Regions of Operation of MOSTs in Symmetrical CMOS Inv.

Region	v_I	v_O	NMOS	PMOS
1	$v_I \leq V_{TN}$	$V_{OH} = V_{DD}$	Off	Lin
2	$V_{TN} < v_I \leq v_O + V_{TP}$	High	Sat	Lin
3	$v_I \approx V_{DD}/2$	$V_{DD}/2$	Sat	Sat
4	$v_O + V_{TN} < v_I \leq V_{DD} - V_{TP} $	Low	Lin	Sat
5	$v_I \geq V_{DD} - V_{TP} $	$V_{OL} = 0$	Lin	Off

Noise Margins for the CMOS Inverter

High Input - PMOS sat., NMOS lin., so $i_{DSN} = i_{DSP}$

$$K_n \left(v_I - V_{TN} - \frac{v_O}{2} \right) v_O = \frac{K_p}{2} (V_{DD} - v_I + V_{TP})^2 \quad (7)$$

$$K_R (2v_I - 2V_{TN} - v_O) v_O = (V_{DD} - v_I + V_{TP})^2 \quad \text{Note } \boxed{K_R = K_n / K_p} \quad (8)$$

$$v_O = (v_I - V_{TN}) \pm \sqrt{(v_I - V_{TN})^2 - \frac{(V_{DD} - v_I + V_{TP})^2}{K_R}} \quad (9)$$

$$V_{IH} = \frac{2K_R(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{V_{DD} - K_R V_{TN} + V_{TP}}{K_R - 1} \quad (10)$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} \quad (11)$$

For $K_R = 1$,

$$V_{IH} = \frac{5V_{DD} + 3V_{TN} + 5V_{TP}}{8} \quad (12)$$

and

$$NM_H = \frac{3V_{DD} - 3V_{TN} - 5V_{TP}}{8} \quad (13)$$

Low Input - PMOS lin., NMOS sat., $i_{DSN} = i_{DSP}$

$$K_p \left(V_{DD} - v_I + V_{TP} - \frac{V_{DD} - v_O}{2} \right) (V_{DD} - v_O) = K_n (v_I - V_{TN})^2 \quad (14)$$


$$(V_{DD} - 2v_I + 2V_{TP} - v_O)(V_{DD} - v_O) = K_R (v_I - V_{TN})^2 \quad \text{Note } K_R = K_n / K_p \quad (15)$$

$$V_{IL} = \frac{2\sqrt{K_R}(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{V_{DD} - K_R V_{TN} + V_{TP}}{K_R - 1} \quad (16)$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} - 0 \quad (17)$$

For $K_R = 1$,
$$V_{IL} = \frac{3V_{DD} + 5V_{TN} + 3V_{TP}}{8} \quad (18)$$

and
$$NM_L = V_{IL} \quad (19)$$

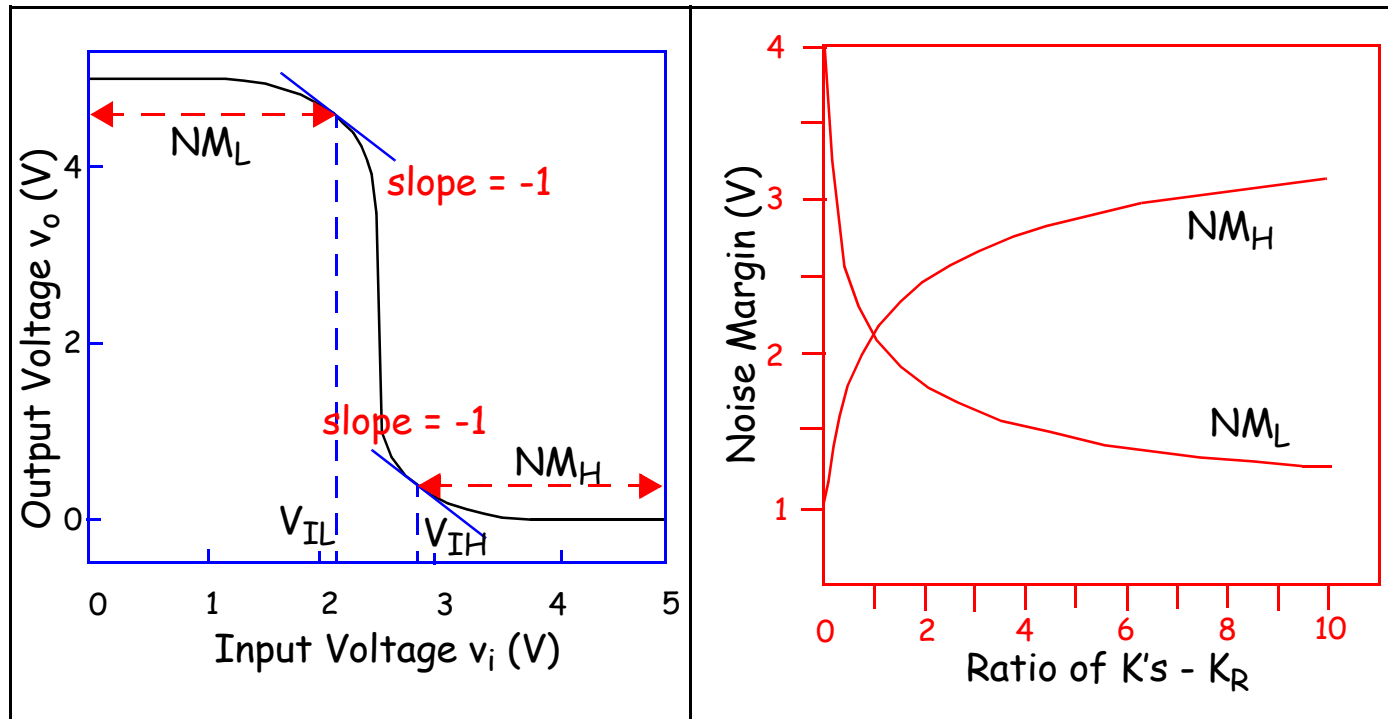

Example: What are the noise margins of a minimum size CMOS inverter in which both W/L ratios are 2/1 with $K_n' = 25 \mu\text{A}/\text{V}^2$ and $K_p' = 10 \mu\text{A}/\text{V}^2$, $V_{DD} = 5.2 \text{ V}$ and $V_{TN} = -V_{TP} = 1 \text{ V}$?

$$K_R = \frac{K_n}{K_p} = 2.5$$

$$V_{IH} = \frac{2K_R(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{V_{DD} - K_R V_{TN} + V_{TP}}{K_R - 1}$$

$$V_{IH} = \frac{2(2.5)(5.2 - 1 - 1)}{(2.5 - 1)(\sqrt{1 + 3(2.5)})} - \frac{5.2 - 2.5(1) - 1}{2.5 - 1} = 2.53 \text{ V}$$


$$\therefore NM_H = V_{DD} - V_{IH} = 5.2 - 2.53 = 2.67 \text{ V}$$

$$V_{IL} = \frac{2\sqrt{K_R}(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{V_{DD} - K_R V_{TN} + V_{TP}}{K_R - 1}$$

$$V_{IL} = \frac{2(\sqrt{2.5})(5.2 - 1 - 1)}{(2.5 - 1)(\sqrt{2.5 + 3})} - \frac{5.2 - 2.5(1) - 1}{2.5 - 1} = 1.83 \text{ V}$$

$$\therefore NM_L = V_{IL} = 1.83 \text{ V}$$

PSPICE EXAMPLE

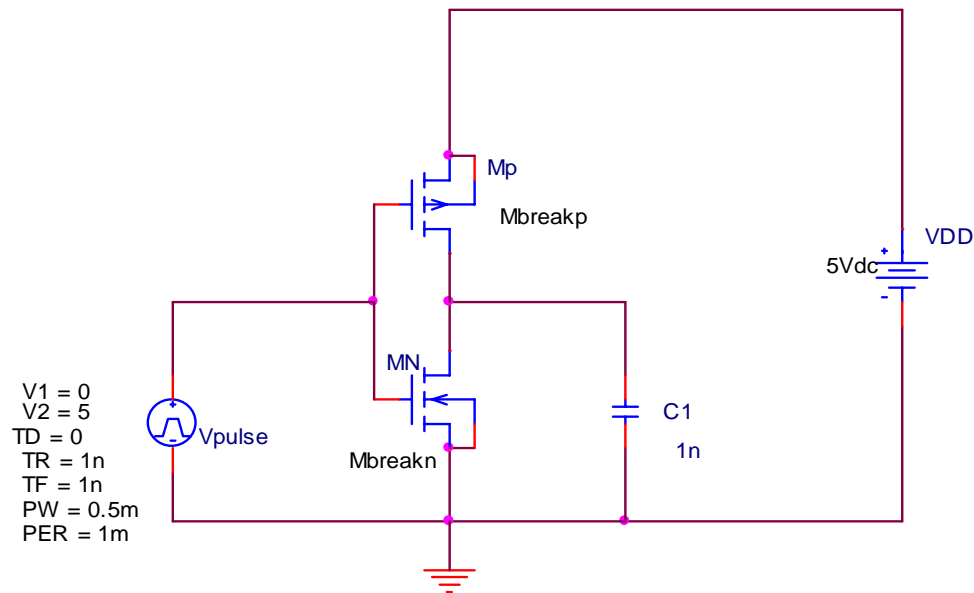

***Libraries:**

*** Local Libraries :**

.LIB ".\example9.lib"

*** From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:**

.lib "nom.lib"

***Analysis directives:**

.TRAN 0 20ms 0 1u

PSPICE EXAMPLE (Cont'd)

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)  
.INC ".\example9-SCHEMATIC1.net"  
**** INCLUDING example9-SCHEMATIC1.net ****  
* source EXAMPLE9  
M_MN      N00163 N00248 0 0 Mbreakn  
V_Vpulse  N00248 0  
+PULSE 0 5 0 1n 1n 0.5m 1m  
V_VDD     N00144 0 5Vdc  
M_Mp      N00163 N00248 N00144 N00144 Mbreakp  
C_C1      0 N00163 1n  
**** RESUMING example9-SCHEMATIC1-Example9.sim.cir ****  
.END  
  
**** MOSFET MODEL PARAMETERS
```

```
*****
```

PSPICE EXAMPLE (Cont'd)

```
      Mbreakn      Mbreakp
      NMOS         PMOS
      LEVEL 1      1
L 100.000000E-06 100.000000E-06
W 100.000000E-06 100.000000E-06
VTO 1          -1
KP 500.000000E-06 500.000000E-06
GAMMA 0        0
PHI .6         .6
LAMBDA 0       0
```

```
**** INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C
```

```
*****
```

```
NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE
(N00144)  5.0000 (N00163)  5.0000 (N00248)  0.0000
```

PSPICE EXAMPLE (Cont'd)

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V_Vpulse	0.000E+00
V_VDD	-5.010E-12

TOTAL POWER DISSIPATION 2.51E-11 WATTS

JOB CONCLUDED

TOTAL JOB TIME 2.79

PSPICE EXAMPLE (Cont'd)

