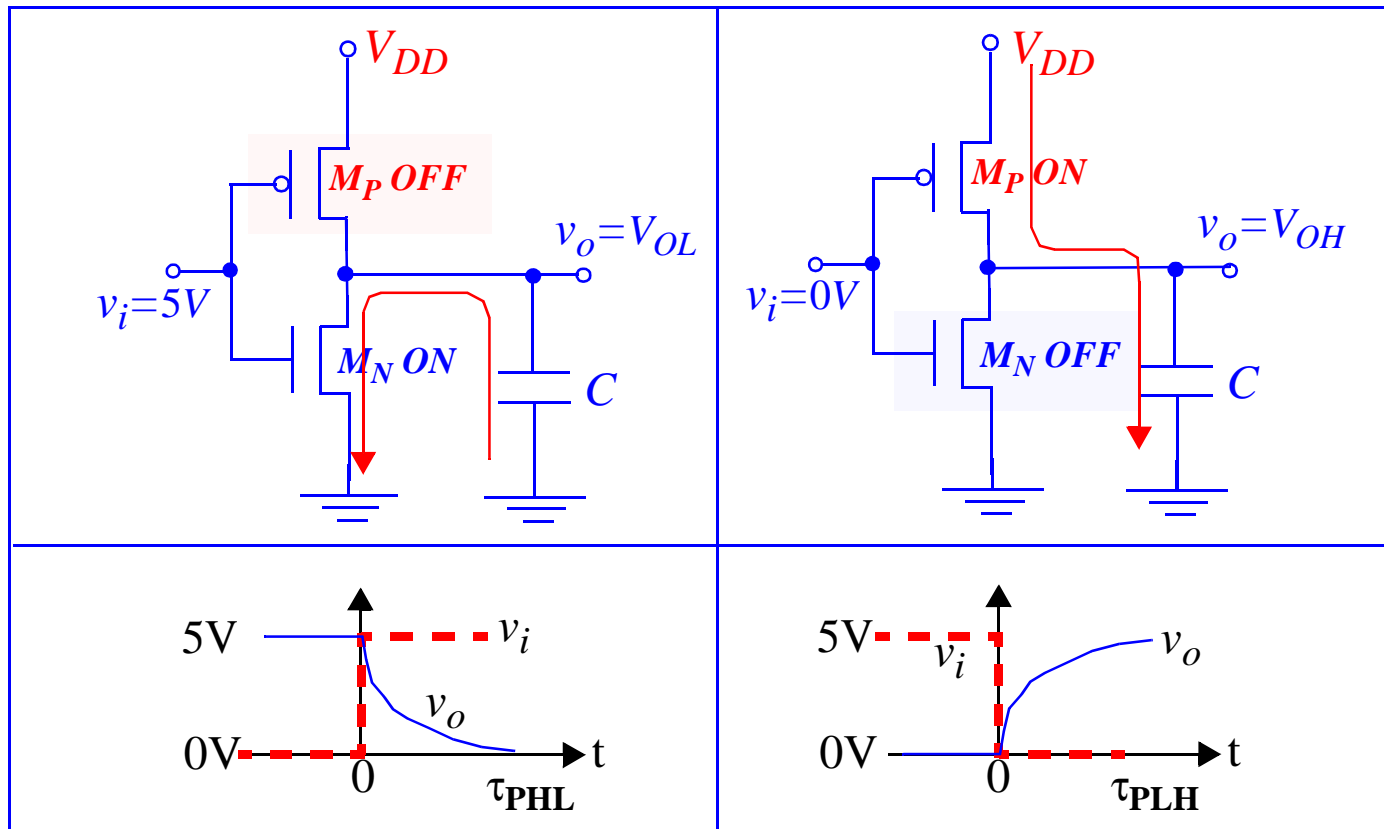


# Lecture #24

## CMOS Logic Design

- Describe and analyze the dynamic behavior of the CMOS logic inverter.
- Describe and analyze basic CMOS NOR and NAND logic gates.
- Describe and analyze MOS transmission gates and their use in MOS logic circuits.
-

## Dynamic Behavior of CMOS Inverter



$$\frac{k_n}{2}(v_{GS} - V_{TN})^2 = -C \frac{dv_o}{dt} \quad \text{for} \quad V_{DD} - V_{TN} \leq v_o \leq V_{DD}$$

$$k_n \left( v_{GS} - V_{TN} - \frac{v_o}{2} \right) v_o = -C \frac{dv_o}{dt} \quad \text{for} \quad 0.5V_{DD} \leq v_o \leq V_{DD} - V_{TN}$$

$$\tau_{PHL} = R_{onn} C \left\{ \ln \left[ 4 \left( \frac{V_{DD} - V_{TN}}{V_{DD} + V_{OL}} \right) - 1 \right] + \frac{1}{2} \right\} \quad \text{with} \quad R_{onn} = \frac{1}{K_n (V_{DD} - V_{TN})}$$


For CMOS inverter with  $V_{DD} = 5V$ ,  $V_{TN} = 1V$  and  $V_{OL} = 0V$ .

$$\tau_{PHL} = 1.29 R_{onn} C = 0.322 \frac{C}{K_n}$$

The L to H propagation delay with  $V_{DD} = 5V$ ,  $V_{TP} = -1V$  and  $V_{OH} = 5V$ .

$$\tau_{PLH} = 1.29 R_{onp} C = 0.322 \frac{C}{K_p} \quad \text{for} \quad R_{onp} = \frac{1}{K_p (V_{DD} + V_{TP})}$$
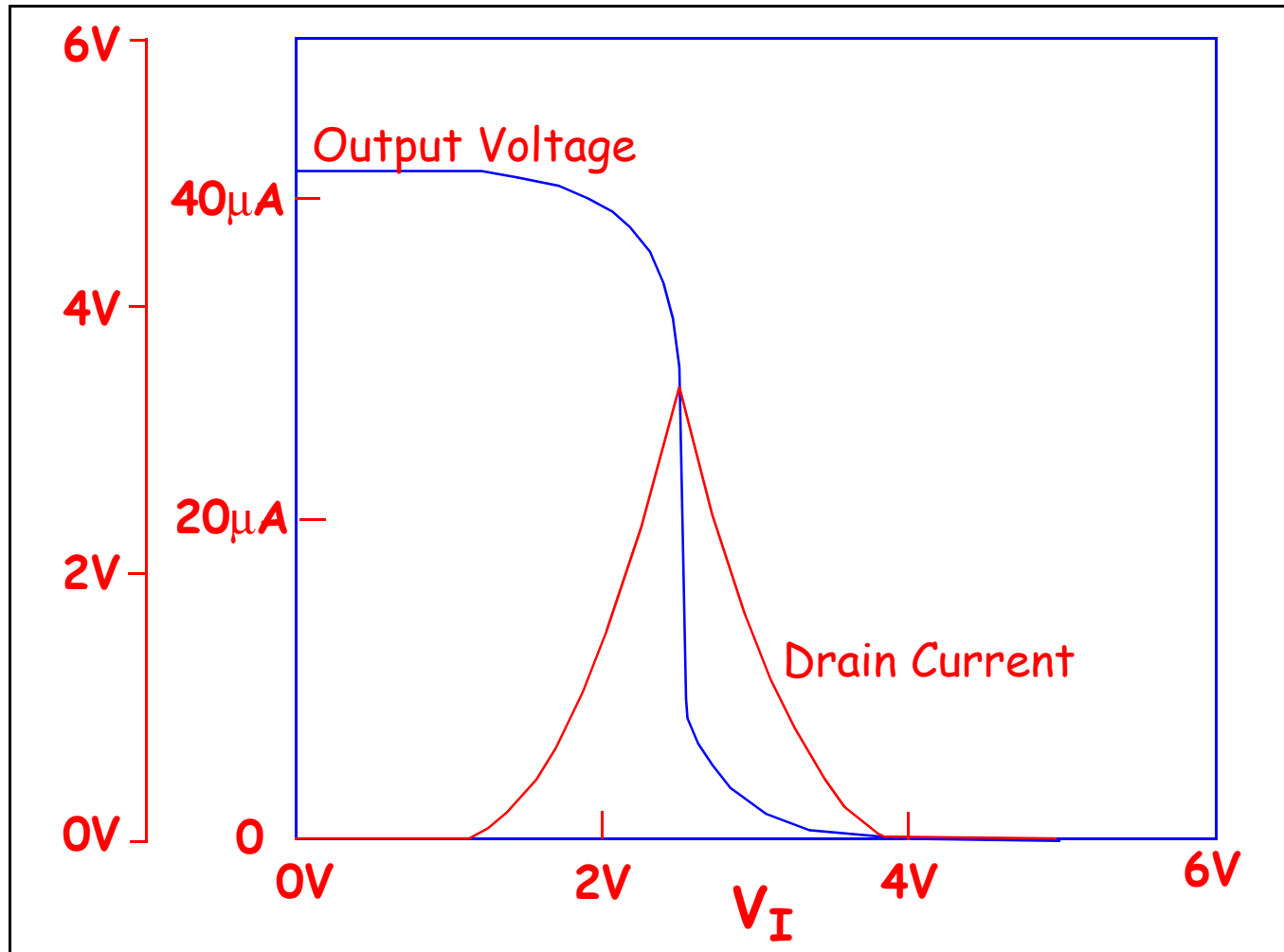
## Static and Dynamic Power Dissipation in CMOS



Output Voltage and Supply Current versus Input Voltage  
for Symmetrical CMOS Inverter

Dynamic power dissipation is  $P_D = CV_{DD}^2 f$

Switching power dissipation -  $i_{DS} = 0$  for  $v_I \leq V_{TN}$  and  $v_I > (V_{DD} - |V_{TP}|)$ .

For  $V_{TN} \leq v_I \leq (V_{DD} - |V_{TP}|)$ ,  $i_{DS} \neq 0$  and the current peaks when  $v_I = v_O = V_{DD}/2$

For high speed CMOS,  $P_{SW} \sim 0.2 \text{ to } 0.3 P_D$  (24)

**Example:** A CMOS inverter has  $V_{TN} = -V_{TP} = 1V$ ,  $K_n' = 20\mu A/V^2$ ,  $K_p' = 15\mu A/V^2$ ,  $(W/L)_N = (W/L)_P = 20/1$  and  $V_{DD} = 4.8V$ . What is the peak current in the logic gate and at what input voltage does it occur.


$$\frac{K_n'}{2} \left(\frac{W}{L}\right)_N (v_{GS} - V_{TN})^2 = \frac{K_p'}{2} \left(\frac{W}{L}\right)_P (v_{SG} + V_{TP})^2$$

$$\frac{20 \times 10^{-6}}{2} \left(\frac{20}{1}\right) (v_I - 1)^2 = \frac{15 \times 10^{-6}}{2} \left(\frac{20}{1}\right) (4.8 - v_I - 1)^2 \Rightarrow 1.15(v_I - 1) = 3.8 - v_I$$


$$\therefore v_I = \frac{3.8 + 1.15}{1.15 + 1} = 2.30V$$

$$\therefore i_{peak} = \frac{20 \times 10^{-6}}{2} \left(\frac{20}{1}\right) (2.30 - 1)^2 = 338\mu A$$


## CMOS NOR and NAND Gates

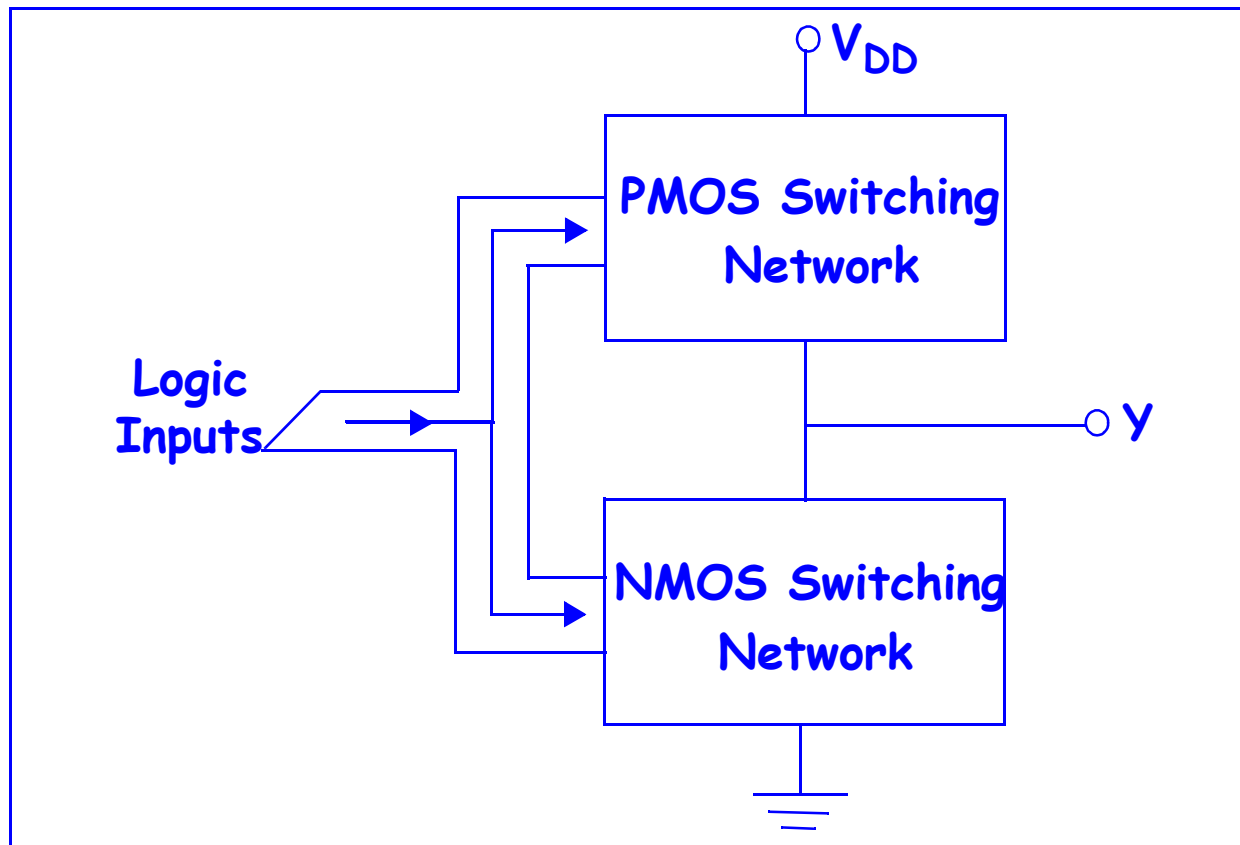

## Three Input NOR Gate

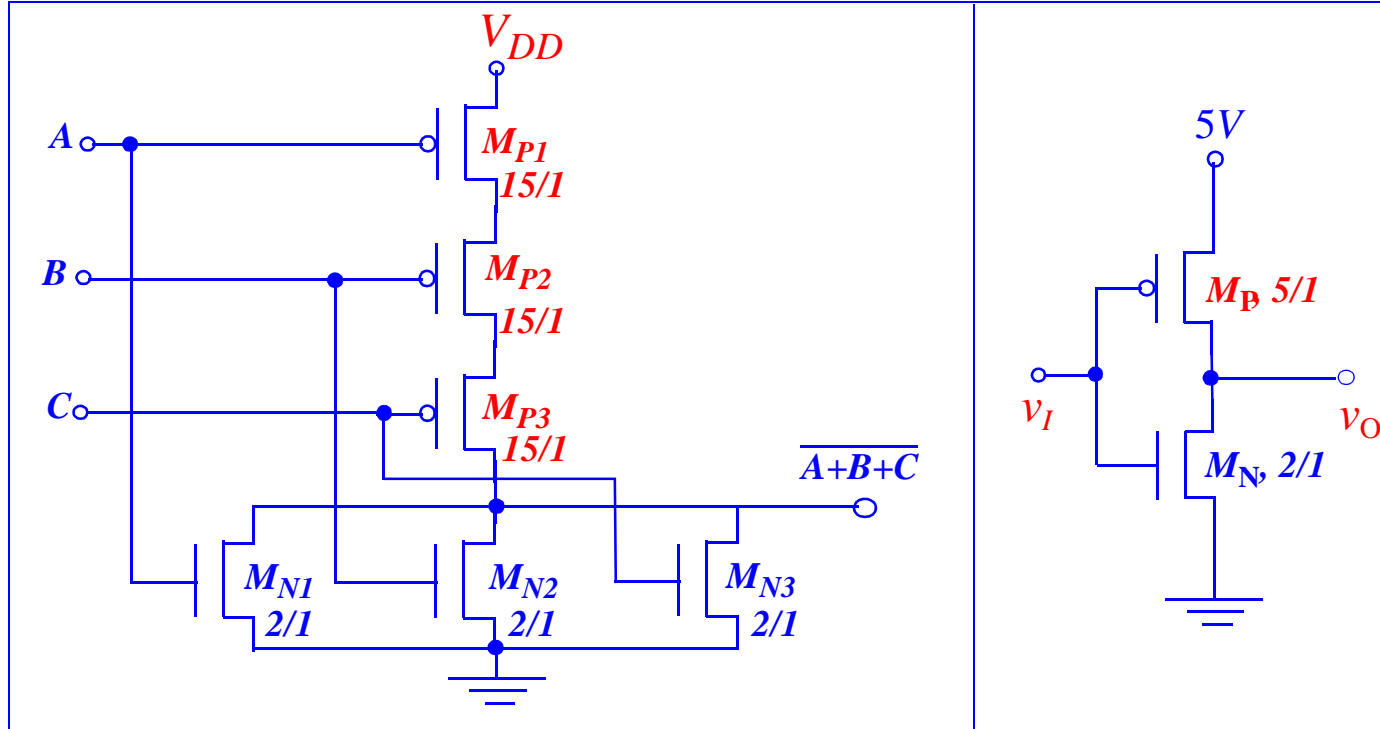

## Three Input NAND Gate

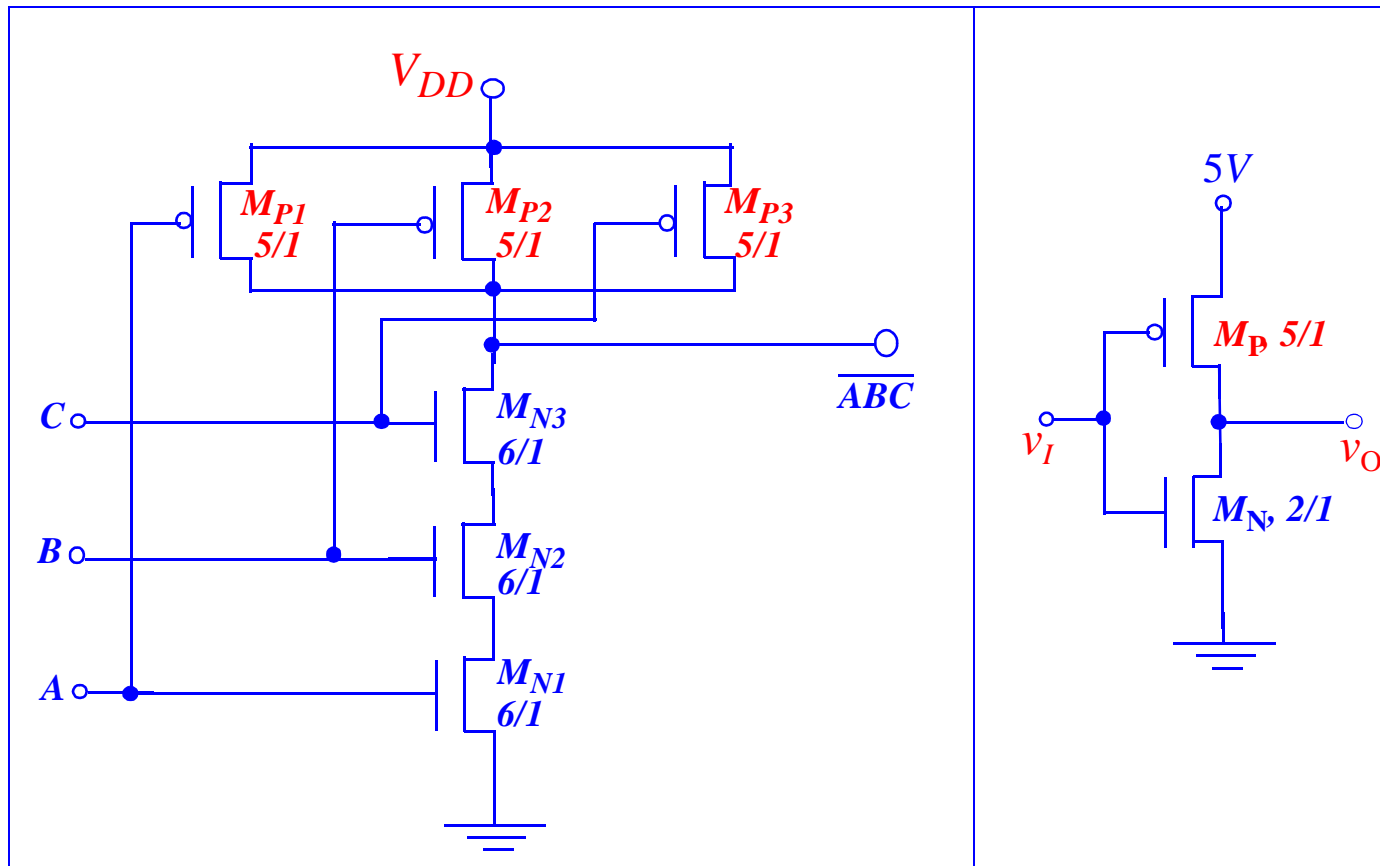



## MOS Transmission Gate


Useful in analog and digital design.

It is a bi-directional resistive connection between  $v_I$  and  $v_O$ .

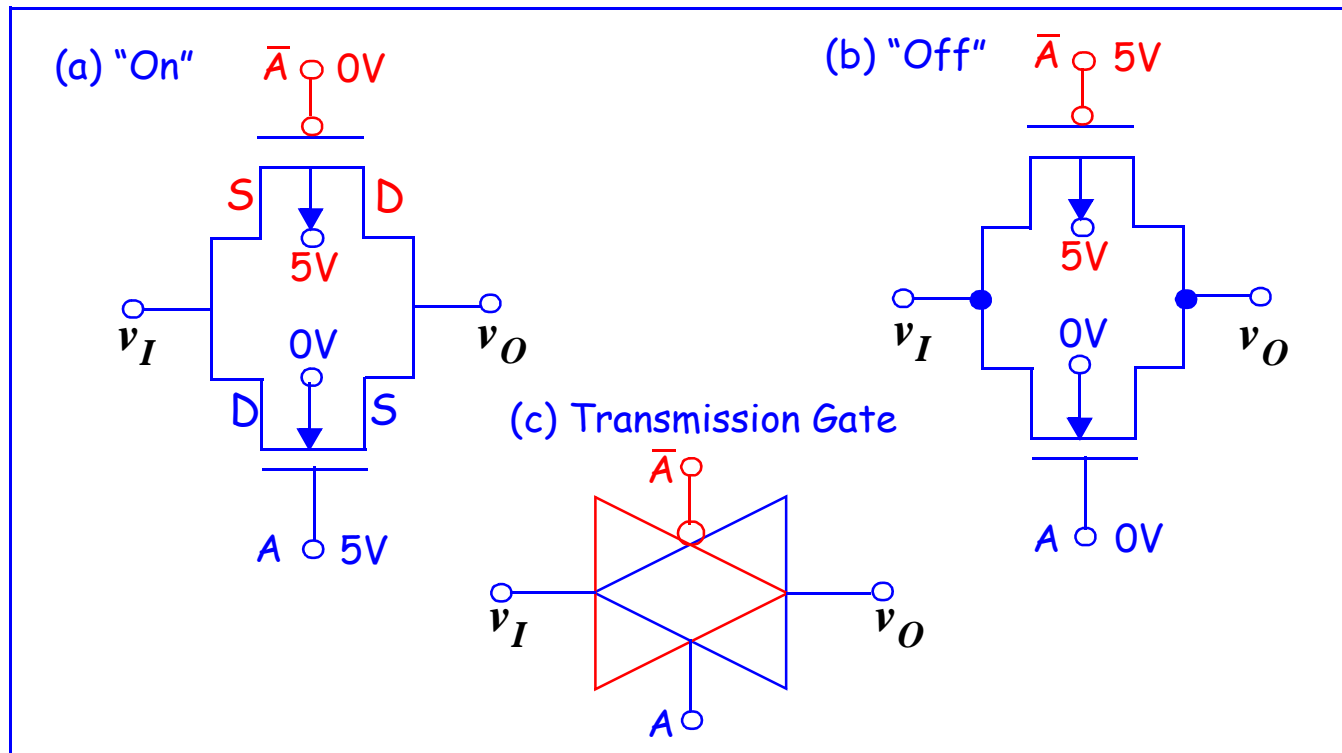 The equivalent resistance is 
$$R_{EQ} = \frac{R_{onp} R_{onn}}{R_{onp} + R_{onn}}.$$





 

$R_{onp} = \infty$  for  $v_I \leq 1.36V$  PMOS is OFF.

$R_{onn} = \infty$  for  $v_I \geq 3.64V$  NMOS is OFF. Can use  $R_{on} \propto 1/K$  in design.