

## Lecture #25

### Chapter 5 of Jaeger, Chapter 2 of Spencer

### Bipolar Junction Transistors

#### Outline/Learning Objectives:

- Describe the physical structure of the bipolar junction transistor (BJT).
- Identify the npn and pnp BJT circuit diagram symbols.
- Describe qualitatively and quantitatively the physical operating principles of the BJT.
- Describe qualitatively and quantitatively the i-v characteristics (output and transfer) of the BJT.
- Determine the regions of operation (cutoff, forward-active, and saturation).

•


#### Selected problems:

- 5.32, 5.61, 5.65, 5.73, 5.74, 5.82, 5.91, 5.95, 5.98

•


•

## Physical Structure of the BJT

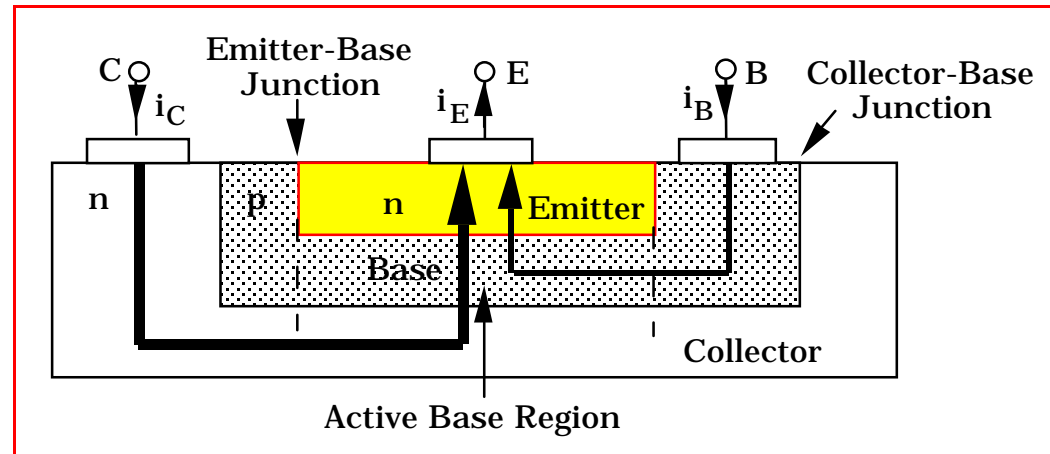


# Simplified Cross-Section of an npn BJT

Currents are for "Normal" Operation

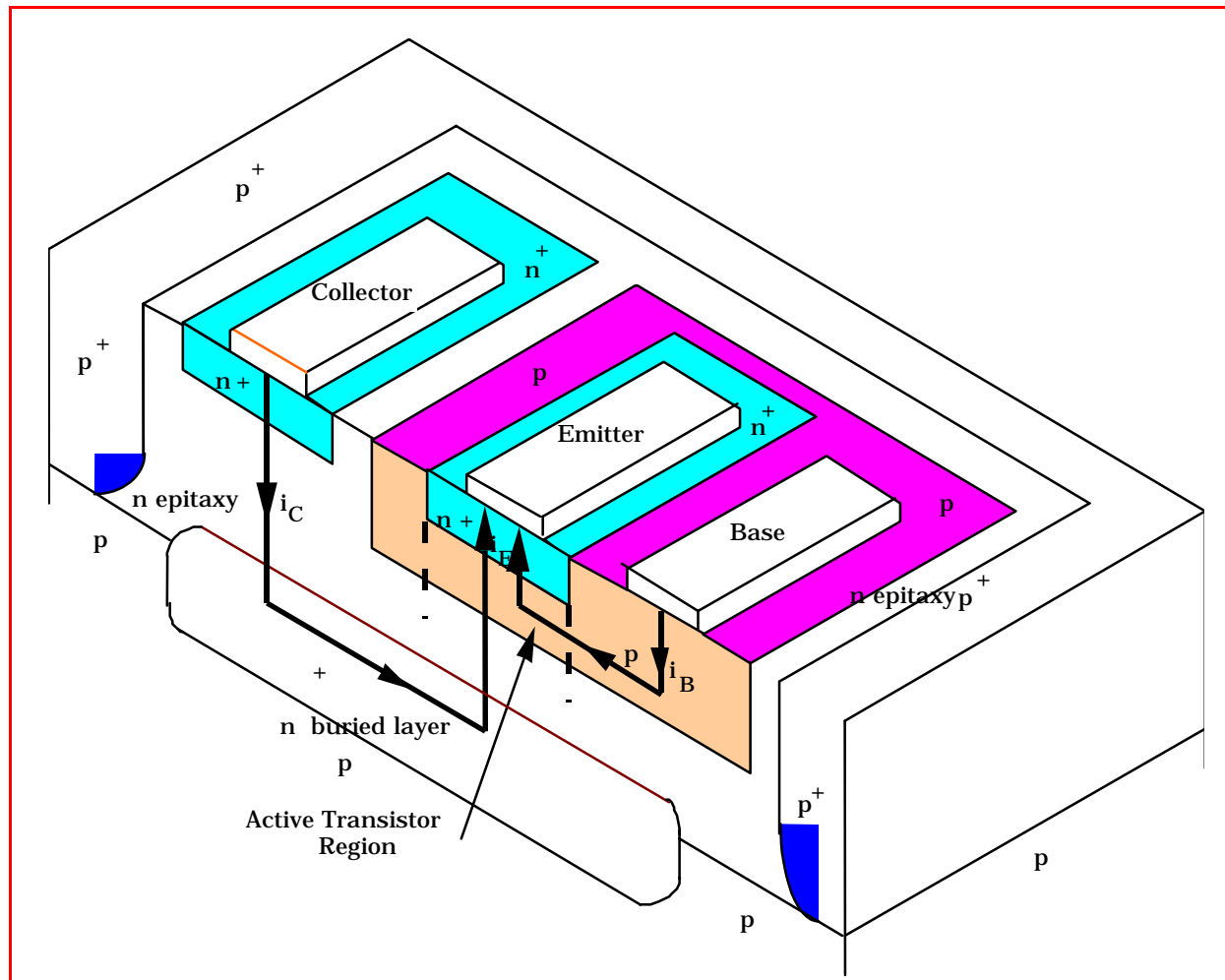

## Idealized npn BJT and Circuit Symbol

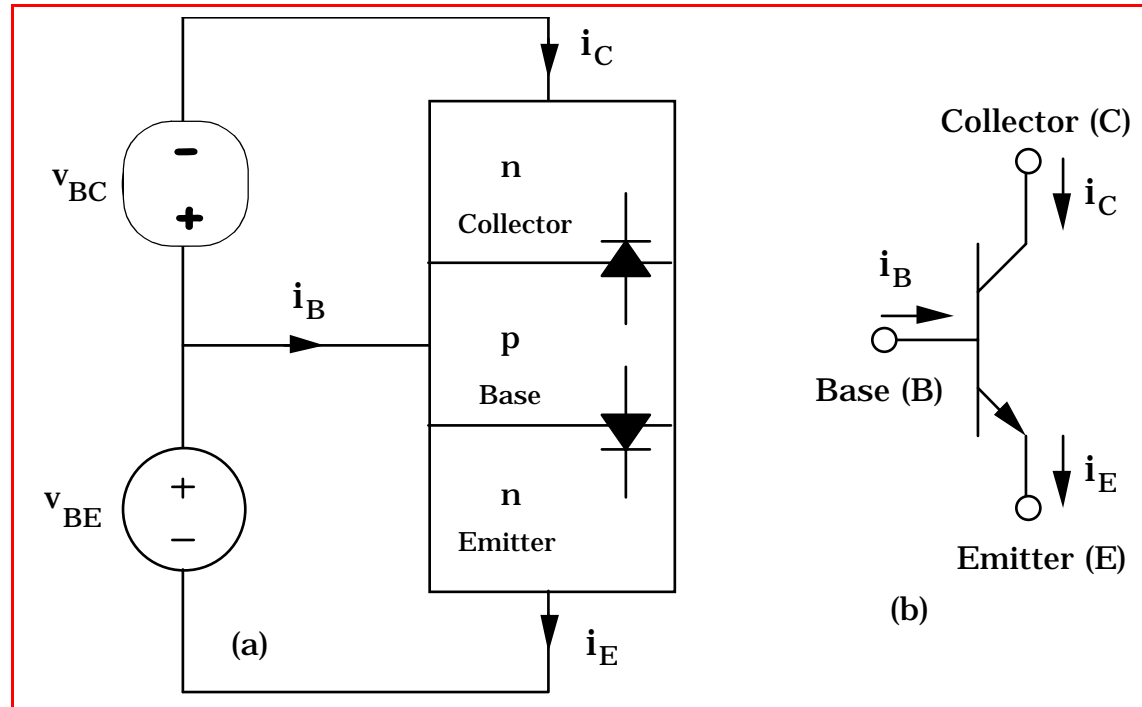

## Forward Characteristics

BE voltage  $\rightarrow i_E$

$i_E$  is composed of  $i_F$  &  $i_B$

$$i_C = i_F = I_S \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\}$$

with  $10^{-18} \text{ A} \leq I_S \leq 10^{-9} \text{ A}$


$I_S$  is proportional to the cross-sectional area of the active base region.

$$i_B = \frac{i_F}{\beta_F} = \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} \quad \text{with } 20 \leq \beta_F \leq 500.$$

$$i_E = i_C + i_B = \left( I_S + \frac{I_S}{\beta_F} \right) \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} = \frac{I_S}{\alpha_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} \quad \text{with } 0.95 \leq \alpha_F < 1.$$

$$\alpha_F = \frac{\beta_F}{\beta_F + 1} \quad \text{and} \quad \beta_F = \frac{\alpha_F}{1 - \alpha_F}.$$
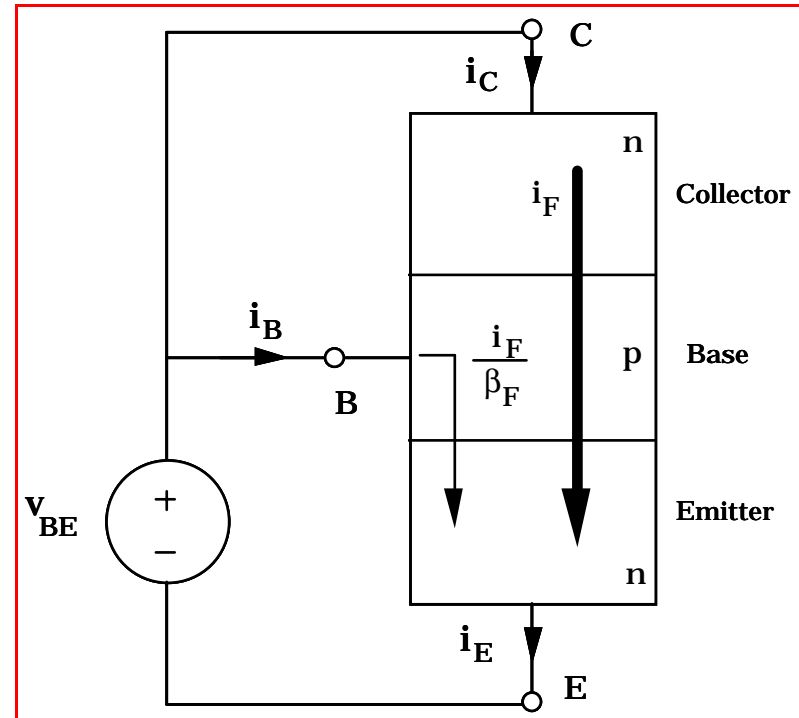
$$i_C = \beta_F i_B, \quad i_E = i_B + i_C = (\beta_F + 1) i_B \quad \text{and} \quad i_C = \alpha_F i_E.$$



## Reverse Characteristics

BC voltage  $\rightarrow i_R$  &  $i_R/\beta_R$


$$i_R = I_S \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\} \text{ and } i_E = -i_R$$

$$i_B = \frac{i_R}{\beta_R} = \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\}$$

$0 < \beta_R \leq 20$  and  $\beta_R$  is the reverse CE current gain.

$$i_C = i_E - i_B = -\left(I_S + \frac{I_S}{\beta_R}\right) \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\} = \frac{-I_S}{\alpha_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\} \text{ with } 0 < \alpha_R \leq 0.95.$$
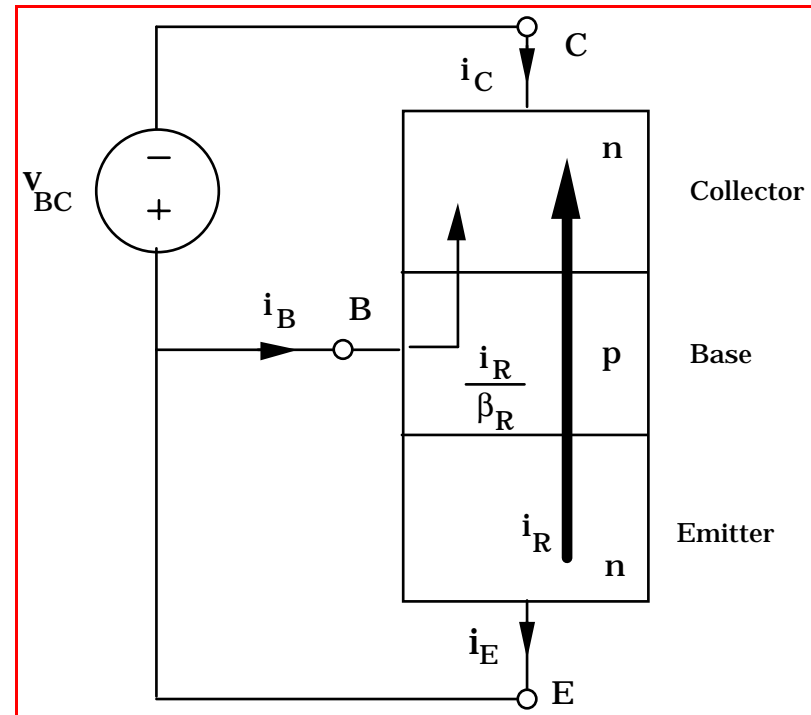
$$\alpha_R = \frac{\beta_R}{\beta_R + 1} \text{ and } \beta_R = \frac{\alpha_R}{1 - \alpha_R}.$$



$\alpha_F$ or $\alpha_R$	$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$ or $\beta_R = \frac{\alpha_R}{1 - \alpha_R}$
0.1	0.11
0.5	1
0.9	9
0.99	499

### Full Transport Model Equations - Arbitrary Bias Conditions

$$i_C = I_S \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right\} - \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\}.$$

$$i_E = I_S \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right\} + \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\}.$$

$$i_B = \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} + \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\}.$$


Require 4 parameters -  $I_S$ ,  $\beta_F$ ,  $\beta_R$  and  $T$  to characterize an individual BJT.

## Example

Determine  $i_C$ ,  $i_E$  and  $i_B$  if  $I_S = 10^{-15} \text{ A}$ ,  
 $V_T = 25 \text{ mV}$ ,  $\beta_F = 100$  and  $\beta_R = 2$ .

$$V_{BB} = V_{BE} = 0.7 \text{ V and}$$
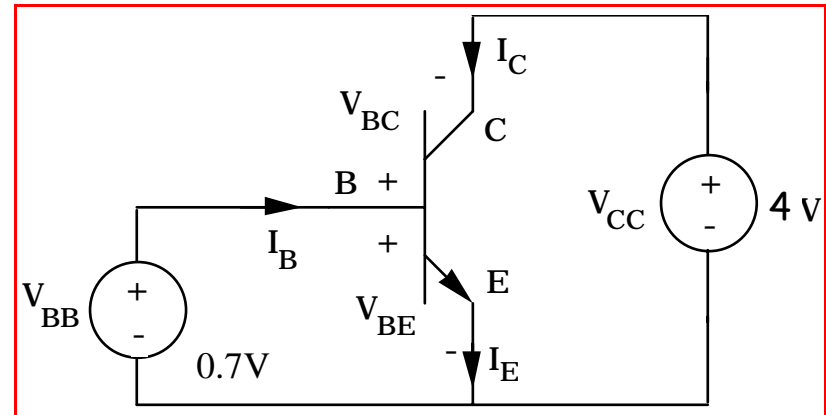
$$V_{BC} = V_{BB} - V_{CC} = -3.3 \text{ V}$$




$$I_C = I_S \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right\} - \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\} = \mathbf{1.45 \text{ mA}}$$

$$I_E = I_S \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right\} + \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} = \mathbf{1.46 \text{ mA}}$$

$$I_B = \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right\} + \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right\} = \mathbf{14.5 \mu\text{A}}$$




## PNP Transistor

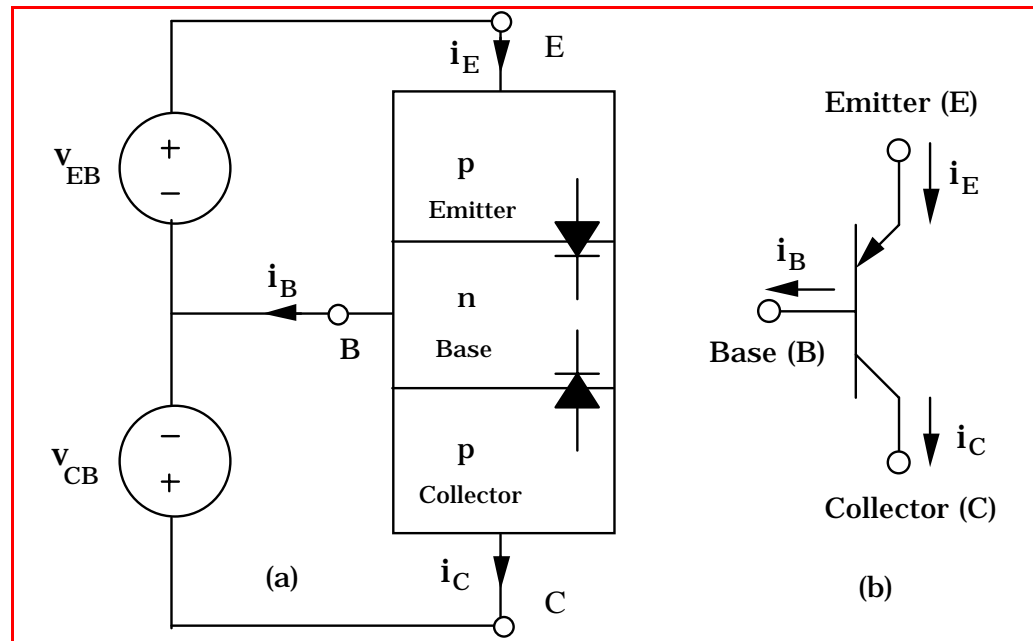

$$i_C = I_S \left\{ \exp\left(\frac{v_{EB}}{V_T}\right) - \exp\left(\frac{v_{CB}}{V_T}\right) \right\} - \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right\} .$$

$$i_E = I_S \left\{ \exp\left(\frac{v_{EB}}{V_T}\right) - \exp\left(\frac{v_{CB}}{V_T}\right) \right\} + \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right\} .$$
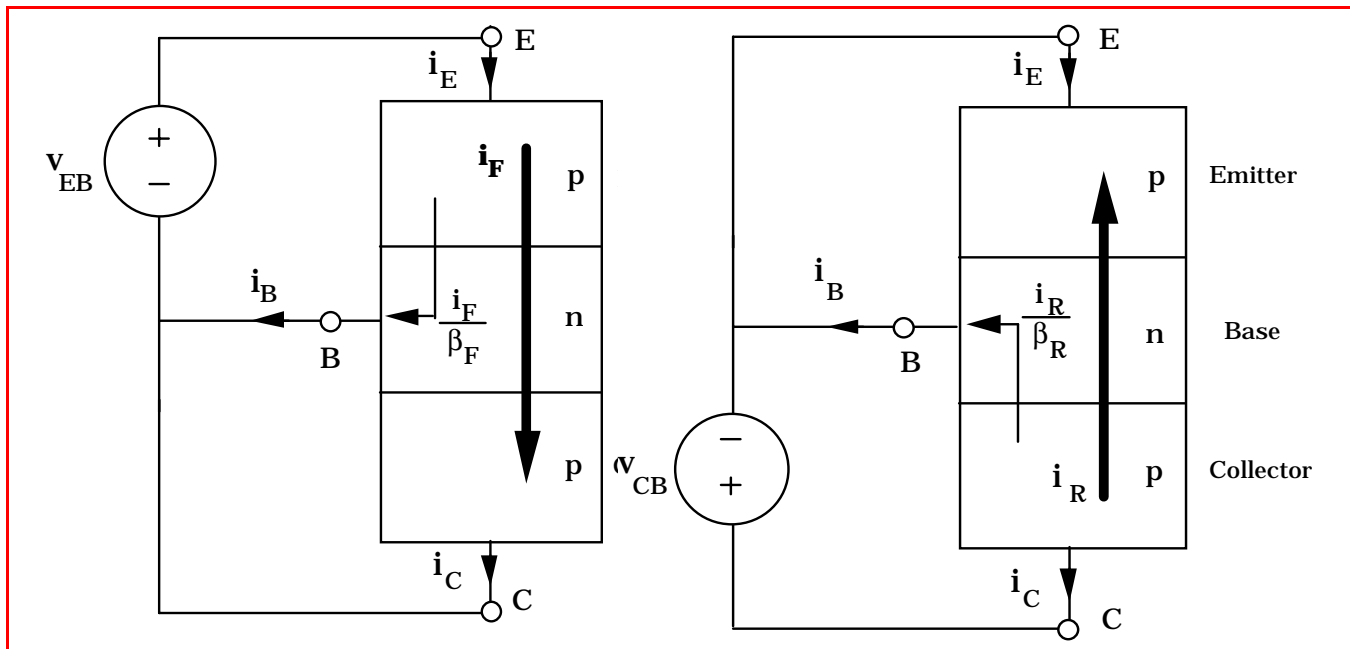
$$i_B = \frac{I_S}{\beta_F} \left\{ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right\} + \frac{I_S}{\beta_R} \left\{ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right\} .$$



## Operating Regions of the Bipolar Transistor

Each pn junction may be independently biased.

Have 4 regions of operation.

Both pn junctions reverse biased - cut-off region.

Both pn junctions forward biased - saturation region (closed switch).

**BE junction forward and BC junction reverse biased** - forward active region (normal mode). Have high current, high voltage and high power gains. ECL logic switch between cut-off and forward active (fastest bipolar logic).

**BE junction reverse and BC junction forward biased** - reverse active region (inverse-active mode). Have low common emitter gain and this mode is not often used. It is used in TTL circuits and for some analog switching applications.

<b>Base-Emitter Junction</b>	<b>Base-Collector Junction</b>	
	Forward Bias	Reverse Bias
<b>Forward Bias</b>	<b>Saturation Region (Closed Switch)</b>	Forward-Active Region (good amplifier)
<b>Reverse Bias</b>	Reverse-Active Region (poor amplifier)	<b>Cut-Off Region (open switch)</b>