

Lecture #29

Small-Signal Modeling and Linear Amplification - Part 2: BJTs

Outline/Learning Objectives:


- Describe the BJT as an amplifier.
- Define and describe the small-signal-model of the BJT.
- Analyze BJT amplifiers using a two-part process:
- dc Analysis: (1) construct the dc equivalent circuit; (2) solve for the Q-point.
- ac Analysis: (3) construct the ac equivalent circuit; (4) replace the BJT by its small-signal model; (5) solve the ac circuit.
- Analyze the BJT common-emitter (C-E) amplifier.
- Use the electronics laboratory to investigate the electrical behavior of simple circuits and devices.
-

Transistor as an Amplifier

- Small signal parameters of bipolar junction transistor (BJT)
- Voltage gain (A_V), input resistance (R_{IN}), output resistance (R_{OUT})
- Maximum input and output signal amplitudes

The Bipolar Junction Transistor Amplifier

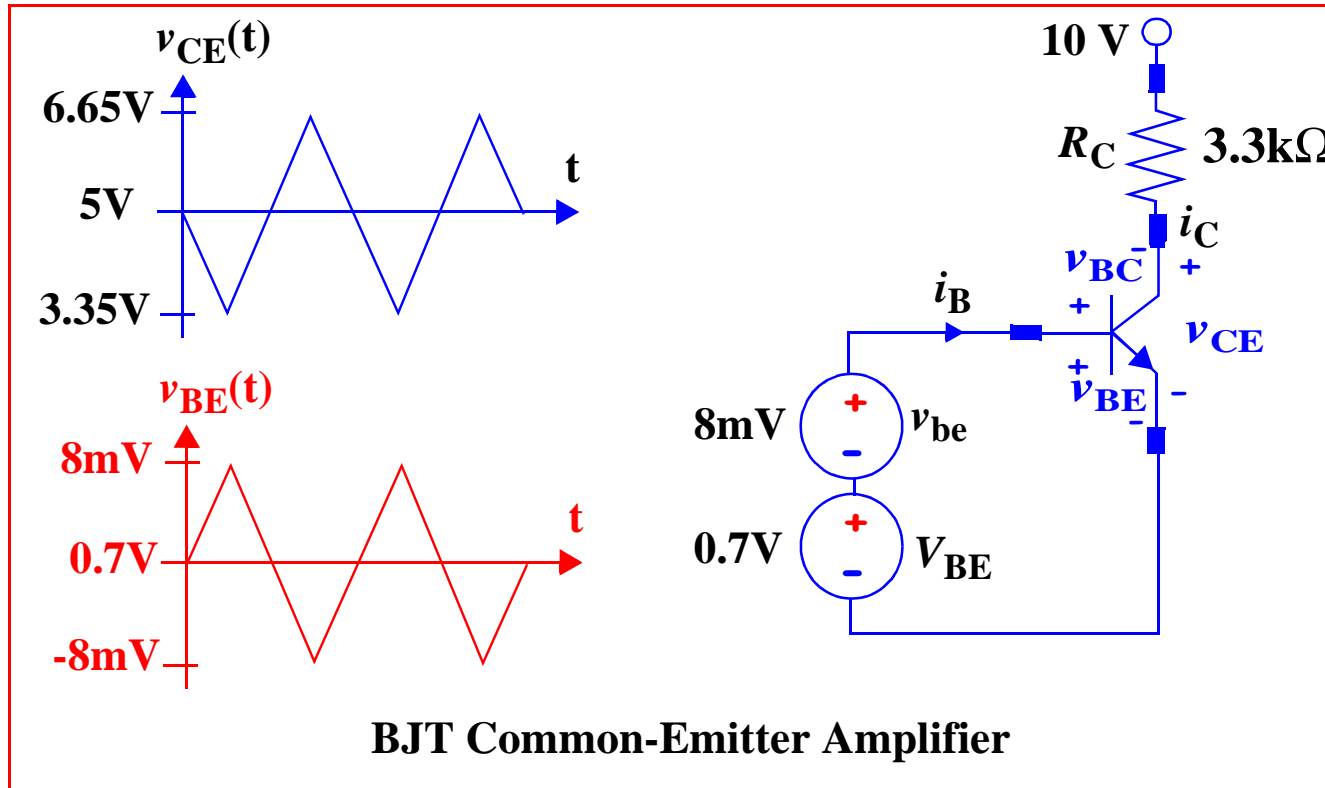
$$v_{BE} = V_{BE} + v_{be} \text{ and } 10 = v_{CE} + i_C R_C \text{ (Load-Line Equation)}$$



$$i_B = 15\mu\text{A}, i_C = 1.5\text{mA} \text{ since } \beta = 100$$

$$\text{Q-point is } i_B = 15\mu\text{A}; V_{BE} = 0.7\text{V}; i_C = 1.5\text{mA}; V_{CE} = 5\text{V}$$
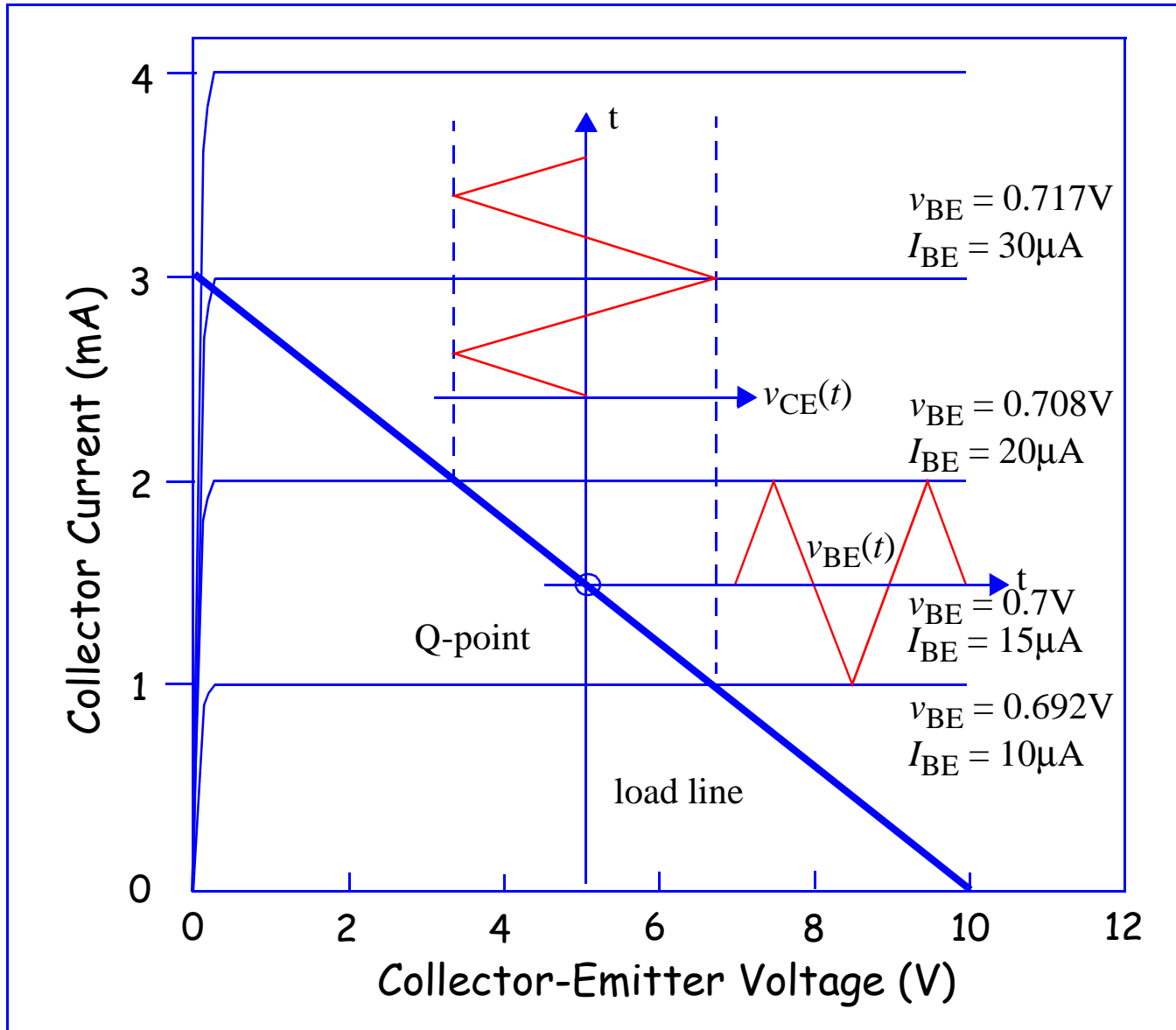
$$A_V = \frac{v_{CE}}{v_{BE}} = \frac{1.65 \angle 180}{0.008 \angle 0} = 206 \angle 180 = -206$$



Small-Signal Modeling

$$\mathbf{i}_1 = y_{11}\mathbf{v}_1 + y_{12}\mathbf{v}_2; \mathbf{i}_2 = y_{21}\mathbf{v}_1 + y_{22}\mathbf{v}_2$$

$$\mathbf{i}_b = y_{11}\mathbf{v}_{be} + y_{12}\mathbf{v}_{ce}; \mathbf{i}_c = y_{21}\mathbf{v}_{be} + y_{22}\mathbf{v}_{ce}$$


$$v_{BE} = V_{BE} + v_{be} \text{ and } v_{CE} = V_{CE} + v_{ce}$$

$$i_B = I_B + i_b \text{ and } i_C = I_C + i_c.$$

$$v_{be} = \Delta v_{BE} = v_{BE} - V_{BE} \text{ and}$$

$$v_{ce} = \Delta v_{CE} = v_{CE} - V_{CE}.$$
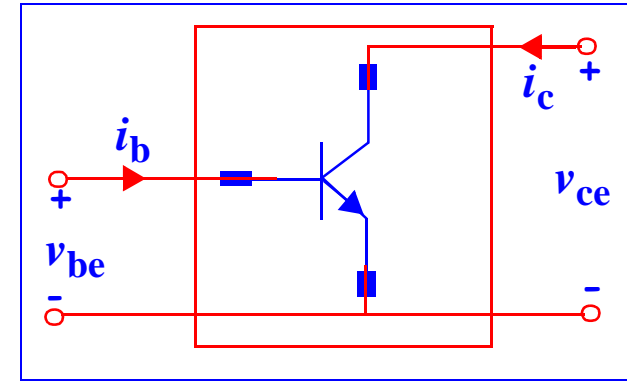
$$i_b = \Delta I_B = i_B - I_B \text{ and } i_c = \Delta I_C = i_C - I_C.$$



$$y_{11} = \left. \frac{\mathbf{i}_b}{\mathbf{v}_{be}} \right|_{\mathbf{v}_{ce}=0} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q-P}; \quad y_{12} = \left. \frac{\mathbf{i}_b}{\mathbf{v}_{ce}} \right|_{\mathbf{v}_{ce}=0} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q-P}$$

$$y_{21} = \left. \frac{\mathbf{i}_c}{\mathbf{v}_{be}} \right|_{\mathbf{v}_{be}=0} = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-P}; \quad y_{22} = \left. \frac{\mathbf{i}_c}{\mathbf{v}_{ce}} \right|_{\mathbf{v}_{be}=0} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q-P}$$



$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right) \left[1 + \frac{v_{CE}}{V_A}\right]; \quad \beta_F = \beta_{F0} \left[1 + \frac{v_{CE}}{V_A}\right]; \quad i_B = \frac{I_S}{\beta_{F0}} \exp\left(\frac{v_{BE}}{V_T}\right).$$

β_{F0} is the value of β_F extrapolated to $v_{CE} = 0$.

Things To Remember

Y parameters have equivalent circuit representation

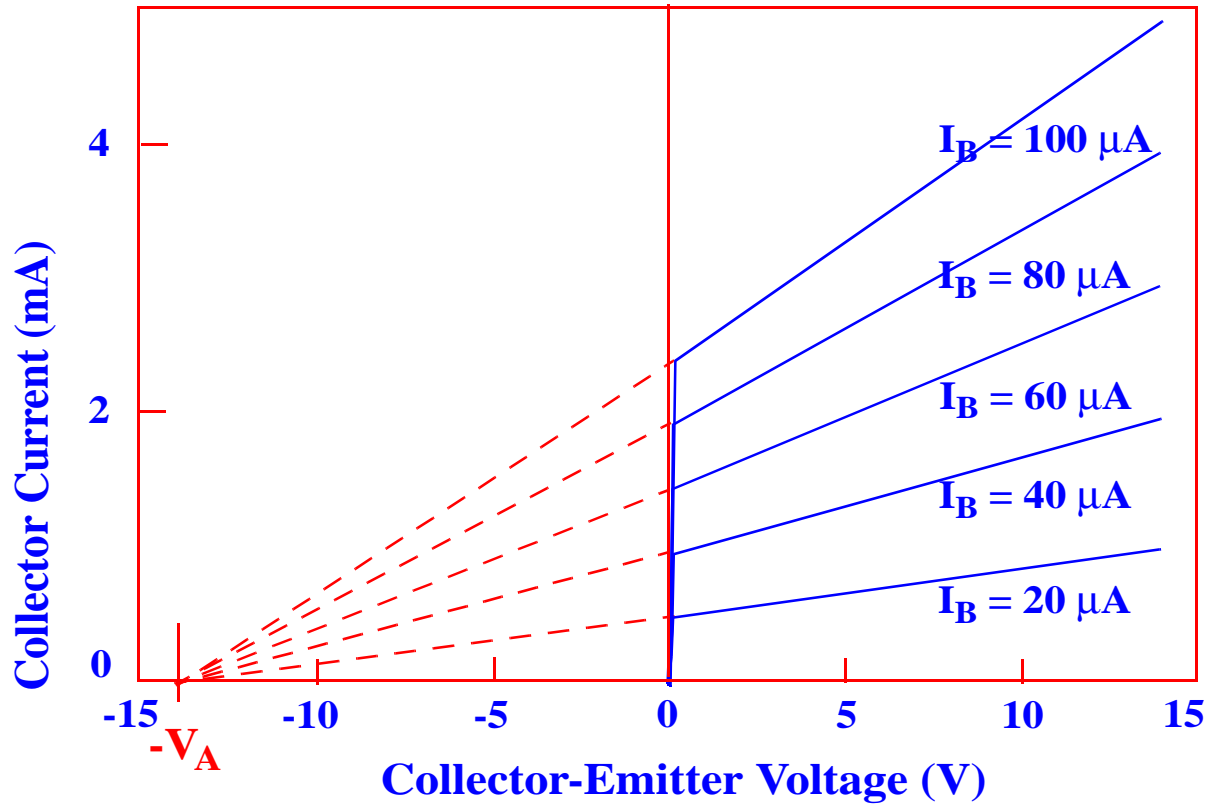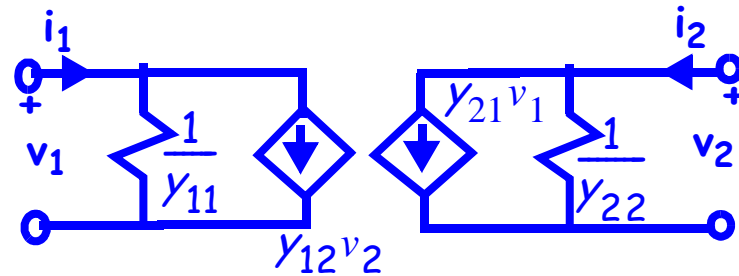The current gain is actually a function of both the BE and BC voltages



$$y_{12} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q-P} = 0$$

$$y_{21} = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-P} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] = \frac{I_C}{V_T} = g_m$$


$$y_{22} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q-P} = \frac{I_S}{V_A} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_A + V_{CE}} = \frac{1}{r_o}$$

$$y_{11} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q-P} = \frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} - \frac{i_C \partial \beta_F}{\beta_F^2 \partial v_{BE}} = \frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} - \frac{i_C \partial \beta_F \partial i_C}{\beta_F^2 \partial i_C \partial v_{BE}}$$

$$y_{11} = \frac{1}{\beta_F} \frac{\partial i_C}{\partial v_{BE}} \left(1 - \frac{i_C \partial \beta_F}{\beta_F \partial i_C}\right) = \frac{I_C}{\beta_F V_T} \left(1 - \frac{i_C \partial \beta_F}{\beta_F \partial i_C}\right) = \frac{I_C}{\beta_0 V_T} = \frac{1}{r_\pi}$$

Here, $\beta_0 = \frac{\partial i_C}{\partial i_B}$ is the small-signal common-emitter current gain.

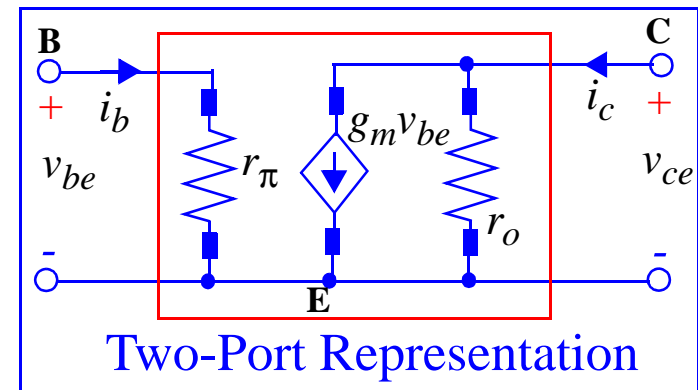The Hybrid-pi small-signal model of the BJT is as shown.



For $\beta_0 = 100$, $V_A = 75V$, $V_T = 25mV$ and, $V_{CE} = 10V$, we get

I_C	g_m	r_π	r_o	μ_f
1 μA	4×10^{-5} S	2.5 M Ω	85 M Ω	3400
10 μA	4×10^{-4} S	250 k Ω	8.5 M Ω	3400
100 μA	0.004 S	25 k Ω	850 k Ω	3400
1 mA	0.04 S	2.5 k Ω	85 k Ω	3400
10 mA	0.4 S	250 Ω	8.5 k Ω	3400

Summary: $y_{11} = I_C / (\beta_0 V_T) = 1/r_\pi$ and $y_{12} = 0$

$y_{21} = I_C / V_T = g_m$ and $y_{22} = I_C / (V_A + V_{CE}) = 1/r_o$

Small-Signal Current Gain


$$\beta_0 = g_m r_\pi$$

$$\frac{\partial \beta_F}{\partial i_C} > 0 \text{ for } i_C < I_M$$

$$\frac{\partial \beta_F}{\partial i_C} < 0 \text{ for } i_C > I_M$$

where

$$\beta_0 = \frac{\beta_F}{1 - I_C \left(\frac{1}{\beta_F} \frac{\partial \beta_F}{\partial i_C} \right)} \Bigg|_{Q-P}$$

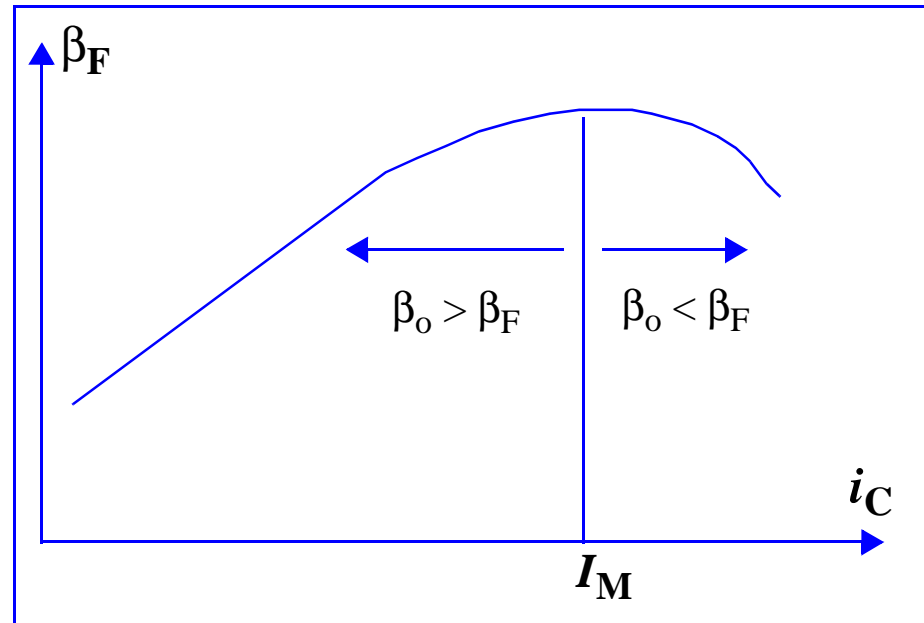


Amplification Factor (p. 600)

$$\mu_f = g_m r_o = \frac{I_C}{V_T} \cdot \frac{V_A + V_{CE}}{I_C} = \frac{V_A + V_{CE}}{V_T} \approx \frac{V_A}{V_T}$$

This is the maximum voltage gain an individual transistor can provide.

Equivalent Forms of Small-Signal Model
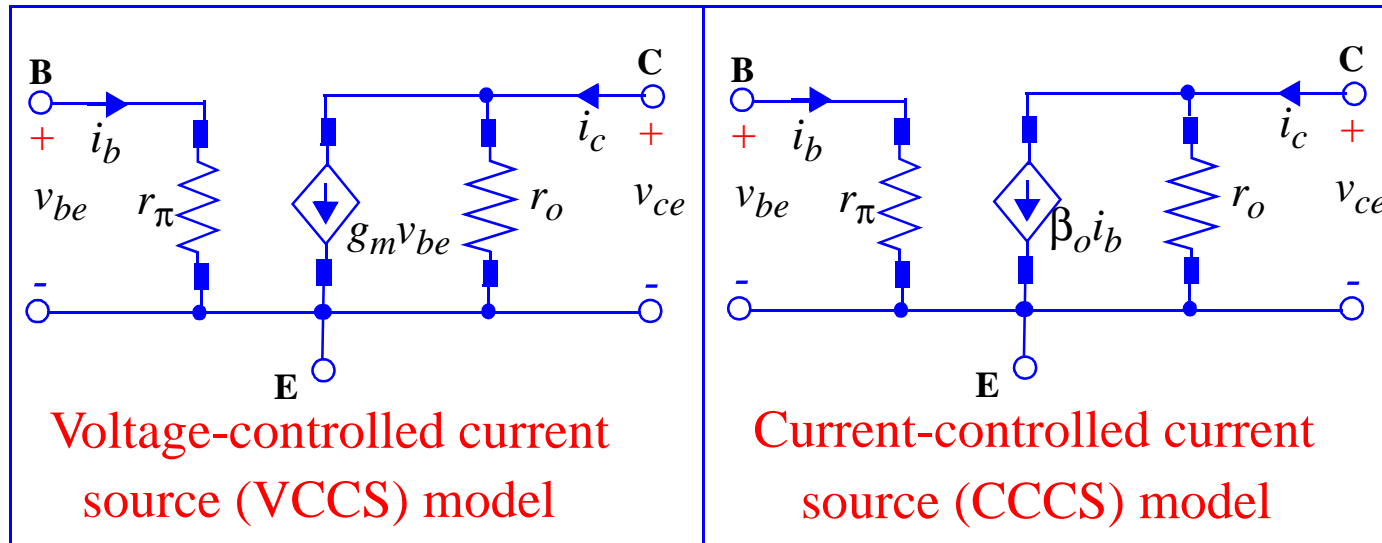
$$v_{be} = i_b r_\pi, \quad g_m v_{be} = g_m r_\pi i_b = \beta_o i_b \quad \text{and} \quad i_c = \beta_o i_b + \frac{v_{ce}}{r_o} \approx \beta_o i_b$$



Definition of Small-Signal for the BJT (p. 602)

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right) = I_S \exp\left(\frac{V_{BE} + v_{be}}{V_T}\right)$$

$$I_C + i_c = \left\{ I_S \exp\left(\frac{V_{BE}}{V_T}\right) \right\} \exp\left(\frac{v_{be}}{V_T}\right) = I_C \exp\left(\frac{v_{be}}{V_T}\right)$$

Using $i_C = I_C \left[1 + \frac{v_{be}}{V_T} + \frac{1}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{1}{6} \left(\frac{v_{be}}{V_T} \right)^3 + \dots \right]$ and $i_c = i_C - I_C$, we get

from $i_c = i_C - I_C$ that $i_c = I_C \left[\frac{v_{be}}{V_T} + \frac{1}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{1}{6} \left(\frac{v_{be}}{V_T} \right)^3 + \dots \right]$.

Now linearity requires that $\frac{1}{2} \left(\frac{v_{be}}{V_T} \right)^2 \ll \frac{v_{be}}{V_T}$ or $v_{be} \ll 2V_T$.

Using a factor of 10 to satisfy the inequality, we get, $|v_{be}| \leq 5mV$.

Now, we can write that $i_C \approx I_C \left[1 + \frac{v_{be}}{V_T} \right] = I_C + g_m v_{be}$.

$$\frac{i_c}{I_C} = \frac{i_C - I_C}{I_C} = \frac{g_m v_{be}}{I_C} = \frac{v_{be}}{V_T} \leq \frac{5mV}{25mV} = 0.20.$$

A 5 mV change in v_{BE} corresponds to a 20% deviation in i_C from its Q-point as well as a 20% change in i_E since $i_E \sim i_C$.

Summary of BJT Small-Signal Parameters

Parameter	BJT
Transconductance g_m	I_C/V_T
Input Resistance R_{IN}	$r_\pi = \beta_o/g_m = \beta_o V_T/I_C$
Output Resistance R_{OUT}	$(V_A + V_{CE})/I_C \approx V_A/I_C$
Amplification Factor μ_f	$g_m r_o = (V_A + V_{CE})/V_T$
Small-Signal Requirement	$v_{be} \leq 5mV$

Small-Signal Model for the pnp BJT

This is identical to that of the npn transistor.

Remember that the dc currents in a pnp transistor flow in an opposite direction to that in a npn transistor.