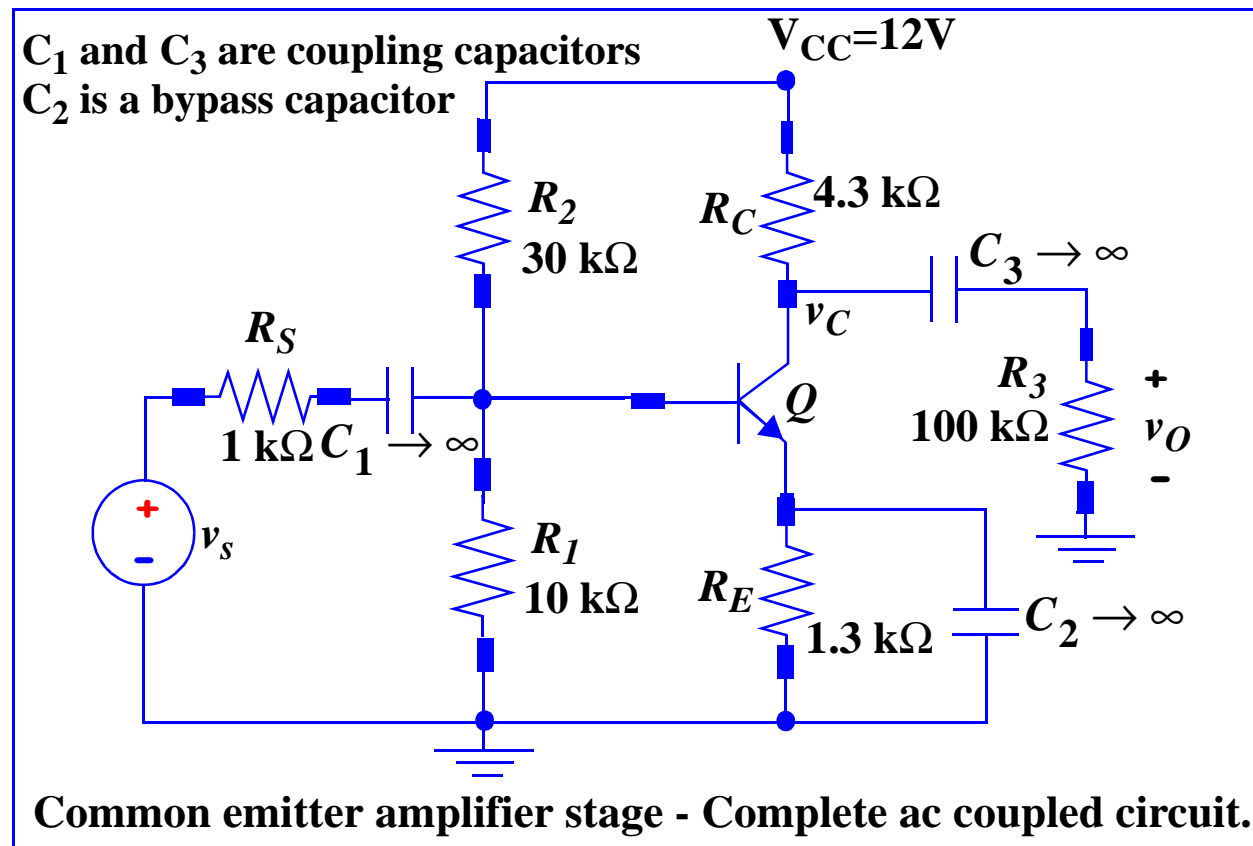


Coupling and Bypass Capacitors

Coupling capacitors (or dc blocking capacitors) are used to decouple ac and dc signals so as not to disturb the quiescent point of the circuit when ac signals are injected at the input.

Bypass capacitors are used to force signal currents around elements by providing a low impedance path at the frequency.



Circuit Analysis - dc & ac Equivalent Circuits


DC Analysis

1. Find dc equivalent circuit. C 's replaced by open circuits and L 's replaced by short circuits.
2. Find Q-point from dc equivalent circuit using appropriate large-signal model for transistor.


AC Analysis

3. Find ac equivalent circuit. C 's replaced by short circuits and L 's replaced by open circuits. DC voltage sources are replaced by ground connections and dc current sources by open circuits in ac equivalent circuit.
4. Replace transistor by small-signal model.
5. Analyze ac characteristics from small-signal ac equivalent circuit.
6. Combine results from #2 and #5 to get total voltages and currents in complete network.

BJT Common-Emitter Amplifier

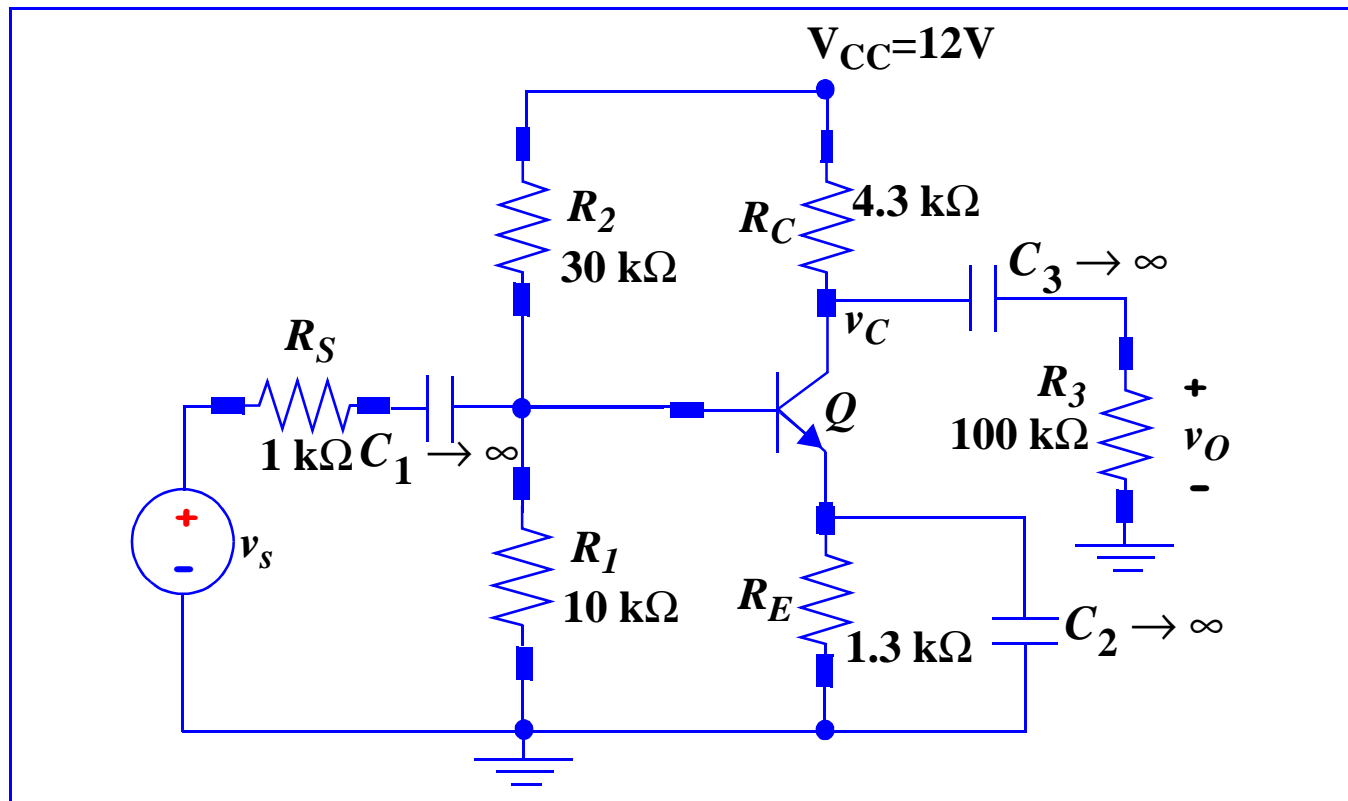




DC Analysis

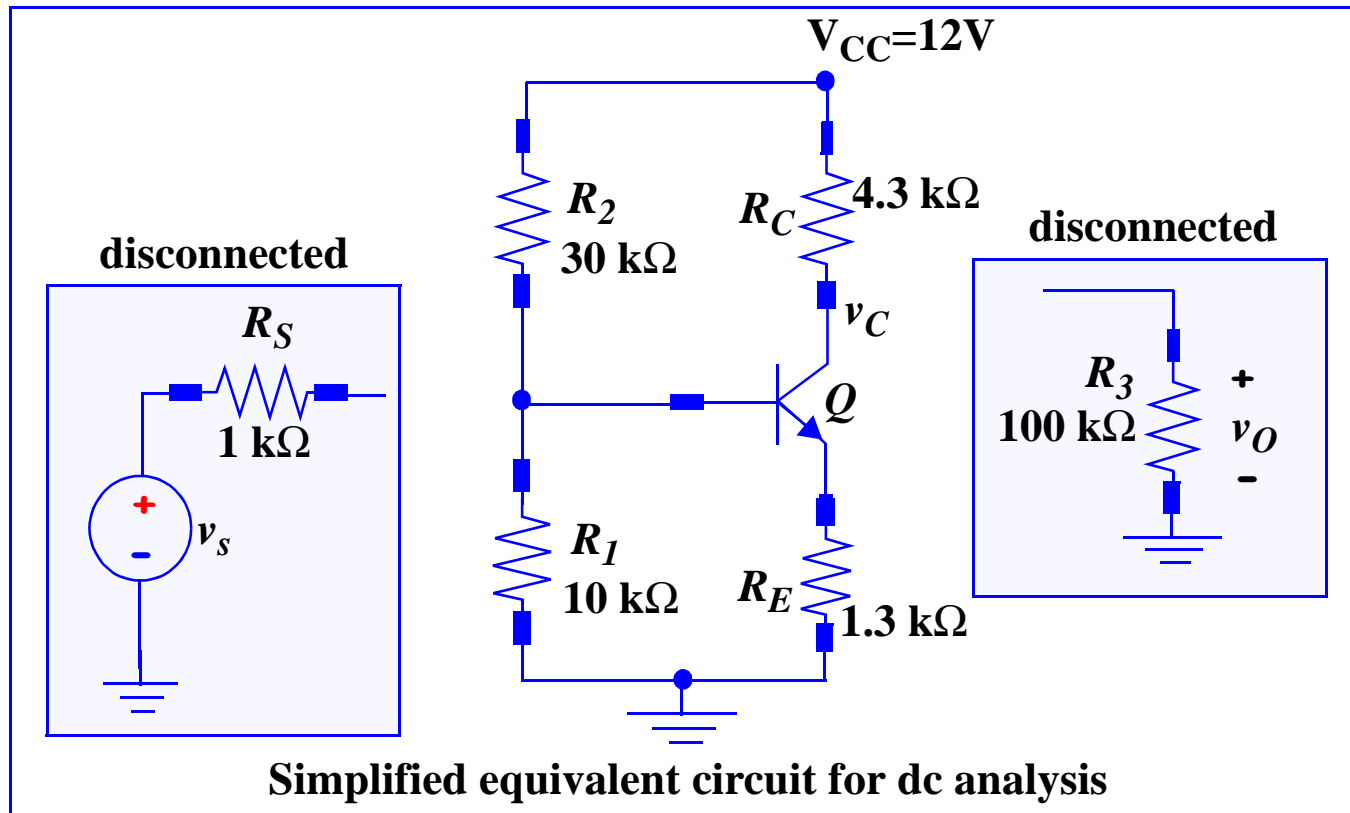


The Q-point is $I_C = 201.5 \mu\text{A}$, $V_{CE} = 4.30 \text{ V}$.

AC Analysis

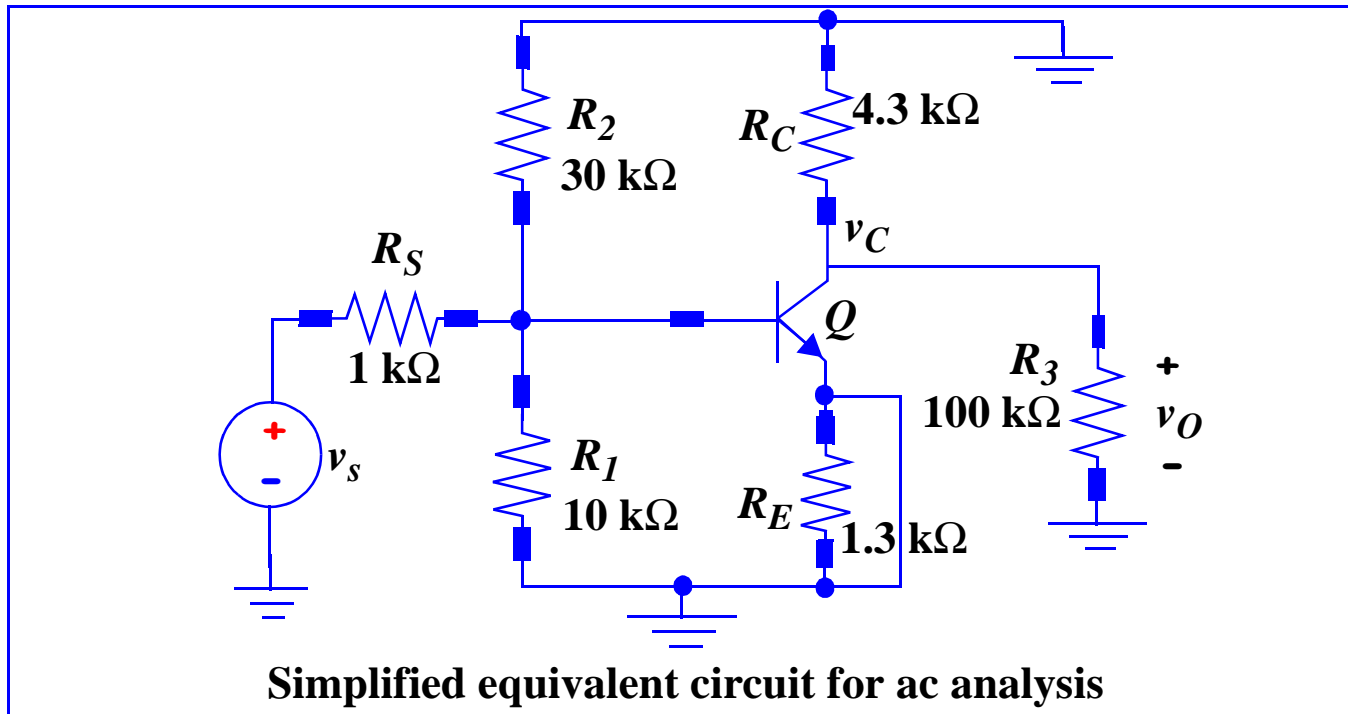

 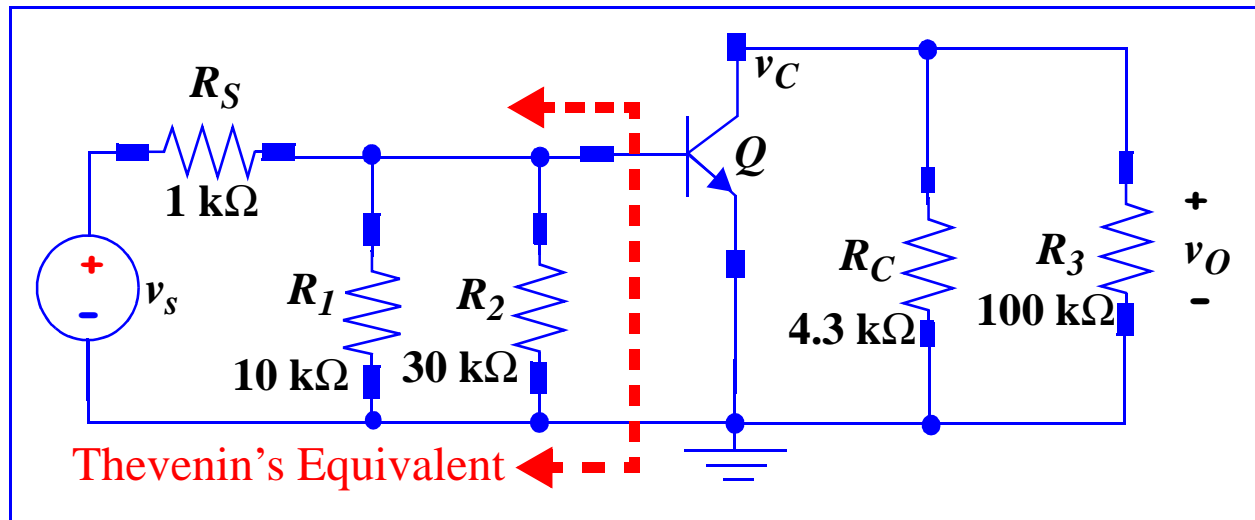

Simplified ac equivalent circuit.

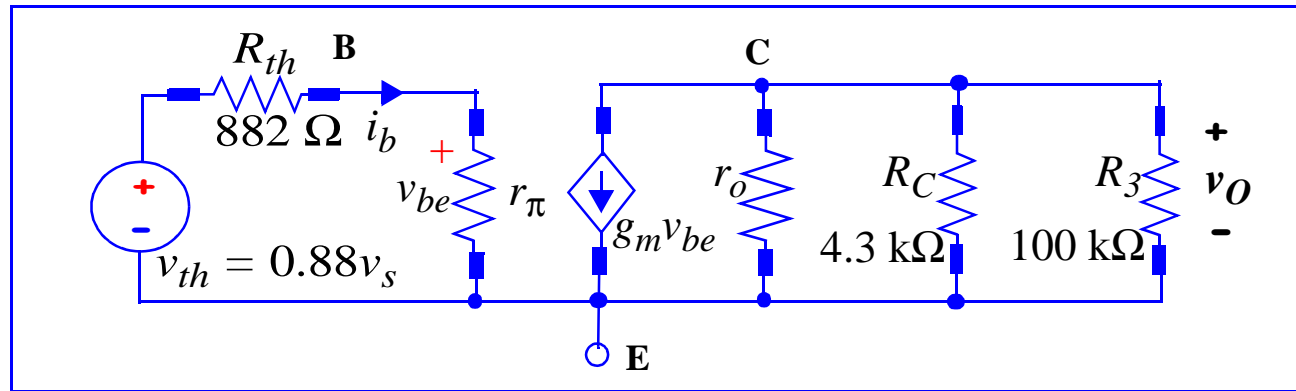

AC Equivalent Circuit with BJT replaced with its SS model.


Final equivalent circuit of common-emitter amplifier.

$$R_B = R_1 \parallel R_2; R_{th} = R_S \parallel R_B;$$

$$v_{th} = \frac{R_B}{R_S + R_B} v_s$$

$$v_{be} = v_{th} \cdot \frac{r_\pi}{r_\pi + R_{th}}$$

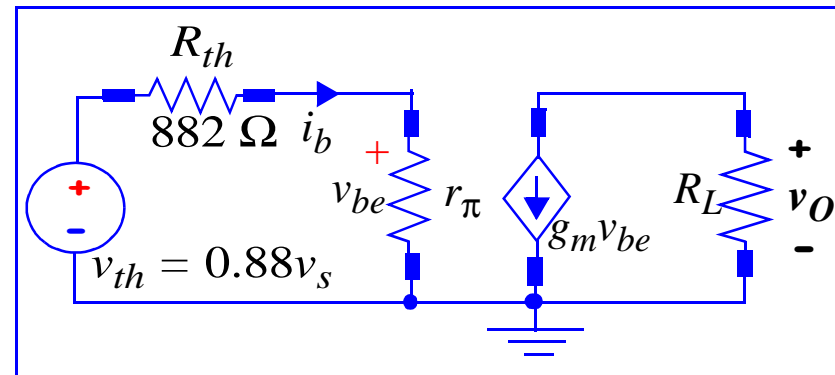The load resistance is $R_L = r_o \parallel R_C \parallel R_3$



Final equivalent circuit of common-emitter amplifier.

$$R_B = R_1 \parallel R_2; R_{th} = R_S \parallel R_B;$$

$$v_{th} = \frac{R_B}{R_S + R_B} v_s$$


$$v_{be} = v_{th} \cdot \frac{r_\pi}{r_\pi + R_{th}}$$

The load resistance is $R_L = r_o \parallel R_C \parallel R_3$

Voltage Gain $A_{V,th} = \frac{v_o}{v_{th}} = - \frac{g_m v_{be} R_L}{v_{th}}$

$$A_V = \frac{v_o}{v_s} = \frac{-g_m r_\pi R_L}{r_\pi + R_{th}} \left(\frac{R_B}{R_S + R_B} \right) = \frac{-\beta_o R_L}{r_\pi + R_{th}} \left(\frac{R_B}{R_S + R_B} \right)$$
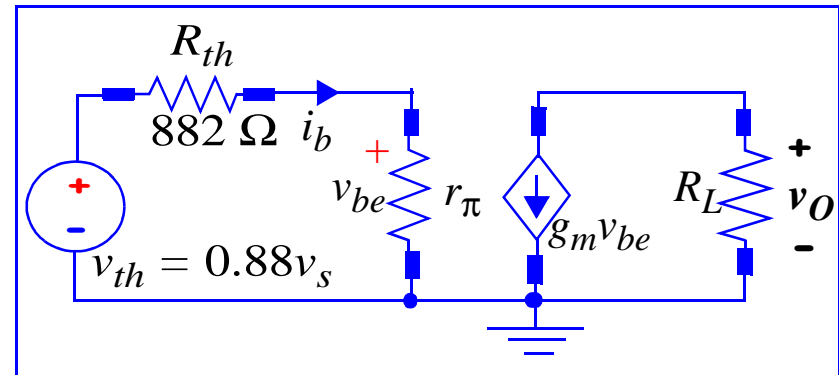
$$A_V = \frac{v_o}{v_s} = \frac{-g_m R_L}{1 + \frac{R_{th}}{r_\pi}} \cdot \frac{1}{1 + \frac{R_S}{R_B}}$$



Model Simplifications

Generally $R_S \ll R_B$ and $R_{th} \ll r_\pi$, so $A_V = -g_m R_L = -g_m (r_o \parallel R_C \parallel R_3)$.

This is the mismatched condition.

Design Guide for CE BJT Amplifier

Typically, $r_o \gg R_3$ and in design, $R_3 \gg R_C$, so $r_o \parallel R_C \parallel R_3 \approx R_C$.

Therefore, $A_V = -g_m R_L \approx -g_m R_C = \frac{-I_C R_C}{V_T}$.

Putting $I_C R_C = \zeta V_{CC}$ with $0 \leq \zeta \leq 1$, we get $A_V \approx \frac{-\zeta V_{CC}}{V_T} \approx -40\zeta V_{CC}$.


For $\zeta = 0.25$, we get, $A_V \approx -10V_{CC}$


Upper Bound for CE Voltage Gain

Letting $R_L \rightarrow r_o$ and in design, $R_3, R_C \rightarrow \infty$, we get

$$A_V = -g_m r_o = -\mu_f.$$


Input Resistance of CE BJT Amplifier

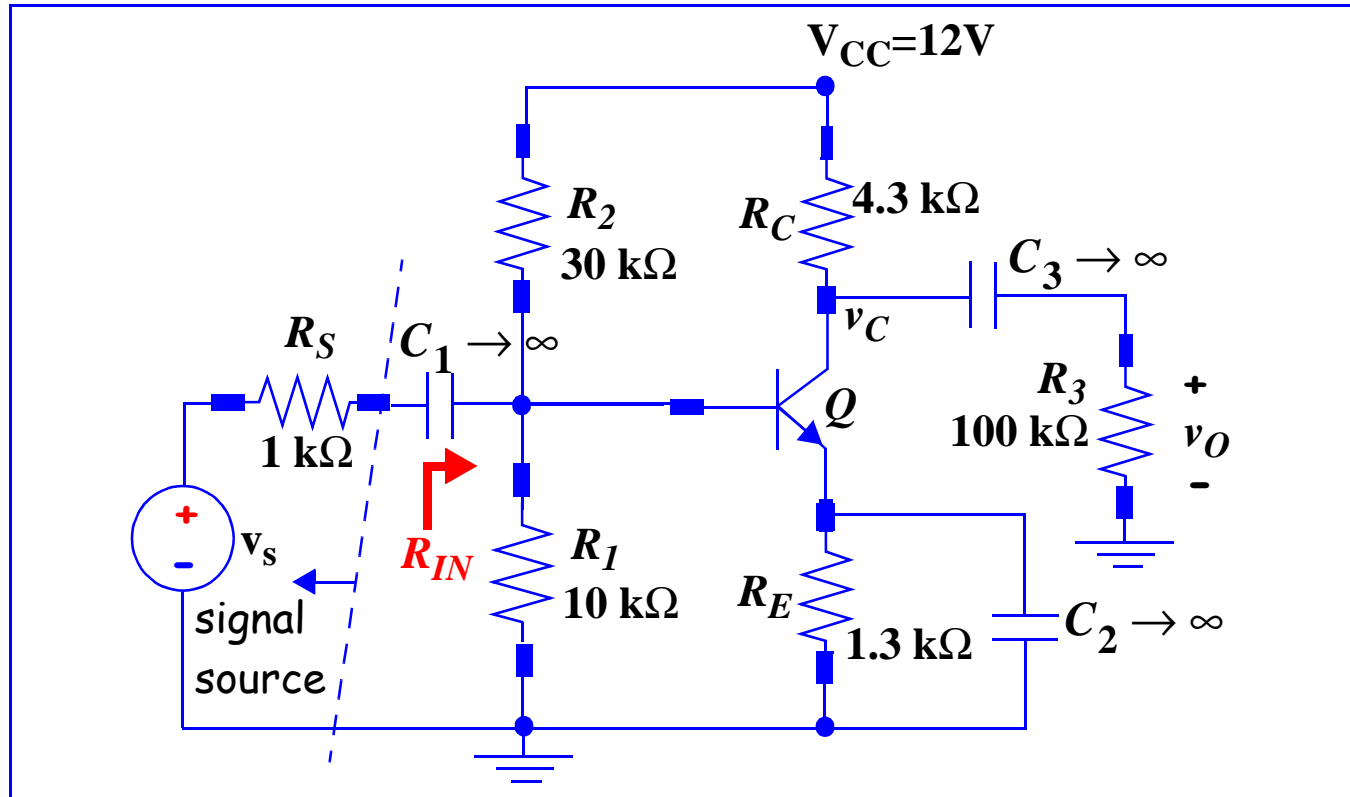


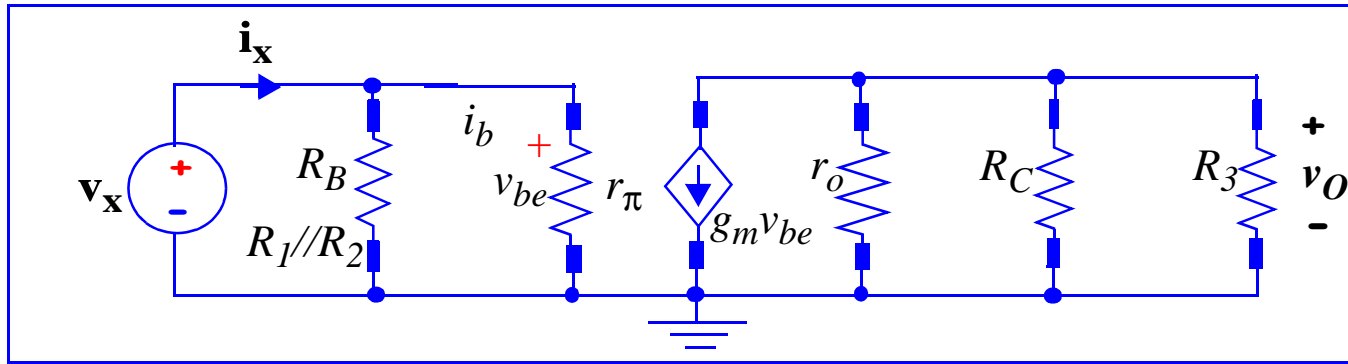

$$v_x = i_x (R_B \parallel r_\pi) \text{ and } R_{IN} = \frac{v_x}{i_x} = R_B \parallel r_\pi = R_1 \parallel R_2 \parallel r_\pi$$

Output Resistance of CE BJT Amplifier

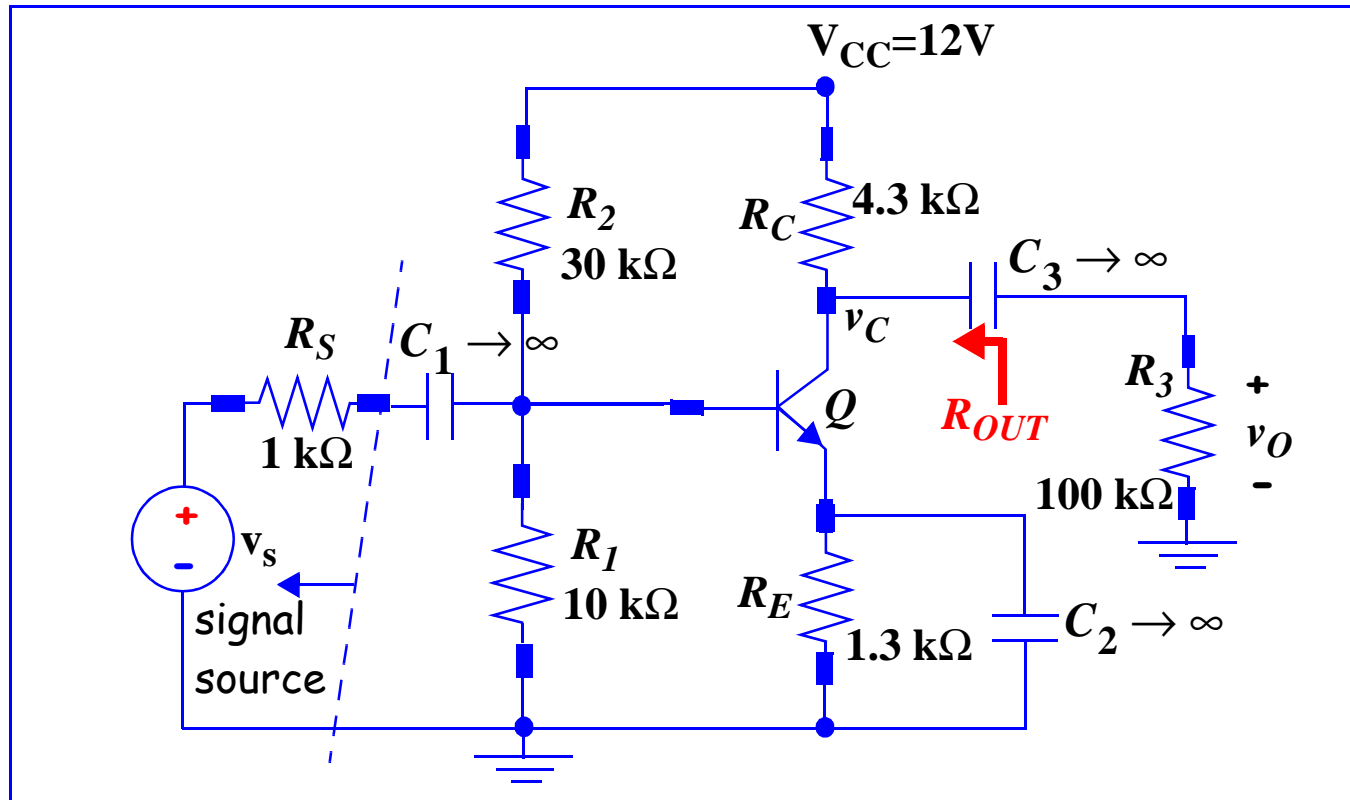


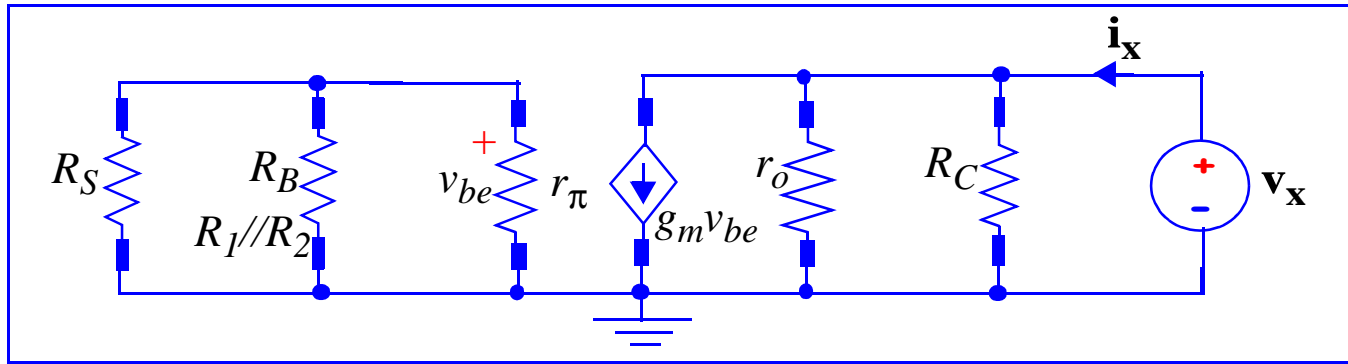

$$i_x = \frac{v_x}{R_C} + \frac{v_x}{r_o} + g_m v_{be}. \text{ No excitation at the base node, so } v_{be} = 0.$$

$$R_{OUT} = \frac{v_x}{i_x} = R_C \parallel r_o. \quad I_C r_o \approx V_A \quad \text{and} \quad I_C R_C \approx \frac{V_{CC}}{2}.$$

PSPICE EXAMPLE

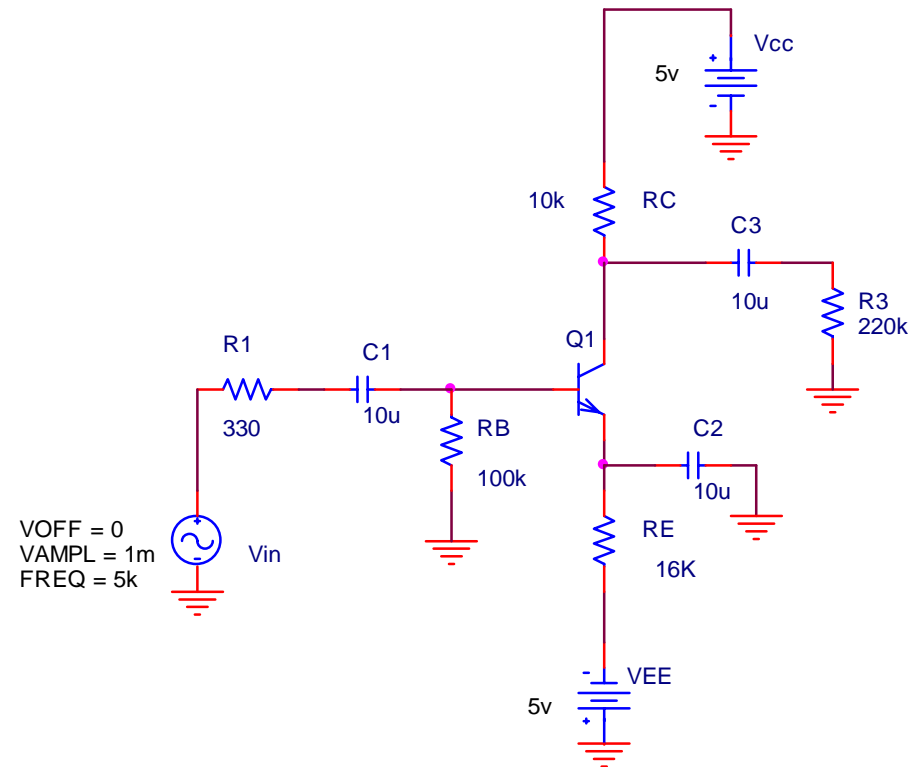

***Libraries:**

*** Local Libraries :**

.LIB ".\example12.lib"

*** From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:**

.lib "nom.lib"

***Analysis directives:**

.TRAN 0 5ms 0 1u

.PROBE V(*) I(*) W(*) D(*) NOISE(*)

.INC ".\example12-SCHEMATIC1.net"

PSPICE EXAMPLE (Cont'd)

**** INCLUDING example12-SCHEMATIC1.net ****

* source EXAMPLE12

```
R_RC      N00280 N00349 10k
R_RE      N00334 N00307 16K
R_R3      0 N00527 220k
V_Vin     N00822 0
+SIN 0 1m 5k 0 0 0
R_R1      N00726 N00822 330
R_RB      N00656 0 100k
C_C1      N00726 N00656 10u
V_Vcc     N00349 0 5v
C_C3      N00280 N00527 10u
V_VEE     0 N00334 5v
C_C2      N00307 0 10u
Q_Q1      N00280 N00656 N00307 Qbreakn
```

**** RESUMING example12-SCHEMATIC1-Example12Profile.sim.cir ****

.END

**** BJT MODEL PARAMETERS

```
Qbreakn
NPN
IS 100.000000E-18
BF 65
NF 1
VAF 1.000000E+03
BR 1
NR 1
CN 2.42
```

PSPICE EXAMPLE (Cont'd)

D .87

*** INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N00280)	2.6024	(N00307)	-1.1050	(N00334)	-5.0000	(N00349)	5.0000
(N00527)	0.0000	(N00656)	-.3678	(N00726)	0.0000	(N00822)	0.0000

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
------	---------

V_Vin	0.000E+00
-------	-----------

V_Vcc	-2.398E-04
-------	------------

V_VEE	-2.434E-04
-------	------------

