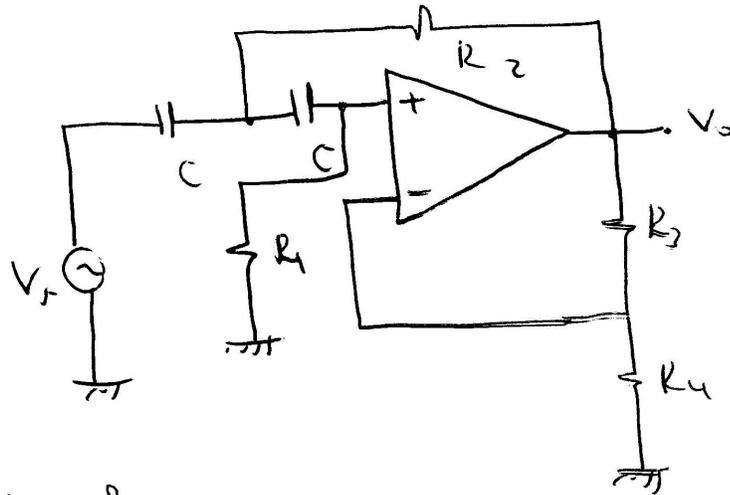



Quiz 1 Answers

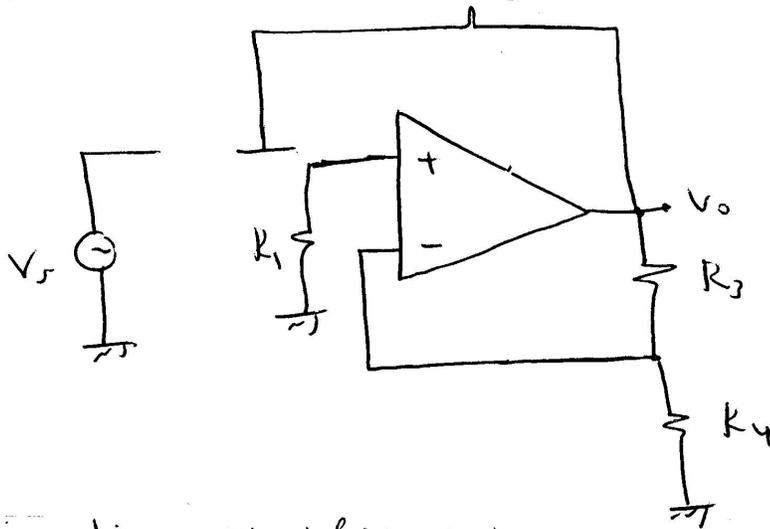(1)



at low frequencies


$\frac{1}{Cs} \rightarrow \infty$ & circuit becomes



Noninverting amplifier with
Zero input $\Rightarrow V_o = 0$ regardless of V_s

gain = 0

②

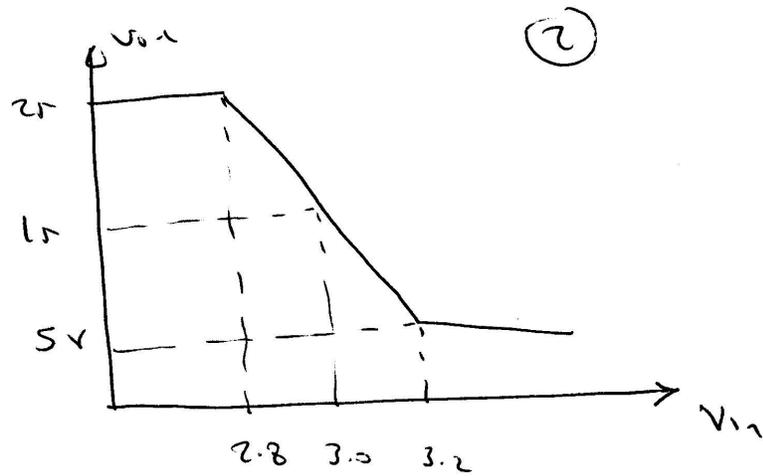


②

$$g_{air} = \frac{\Delta y}{\Delta x} = \frac{5 - 15}{3.2 - 3.0} = \frac{-10}{0.2} = -50$$

$$\begin{aligned} V_{out} &= 15 + g_{air} \times V_{in} \\ &= 15 - 50 \times 0.1 \sin \omega t \\ V_{out} &= 15 - 5 \sin \omega t \end{aligned}$$

③

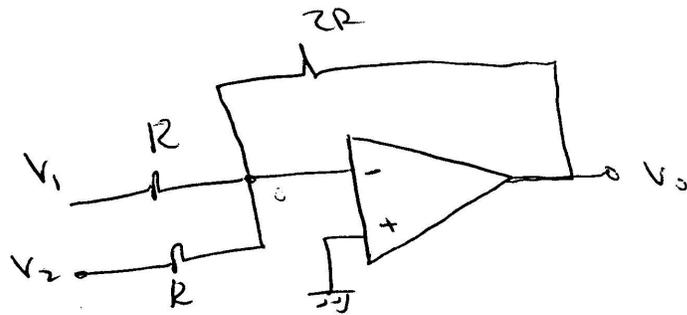


$$\begin{aligned} V_o &= -2(V_1 + V_2) \\ V_o &= A_{CM} \left(\frac{V_1 + V_2}{2} \right) + A_d (V_1 - V_2) \\ \therefore A_d &= 0 \\ A_{CM} &= -4 \end{aligned}$$

Student Name:

ID:

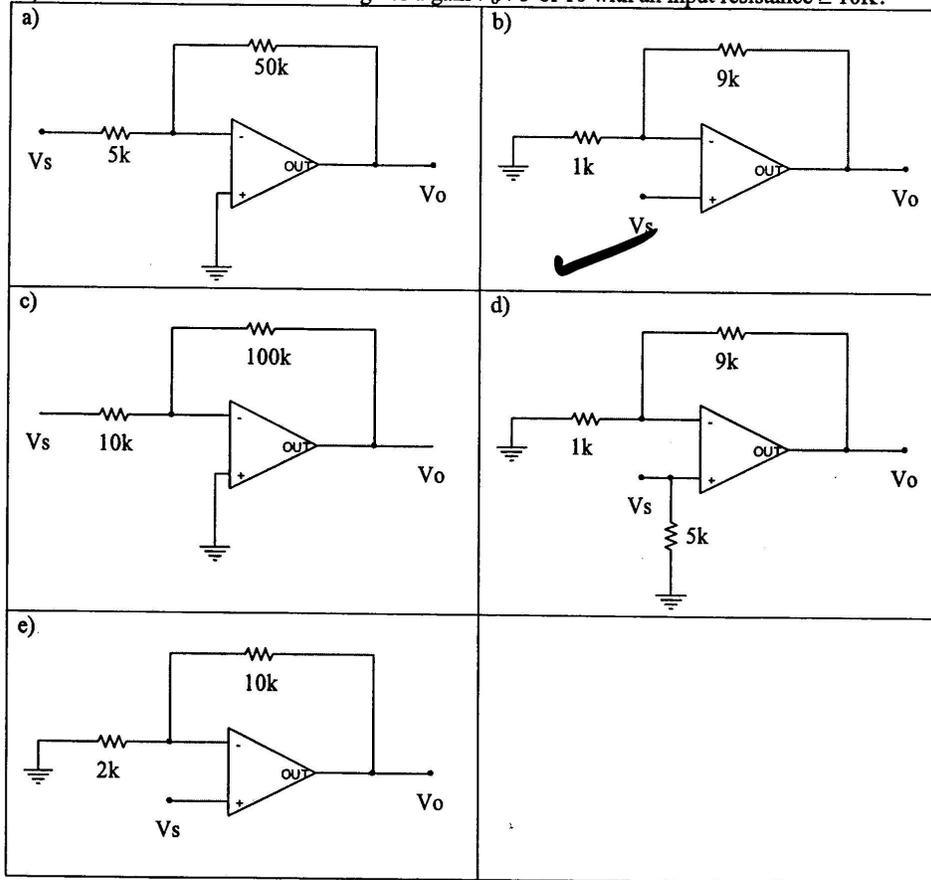4) Which one of the shown circuits gives a gain V_o/V_s of 10 with an input resistance $\geq 10K$?



5) A 5-bit A/D converter has $V_{Ref}=10V$. The digital output word and the quantization error corresponding to an input $V_{in}=4.375V$ are

- a) 01110, 0
- b) 01101, -ve
- c) 01111, +ve
- d) 10000, +ve
- e) 01011, -ve

⑤

$$4.375 = (z^{-1}b_1 + z^{-2}b_2 + z^{-3}b_3 + \dots) \big|_{z=0}$$


$$0.4375 = b_1 z^{-1} + b_2 z^{-2} + b_3 z^{-3} + b_4 z^{-4} + b_5 z^{-5}$$

or

$$1/4 = 16b_1 + 8b_2 + 4b_3 + 2b_4 + b_5$$

$\therefore b_1 = 0, b_2 = 0, b_3 = 0, b_4 = 1, b_5 = 0$


01110 error = 0

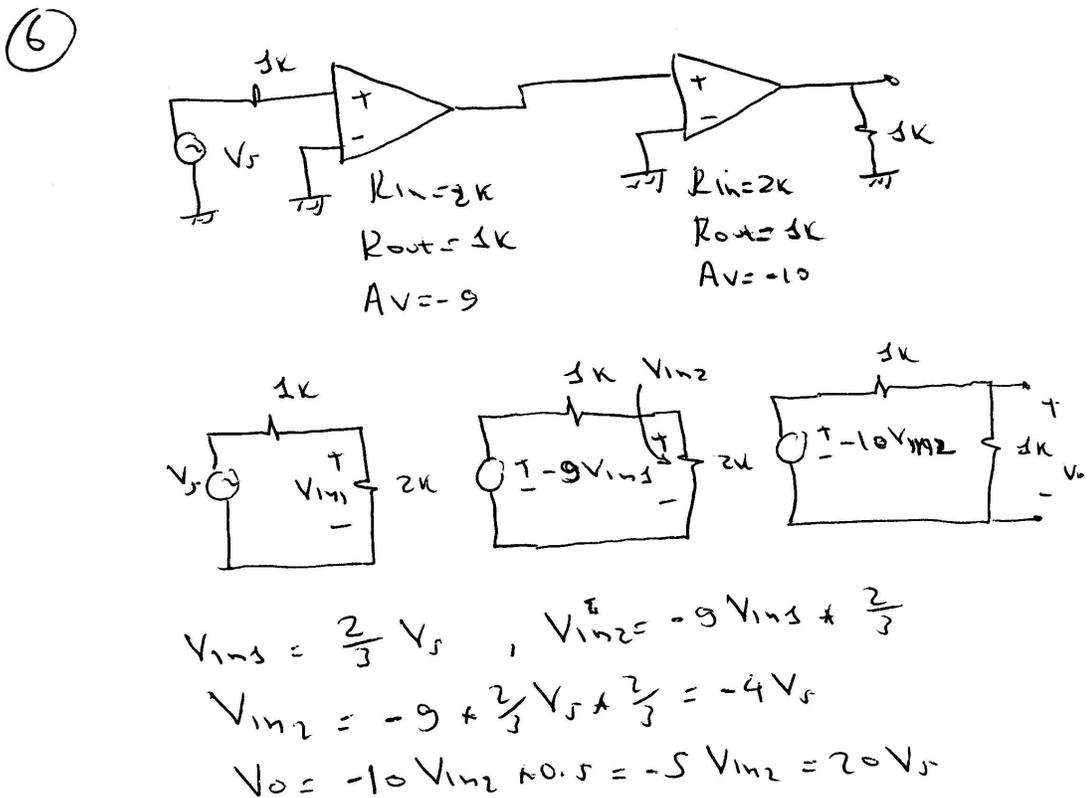


(7)

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

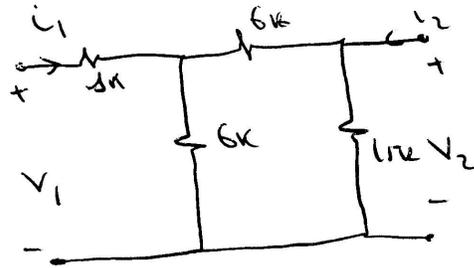


To get h_{11} & h_{21} we set $V_2 = 0$

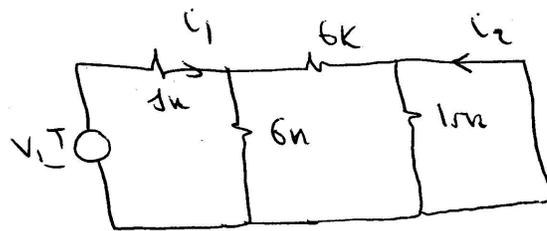

$$\frac{V_1}{i_1} = h_{11} = 4k$$

$$h_{21} = \frac{i_2}{i_1} = -0.5$$

(8)

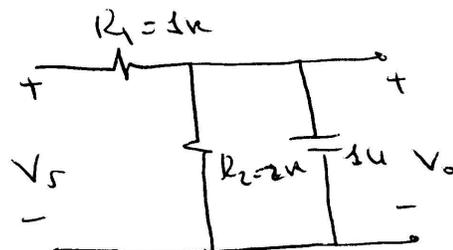

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{R_2 \times \frac{1}{sC}}{R_1 + \frac{R_2 + \frac{1}{sC}}{R_2 + \frac{1}{sC}}} V_s = \frac{R_2}{1 + sCR_2} V_s$$

$$\frac{V_o}{V_s} = \frac{R_2}{R_2 + R_1(1 + sCR_2)} = \frac{R_2}{R_2 + R_1 + sCR_1R_2}$$

$$\therefore \frac{V_o}{V_i} = \frac{R_2}{(R_1+R_2)} \times \frac{1}{1 + \frac{sCR_1R_2}{(R_1+R_2)}} = \frac{A}{1 + \frac{s}{\omega_H}}$$

$$\therefore A = \frac{R_2}{(R_1+R_2)} = \frac{2k}{2k+2k} = 0.666$$

$$\omega_H = \frac{(R_1+R_2)}{R_1R_2C} = \frac{3k}{2 \times 10^6 \times 10^{-6}} = 1.5k \text{ rad/sec}$$
