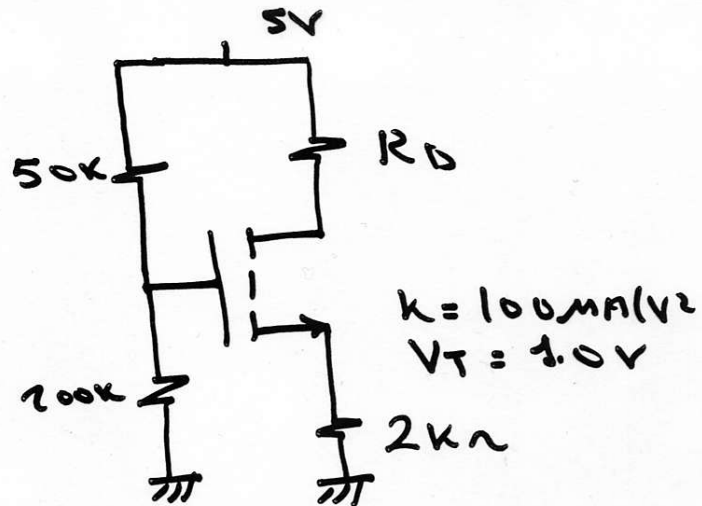


①



If $I_{DS} = 0.29 \text{ mA}$, what is the largest value of R_D to remain in saturation?

$$V_G = 5 \times \frac{200}{250} = 4 \text{ V}$$

$$V_S = 0.29 \times 10^{-3} \times 2\text{k} = 0.58 \text{ V}$$


$$\therefore V_{GS} = V_G - V_S = 3.42 \text{ V}$$

$$V_{GS} - V_{TN} = 2.42 \text{ V}$$

$$\therefore V_{DS} \gg 2.42 \Rightarrow 5 - 0.29 R_D \gg 2.42$$

$$R_D \leq 8.35 \text{ k}\Omega$$

(2)

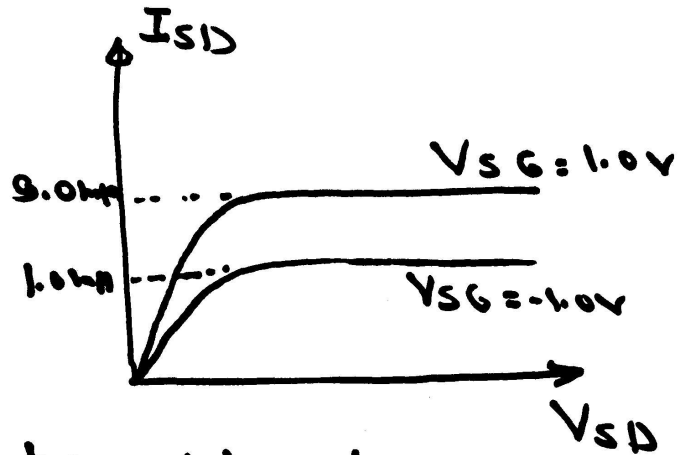

Determine transistor type
and threshold voltage

Answer:

$$1.0 \times 10^{-3} = \frac{k_p}{2} (V_{SG_1} + V_{TP})^2 \quad \text{--- (1)}$$

$$9.0 \times 10^{-3} = \frac{k_p}{2} (V_{SG_2} + V_{TP})^2 \quad \text{--- (2)}$$

divide (2) by (1)

$$9 = \frac{(V_{TP} + 1)^2}{(V_{TP} - 1)^2}$$


$$\pm 3 = \frac{V_{Tp} + 1}{V_{Tp} = 1} \quad (5)$$

$$V_{Tp} = +2V \quad \text{or} \quad V_{Tp} = +0.5V$$

$V_{Tp} = 0.5V$ is rejected

\therefore transistor is depletion PMOS

with $V_{Tp} = 2V$

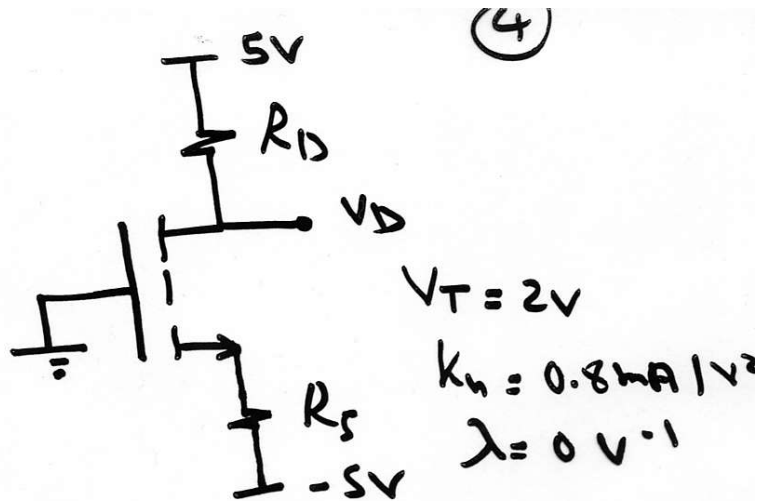

Determine R_D and R_S such that
 $I_{DS} = 0.4 \text{ mA}$, $V_D = 1V$

Answer: transistor must be saturated
 because $V_S < -2V$ for $V_{GS} > V_T$

$$V_{DS} = V_D - V_S = 1 - V_S > 0 - V_S - 2$$

$$\text{or } -V_S + 1 > -V_S - 2$$

$$I_{DS} = \frac{k_n}{2} (V_{GS} - 2)^2$$

$$0.4 \times 10^{-3} = \frac{0.8 \times 10^{-3}}{2} (V_{GS} - 2)^2$$

$$\therefore \pm 1 = V_{GS} - 2 \implies V_{GS} = 3V$$

$$0V \quad V_S = -3V \quad (5)$$

$$\therefore R_S = \frac{2.0}{0.4 \times 10^{-3}} = 5k\Omega$$

$$\text{and } R_D = \frac{4}{0.4 \times 10^{-3}} = 10k\Omega$$