

If $V_1 = V_2 = V_{in}$, what is the value of V_o ?


$$V^+ = \frac{V_2}{2} \text{ because } i^+ = 0$$

$$\text{But as } V^- = V^+ \implies V^- = \frac{V_2}{2}$$


$$\text{Because } i^- = 0 \text{ we have } V^- = \frac{V_o}{2} + \frac{V_1}{2}$$

$$\therefore \frac{V_o}{2} + \frac{V_1}{2} = \frac{V_2}{2} \implies V_o = V_2 - V_1 = 0V$$

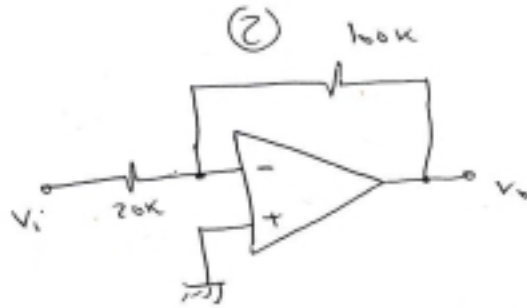
What is the input resistance looking into V_2 ? looking into V_1 ? what is the output resistance?



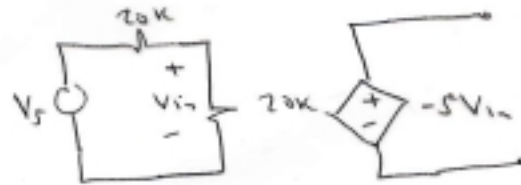What is the value of the output voltage if the input is connected to a source with $V_s(t) = 0.1 \sin \omega t$ & $R_s = 20k\Omega$?


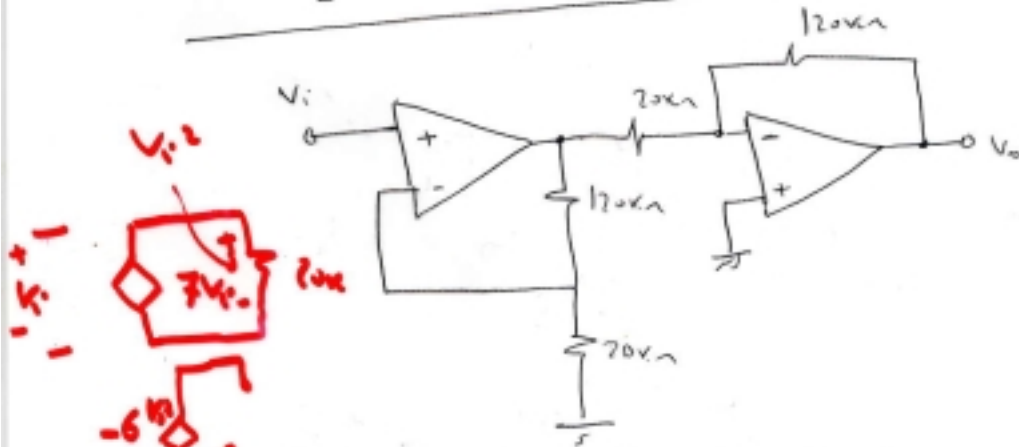
$$V_{in} = \frac{V_s}{2} \Rightarrow V_o = -5V_{in} = -0.25 \sin \omega t$$



What is A_v , R_{in} & R_{out} for the shown amplifier!




(3)

$$A_V = A_{V1} + A_{V2}$$
$$= \left(1 + \frac{120k}{20k}\right) * \left(-\frac{120k}{20k}\right)$$

$$A_V = 7 * -6 = -42$$

$$R_{in} = \infty, \text{ } R_{out}$$

To get R_{out} we form the circuit

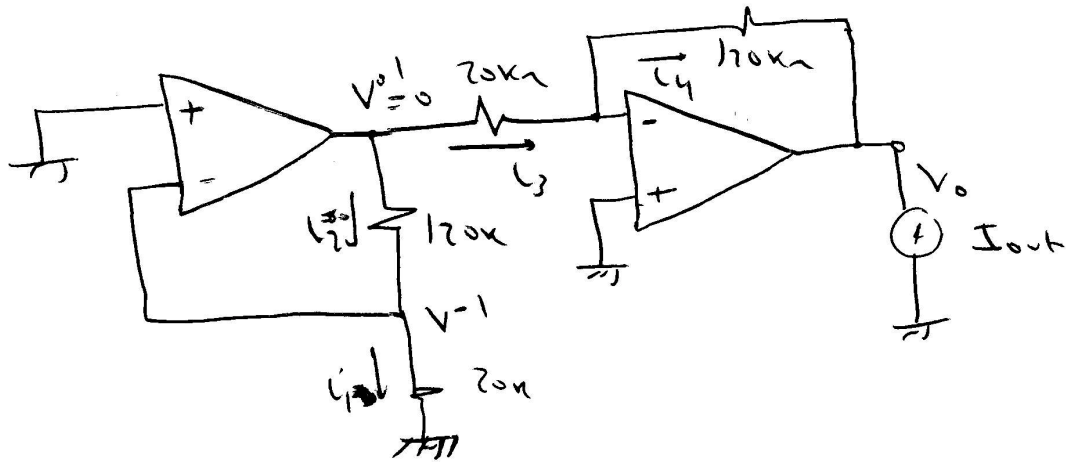



$$V^{+1} = 0 = V^{-1} \Rightarrow i_1 = 0 = i_2 \Rightarrow V_o = 0$$

$$V^{+2} = 0 \Rightarrow i_3 = 0 = i_4 \Rightarrow V_o = 0$$

$$\therefore \frac{V_o}{I_{out}} = 0 \quad R_{out} = 0$$

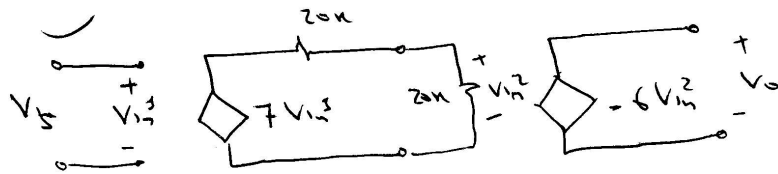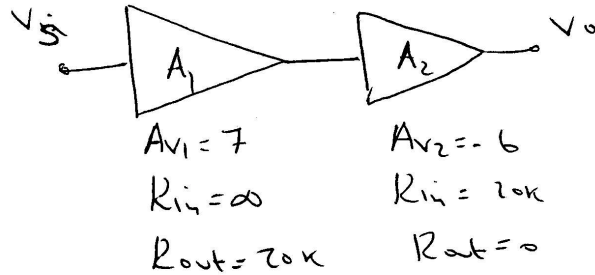(4)


Repeat the previous example for the shown circuit




$$V_{in}^2 = 7V_{in}^1 \times \frac{20k}{20k + 20k} = \frac{7}{2} V_{in}^1 = \frac{7}{2} V_s$$

$$V_o = -6 V_{in}^2 = -\frac{42}{2} V_s = -21$$

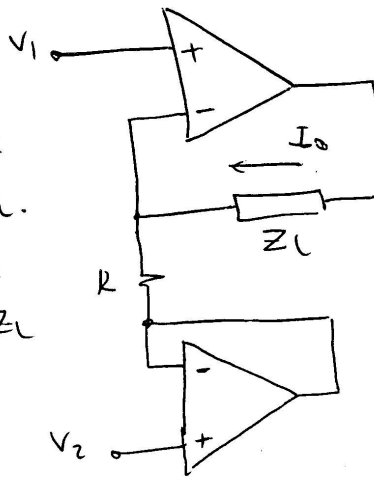Find I_o
 as a function of
 V_1, V_2, R and Z_L .
 what is R_{out}
 looking into Z_L




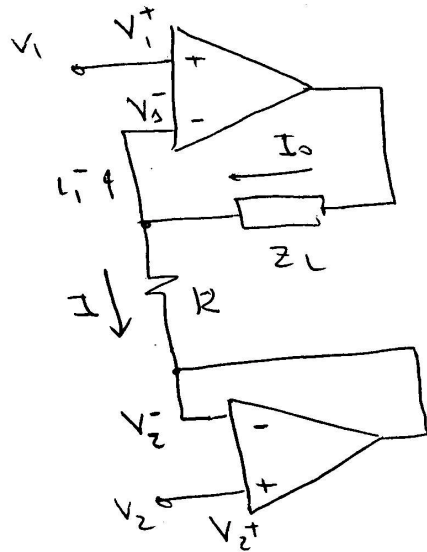

$$V_1^+ = V_1 = V_1^- \quad \text{and} \quad V_2^+ = V_2 = V_2^-$$

$$I = \frac{V_1^- - V_2^-}{R} = \frac{V_1 - V_2}{R} = I_0 \quad \text{because } \bar{i}_i = 0$$
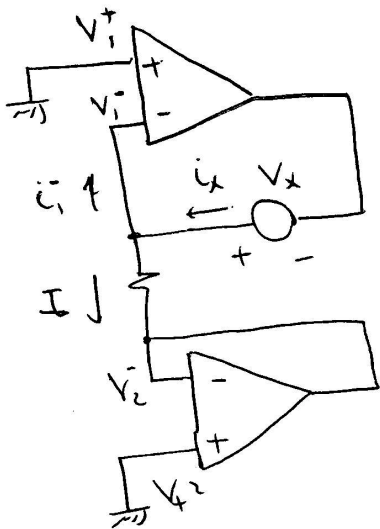
$$\therefore I_0 = \frac{V_1 - V_2}{R} \quad (\text{independent of } Z_L)$$



$$V_1^+ = 0 = V_1^-$$

$$V_2^+ = 0 = V_2^-$$

$$I = \frac{0 - 0}{R} = 0$$

$$\text{but } i_x = I \quad (\text{because } \bar{i}_i = 0)$$

$$\therefore i_x = 0$$

$$\therefore R_{out} = \frac{V_x}{i_x} = \infty$$

